

E U R O P E A N E D I T I O N

# EDN<sup>®</sup>

THE DESIGN MAGAZINE OF THE ELECTRONICS INDUSTRY

JULY 6, 1995

**NEW PRODUCT INTRO**

Software-development  
tool creates C programs  
automatically pg 15

11 SEP 1995

**NEW!**  
**COMPONENTS**  
**SHOWCASE**  
pg 119

Table of Contents pg 4

Out in Front pg 15

Portable hardware  
makes experiments  
interactive pg 53

Design Ideas pg 64

Optimize sensor  
systems using fixed  
components pg 85

Cryptography pg 99

Options dot the  
programmable-logic  
landscape pg 107

Jack Ganssle  
Living to learn pg 165




**DILBERT** pg 16

**Cover Story:**  
***Delivering the  
high-speed clock***  
**pg 32**


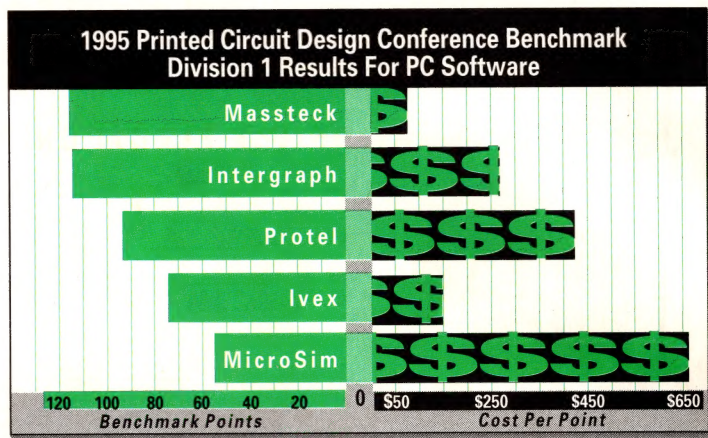
# When You See These Numbers, You'll Do What We Did. Buy MaxEDA.



We're proud to announce that OrCAD has acquired Massteck™ — the clear leader in PCB design price/performance.

And now you too can acquire Massteck's MaxEDA™ — and for a limited time, save \$2,000.

That means for under \$3,000, you'll get an extremely affordable solution for doing high-end work on desktop PCs. OrCAD's new version of MaxEDA includes a powerful 16-layer push-and-shove autorouter, auto-interactive routing, automatic matrix placement and test-point generation, online DRC and auto-DFM.

And as part of the OrCAD Design Desktop™ for Windows®, MaxEDA is tightly integrated with

our OrCAD Capture™ for Windows. With support for forward- and back-annotation, pin and gate swap, and cross-probing of components and nets. You can pass layer assignments, net priorities and component attributes from OrCAD Capture to MaxEDA — and back again.

MaxEDA Gold™ adds automatic cluster placement, interactive push-and-shove component placement and a complete set of translators for layout products from PADS, P-CAD, Protel and more — all at a special price of \$7,995.

But only for a limited time, so call today.

**For more information, detailed data sheets or to order, send email to [info@orcad.com](mailto:info@orcad.com) or call OrCAD DIRECT at (800) 671-9505.**

#### Limited Time Offer

Save \$2,000 On MaxEDA

Call Now


(800) 671-9505

**OrCAD®**   
Bringing Electronic Design to the Desktop

OrCAD is a registered trademark and Massteck, MaxEDA, MaxEDA Gold, OrCAD Capture and OrCAD Design Desktop are trademarks of OrCAD, Inc. Windows is a registered trademark of Microsoft Corporation. All other trademarks are marks of their respective owners. Prices are subject to change without notice.



# PROTOTYPE TO PRODUCTION

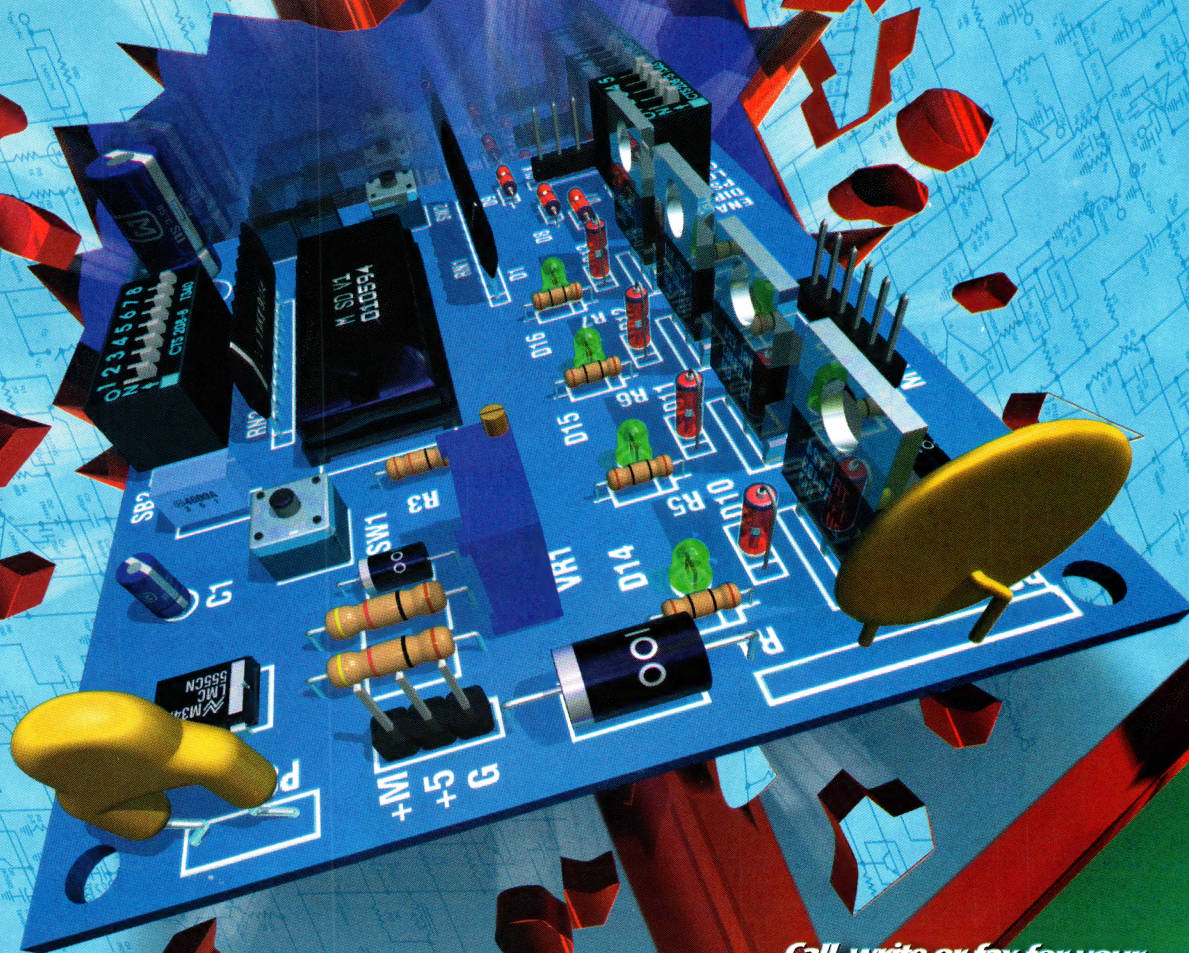

On orders placed by  
5:00 p.m. central time

**DIGI-KEY: Your Ultimate Source  
For Quality Electronic Components!**

- #1 for Availability of Product
- #1 for On-Time Delivery
- #1 for Overall Performance

Call, write or fax for your  
**FREE CATALOG** today!


**Digi-Key**  
CORPORATION

**1-800-344-4**

701 Brooks Ave. South, Thief River Falls, MN 56201  
Fax: 218-681-1111




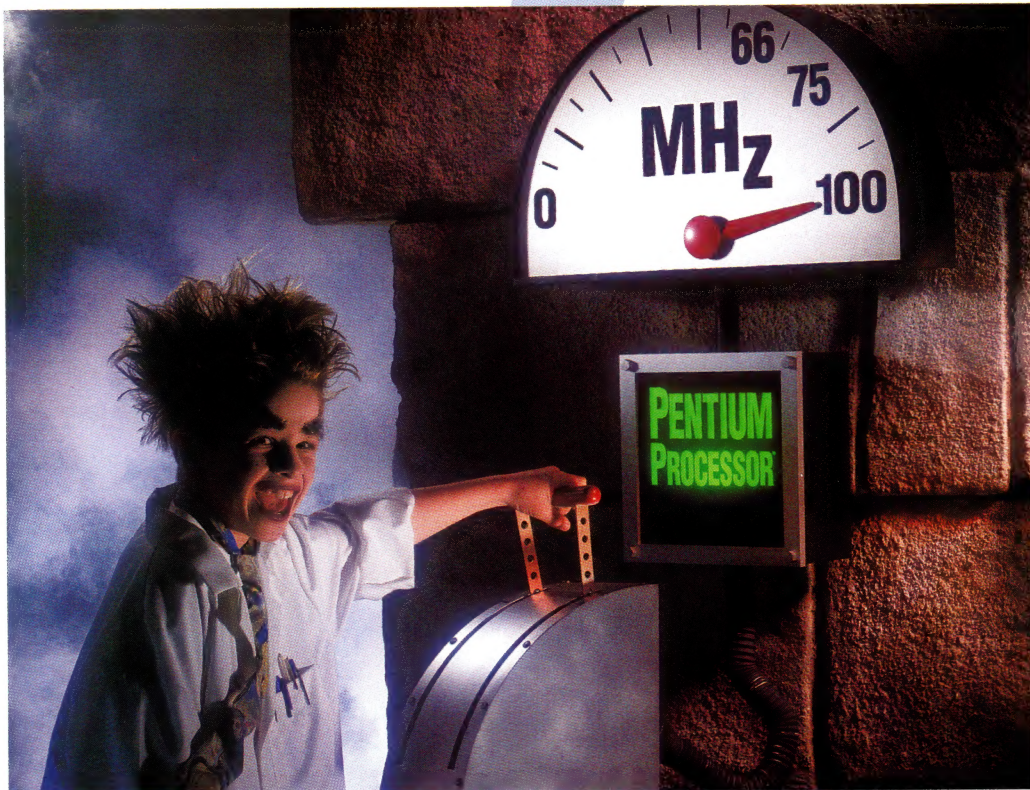
# Push your processor to the max with the Siliconix dc-to-dc controller IC.



The new Si9145 dc-to-dc switchmode controller IC is the only device that gives you full Pentium® processor performance.

#### Si9145 TRANSIENT RESPONSE

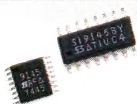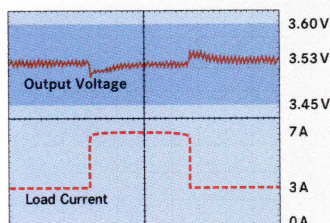

Finally, there's a way to push your Pentium processor designs to full speed. The Siliconix Si9145 features wide-bandwidth feedback for fast response to large amplitude load step demands. That's important because response time is critical to maintain tight regulation and performance in power supplies for high-speed processors like the Pentium chip.

What's more, the Si9145 is available in both small-outline and TSSOP packages. Combine it with low-profile surface-mount inductors and capacitors, and you have a smaller dc-to-dc converter with the industry's lowest voltage

ripple and the best transient response. Just the thing for reducing PCB size!

Use the Si9145 with a LITTLE FOOT® or LITE FOOT™ power MOSFET for a complete surface-mount solution for lower-power dc-to-dc boost or synchronized buck conversion.


So if you'd like to push your processors to the max, call **1-800-554-5565, ext. 950**, and we'll send you a free Si9145 Design Guide.

## TEMIC

Siliconix, A Member of TEMIC



# VOLTAGE CONTROLLED OSCILLATORS

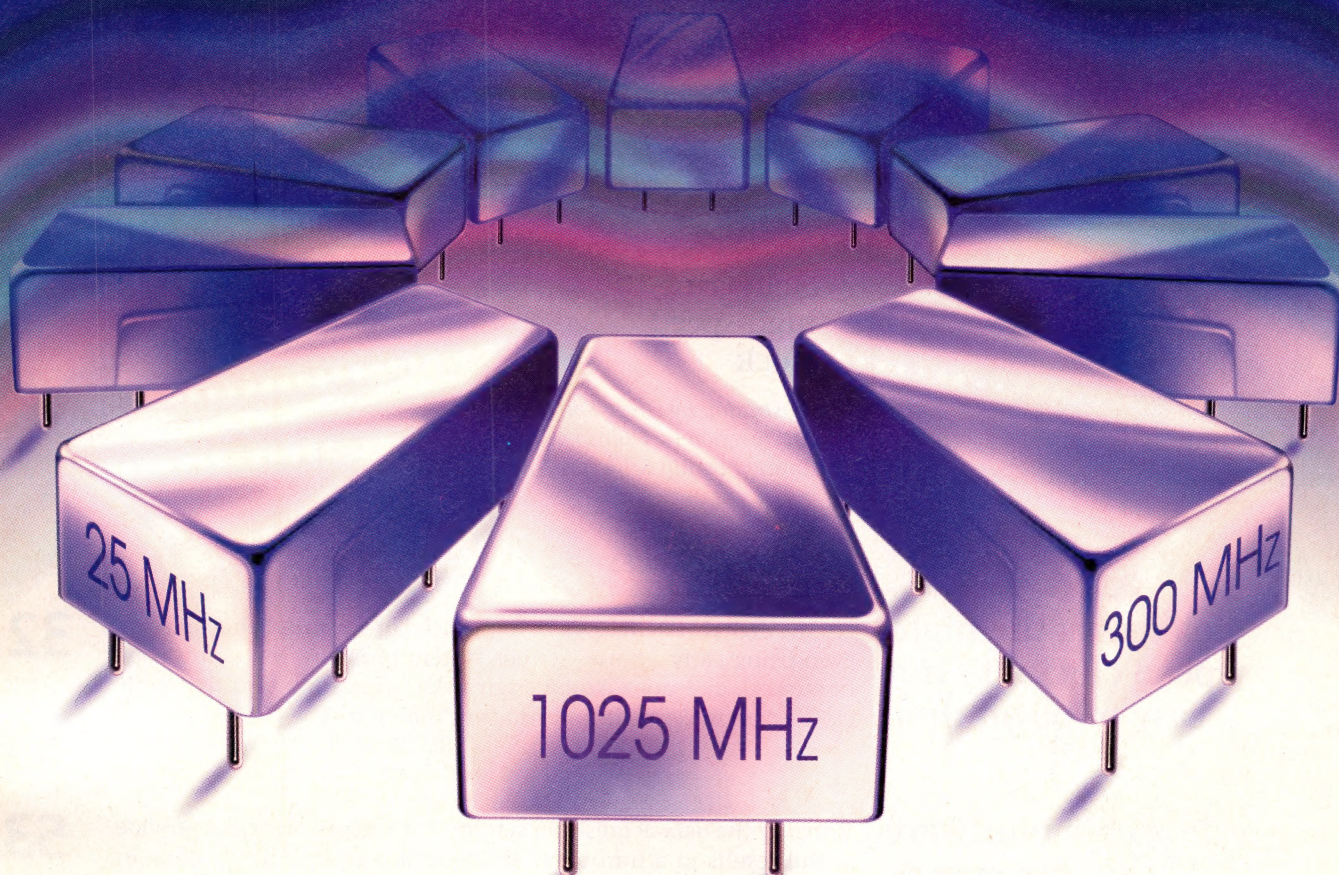

**25 to 1025 MHz (+7dBm output) From \$11<sup>95</sup>** (5-49)

It's a fact! With Mini-Circuits new POS family of shielded, laser sealed voltage controlled oscillators, you pay less but get more... top notch quality, superior performance and value pricing.

Features include wide-band models with near octave bandwidth and linear tuning. Low SSB phase noise characterized at 100Hz to 1MHz offsets. Excellent harmonic suppression, typically more than 25dB. RF power output typically +7dBm, excellent for driving level 7 mixers. Miniature size, only 0.4 X 0.8 inch board space. Hermetically sealed and ruggedly constructed for tough environments. Best of all, Mini-Circuits high performance, highly reliable VCO's can be yours at value prices starting at only \$11.95 each (qty. 5-49). To order from stock, call Mini-Circuits today.

**Mini-Circuits...we're redefining what VALUE is all about!**

#### DESIGNER'S KITS:

K-POS1 \$124.95 (contains 1ea. all models).

K-POS2 \$79.95 (contains 1ea. all models except POS-75, -150, -300).

Model No.	Freq. Range (MHz) Min.	Phase Noise (dBc/Hz) SSB @10kHz Typ.	Harmonics (dBc) Typ.	Power 12V DC Current mA	Price (Qty. 5-49) \$ ea.
POS-50	25-50	-110	-19	17	11.95
POS-75	37.5-75	-110	-27	17	11.95
POS-100	50-100	-107	-23	18	11.95
POS-150	75-150	-103	-23	18	11.95
POS-200	100-200	-102	-24	18	11.95
POS-300	150-280	-100	-30	18	13.95
POS-400	200-380	-98	-28	18	13.95
POS-535	300-525	-93	-26	18	13.95
POS-765	485-765	-85	-21	22	14.95
POS-1025	685-1025	-84	-23	22	16.95

Notes: Tuning voltage 1 to 16V required to cover freq. range.  
Operating temperature range: -55°C to +85°C.

## Mini-Circuits®

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661


For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRC

**CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.**

CIRCLE NO. 185

4 • EDN NOV 1989

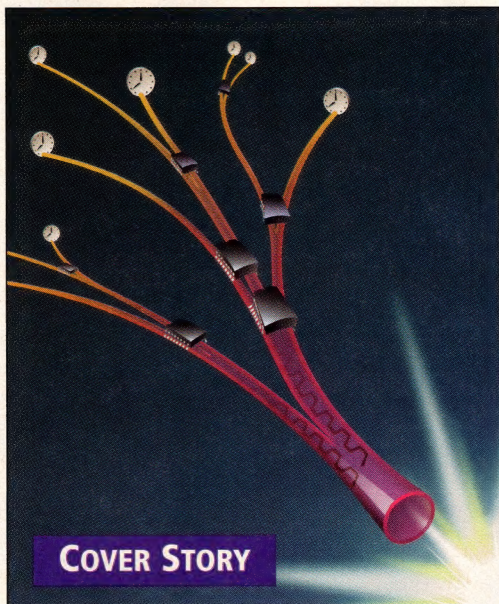

**COVER STORY****EDN****DESIGN FEATURES**

## Delivering the high-speed clock: It's not easy to be on time

For the digital system clock in high-speed processors, being late—or even being early—causes serious system problems. By doing your homework and not taking design risks, you can ensure that your clock edges make their transitions in the right time window.

—Bill Schweber, Technical Editor

## Portable hardware makes experiments interactive

Bringing the data-acquisition system to the experiment can provide useful results in a hurry. But, if you're not careful, subtle flaws in what should be invisible software can stymie your hardware installation.

—Dan Strassberg, Senior Technical Editor

## Optimize sensor systems using fixed components

A design method that uses device-to-device variations, temperature effects, and component tolerances allows you to configure optimum amplifier and ADC circuitry for sensor systems.

—Eric Jacobsen and Jeff Baum, Motorola Sensor Products

## Cryptography is key to securing proprietary information

Computer and communications technologies are converging. Satellite and cable TV, electronic mail, and smart bank cards are among the slew of applications involved. Some applications routinely risk transmitting valuable information over low-security channels. By using cryptography, however, you can encode proprietary data and prevent its misuse.

—Antony Watts, SGS-Thomson Microelectronics

## Options dot the programmable-logic landscape

PLDs have emerged as indispensable tools for system designers. They have evolved from fast prototyping tools into production devices that quickly get your designs to market, when anticipated volumes don't justify the cost of a full ASIC design.

—Richard Kapusta, Cypress Semiconductor Corp



## Portable hardware 53

## Delivering the high-speed clock 32

Illustration by Gregg Dinderman  
Art direction by Chinsoo Chung  
Concept by Bill Schweber

32

53

85

99

107




## OUT IN FRONT

- Software-development tool creates C programs automatically 15
- BBS is back on-line 15
- Analog-line-card telecomm codec simplifies design 15
- Cyrix offers 586-class processor 16
- Delay calculator targets submicron designs 16



Dilbert

16

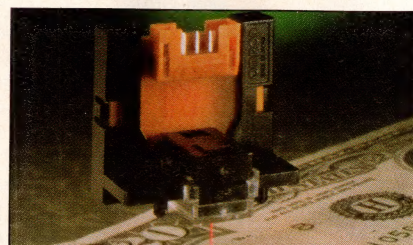

- Optical sensor detects 10- $\mu$ m displacement 18
- PC chip set includes complete secondary cache 18
- Repeater controller handles fast Ethernet connections 20

- Spread-spectrum IC is core of transparent-modem link 20
- Visual-media accelerator employs 170-MHz RAMDAC 22
- Five vendors announce PCMCIA data-acquisition cards 24
- Math software integrates with Lotus Notes and the World Wide Web 24

### EDN

### DESIGN IDEAS

- Video fader preserves synchronization 64
- Behavioral Spice model emulates VCO 65
- Circuit guards against battery reversal 66
- Measure inductance with dc superimposed 68
- "Zero-power" A/D converter uses printer port 70
- Serial-interface IC supplies bipolar voltages 72

### EDN

### COLUMNIST

- Living to learn 165
- Spend time in good bookstores. Never has so much information been available in so many easily digestible forms.
- Jack Ganssle, *Embedded-Systems Contributing Editor*

### EDN

### PRODUCTS

- Components Showcase 119
- Integrated Circuits 129
- Electronic Design Automation 140
- Embedded Systems 144
- Microprocessors 149
- Test & Measurement 150
- Literature 154

### EDN

### DEPARTMENTS

- Editorial 8
- Editorial Staff 8
- Career Opportunities 160
- International Advertisers Index 163

EDN® (ISSN 0012-7515, GST#123397457, C.P.C. Int'l Pub Mail #0280844) is published 39 times per year, biweekly with one additional issue per month, except December which has two issues. EDN is published by Cahners Publishing Company, 8773 South Ridgeline Blvd., Highlands Ranch, CO 80126-2329. Cahners Publishing Company is a division of Reed Elsevier, Inc., 275 Washington Street, Newton, MA 02158-1630. Robert L. Krakoff, Chairman and Chief Executive Officer; Jackie Daya, Vice President and Chief Financial Officer; William Rakay, Senior Vice President/General Manager, Boston Division. Circulation records are maintained at Cahners Publishing Company, 8773 South Ridgeline Blvd., Highlands Ranch, CO 80126-2329. Telephone (303) 470-4445. Second-class postage paid at Littleton, CO 80126 and additional mailing offices. **POSTMASTER: Send address changes to EDN®, PO Box 7500, Highlands Ranch, CO 80126-7500.** EDN® copyright 1995 by Reed Elsevier Inc. Rates for non-qualified subscriptions, including all issues: US, \$135.90 one year, \$231.95 two years; Canada, \$199.90 one year, \$340.95 two years (includes 7% GST, GST#123397457); Mexico, \$189.90 one year, \$323.95 two years; all others surface \$249.90 one year, \$425.95 two years; air expedited surcharge add \$104.00 one year, \$208.00 two years. Except for special issues where price changes are indicated, single copies are available for \$10.00 US and \$15.00 foreign. Please address all subscription mail to EDN®, 8773 South Ridgeline Blvd., Highlands Ranch, CO 80126-2329. EDN® is a registered trademark of Reed Properties Inc., used under license.

(Printed in USA)






©1995 Hewlett-Packard Company.

For more information on our workstation solutions: 1-800-HP KNOWS or <http://www.wsg.hp.com>





More. Better. Faster.

What computer system  
do you have?

---

For serious engineering, you need serious performance. HP 9000 J-Class VISUALIZE workstations give you exactly that. The world's fastest 3-D graphics. And the world's best price performance. You need to deliver more, better, faster. We already have.

If the business decisions are yours,  
the computer system should be ours.




HEWLETT®  
PACKARD

Computer Systems


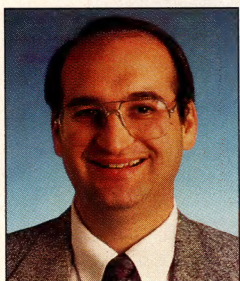
# Entertainment, communication, and education: the real convergence



Much has been written about the convergence of computers, communications, and consumer products. This is a supply-side-centric view of the electronics market. In reality, consumers don't care whether you classify a printer/fax/scanner for the home as a computer, communications, or consumer product. They buy it because it performs useful tasks. In fact, the tasks convergence products perform meet the three main consumer needs of modern civilization.

After satisfying the basic needs of food, shelter, transportation, and health, people spend their money on entertainment, communication, and education. I call these three categories the three pillars of modern civilization (the information society). This is a consumption-centric view of

the electronics market. Like the converging products that are so hard to classify, it's often very hard to decide which of the three pillars a product represents.

A CD-ROM-based encyclopedia, such as Microsoft's "Encarta," is as entertaining as it is educational. A game such as "Sim City" is as educational as it is entertaining. Interactive TV will satisfy needs in all three categories. A universal TV/video phone/computer clearly falls into all three categories and is likely to become the

next big consumer product after the PC. My condolences to the companies scrambling to be king of the set-top-box hill.

Products that fall into one or more of these three

categories will be the big sellers of the late 1990s. If you compete in these markets or if your company *should* compete in these markets, take a long look at how well your planned products will satisfy the consumer needs for entertainment, communication, and education.

**After satisfying the basic needs of food, shelter, transportation, and health, people spend their money on entertainment, communication, and education.**



**Jesse H. Neal**  
Editorial Achievement Award  
1990 Certificate, Best Editorial  
1990 Certificate, Best Series  
1987, 1981 (2), 1978 (2), 1977,  
1976, 1975.

**American Society of**  
**Business Press Editors Award**  
1994, 1991, 1990, 1988, 1983, 1981

*Steven H. Leibson*

**STEVEN H. LEIBSON**  
EDITOR IN CHIEF

Send me your comments via fax at (617) 558-4470, or on the EDN Bulletin Board System at (617) 558-4241, 300/1200/2400 8,N,1. From the Main System Menu, enter ss/soapbox and select W to write us a letter.

## HOME OFFICE

275 Washington St, Newton, MA 02158  
EDN Bulletin Board: (617) 558-4241  
MCI: EDNBOS; fax (617) 558-4470;  
phone (617) 964-3030

To send a message to an EDN editor via Internet, add @MCI.MAIL.COM to the MCI address.

## PUBLISHER

Jeffrey Patterson (617) 558-4454

## EDITOR IN CHIEF

Steven H. Leibson (617) 558-4214;  
MCI: ednleibson

## EXECUTIVE EDITOR

Gary Legg (617) 558-4404; MCI: ednlegg

## MANAGING EDITOR

Joan Lynch (617) 558-4215; MCI: ednmorrow

## SENIOR TECHNICAL EDITORS

Dan Strassberg (617) 558-4205

MCI: ednstrassberg

Bill Travis (617) 558-4471 MCI: edntravis

## TECHNICAL EDITORS

John A. Gallant (617) 558-4666

MCI: edngallant

Markus Levy (916) 939-1642; fax: (916) 939-1650; MCI: ednlevy

Jim Lipman (510) 606-1370; fax: (510) 606-1177; MCI: ednlipman

Richard A. Quinnell (408) 685-8028 (phone/fax); MCI: ednquinnell

Bill Schweber (617) 558-4484; fax: (617) 558-4470; MCI: ednschweber

Maury Wright (619) 748-6785; fax: (619) 679-1861; MCI: ednwright

**SPECIAL PROJECTS EDITOR**

Doug Conner (805) 461-9669; fax: (805) 461-9640; MCI: edndconner

## SENIOR ASSOCIATE EDITORS

Frances T. Granville (617) 558-4344

James P. Leonard (617) 558-4324

## ASSOCIATE EDITOR

Anne Coyle (617) 558-4333

## EDITORIAL AND ART PRODUCTION

Diane Malone, Manager (617) 558-4303

Ken Racicot, Senior Art Director (617) 558-4708

Chinsoo Chung, Associate Art Director

(617) 558-4446

Patricia Shaughnessy, Production Editor

(617) 558-4206

## CONTRIBUTING TECHNICAL EDITORS

David Brubaker, Jack Ganssle,

Robert Pease, Don Powers,

Anne Watson Swager

## ASSISTANT TO EDITOR IN CHIEF

Kathy Leonard (617) 558-4405; MCI: ednleonard

## EDITORIAL SERVICES

Helen Benedict (617) 558-4681; MCI: ednbos

## PRODUCTION

Andrew Jantz, Group Manager (617) 558-4372

Karen Banks, Production Manager

(617) 558-4441

Rich DeYoung, Associate Production Manager

(617) 558-4604

## EDN SPECIAL EUROPEAN ISSUES

Brian Kerridge, Editor, 22 Mill Rd, Loddon,

Norwich NR14 6DR, UK

(508) 528435; fax (508) 528430

MCI: ednkerridge

## EDN ASIA

Mike Markowitz, Editor, Cahnners Asia Ltd

19th Floor, Eight Commercial Tower

8 Sun Yip St, Chai Wan, Hong Kong

Phone (011) (852) 2965-1555;

fax (011) (852) 2976-0706

## EDN PRODUCTS

301 Gibraltar Dr, Box 650, Morris Plains, NJ 07950

Phone (201) 292-5100; fax (201) 292-0783

## VP/GROUP PUBLISHER

Terry McCoy, Jr. (201) 292-5100, ext 317

## ASSOCIATE PUBLISHER

Steven P. Wirth (201) 292-5100, ext 380

## EDITORIAL DIRECTOR

Richard Cunningham (702) 646-2470

## EDITOR-IN-CHIEF

Bruce Bennett (201) 292-5100, ext 390

## ASSOCIATE EDITOR

Heidi Bauer (201) 292-5100, ext 322

## PRODUCTION MANAGER

Jacqueline Sammarco (201) 292-5100, ext 289

## CUSTOMER SERVICE MANAGER

Tara Poli (201) 292-5100, ext 318

## DESIGN DIRECTOR

John M. Angelini

## ART DIRECTOR

Beverly Blake



**N a t i o n a l ' s   n e w**

**D a t a   A c q u i s i t i o n**

**S y s t e m - o n - a - c h i p**

**i s   s o   m o m e n t o u s   t h a t . . .**



**Mother Nature gave you an easy**



**More  
than a  
12-bit  
ADC**

**And our design tools make it easy to use ~**

The LM12434/8. National's programmable 12-bit serial I/O Data Acquisition System-on-a-chip can shave weeks off your design time. Featuring ten integrated functions, the LM12434/8 is fully capable of stand-alone operation. It will significantly simplify your design and reduce debug time. ~ Moreover, our remarkable new WaveVision design tool makes this versatile chip a snap to design in. This intuitive Windows™-based tool clearly simulates the full functionality of the part, configures a DAS for





way to remember

how many functions it has.



operation, and evaluates the performance of the device in your design. In 10 minutes, you'll be a pro. ~ There is, of course, much more to tell. Like the LM12434/8's industry-leading speed of 140kS/s throughput while consuming only 45mW from a 5V supply, and its eye-popping price of \$12.90 (per 1000 pieces)...but the clock's ticking. So get your free WaveVision software and a complete product information kit today. Call 1-800-NAT-SEMI, Ext. 357, fax your request to 1-800-888-5113, or return the attached reply card.




**National**  
Semiconductor



Display equipment acts as the eyes of machines. Your machines will have an entirely new outlook with a Samsung VFD (Vacuum Fluorescent Display) module. Our VFD modules provide your industrial machines, automobiles, home appliances and other display equipment with a new level of wide viewing angle, vivid contrast, and manifold character representations. Brighten your machines with Samsung VFD modules.

Shed a Bright Light on Your Machines

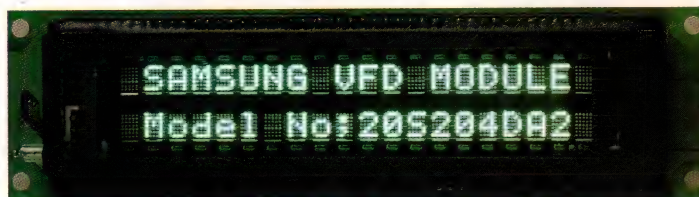

#### VFD MODULES

MODEL	CHARACTER FORMAT & SYMBOLS	No of Digits (Row X Column)	CHARACTER DIMENSIONS			OUTER DIMENSIONS			ELECTRICAL CHARACTERISTICS			INTERFACE				
			CH (mm)	CW (mm)	CP (mm)	L (mm)	H (mm)	T (mm)	V <sub>cc</sub> (Vdc)	I <sub>cc</sub> (mA)	L (Typ) (Ht-L)	Parallel Input	Serial Input	Self Test	Device Select	Busy Out
20S102MA4		1-20	5.0	3.5	4.7	150.0	30.0	26.6	5.0	150	200	○	○	○	○	○
20S204DA2		2-20	5.0	3.5	5.1	155.0	43.0	28.0	5.0	350	250	○	○	○	○	○
40S102MA4		1-40	5.05	3.55	4.75	240.0	40.0	30.0	5.0	350	200	○	○	○	○	○
40S201MA4		2-40	5.05	3.55	4.75	240.0	60.0	29.0	5.0	800	200	○	○	○	○	○
12L101MK1		1-12	11.4	8.7	12.5	200.0	50.0	28.6	5.0	550	250	○	○	○	○	○

#### Headquarter

Daekyung Bldg. 120 2-Ka, Taepyeong-Ro. Choong-Ku Seoul TEL:822-727-3331~3, 3351~3 FAX: 822-727-5949, 727-3389

#### European Office

SAMSUNG Haus AM UNISYS Park 1 65843 Sulzbach, Frankfurt, Germany TEL:49-6196-74001~5 FAX: 49-6196-758149

#### Hong Kong Office

66F Central Plaza 18 Harbour Rd., Wanchai, Hong Kong TEL:852-2862-6053 FAX: 852-2866-2548

#### Samtron Display Inc.

18600 Broadwick St., Rancho Dominguez, CA 90220, U.S.A. TEL:310-537-7000 FAX:310-537-1033

CIRCLE NO. 10

**SAMSUNG**

DISPLAY DEVICES



# EDN OUT IN FRONT

WHAT'S HOT IN THE DESIGN COMMUNITY


EDITED BY FRAN GRANVILLE

## Software-development tool creates C programs automatically

You can write event-driven, graphical-interface ANSI C programs in minutes rather than hours by using CodeBuilder, a utility in Version 3.1 of National Instruments' LabWindows/CVI visual-development software package for Windows PCs and Sun SPARCstations. CodeBuilder not only speeds program writing, but also reduces errors and produces more consistent and maintainable code than human programmers do. You begin by using the User-Interface Editor to assemble knobs, pushbuttons, gauges, and charts on the screen. You then insert acquisition and control code from LabWindows/CVI libraries.

New, configurable Extended Control-Hierarchy Objects (ECHOs), including a new timer control, act as instrument drivers, handling low-level hardware programming of data-acquisition boards and making it easy to display acquired data graphically. A new color-intensity plot capability lets you show 3-D plots in 2-D, with color representing the Z-axis position.

Customizable on-screen tool bars present all the common source-code editing and debugging functions. Pointing at a tool-bar button automatically displays tips on how to use the tool. The package provides the tools to develop drivers for VXI instruments in accordance with guidelines of the VXIplug&play Systems Alliance. The package includes the interface-independent I/O drivers of the Virtual Instrument Systems Architecture (VISA) Transition Library (VTL).

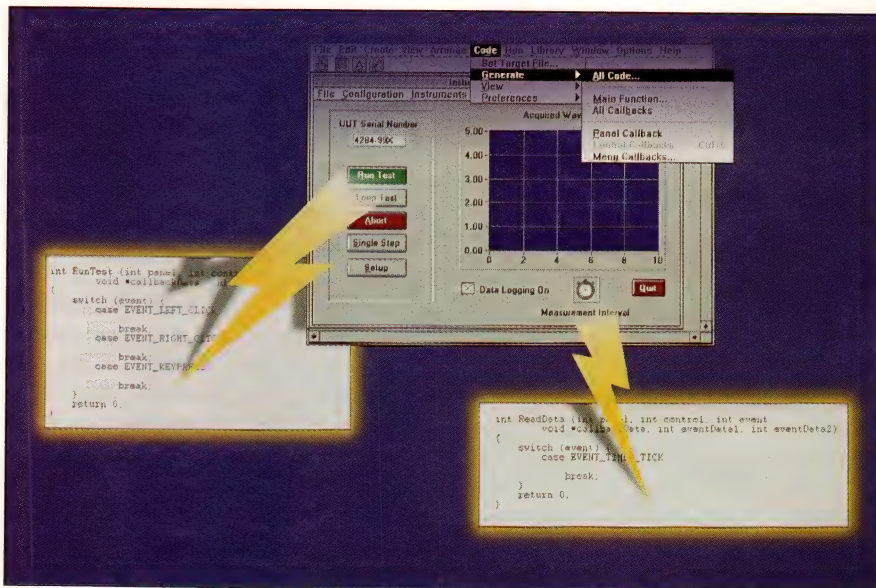

**LabWindows/CVI includes customizable ECHO controls that simultaneously provide flexibility and standardization. A CodeBuilder utility pulls in C code that is more consistent and maintainable than code created by human programmers.**

To run LabWindows/CVI V3.1, Windows users need 20 Mbytes of hard-disk space and a Borland, Watcom, or Symantec C compiler. Sun users must have 32 Mbytes of disk-swap space and 12 Mbytes of disk space. Sun users who plan to incorporate external C objects must use the Sun ANSI C Compiler or the Gnu C Compiler. Prices begin at \$995. Shipments begin this quarter.

—by Dan Strassberg

**National Instruments Corp**, Austin, TX. (512) 794-0100.

**Circle No. 445**

## BBS is back on-line



EDN's computer bulletin-board system (BBS) is now back on-line, after having experienced some technical difficulties. We apologize for any inconvenience you may have experienced. To access the BBS, phone (617) 558-4241 with modem settings 300/1200/2400 8,N,1, (9600 baud=(617) 558-4580).

## Analog-line-card telecomm codec simplifies design

AT&T Microelectronics' T7504 codec performs A/D conversion for four voice channels ( $\mu$ -law/A-law companding PCM), using a single 5V supply. The device suits analog line

cards for use in central-office, loop-carrier, and private-phone-exchange applications. In addition to the converters, the IC includes transmit and

(continued on pg 16)



receive filters, S/H and autozero circuitry, and a precision reference to interface voice-telephone circuits to a time-division-multiplexed system. The T7504 assigns PCM data to any time slot on a per-channel basis, operating from a 2.048- or 4.096-MHz master clock.

The device, which comes in a 28-pin DIP or PLCC, requires 37-mW/channel typical operating power; you can power down each

channel to cut power consumption to 1 mW/channel. The codec has differential architecture for high noise immunity and meets D3/D4 and CCITT G.711-G.714 requirements. AT&T fabricates the T7504 in latch-up-free CMOS technology; it costs \$6.20 (10,000).

—by Bill Schweber

**AT&T Microelectronics**, Allentown, PA.  
(800) 372-2447.

**Circle No. 446**

## Cyrix offers 586-class processor

When it arrives in the third quarter, the M1 processor from Cyrix will potentially outperform Intel's Pentium at the expense of a considerably larger die size. This strategy has taken Cyrix beyond the reach of 586-class pricing. To compete effectively at the 586 level, Cyrix followed the successful approach it took with its 486 and made it pin-compatible with the 386. Specifically, Cyrix has developed the 5x86, a scaled-down M1 with a 64-bit internal architecture in a 486 footprint. Although the 5x86 has only a 32-bit external bus, the CPU features static-branch prediction, an 80-bit floating-point unit, and a 16-kbyte, unified, write-back cache. Cyrix expects the 100-MHz 5x86 to deliver performance comparable to a 75-MHz Pentium and sell for \$147 (1000).

—by Markus Levy

**Cyrix Corp**, Richardson, TX. (800) 462-9749.

**Circle No. 447**

## Delay calculator targets submicron designs

Integrated Silicon Systems (ISS) has developed  $\Psi$ Time, a delay calculator that addresses the problems of calculating delays in interconnect-dominated submicron chips. These problems are due to the difficulty in simultaneously and accurately modeling the gate delay, interconnect delay, and input waveform on a net. The  $\Psi$ Time product lets you more accurately calculate on-chip delays by combining the gate-timing model, the RC network being driven, and the input rise time to generate a driving-point waveform for each extracted net. Separately calculating resistance and capacitance,  $\Psi$ Time interactively tunes the driver model while determining the RC network's "effective" capacitance. The tool then uses the converged effective capacitance and gate-timing model, using the updated driver model to drive the RC network to calculate gate delay and interconnect delay. The  $\Psi$ Time product calculates point-to-point interconnect delays from the driving point in the circuit to each load point in the RC network. It also calculates separate values for effective capacitance, gate delays, and interconnect delays for each specified input edge rate on a net.

Input RC data formats to  $\Psi$ Time include Spice and Standard Parasitic Format (SPF). You can input k-factor, table, Thevenin, and ISS's  $\Psi$ Drive models to  $\Psi$ Time. You can output Standard Delay Format (SDF) and Motive IDD and ISS formats. The tool can be used with both prelayout RC estimates and postlayout RC-extracted data. The  $\Psi$ Time product runs on Digital Equipment Corp, Hewlett-Packard, IBM, and Sun workstations. Prices start at \$25,000.


—by Jim Lipman

**Integrated Silicon Systems**, Research Triangle Park, NC. (919) 941-6600.

**Circle No. 448**
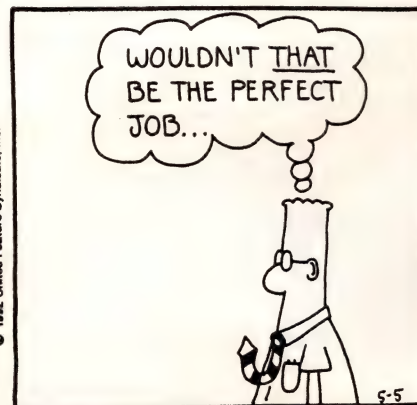
## DILBERT® by Scott Adams

DILBERT: ©1989 United Feature Syndicate, Inc.



EMAIL: scottadams@aol.com



# It's Plug and Play Time

Looking for a quick and simple way to upgrade your system to Plug and Play? Dallas Semiconductor—the world's leader in computer timekeepers—introduces a family of Plug and Play timekeepers. Each timekeeper comes with extra RAM to store data that tells the computer where all the resource assignments are set. Systems access the timekeeper's extra RAM via software instead of hardware for full Plug and Play capability.

## **Simplest and Cheapest Timekeeping Solution**

- Most systems can be upgraded to Plug and Play simply by changing out the BIOS and the clock. Unlike flash-based solutions, no redesign is required.
- Store the BIOS in One-Time-Programmable (OTP) ROM and use a Dallas clock for the lowest cost Plug and Play timekeeping solution.
- Dallas' Plug and Play solution does not require additional upper memory, thus saving system resources.

## **Increased Flexibility**

- You can store the BIOS in Flash or ROM.
- With the range of memory densities available in the Dallas Plug and Play family, you can design one system that will be adaptable across the gamut from low-end to high-end PCs.



## **Advanced Power Management Features**

- A kickstart input powers on the system with a single keystroke or via a modem ring detect signal.
- A wake-up alarm wakes up the system at a pre-set time; the system then performs its tasks and shuts itself down.
- Our clocks give your system the ability to perform "Soft Power On," complying with the PC '95 Hardware Design Guide recommendation.

## **Unique Extras**

- An SMI (System Management Interrupt) recovery stack on-chip guarantees the integrity of BIOS execution.
- Each chip is laser-etched with a guaranteed-unique, 64-bit serial number to help you keep track of your systems.

Device Number	Extended RAM	Operating Voltage
DS1685/DS1687	128 Bytes	3V or 5V
DS17285/DS17287	2K Bytes	3V or 5V
DS17485/DS17487	4K Bytes	3V or 5V
DS17885/DS17887	8K Bytes	3V or 5V

*For more information on the Dallas Semiconductor family of Plug and Play clocks, give us a call at (214) 450-0448.*





## Optical sensor detects 10- $\mu$ m displacement


A new optical sensor combines an LED with a position-sensing diode (PSD) to detect position changes as small as 10  $\mu$ m. Unlike other optical sensors that work by measuring the intensity of reflected light, the Z4D-A01 from Omron Electronics measures the position of a reflected spot of light on the surface of the device's PSD chip. The Z4D-A01 then uses the geometric principle of similar triangles to determine displacement of a sensed object from an initial location (Fig 1). Omron anticipates use of the sensor in products that measure the thickness or position of a sheet of paper.



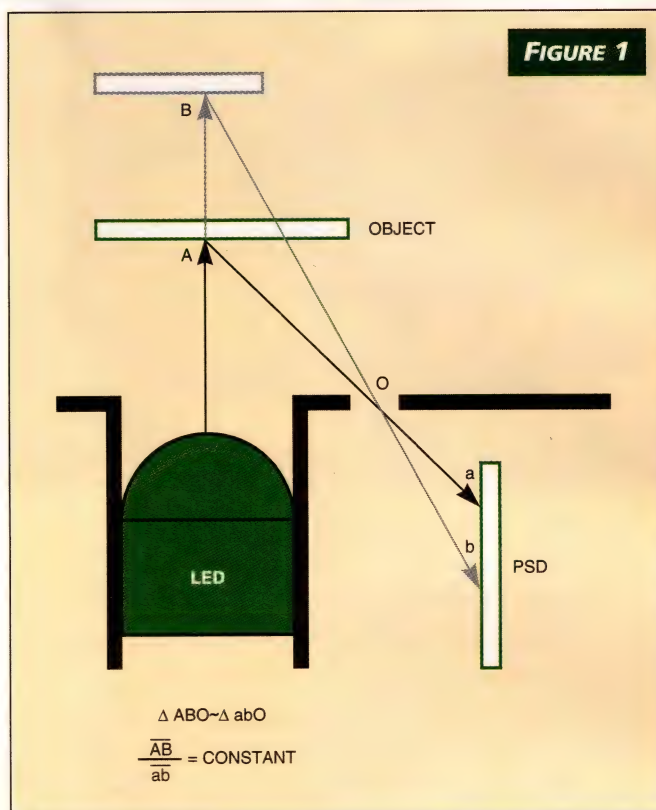**Omron's Z4D-A01 optical sensor targets applications that need to measure the thickness of paper.**

Unlike sensors that provide a single output from a photodiode or phototransistor, the Z4D-A01 provides two outputs from its PSD. Each output current is inversely proportional to the distance from the current's corresponding electrode to an incident spot of light on the PSD's surface. The Z4D-A01's LED creates the spot by reflecting light off the object whose displacement must be measured. As the object moves, so does the incident spot of light, thus altering the PSD's two output currents. The ratio of the two currents determines the spot's location, and application of the principle of similar triangles (ABO and abO in Fig 1) then allows computation of the sensed

measuring the intensity of reflected light, the Z4D-A01 from Omron Electronics measures the position of a reflected spot of light on the surface of the device's PSD chip. The Z4D-A01 then uses the geometric principle of similar triangles to determine displacement of a sensed object from an initial location (Fig 1). Omron anticipates use of the sensor in products that measure the thickness or position of a sheet of paper. Omron marketer Chris Corder expects to see the device in copiers, printers, fax machines, and money changers.



**By applying the two outputs of a position-sensing diode to the principle of similar triangles, the Z4D-A01 optical sensor can measure very small object displacements.**

object's displacement (AB) from a previous location.

The \$45 Z4D-A01 has a maximum sensing distance of about 6.5 mm. It works with a microcontroller that needs an A/D converter having at least 10 bits to take advantage of the sensor's maximum resolution. The screw-mount sensor operates on 5V dc and has an attached standard connector for use in remote-sensing applications.

—by Gary Legg

**Omron Electronics Inc.**, Schaumburg, IL. (800) 556-6766.

**Circle No. 449**

## PC chip set includes complete secondary cache

Cypress Semiconductor has introduced a Pentium-based PC chip set that integrates all standard I/O and bus interfaces along with a complete 128-kbyte secondary-cache-memory

subsystem. Cypress expects the three-chip 3.3V hyperCache chip set to cost \$48 (1000) and be available for initial sampling in August.

The set's first chip, the CY82C691, performs system and memory-interface functions. It provides CPU and PCI bus interfaces, a cache controller that can handle as much

as 1 Mbyte of secondary cache, and an integral 8k $\times$ 21-bit cache tag RAM. The device also provides DRAM control for as many as six banks (768 Mbytes max) of mixed fast-page and extended-data-out DRAMs. The controller also allows direct DRAM access for unified graphics/main-memory designs.

The CY82C692 provides a 128-kbyte, two-way set-associative, pipelined cache memory with 3-1-1-1 performance at 66-MHz bus-clock speeds. In addition to the memory block, the device offers a wraparound counter for both Intel and linear burst access, eight-deep FIFO memories for PCI bus

(continued on pg 20)





## INTERNAL MEMO

**CONFIDENTIAL**

TO: Marketing  
FROM: Engineering  
RE: ARE YOU NUTS — New Windows Schematics for Just \$199??

John — just heard about your wild new promotion —

**For only \$199 engineers can switch from another schematic entry product to our new MicroSim Schematics for Windows!** Are you nuts? This program is comparable to those costing \$1,000 or more from other companies. It has a symbol library with over 32,000 components, an **OrCAD translator**, and tight integration with MicroSim's entire family of products. Plus, it's compatible with MicroSim PCBoards and many other PCB layout packages. We're even shipping it without a security plug! It's a killer package...and the perfect upgrade for an OrCAD DOS user.

And I can't believe you set a **special introductory price of just \$479** for those who aren't using a schematic entry product. That hurts...OrCAD's Windows product is priced at \$995! I know you want to make a big splash, but don't kill the goose that laid the golden egg. OK?

### MicroSim™ Schematics Schematic Capture User's Guide

*This package  
is worth three  
times as much as  
you priced it,  
John!*

Call 800-245-3099 for more information or to order MicroSim Schematics for Windows.

MicroSim is a trademark of MicroSim Corporation. Copyright © 1995 MicroSim Corporation. All rights reserved.



buffering, parity checking, bus-size conversion logic, and data-steering logic. The C692 also offers a 64-bit port to an optional, \$14 CY82C694 128-kbyte expansion cache memory. The C694 performs as the C692 but has only the memory block.

The third chip, the

CY8C693, integrates I/O bus and peripheral control. It offers both ISA and PCI bus interfaces, handling as many as five PCI bus masters. It also includes DMA and interrupt control along with a tunable real-time clock, battery-backed SRAM, PS/2 mouse and keyboard

interfaces, an IDE interface with bus mastering, and power-management circuitry. The chip's on-board bus drivers offer selectable 8-, 12-, and 24-mA drive levels, eliminating the need for external bus drivers.

Cypress's schedule for the hyperCache chip set

calls for production ramp-up beginning in November. Cypress also plans to migrate the design to its RAM3 process in 1996 to produce a single-chip version.

—by Richard A Quinnell  
**Cypress Semiconductor**, San Jose, CA. (408) 943-2600. **Circle No. 450**


## Repeater controller handles fast Ethernet connections

The one-chip BCM5012 repeater controller from Broadcom supports 100BaseT4, 100BaseTX, and 100-Base-FX fast Ethernet connections and network management. With the company's BCM5000 10/100BaseT4 fast- $\Phi$  transceiver chip, the repeater controller enables network manufacturers to design 100-Mbps networks.

The BCM5012 meets IEEE 802.3 specifications and connects to any media type, including CAT 3, 4, and 5 unshielded twisted pair (UTP), shielded twisted pair, and fiber-optic media.

The device integrates features that allow system managers to operate and troubleshoot networks using the same software across multiple physical layers. The BCM5012 facilitates network management by Simple Network Management Protocol software through a collection of all the IEEE 802.3 management-information blocks. The chip also includes dedicated port connections for a local media-access-control layer and  $\mu$ P.

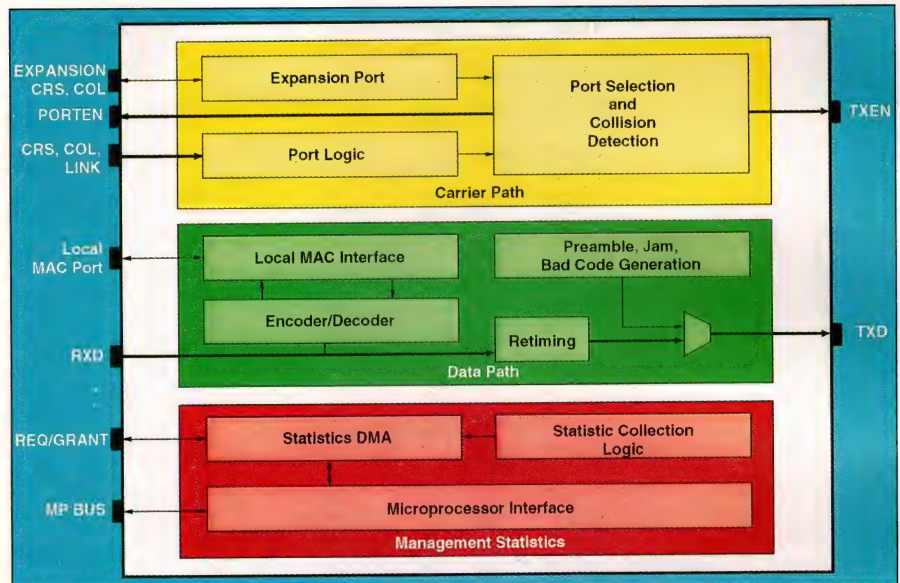The chip can handle 10 stackable repeater hubs with 13 repeater ports on each hub and thus handles the popular repeater model that uses 12 ports of a primary fast-Ethernet connection. You can use the other port as a translational port that handles other connections or a fiber-optic uplink. Using this repeater model in a 10-stacked hub configuration, manufacturers can support 130 ports



**The BCM5012 100BaseT repeater controller has its own system-management resources.**

with various fast-Ethernet connections in a single stack.

A typical 12-port 100BaseT4 repeater-hub application uses a BCM5012 and 12 of the company's BCM5000 chips. The single-chip BCM5000 handles 100BaseT4, 10BaseT, and 10BaseT full-duplex Ethernet on CAT 3, 4, and 5 UTP cable. The company uses DSP for

adaptive equalization. DSP enables 100BaseT4 connections to achieve an S/N ratio that's 3 dB better than that of the ideal linear analog method. The BCM5012 comes in a 208-pin PQFP and costs \$108 (1000).

—by John Gallant  
**Broadcom Corp.**, Los Angeles  
CA. (310) 443-4490.

**Circle No. 451**

## Spread-spectrum IC is core of transparent-modem link

Using techniques of narrowband FM along with analog circuitry, Wireless Logic's WLT9009 can serve as the core of a full-duplex wireless link. A complete system using this IC functions as a 900-MHz spread-spectrum wireless link, interfacing between a roving unit (such as a PC) and a wired modem. It is transparent to both link endpoints and supports modem modulation and protocols up to 19.2 kbps. Application range is several hundred meters, even within buildings.

(continued on pg 22)




**12 Bits, 1  $\mu$ A, 3 V – 5 V**

# At 200 kSPS, You Can Now Make Your Low-Power ADC Decision Very Fast.

Introducing the AD785x, the first family of 12-bit ADCs to combine the high performance, minimal power consumption, small package size and low cost required for today's portable applications.
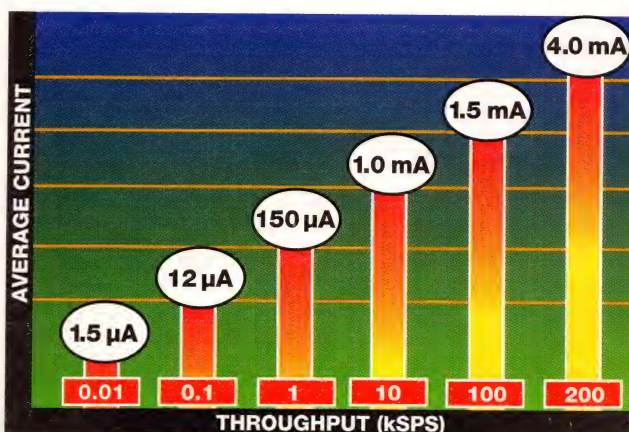
## More Samples per $\mu$ A

As the chart shows, the AD785x series delivers excellent throughput with negligible current consumption – up to twice the samples per  $\mu$ A as the competition. In addition, the partial- and full-sleep modes enable you to bring power consumption to an absolute minimum. Whether your system calls for 3-V or 5-V operation, all members of the AD785x family offer the industry's best throughput-to-current ratio.



put, micropower consumption, programmable serial or a parallel interface, single or eight chan-

	AD7853/L	AD7858/L	AD7854/L	AD7859/L	AD7896
Throughput (kSPS)	200/100	200/100	200/100	200/100	100
Power @ 3 V (mW max)	16.5/5.4	16.5/5.4	16.5/5.4	6.5/5.4	12
Supply Range (Volts)	( All are 3.3 V $\pm$ 10% & 5 V $\pm$ 10% )				2.7-5.5
Channels-Interface	1-Serial	8-Serial	1-Parallel	8-Parallel	1-Serial
Smallest Package	24-SSOP	24-SSOP	28-SSOP	44-PQFP	8-SOIC
Price* (\$)	8.95/6.45	9.85/6.95	9.35/7.45	11.60/8.75	6.75

nels, no one offers you more choices, more affordably, than Analog Devices.

To determine which ADC is best for your application, and to request a data sheet and a sample, our new

## System Calibration


Self- and system-calibration features, including autocalibration on power-up, ensure accurate operation over temperature and time. Add in superior ac/dc characteristics like 70 dB SNR and  $\pm 0.5$  LSB INL, and you also have an ideal ADC for instrumentation applications.

## More Choices – By Far

Whether your design calls for higher through-
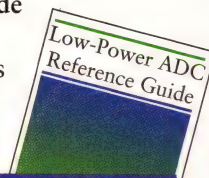
## Low-Power ADC Reference Guide

is the place to start. To receive a copy, contact the Analog Devices office or sales representative listed below.



**For a Low-Power ADC Reference Guide with sample and technical information, contact the Analog Devices office or sales representative listed below.**



Analog Devices Europe: Austria (222) 88 55 04-0, Belgium (3) 2482619, Denmark (42) 84 58 00, France (1) 46744500, Germany 089/57005-0, 030/391 90 35, 04181/80 51, 0221/68 60 06, 0711/88 11 33, Israel (9) 911 415, Italy (2) 665 00 120, (11) 24 87 789, (6) 86 200 306, Netherlands (1620) 815 00, Sweden (8) 282 740, Switzerland (1) 820 01 02, (21) 803 25 50, United Kingdom 0932 266000

\* USD 1,000s, recommended resale, FOB U.S.A.



Using this chip, user data modulates a high frequency via a VCO, and the VCO output mixes with a pseudorandom-noise (PN) sequence. The result is a biphase FM signal. The corresponding receiver down-converts the FM signal and then demodulates it back to baseband. Unlike baseband despread techniques, which result in relatively wide, 4-MHz signals that are open to noise and hard to filter, this RF despread provides superior noise and range perfor-

mance, with 30-kHz IF reducing interference energy. Process gain is 23 dB.

The WLT9009 spread-spectrum signal processor contains two PN sequence generators, with 2048- and 8192-bit sequence lengths, and has a patent-pending frequency-diversity scheme for increased robustness. The device comes in a 64-lead PQFP and costs \$16 (10,000).

—by Bill Schweber

**Wireless Logic Inc,**  
San Jose, CA. (408) 246-1538. **Circle No. 452**

## Visual-media accelerator employs 170-MHz RAMDAC

Cirrus Logic bases its new CL-GD5462 64-bit visual-media accelerator on a 500-Mbyte/sec memory architecture. The device lets a PC simultaneously display three video windows at 30 frames/sec with high-resolution graphics. The 64-bit graphics engine includes a 170-MHz RAMDAC and offers a 500-Mbyte/sec memory bandwidth. The chip also has dual 170- and 250-MHz programmable clock synthesizers to support noninterlaced graphics resolution as high as 1600×1200 pixels. It also handles color depths as high as 32 bits/pixel, which includes 24-bit true color with an 8-bit alpha channel. The chip supports vertical refresh rates greater than 85 Hz.

Standard features include support for Peripheral Component Interconnect (PCI) 2.1 and VL bus interfaces with optimization for PCI burst modes, plug-and-play compatibility, "green-PC" power-management functions, and support for a multimedia interface.

You can scale all display windows in X and Y directions from icon size to full screen, and you can arbitrarily occlude—position and overlap—video windows anywhere on the screen. The chip also converts YUV-encoded data to RGB data for PCs. The CL-GD5462 costs \$49 (1000).—by John Gallant

**Cirrus Logic Inc,** Fremont, CA. (510) 226-2123. **Circle No. 453**

## 50M-sample/sec arbitrary-waveform generator doubles as 64-bit pattern generator

Deep within most arbitrary-waveform generators lies the heart of a digital pattern generator. Only a few vendors provide hardware that lets you unlock the pattern-generation capabilities, however. Also, most waveform generators that produce digital patterns create rather narrow ones. In the case of Wavetek Corp's Model 296, though, the patterns can be 64 bits




A graphics screen and graphical user interface simplify waveform creation and editing with Wavetek's Model 296 four-channel, 50M-sample/sec arbitrary-waveform generator. The generator can also function as a generator of 64-bit-wide digital patterns or of waveforms and patterns simultaneously.

wide. That's because the 50M-sample/sec generator has four independent channels, and you can phase-lock their variable-frequency clocks. Each channel can generate 12-bit-resolution analog waveforms or 16-bit-wide digital patterns, so you can simultaneously create analog waveforms and digital patterns. Maximum waveform amplitude is 15V p-p (80V p-p optional).

Each channel has a 128k-word-deep pattern memory; a 512k-word-deep memory is optional. To effectively increase the pattern depth still further, you can divide the memory into waveform segments and link up to 4095 segments into one waveform. You can also create complicated waveforms by summing the outputs of two or more channels on the internal bus. The generator can download waveforms via its floppy-disk drive or RS-232C and IEEE-488 interfaces. A built-in graphics screen and mouse-controlled graphical user interface simplify waveform creation and editing. \$7245.

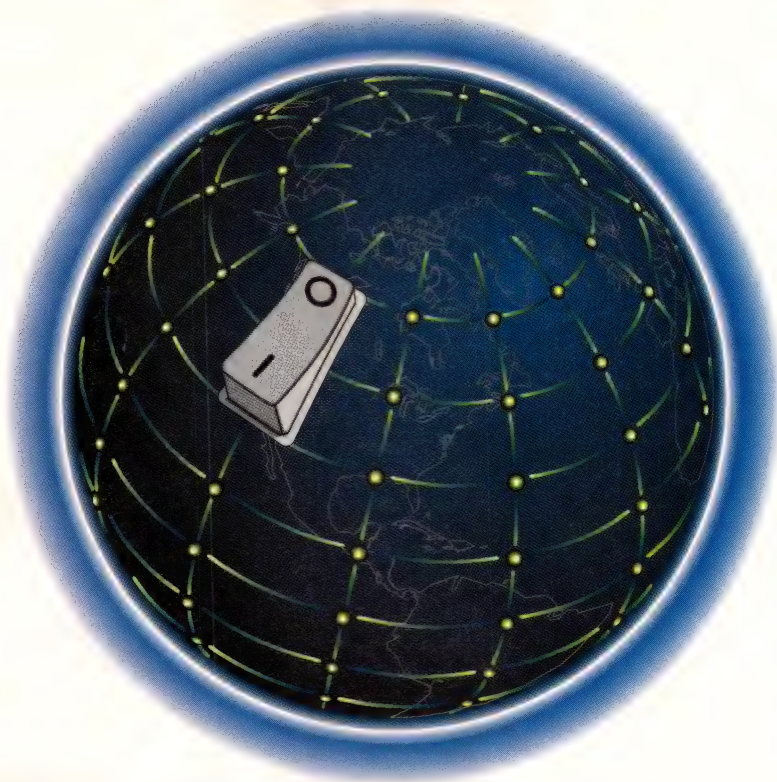—by Dan Strassberg  
**Wavetek Corp,** San Diego, CA. (619) 279-2200.  
**Circle No. 454**





## Turn yourself on... to on-line, real-time technical assistance and product sourcing.

With **HAMILTON HALLMARK'S** new home page on the Internet Worldwide Web – the only address on the **INTERNET** for on-line designs, technical assistance, plus product sourcing in real-time.

Design engineers can dial up Hamilton Hallmark's home page **24 hours a day, 7 days a week** to access valuable information such as **reference designs, application notes and product cross references**. Receive on-line design advice from the staff of experienced design engineers at our **TECHNICAL SUPPORT CENTER (TSC)**, experts in microprocessors, data acquisition, embedded controllers, programmable logic and much more.

Or, tap into our engineers' research tools: • Product data sheets • Product catalogs on CD-ROM • The IC Master Catalog • A comprehensive technical library with over 170 trade and technical journals • The TSC newsletter, featuring articles on designs built with products from the Hamilton Hallmark line card • Ready-made technical presentations

Hamilton Hallmark's new home page also offers the latest way to surf and source on the information superhighway. It provides access to industry **lead-time and pricing trends** by product commodity via Hamilton Hallmark's product planners and market barometers.

Now there's one, **instant and up-to-date source** for information that eliminates costly, time-consuming research, expedites information exchange, and helps you get product to market faster – **HAMILTON HALLMARK'S** home page. **SO BOOT UP AND LOG ON.** Because if information is power, you need a power tool. For more information on Hamilton Hallmark's home page services, call us toll-free at 1-800-605-3294, ext. H108, or on the **INTERNET:**

**<http://www.tsc.hh.avnet.com>**

HAMILTON  HALLMARK  
An Avnet Company

*We take you to the leaders.*



## Five vendors announce PCMCIA data-acquisition cards

If you judge by the number of companies introducing PCMCIA data-acquisition cards, the tiny plug-ins constitute one *hot* product category. In a recent four-week period, at least five companies announced such cards.

For example, both Intelligent Instrumentation and Soltec announced pairs of 12-bit models for \$595 each. Each unit scans eight differential inputs and takes 30k samples/sec. Each company offers one card that provides gains of 1, 2, 4, and 8 and another that provides gains of 1, 10, 100, and 1000. All of these cards provide four digital inputs and four digital outputs. The vendors also supply signal-termination units. For \$225, you can buy extra copies of Intelligent Instrumentation's unit, which includes thermocouple cold-junction com-

pensation and a voltage reference.

IOtech has announced two cards—a 12-bit unit that costs \$695 and a 16-bit unit that costs \$895. Each card takes 100k samples/sec and accepts eight differential or 16 single-ended inputs.

Keithley Metrabyte has announced three 12-bit cards, each at \$599. All accept eight differential or 16 single-ended analog signals and provide eight digital outputs and four digital inputs. Two units take 34k samples/sec and offer programmable gain (1, 2, 4, and 8 on one; 1, 10, 100, and 1000 on the other). The third unit offers a fixed gain of 1 but takes 140k samples/sec.

National Instruments has expanded its line to five cards, three of which convert analog inputs with 12-bit resolution. Of these, two take 100k samples/sec: A \$695 unit that accepts eight single-ended or four differential analog inputs also offers two DAC outputs, 24 digital I/O lines, and three counter/timers. A

\$595 unit that accepts 16 single-ended or eight differential inputs offers 16 digital I/O lines and two counter/timers. A \$395 50k-sample/sec unit that accepts eight single-ended inputs offers eight digital I/O lines and two counter/timers. Models without ADCs include a \$195 unit that provides 24 digital I/O lines and a \$325 unit that provides 16 digital I/O lines and two DAC outputs. For more information on these products, also see "Portable hardware makes experiments interactive," pg 53.—by Dan Strassberg

**Intelligent Instrumentation,** Tucson, AZ. (520) 573-0887.

**Circle No. 455**

**IOtech Inc,** Cleveland, OH.

(216) 439-4091. **Circle No. 456**

**Keithley Metrabyte,** Taunton, MA. (508) 880-3000.

**Circle No. 457**

**National Instruments Corp,** Austin, TX. (512) 794-0100.

**Circle No. 458**

**Soltec Corp,** San Fernando, CA. (818) 365-0800. **Circle No. 459**

## Flash devices target serial EEPROM

Xicor has announced samples of SerialFlash, the first commercially available serial flash memory. These devices use the serial-peripheral-interface (SPI) bus protocol or the two-wire serial interface to allow access to and writing of the memory's stored data. The devices operate at a maximum data rate of only 1 MHz, but this speed is sufficient for the EEPROM applications SerialFlash targets. Other features include a 1.8 to 3.6V program and read operation, data protection on each of four write blocks, and 0.9-mm TSSOP packaging. The serial flash is available in 8-, 16-, 32-, and 64-kbyte densities for \$2.95, \$2.50, \$1.75, and \$1.50, respectively. Xicor designates the devices as X2yF008, X2yF016, X2yF032, and X2yF064 (where y=5 for the SPI version and y=4 for the two-wire version).—by Markus Levy

**Xicor Inc,** Milpitas, CA. (408) 432-8888.

**Circle No. 462**

## Math software integrates with Lotus Notes and the World Wide Web

With its latest release, a mathematical software package that has won the hearts of engineers and experimenters turns into something unusual, if not unique—groupware for techies. **MathCad V6.0 integrates with Lotus Notes to allow work-group members to review, revise, and comment on MathCad documents and to distribute modified and annotated documents among their peers. Without leaving MathCad, you can also download and manipulate work sheets from the Internet's World Wide Web. You can merge such work sheets or portions of them into your own documents and you can follow hot links to other MathCad documents. A further benefit of compatibility with Notes is MathCad's ability to track a document's revision history.**

The new release also adds advanced visualization and animation tools and an interactive programming language based on extensible math notation. **MathCad V6.0 is a 32-bit Windows application that runs under Windows V3.1, Windows for Workgroups, Windows NT, and Windows 95. A Macintosh version of the products will appear in early 1996. MathCad V6.0 Plus Professional Edition costs \$349.95; registered users of V5.0 who wish to upgrade pay \$149.95. MathCad V6.0 Standard Edition costs \$129.95 and \$49.95 to V5.0 users who wish to upgrade.**—by Dan Strassberg

**Mathsoft Inc,** Cambridge, MA. (617) 577-1017. **Circle No. 460**



SONY

## ENABLING TECHNOLOGY.

It's the laptop of your customers' dreams. Yet it's not pie-in-the-sky. Sony has the guts – the enabling technology – for you to breakthrough now. Simply, Sony parts will make it go faster, remember more, communicate better, use less power, both take and show video pictures, playback, decompress MPEG-1 CD-ROM images, and even turn tiny LCD images into wall-size productions. Now it's up to you. Call 1-800-288-SONY.

We make the chips. You make the history.

CIRCLE NO. 16



©1995 Sony Semiconductor Company of America  
and TriStar Pictures, Inc. all rights reserved.



# EDN OUT IN FRONT

## FPGA co-processor targets embedded control

Xilinx's SRAM-based XC6200 family of field-programmable gate arrays (FPGAs) for co-processing applications is the first  $\mu$ P-compatible FPGA series for the embedded-control market. The targeted applications include high-bandwidth and computation-intensive functions, such as laser printers, video- and image-processing systems, telecommunications equipment, and encryption/decryption and encoding/decoding circuits.

Unlike conventional FPGA architectures, the XC6200 family has a standard  $\mu$ P interface, which simplifies overall hardware design. The XC6200 also includes the FastMap memory-mapped I/O interface. FastMap comprises a  $\mu$ P-compatible address bus, a data bus, and control lines. Direct access to all internal logic registers through the FastMap bus interface permits simple access by C-language application programs.

The architecture meets the in-system configuration needs of co-processor applications, in which algorithms must change in real time. Examples of these applications include wavelet compression and decompression; 27.5-MHz video compression; four-tap FIR-filter biasing; and multispectral-image enhancement. The FastMap  $\mu$ P bus interface lets you reconfigure the chip in less than 200  $\mu$ sec. The interface configures the logic array and is configurable as 8, 16, and 32 bits wide. The chip can configure as many as 32 bits in approximately 40 nsec.

The XC6200 also features distributed memory, which means that you can use a basic cell for either logic or memory. Each logic cell contributes 2 bytes of memory. With distributed memory, a device with 16,384 cells can provide 32,768 bytes of memory. The device's fast reconfiguration capability lets you dynamically change the number of cells used as logic and the number used as memory.

Each XC6200 device comprises a large array of simple 4 $\times$ 4-bit configurable cells in a fine-grained architecture that implements data-path and data-processing functions for embedded control. Cells contain a function unit that can simultaneously implement a logic function and an independent routing area for intercell communication.

Device density ranges from 8000 to 64,000 gates, making the XC6200 suitable for data-path and structured-logic designs. An 8000-gate device costs \$25 to \$30 (10,000), and a 64,000-gate device costs \$200 to \$250 (10,000).—by John Gallant

**Xilinx Inc.**, San Jose, CA. (408) 559-7778.

Circle No. 461

*Get the edge...*  
*...with Distribution Support*

### AUSTRIA

**Avnet E2000 GmbH**  
Tel. +43 1 9112847  
Fax. +43 1 9113853

**EBV Elektronik**  
Tel. +43 1 8941774  
Fax. +43 1 8941775

**Eurodis Electronics GmbH**  
Tel. +43 1 610630  
Fax. +43 1 6106215

**Spoerle Elektronik**  
Tel. +43 1 3187200  
Fax. +43 1 3692273

### BELGIUM

**EBV Elektronik**  
Tel. +32 2 7209936  
Fax. +32 2 7208152

**Farnell Electronic Services**  
Tel. +32 2 7253533  
Fax. +32 2 7254135

**Diode Spoerle**  
Tel. +32 2 7254660  
Fax. +32 2 7254511

### DENMARK

**Avnet Nortec A/S**  
Tel. +45 44880800  
Fax. +45 44880888

**GB Topcomp Electronics**  
Tel. +45 33883950  
Fax. +45 33883955

### FRANCE

**Arrow Electronique**  
Tel. +33 1 49784978  
Fax. +33 1 49780596

**Avnet**  
Tel. +33 1 49652500  
Fax. +33 1 49652769

**Farnell Electronic Services**  
Tel. +33 1 69858383  
Fax. +33 1 69858399

**Tekelec Airtronic**  
Tel. +33 1 46232425  
Fax. +33 1 45072191

### FINLAND

**GB Topcomp Electronics**  
Tel. +358 0 2994001  
Fax. +358 0 2994188

### GERMANY

**Avnet E2000 GmbH**  
Tel. +49 89 4511001  
Fax. +49 89 45110129

**EBV Elektronik Vertriebs GmbH**  
Tel. +49 89 456100  
Fax. +49 89 464488

**Farnell Electronic Services GmbH**  
Tel. +49 7141 487300  
Fax. +49 7141 487210

**Glyn GmbH**  
Tel. +49 6126 590222  
Fax. +49 6126 590111

**SASCO HED Semiconductor**  
Tel. +49 89 4611211  
Fax. +49 89 4611271

**Rein Components GmbH**  
Tel. +49 2153 7330  
Fax. +49 2153 733575

**Spoerle Elektronik**  
Tel. +49 6103 3040  
Fax. +49 6103 304201

### ITALY

**Avnet Adelsy**  
Tel. +39 2 38103100  
Fax. +39 2 38002988

**Compel S.P.A.**  
Tel. +39 362 553991  
Fax. +39 362 553967988

**Eurodis Fanton**  
Tel. +39 2 48920341  
Fax. +39 2 4597913

**Farnell Electronic Services**  
Tel. +39 2 824701  
Fax. +39 2 8242831

**Lasi Elettronica (Div. Silverstar)**  
Tel. +39 2 661431  
Fax. +39 2 66101385

### NETHERLANDS

**Diode Spoerle**  
Tel. +31 3402 91234  
Fax. +31 3402 35924

**Diode Spoerle**  
Tel. +31 40 545430  
Fax. +31 40 535540

**EBV Elektronik**  
Tel. +31 3465 62353  
Fax. +31 3465 64277

**Farnell Electronic Services**  
Tel. +31 79 613161  
Fax. +31 79 613169

**Rein Elektronik B.V.**  
Tel. +31 40 431775  
Fax. +31 40 435522

### NORWAY

**GB Topcomp Electronics**  
Tel. +47 66841815  
Fax. +47 66841917

### SPAIN

**Lober S.A.**  
Tel. +34 1 3102925  
Fax. +34 1 3104797

**Unitronics S.A.**  
Tel. +34 1 542504  
Fax. +34 1 5427896

### SWEDEN

**GB Topcomp Electronics**  
Tel. +46 8 7574175  
Fax. +46 8 7574798

### SWITZERLAND

**Avnet E2000 GmbH**  
Tel. +41 1 7221330  
Fax. +41 1 7221340

**EBV Elektronik**  
Tel. +41 1 7401090  
Fax. +41 1 7415110

**EBV Elektronik**  
Tel. +41 21 3112804  
Fax. +41 21 3112807

**Eurodis Electronic A.G.**  
Tel. +41 21 3112804  
Fax. +41 1 8433475

**Fabrimex Distribution A.G.**  
Tel. +41 24 218141  
Fax. +41 24 219222

**Fabrimex Spoerle A.G.**  
Tel. +41 1 8746262  
Fax. +41 1 8746200

**Farnell A.G.**  
Tel. +41 1 2046111  
Fax. +41 1 2046454

### UNITED KINGDOM

**Abacus Group**  
Tel. +44 1635 33311  
Fax. +44 1635 38432

**Arrow - Jernyn**  
Tel. +44 1234 270777  
Fax. +44 1234 214674

**Avnet Access**  
Tel. +44 1462 480888  
Fax. +44 1462 488567

**Farnell Electronic Services**  
Tel. +44 1279 626777  
Fax. +44 1279 441687

**HB Electronics**  
Tel. +44 1204 525544  
Fax. +44 1204 384911

### Toshiba European Headquarters:

**Toshiba Electronics Europe GmbH**

Hansaallee 181  
D-40549 Düsseldorf  
Tel: +49 211 52960  
Fax: +49 211 5296400

**Toshiba Electronics (UK) Ltd**  
Tel: +44 1276 694600  
Fax: +44 1276 694800

**Toshiba Electronics Scandinavia AB**  
Tel: +46 8 7040900  
Fax: +46 8 808459

**Toshiba Electronics France S.A.R.L.**  
Tel: +33 1 48124812  
Fax: +33 1 48945115

**Toshiba Electronics Italiana S.R.L.**  
Tel: +39 39 68701  
Fax: +39 39 6870205

**Toshiba Electronics Espana S.A.**  
Tel: +34 1 660 6700  
Fax: +34 1 660 6799

In Touch with Tomorrow  
**TOSHIBA**



# Get The Edge in OPTO

## COUPLERS

Technology leadership is our business - and it shows.

Toshiba extends the frontiers of innovation in semiconductor technology. As one of the world's leading Opto manufacturers, we provide high-reliability solutions that offer the optimum performance/price ratio for your design.


Take our Photo Couplers. Toshiba was the world's first to offer an SMD outline, and still offers the widest line-up available today to complement industry-standard SIL and DIL package styles.

With acknowledged high reliability, resulting from the latest volume production techniques, and all international safety approvals - UL, VDE, BSI and Semco - you can see why Toshiba couplers really are the "quality" choice.

Specify Toshiba Photo Couplers, and you automatically build in a competitive advantage.

CIRCLE NO. 5

In Touch with Tomorrow  
**TOSHIBA**

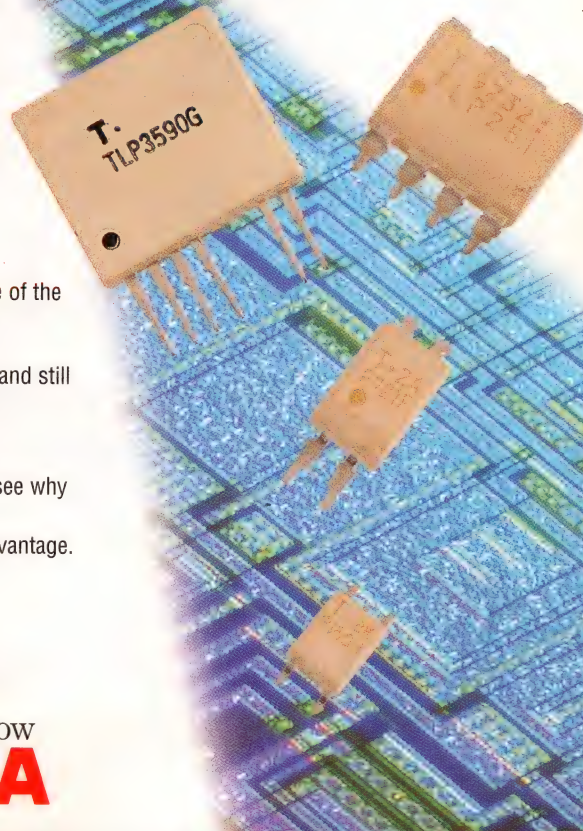







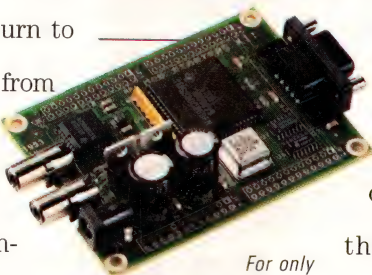
## Accelerate performance while reducing costs.



When driving toward real-time processing and cost-effective functionality at the best value, turn to Digital Signal Processing Solutions from Texas Instruments. With TI DSP Solutions, you have the raw processing power available to compress/decompress information as well as encode and decode at rates required for real-time audio and video applications. Like cellular communications, modems, multimedia audio, voice recognition, imaging and videoconferencing.



*For only \$99, you can get the TI 'C2x DSP Starter Kit. It offers you a low-cost, easy-to-use tool for initial understanding of TI DSP Solutions. And includes board, assembler and debugger software, sample programs and documentation.*

real-time processing. Combine them with our Mixed-Signal DSP peripherals that have optimised interfaces, I/O ports and addressing features for accessing real-world data. And you can create price/performance solutions that will help you win in today's marketplace. For example, TI has DSP and Mixed-Signal Solutions for your applications from as little as \$10.\*

**Test-drive the TI TMS320C2x DSP Starter Kit for \$99.** TI DSP Solutions can help you stay ahead on the price/

**DSP Solutions from \$10 to 2 Billion Operations Per Second.** Select from over 100 TMS320 DSPs that were created specifically for

performance curve. For more information on the 'C2x DSP starter kit, please circle the reader service number below.



Cellular Phone

	1988	1995
Talk Time	2 hours	3 hours
Size	8"x3"x2"	5.5"x2.3"x1"
Weight	2 pounds	0.5 pound



Digital Telephone Answering Device

	1988	1995
Reliability	Tape-Based	Solid-State
Caller ID	No	Yes
Mailboxes	No	Yes



Fax Modem

	1988	1995
Baud Rate	2,400 bps	28,800 bps
Capability	Data/Fax	Data/Fax/Voice
Format	PC Half Card	PCMCIA



Hard Disk Drive

	1988	1995
Access Time	60 ms	12 ms
Size	3"x6"x8"	5.8"x4"x0.9"
Density	20 Mb	400 Mb

EXTENDING YOUR REACH™

 **TEXAS  
INSTRUMENTS**

\* Pricing, U.S. dollars, in quantities of 10,000.  
© 1996 TI



# DELIVERING THE HIGH-SPEED CLOCK:

## IT'S NOT EASY TO BE ON TIME


BILL SCHWEBER, TECHNICAL EDITOR

**T**he high-speed clocks that are the pulses of today's processor-based circuits rank after dc power as the second most widely distributed signal in the system. Ironically, though, they are at the opposite end of the frequency spectrum from power. They are timing pulses—the minimal essence of digital information—but their ~100-MHz rates mean they are subject to all the vagaries of the stormy analog world.

Yet, reliable clock generation and distribution are critical in your high-performance PC or communication system. Clock-related failures are notoriously intermittent, varying with temperature, power-supply rails, internal loading, and many other hard-to-quantify factors. If your clocks aren't up to spec, you'll be chasing seemingly unrelated and irreproducible failures in the memory, I/O, CPU, and other areas.

Good clock system design

is neither easy nor magical. It requires you to use basic engineering techniques carefully and thoroughly for error budgeting, worst-case analysis, verification, layout consideration, power and grounding, and minimizing noise. To these problems, add refusing to cross your fingers and hope for the best, because timing margins are too tight for you to rely on good luck. The reality is that a *statistically stable*

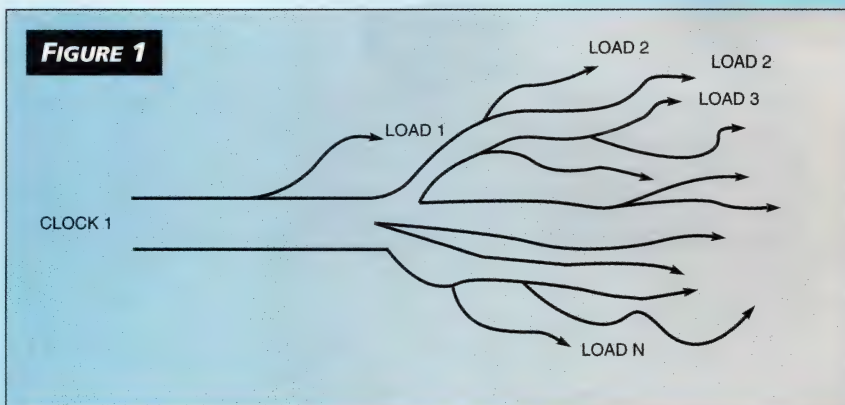

Signal distribution has a simple goal: to ensure that clock signals reach all ICs within a specified amount of skew.





For the digital system clock in high-speed processors, being late—or even being early—causes serious system problems. By doing your homework and not taking design risks, you can ensure that your clock edges make their transitions in the right time window.

Illustration by Gregg Dinderman



## HIGH-SPEED CLOCKS

design, with guaranteed clock generation and distribution timing, is achievable: The proof is the millions of reliable PCs in use, with their relatively low soft-failure rates.

### Start by mapping your needs

Keep in mind your fundamental objective: to ensure that your system's ICs get their needed clocks without waveform degradation in sufficiently close synchronization (small enough skew) with respect to each other. Start by making a clock-load inventory: what clock frequencies does your system need for which functions (memory, CPU, I/O, and so on) and locations (which ICs and where they reside)? A typical Pentium-based PC needs processor, Peripheral Component Interconnect, a floppy-drive-adaptor, keyboard-controller, and system-reference clock frequencies.

The CPU clock usually has the highest frequency in the system, but high-resolution video-display circuitry can have comparable or higher clock rates. As CPU speeds increase (Table 1), their designers realize that it's unrealistic to expect a more-than-100-MHz signal to reach the CPU with proper timing and integrity. Above 50 to 100 MHz, switching noise becomes a major problem. Instead, CPUs incorporate an internal PLL to multiply the supplied clock rate up to the desired internal frequency or frequencies. For example, the PowerPC 601 CPU from Apple, IBM, and Motorola internally derives its 245-MHz clock from a supplied 75-MHz clock. Result: At the cost of a little extra internal silicon, the CPU and its various subsections come with clocks, taking some of the burden off you. Table 2 lists some representative clocks.

Your design challenge is to make sure that all clocks in the system are properly timed with respect to the CPU clock. Working against this objective are the laws of physics: Differing propagation time, or "time of flight," in each path leads to skew in

**TABLE 1—PROCESSORS AND THEIR BUS-CLOCK RATES**

Vendor	Processor	Clock rate (MHz)
Apple/IBM/Motorola	PowerPC	80
Digital Equipment Corp	Alpha	>100
Intel	Pentium	60, 66
Intel	P54C	99
Intel	486	66, 99
Mips	R4400SC	150

signal-arrival times among the loads.

Skew is analogous to a fixed offset (see box, "Simple function, but unusual specs"). As long as time of flight remains constant, you can design in suitable delays to equalize it properly (deskw) in all branches. The real problem is the jitter—minute, apparently random variations in skew. Jitter comes from unavoidable variations in propagation delays due to component tolerances, power-supply and other noise, pc-board variability, and other factors. A buildup of jitter can soon overwhelm your relatively small skew-tolerance budget. Even production device-to-device variation, normally not a major concern for circuit designers, is an issue you must take into account.

At the same time, you have to maintain signal fidelity and integrity throughout, with a clock waveform at the load that has essentially the same waveshape, including rise and fall times, slew rates, and overshoot and ringing, as it has at the source. To make matters worse, fast slew rates and sharp waveform corners also generate EMI that can affect adjacent circuit performance and cause you regulatory-approval difficulties.


### Live within a budget

Once you define your system needs, work on a distribution strategy. Here's where the serious engineering work begins. You lay out a tree, branch, and leaf topology (Fig 1) that provides required clock signals in the right places. A large computer system can have half a dozen levels of intermediate buffering in contrast to a single-board PC, which can have just one buffer level.

You then begin work on timing analysis and error budgets, so that signals emerge from all distribution leaves at precisely the same time. Although the conceptual schematic of signal distribution goes in a "straight line" from a source through all branches to the loads, most layouts physically implement this schematic as a radial pattern

to roughly equalize signal-path lengths. Eventually, you must more precisely equalize signal-path lengths, but a radial design is a starting point. Your constraint is the longest path delay for the clock; you must delay all other signals to match this time.

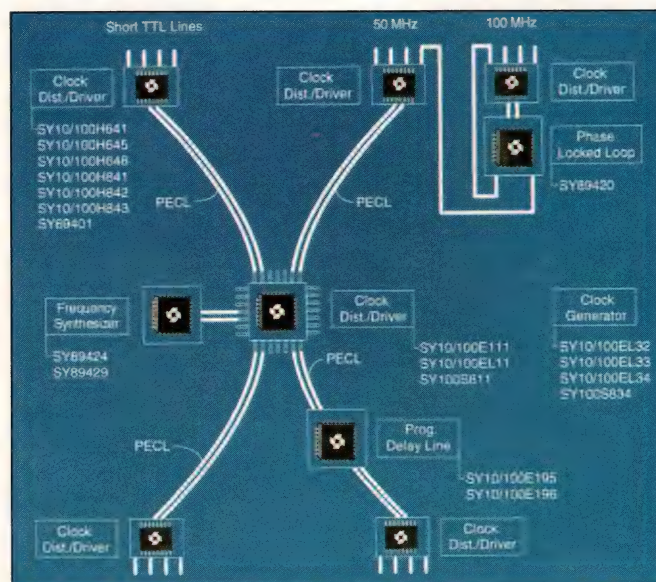How much precision in the delay is enough depends on the specifications for the processor and peripheral functions. Typically, you have only a few hundred picoseconds or less of skew allowance between clocks at the various loads. Skew comes from differences in physical path lengths, as well as propagation delays within the active components. The speed of light in a



**The complete distribution network comprises clock sources, drivers, buffers, and delay elements, in some cases using mixed IC technologies. (Courtesy of Synergy Semiconductor Corp.)**



vacuum is  $\sim 1$  ft/nsec (30 cm/nsec), and signal-propagation speed on a circuit board is roughly one-half that figure. Figured as a propagation delay, this corresponds to delays of 150 to 200 psec/in. (60 to 80 psec/cm).

Skew specs are tight when 1.5 nsec is 10% of a 66-MHz clock-cycle time. With the skew absorbing so much of your clock-cycle time, little timing margin is left at the load. To meet this reduced margin, you may have to use more costly 8-nsec DRAMs in place of less expensive 12-nsec devices, for example. According to Ref 1, you cross a threshold of significantly increased design difficulty when you have more than 10 board-level clock loads combined with a tolerance budget that is less than 10% of the clock period.

### Starting the signal

A typical system needs multiple copies of each clock frequency. For a

representative Pentium-class chip set, you likely need four copies of the processor clock, six of the PCI bus clock, two of the system-reference clock, and one each for the floppy-drive adapter and keyboard controller—a total of 14 clocks. A PLL-based oscillator (Fig 2), such as Integrated Circuit Systems' ICS9159C-02, Cypress Semiconductor Corp's CY2254, IC Works' W48C60-402, or Integrated Device Technology's IDT74FCT3907, provides all 14 signals from a single 14.31818-MHz crystal, the de facto standard crystal frequency that most PC clock ICs use.

If the PLL provides all the signals you need, then your task is relatively simple: Work out the propagation times to the loads on your circuit board without intermediate active components—the basic time-of-flight calculation. Then, determine what compensating delays you need. At these clock rates, you

most likely use transmission-line techniques for interconnection on your circuit board beyond a few inches of travel to maintain signal-shape integrity and to control propagation speed.

Stripline or microstrip layout (Fig 3) gives a fixed-impedance path, with propagation velocities you can calculate. The actual speed is a function of the nominal speed and the load at the end of the line, so factor that in, as well. Design impedances of 60 to 70  $\Omega$  are common, with signal velocity of 0.55 to 0.6  $c$ .

The distribution net for a simple and common point-to-point topology looks like a set of series-terminated transmission lines driving single loads (Fig 5). For first-order analysis, add the propagation delays to find the slowest path and minimize sources that cause delays on the faster clock paths or speedups on the slower ones. Use the skew and clock-arrival tolerance data to

## SIMPLE FUNCTION, BUT UNUSUAL SPECS

As with so many other specialties, clock generation and distribution has its own subculture of critical specs. The Joint Electronic Device Engineering Council's Standard 99 defines the following four basic types of skew for clock drivers:


- **Input skew:** the difference in propagation delay for a defined device output, originating from more than one input to the device; this skew is typically used with multiple-input gates.

- **Output, or pin-to-pin skew:** the difference in propagation delay between fastest and slowest outputs on a single device with a single input.

- **Pulse skew:** the difference between the propagation delay of the high-to-low and low-to-high transitions on the same output for a device at identical operating conditions; this skew lets you quantify the output clock's duty cycle and pulse-width distortion.

- **Process, or part-to-part skew:** the difference in propagation delay between outputs on two identical devices with a common clock under defined conditions.

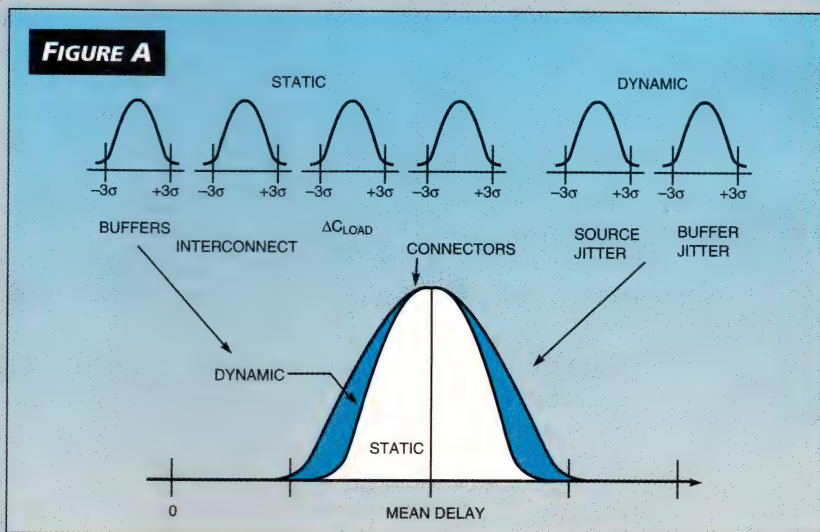Although skew is statically distributed, or time-invariant, you also must contend with dynamically distributed, or time-variant jitter. In time-variant jitter, the signal edge varies from



**Jitter adds to static delays, broadening the uncertainty in clock-edge arrival time at the load.**

one cycle to the next as a result of shifts in the IC's switching threshold. These shifts, in turn, are due to power and ground noise and temperature and supply variations. Jitter—a statistical broadening of the distribution of edge location—normally increases when noise increases or the edge rate of an input to a buffer decreases (Fig A).



# TABLE 2—REPRESENTATIVE CLOCKS

Vendor	Device no.	Name	Description	Features
<b>Applied Micro Circuits Corp</b> Circle No. 315	SQ4406Q	PLL clock generator	12 outputs (three groups of four)	20 to 60 MHz out; 2x, 1x, 1/2x clock; each group: separate power-down; various lead/lag options
	SC3327S	10-output driver	Three outputs at input frequency; seven at one-half frequency	80 MHz, 24-mA drive, 3V, internal series resistor
	SC3368S	14-output driver	Six outputs at input frequency; eight at one-half frequency	Similar to SC3327S
<b>Cypress Semiconductor Corp</b> Circle No. 316	CY2291	Three-PLL clock generator	Eight outputs: four fixed, four configurable	Factory EPROM custom-rate versions, 30 frequency options, selectable shutdown, smooth ramping from 4 to 100 MHz
	CY7B9910 (TTL), CY7B9920 (CMOS) CY2254	Low-skew clock buffer	Generates eight copies, PLL for low skew 1	5 to 80 MHz; 250-psec skew, 500-psec propagation delay, 1-nsec device skew
		Pentium clock synthesizer/driver	14 clock outputs: four CPU, six PCI, one floppy, one keyboard, two reference	3.3V, 200-psec jitter, 200-psec skew (CPU clocks), 500-psec skew (PCI clocks)
<b>IC Works Inc</b> Circle No. 317	W42C27	CPU-frequency generator	Dual output for Pentium and PCI bus	3.3 or 5V, also supports Fibre Channel-Arbitrated Loop with 106.25-MHz output
	W40C06A	Six-output buffer	DC to 66 MHz, each output drives one or two 50Ω lines	3.3 or 5V supply, integral oscillator, 48-mA drive
	W48C60-402	Pentium/PCI bus synthesizer	14 clock outputs: four CPU, six PCI, one floppy, one keyboard, two reference	3.3 or 5V operation
<b>Integrated Circuit Systems Inc</b> Circle No. 318	ICS9159C-02	Clock generator and integrated buffer	14 clock outputs: four CPU, six PCI, one floppy, one keyboard, two reference	100 MHz (5V) or 66 MHz (3.3V), CPU- and bus-clock rates separately selected
	ICS9178-02	Frequency-timing generator for Power PC	14 clocks: two 2x PECL CPU, one TTL CPU; 10 selectable bus	5V: 75 to 245 MHz, 3.3V: 60 to 170 MHz
	ICS9159-07	Frequency-timing generator for NexGen Nx586 CPU	13 outputs: three CPU, seven PCI, one reference, one floppy, one keyboard	Smooth frequency transition for green operation, choose nine clock rates, 65 MHz
<b>Integrated Device Technology Inc</b> Circle No. 319	IDT74FCT3907	PC-clock synthesizer	14 clock outputs: four CPU, six PCI, one floppy, one keyboard, two reference	3.3V, pin-selectable CPU clock at 50/60/66 MHz, 200-psec skew (CPU clocks), 500-psec skew (bus clocks)
	IDT74FCT3932	PLL-based CMOS clock driver	17 three-state outputs: four, eight, five/bank	3.3V, 16 programmable frequency configurations, up to 100 MHz
	49FCT805T series	Low-skew clock driver for datacomm	Dual 1-to-5 output multiplexer	TTL input/output; 3.3, 5V versions; selective shutdown; inverting, noninverting versions
<b>Micro Linear Corp</b> Circle No. 320	ML6500	Programmable adaptive clock manager	PLL clock, eight outputs	Adaptive deskew buffers via feedback, 10- to 80-MHz range, 5-nsec deskew range
	ML6510	Programmable adaptive clock manager	PLL clock, eight outputs	Deskew via reflected waveform; to 130 MHz; 3, 5V outputs
	ML65244	Dual/quad-buffer line driver	Two groups of four outputs	TTL compatible, 1.5-nsec propagation delay
<b>Motorola Inc</b> Circle No. 321	MC100LVE111	Low-voltage one- to nine-line clock driver	Differential input and output, ECL/PECL	50-psec output skew, 75Ω pulldown resistors
	MPC950	Low-voltage PLL clock driver	Nine output, crystal or external reference	Outputs to 250 MHz, output skew 350 psec
	MPC974	PLL clock driver	15 outputs (Three banks of five each)	Can switch between two source-reference clocks' output ratios 1-to-1, 2-to-1, 3-to-1, 3-to-2, 3-to-2-to-1
<b>National Semiconductor Corp</b> Circle No. 322	CGS74CT2524 family CGS700	One to four fan-out clock driver PLL 1-to-9 CMOS clock driver	Family of four devices, 300-psec output skew Fan-out of 9	5V operation, 24-mA drive, eight-pin package; CGS74LCT2524 series is 3V, 12-mA output
	CGS2534V family	Quad-memory-array clock drivers	Four inputs, 16 outputs, to 125 MHz	25 to 160 MHz; 30-mA drive; outputs at 1x, 2x, 4x reference, internal loop filter
				Various inverting, noninverting combinations; output structures, two output (CGS2536)
<b>Quality Semiconductor Inc</b> Circle No. 323	QSS917T-70T, -100T, -133T	CMOS PLL clock driver	Four outputs: Q0-Q4, 2xQin, Qin/2, Q5	Integral loop filter, 70/100/132-MHz clock; 24-mA output drive
	QSS5805T, QSS2805T	CMOS clock driver/buffer	10 outputs: five inverting, five noninverting	5V, 5280x series has 25Ω series resistor for driving unterminated lines
<b>Synergy Semiconductor Corp</b> Circle No. 324	SY89424	Frequency synthesizer	PLL-based, single-output clock to 1 GHz	12.5 to 25 times crystal frequency, selectable
	SY10H842	PECL to TTL one- to four-line clock driver	Single PECL input to four TTL outputs	24-mA output, 1-nsec pin skew, TTL, PECL grounds
	SY10E195	Programmable delay line	2-nsec range, 20-psec steps	Can be cascaded to increase delay range, E196 has analog input for finer resolution
<b>Texas Instruments Inc</b> Circle No. 325	CDC586, CDC2586	3.3V clock driver	12 outputs, up to nine can be selected to run at one-half or two times input frequency	50 to 100 MHz, CDC2856 has internal 26Ω resistor, TTL-compatible inputs and outputs
	CDC351, CDC2351	3.3V, one- to 10-line clock driver	Distribute clock to 10 outputs	32-mA drive, low-voltage-TTL-compatible, output enable control, CDC2351 has internal 26Ω resistor



## Price

\$9 (10,000)

\$3 (10,000)

\$3.50 (10,000)

\$2.28 (10,000)

\$4.95 (10,000)

\$3.10 (10,000)

\$1.12 (10,000)

\$1.09 (10,000)

\$2.87 (10,000)

\$2.95 (10,000)

\$6.95 (10,000)

\$2.90 (10,000)

\$2.85 (10,000)

\$3.95 (10,000)

\$2.60 (10,000)

\$14 (1000)

\$24.25 (1000)

\$7 (1000)

\$20.13 (10,000)

\$10.43 (10,000)

\$13.24 (10,000)

\$1.26 to \$1.90 (1000)

\$5.35 (1000)

\$5.35 (1000)

\$9.25/\$11.57/\$1388 (1000)

\$5.74/\$6.72 (1000)

\$17.85 (1000)


\$8.75 (1000)

\$18.45 (1000)

\$8.84 (1000)

\$4.02 (1000)

FIGURE 2

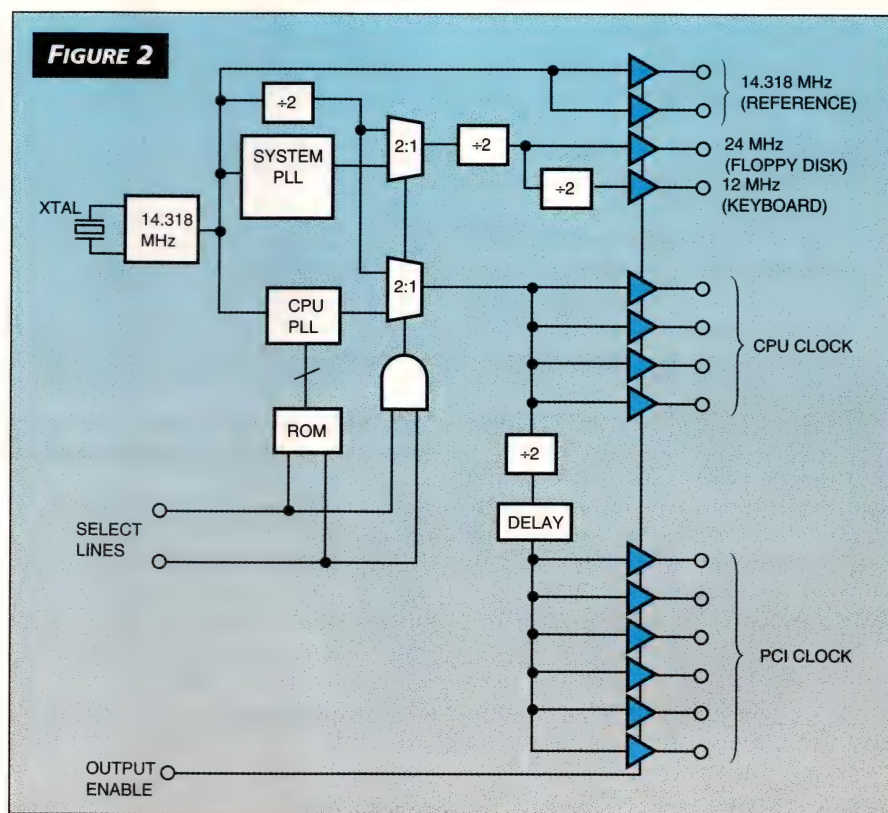

From one crystal, a single PLL can provide all necessary clocks for a PC chip set.

determine your maximum allowable jitter, as follows:

$$\text{tolerance} \geq \text{intrinsic skew} + \text{extrinsic skew} + \text{jitter}$$

or

$$\text{jitter} < \text{tolerance} - \text{intrinsic skew} - \text{extrinsic skew}$$

IC data sheets and specifications for the various loads provide tolerance data and intrinsic output skew. For example, the Pentium specification requires that the clock difference between the CPU and the cache controller be less than 200 psec, and timing between other system functional blocks has similar specifications. Extrinsic skew comprises the sum of variations in the propagation delay of a signal through a loaded transmission line with various loads plus tolerances in the interconnect due to manufacturing variations. Rise and fall times typically slow by 0.5 to 1 nsec per 10 pF for 10- to 50-pF loads. Typical values for interconnect tolerances range from 1 to 50 psec/in. times the length of the interconnect. Ref 1 provides the for-

mulas and IC-vendor application notes.

### Buffers, PLLs offer choices

Once you design your clocks, the real challenge begins. Whether you need more clock copies, clock regeneration for signal integrity, or distribution across a multiboard system, you have two choices: a buffer or a PLL. Each has advantages and shortcomings. You may carefully mix both in a system for the best performance, cost, and reliability trade-off. Also, analyze whether a signal driver should drive more than one load. Point-to-point layout requires more buffers or PLL outputs than using one driver for multiple loads. However, point-to-point layout minimizes tolerancing from variations in load capacitance. Load variations cause timing variations, which increase as the number of loads on a driver increases.

Buffers tend to be lower cost and easier to use than PLLs. A single multi-channel buffer can handle different




## HIGH-SPEED CLOCKS

clock signals, thus easing board layout; many buffers allow you to parallel their outputs for increased drive. In addition, some buffers, such as Applied Micro Circuits Corp's SC3368S, National Semiconductor Corp's CGS2536V, and Texas Instruments Inc's CDC586 family, also provide basic divide-by-2 functions for a half-rate output, which is useful for some systems. As "digital" functions, buffers are somewhat more resistant to supply-rail noise than are PLLs with their closed-loop operation.

Buffers have their drawbacks, however. For example, they have both propagation delay and jitter in the delay. They also have part-to-part and channel-to-channel differences. They also can provide only copies or half-rate versions of the input, so that you need a buffer for each clock frequency.

PLLs offer two features that simpler buffers lack. Due to a PLL's phase-locking servomechanism, the PLL produces a synchronized original rather than a mere regenerated copy, and its output has zero delay with respect to the input. Some PLLs allow you to add some calibrated delay to compensate for delays elsewhere. In addition, PLLs can use internal dividers to produce outputs that are multiples and submultiples of a master clock, and these other clocks can be in noninteger ratios from the master.

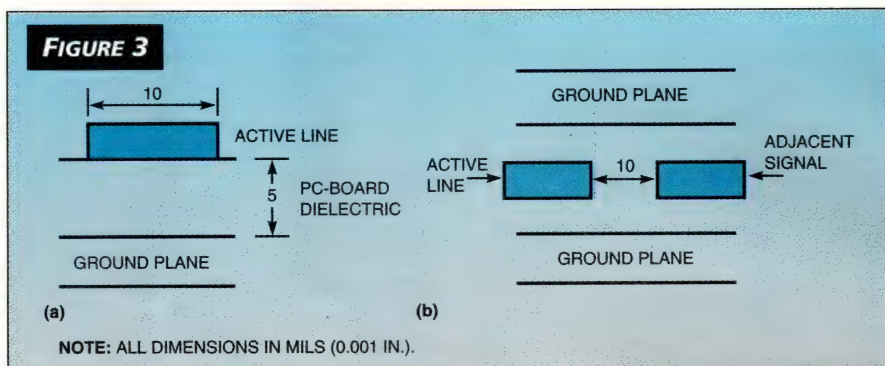PLLs can also help when you don't have control of critical-path signal timing. For example, final timing specs for an ASIC may not be available until relatively far into the design cycle. Fortunately, a PLL can effectively minimize



**Stripline (a) and microstrip (b) trace layouts give you characterized impedance and propagation delays; typical dimensions are shown.**

within a broad span any timing error in the ASIC.

Despite these virtues, PLLs bring new concerns. For example, noise on their supply rails and inputs affects PLLs more than it does buffers. Because PLLs have active, closed-loop functions, this noise and other noise, such as crosstalk, can cause "noise multiplication," unanticipated modes of interaction and unexpected spectral components. Application of PLLs requires both designers and IC vendors to have a thorough understanding of the devices' dynamics and characteristics.

Although using multiple PLLs in a large system seems to solve many problems, such as the need for zero delay and multiple clocks, subtle interactions can develop between the PLLs, especially when their bandwidths are incompatible. Keep power rails clean and keep noise out. Achieving these goals requires good filtering, bypassing, and grounding. Use local power regu-

lation in areas in which you anticipate that passive techniques will not suffice.

### Collect the facts

Whether you do your initial analysis with pencil and paper, a spreadsheet, or electronic-design-automation modeling tools, you need timing data. (See box, "Tools and models offer help—with limitations.") Manufacturer data sheets are vital not only for basic timing specs, but also for information about delays and jitter within an IC and all production units of the IC. Here's where you have to be careful: Check on the quality of this data by looking at test reports. Determine whether specs are based on samples of a few or many production units. Identify which sampling techniques the manufacturer uses for maximum and minimum specs. Find out whether the devices come from related or unrelated production lots and what defines an "unrelated" lot. Determine how the

## VERIFYING YOUR RESULTS

You've built a circuit board that works. But, postpone your celebration until after you verify that the design is statistically stable. Your initial analysis is important in developing a confidence level with a working design because you have to know what timing variations will emerge and where to expect them. Then, you have to simulate these variations with injected signals. Many buffers allow you to put their output into high-impedance, three-state mode to ease signal injection at critical points in your distribution system.

As in all testing, the accuracy and resolution of the test instrumentation must be better than the system under test,

typically by a factor of 10, to provide meaningful results. This limit is a challenge when you're working in the picosecond range. Instruments such as the HP 8133A 3-GHz pulse generator provide less than 1.3-psec rms jitter and about 8-psec worst-case jitter—well within the typical 50-psec Pentium tolerance budget. The HFS 9003 data generator from Tektronix can generate pulses with rise times as low as 250 psec and edge placement accuracy to 5 psec. A 1-GHz or wider bandwidth sampling scope checks clock-waveform timing, including rise time, jitter, and skew, as these signals reach the ICs in your system.



**THE WORLD'S LARGEST SELECTION**

# **POWER SPLITTERS/ COMBINERS**



**2kHz-10GHz** from **\$2<sup>95</sup>**

Choose from over 480 standard off-the-shelf models from 2-way to 48-way; 0°, 90° and 180°; 50 and 75 ohms; covering 2kHz to 10GHz. Mini-Circuits will also supply your special needs such as wider bandwidths, higher isolation, lower insertion loss, and phase matched ports...all at catalog prices with rapid turnaround time. Models include surface mount, plug-in, flat-pack and standard connectorized designs such as SMA, N, TNC, C, and F connectors as well as custom designs. Ultra-miniature surface mount units provide excellent solutions in cellular communications, cable systems and countless wireless applications. All units come with a 1 year guarantee and "skinny" 4.5 sigma repeatability unit-to-unit and production run to production run. Catalog models are guaranteed to ship within one week.

**Mini-Circuits...we're redefining what VALUE is all about!**

CIRCLE NO. 186

 **Mini-Circuits®**

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

**CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.**

F 202 Rev Orig




## HIGH-SPEED CLOCKS

manufacturer chooses the samples and how it distributes the data. Review the basics of statistics and reliability analysis, not to find out whether these ICs will fail catastrophically, but to better understand the meaning of the data-sheet numbers.

Although you must design for worst-case situations, overall error buildup is not necessarily just the sum of the unrelated individual worst-case error values. Such simple addition may inadvertently indicate the need for tighter tolerances or faster memory ICs or suggest a system that may work unreliably. Variations in skew may occur as ICs slow down or speed up with temperature decreases and increases. This correlation may give you some more tolerancing, following careful analysis of the basic data.

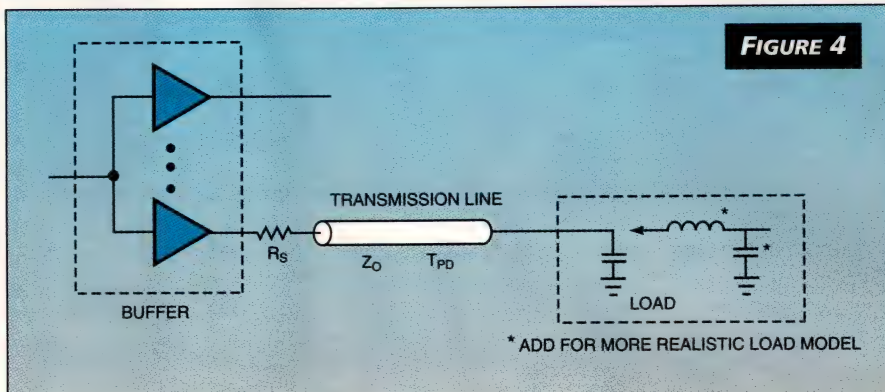Due to the unavoidable path-length and propagation delays in some clock branches, you must add some compen-



**The simplest distribution model has a series-terminated transmission line driving a single load.**

sating delays in other branches. You can use both passive and active approaches, as long as you recognize their trade-offs. The simplest approach is to add some circuit-board tracks to lengthen the faster paths. You can easily calculate the lag time through these

apparently free, "serpentine" delay elements, especially if you use transmission-line techniques. These techniques are also reliable, power-supply-independent, fairly repeatable, and relatively low jitter compared to active devices. Unfortunately, even modest delays

## LOOKING AHEAD

It's logical to predict that the future will bring more 3V clocks, faster clocks, and clocks integrated with the CPU, following the trend of most other electronics. But only the first item is likely. Clock ICs employ processes that can run two to three times faster than most current ICs need to, and some clocks do, such as the 267-MHz Rambus clock. Weighing against that trend, however, are the difficulties and design cost of putting clocks on CPU silicon and of properly distributing clocks that are faster than the current 60 to 100 MHz.

Integrating the clock with the CPU is difficult, because the frequency requirements and fan-out differ among system implementations. A low-jitter, tightly controlled clock is hard to integrate on CPU silicon and entails subtle problems in final silicon implementation that would delay the CPU's release to customers. IC-design and electronic-design-automation tools for clock subsystems differ from and are not as exact as those for CPU logic. In addition, your system's need for multiple clock frequencies and their copies would mean a greater increase in package size and pin count than the CPU and its package can afford. A single clock line from the CPU would still need an external buffer for multiple loads and timing control, so the benefit of an integral clock source may be less than it seems, especially if the CPU IC clock lacks some of the features of stand-alone clock ICs. Finally, physical placement of the clock is critical, and placing it at the CPU reduces the flexibility in location that noise and grounding may demand.

Today's 486- and Pentium-based chip sets have reduced chip count and, consequently, need fewer clock copies and are well-served by integrated generators/buffers. In contrast,

PowerPC and RISC chip sets are less condensed. Clock vendors are tailoring their efforts to provide the clock frequencies and distribution for these families. They're also expanding beyond today's clock frequencies. Clock generators will emerge that provide some of the clock frequencies PCs require. There are yet *more* clocks within PCs for such functions as multimedia.


For example, Integrated Circuit Systems' ICS9120-08 series uses the standard 14.31318-MHz CPU clock crystal to provide standard audio clocks at 16.9344, 25.576, and 33.868 MHz. Oversampling codecs and audio synthesizers in PCs use these values. Despite the relatively low frequencies compared with the processor clocks, good audio performance (16- to 18-bit sound with -96-dB S/N ratio) still requires tightly bounded specs. The IC outputs have 0.01% frequency accuracy and 85-psec,  $1\sigma$  jitter.

High-speed clocks are not just for PCs. Data-communications systems that derive clocking from the incoming data stream must provide a retimed and regenerated clock signal to the decoder. The frequencies for these systems are often faster than those for PC clocks, and jitter specs are correspondingly tighter, but fan-out needs are less. Clock-IC vendors are adapting their technologies to these applications and to video-compression and -decompression systems that operate at several hundred megahertz.

In addition, some computer researchers are investigating the benefits of fully or partially *clockless*, asynchronous CPUs, which might use far less power and have simpler internal circuitry than fully clocked, synchronous devices (**Ref 6**).



# incredible!

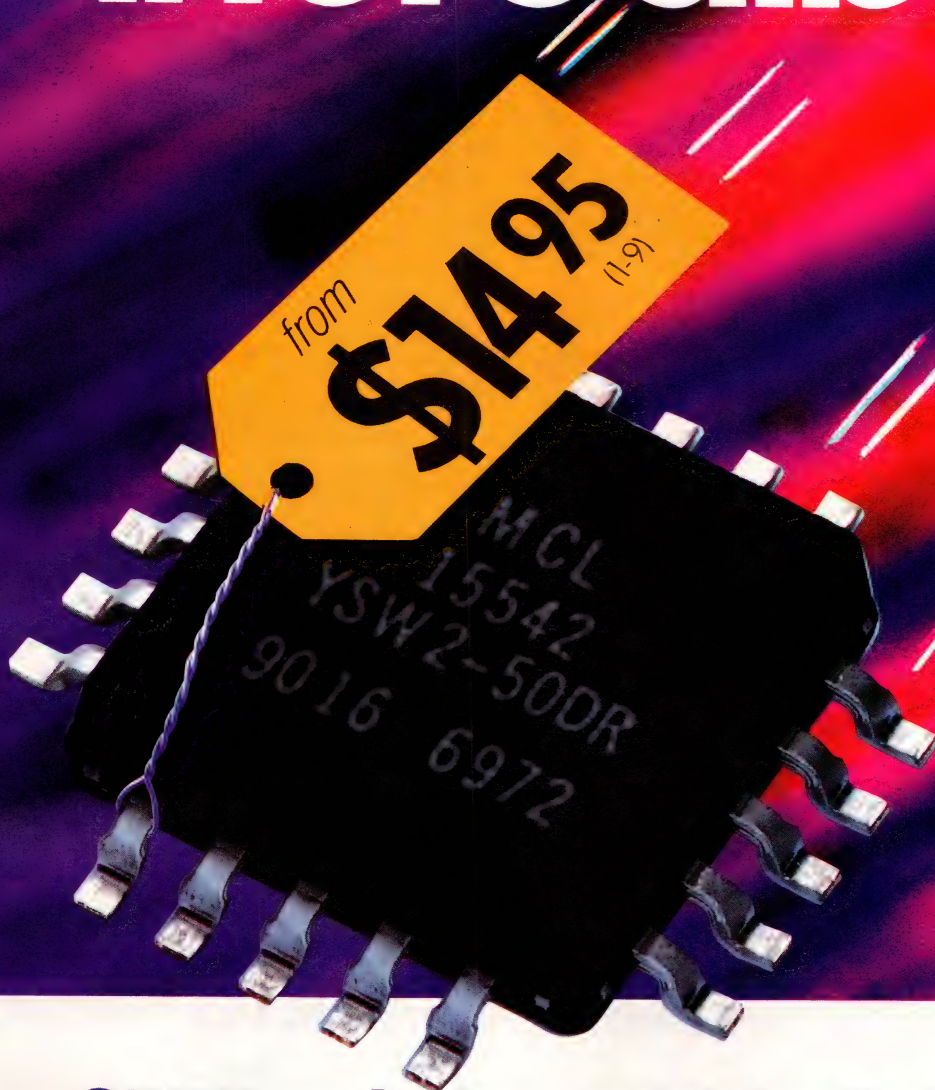


## SPDT switches with built-in driver

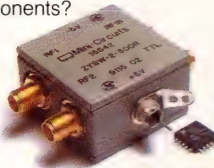**ABSORPTIVE or REFLECTIVE dc to 5GHz**

Truly incredible...superfast 3nsec GaAs SPDT reflective or absorptive switches with built-in driver, available in pc plug-in or SMA connector models, from only \$14.95. So why bother designing and building a driver interface to further complicate your subsystem and take added space when you can specify Mini-Circuits' latest innovative integrated components?

Check the outstanding performance of these units...high isolation, excellent return loss (even in the "off" state for absorptive models) and 3-sigma guaranteed unit-to-unit repeatability for insertion loss. These rugged devices operate over a -55° to +100°C span. Plug-in models are housed in a tiny plastic case and are available in tape-and-reel format (1500 units max, 24mm). All models are available for immediate delivery with a one-year guarantee.



finding new ways...  
setting higher standards

### SPECIFICATIONS (typ)

	Absorptive SPDT			Reflective SPDT		
	YSWA-2-50DR ZYSWA-2-50DR			YSW-2-50DR ZYSW-2-50DR		
Frequency (MHz)	dc-500	500-2000	2000-5000	dc-500	500-2000	2000-5000
Ins. Loss (dB)	1.1	1.4	1.9	0.9	1.3	1.4
Isolation (dB)	42	31	20	50	40	28
1dB Comp. (dBm)	18	20	22.5	20	20	24
RF Input (max dBm)	—	20	—	22	22	26
VSWR "on"	1.25	1.35	1.5	1.4	1.4	1.4
Video Bkthru (mV,p/p)	30	30	30	30	30	30
Sw. Spd. (nsec)	3	3	3	3	3	3
Price, \$	YSWA-2-50DR (pin) 23.95			YSW-2-50DR (pin) \$14.95		
(1-9 qty)	ZYSWA-2-50DR (SMA) 69.95			ZYSW-2-50DR (SMA) 59.95		

## Mini-Circuits®

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718)332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

**CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.**

F141 REV. D

CIRCLE NO. 187

EDN JULY 6, 1995 • 41



## HIGH-SPEED CLOCKS

cost significant circuit-board space, which is generally a precious commodity. Each nanosecond requires approximately 6 in. (15 cm); even a few nanoseconds of delay in each of several branches can quickly consume board space. Any layout changes in your circuit also require recalculation of the serpentine traces and are another constraint on flexibility. Moving the clock-generation and distribution ICs may help, but most circuit boards have local-noise hot and cold spots. Don't make such moves casually.

In the active approach, you can choose delay lines, such as the Synergy SY10E195. Carefully check the stability and repeatability of these adjustments, or you may add jitter uncertainty while correcting for skew. Any compensation scheme is costly if your clocks have a large fan-out. Another approach is to reduce delay by replacing a buffer with a PLL and recalculating system errors and costs.

With so much concern about static delays and dynamic timing issues, another approach is to use adaptive techniques to dynamically adjust clock-signal timing. Micro Linear Corp offers ICs that provide two approaches

to adaptive timing. The eight-channel ML6500 clock manager uses a feedback trace from each load, which the driver uses to measure the timing of the pulse at the load and make necessary vernier adjustments. This approach offers a degree of freedom in handling dynamic errors, but it costs an additional trace per clock line.

The ML6510 takes a different approach. It automatically determines the length of the trace it is driving by measuring the time for reflections to return from the end of the trace. The driver then adjusts a voltage-controlled vernier delay that sends the clock earlier in proportion to the length of the trace. Regardless of which adaptive technique you use, make sure that the overall deskew range, resolution, and stability are sufficient for your circuit.

### Low voltage offers benefits

As in many other areas, designers are increasingly mixing 3 and 5V devices to reduce power consumption. This technique also eases IC-driver design and EMI concerns. Lower signal spans have lower noise margins, however, but this is not a major problem. For mixed-voltage systems, vendors pro-

vide buffers that operate from a 3V supply and that accept 3 and 5V signals.

For "green" or mobile systems, you may need to slow the clock or put it into a power-down mode. Sounds simple, but make sure that your clock is well-behaved when it accelerates to full speed. If the clock ramp-up is not smooth or too rapid, the CPU may lock up when the clock first appears at the wrong time during the transition sequence. Many newer clock-generation ICs guarantee smooth acceleration.

Reducing EMI is always an issue. Radiated signals can affect other parts of your system and produce external interference. Faster slew rates reduce clock skew and jitter, and lower slew rates minimize EMI. Fortunately, vendors shape driver outputs so that the necessary fast slew rates begin and end with rounded corners. These wave-shapes meet signal-transition specs and reduce sharp corners and their corresponding broad signal spectrum.

Clock generation and distribution is a single-supply circuit. To accommodate speeds beyond the range of TTL, clocks often use positive-ECL (PECL), which uses a 5V supply. Vendor application notes give details and equations

## MANUFACTURERS OF CLOCK GENERATION AND DISTRIBUTION ICs

For free information on ICs such as those described in this article, circle the appropriate numbers on the postage-paid Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you read about their products in EDN.

**Applied Micro Circuits Corp**  
San Diego, CA  
(619) 450-9333  
**Circle No. 315**

**Cypress Semiconductor Corp**  
San Jose, CA  
(408) 943-2600  
**Circle No. 316**

**IC Works Inc**  
San Jose, CA  
(408) 922-0202  
**Circle No. 317**

**Integrated Circuit Systems Inc**  
San Jose, CA  
(408) 297-1201  
**Circle No. 318**

**Integrated Device Technology Inc**  
Santa Clara, CA  
(800) 345-7015  
**Circle No. 319**

**Micro Linear Corp**  
San Jose, CA  
(408) 433-5200  
**Circle No. 320**

**Motorola Inc**  
Phoenix, AZ  
(602) 413-3615  
**Circle No. 321**

**National Semiconductor Corp**  
Sunnyvale, CA  
(800) 272-9959  
**Circle No. 322**

**Quality Semiconductor Inc**  
Santa Clara, CA  
(408) 250-8000  
**Circle No. 323**

**Synergy Semiconductor Corp**  
Santa Clara, CA  
(408) 730-1313  
**Circle No. 324**

**Texas Instruments Inc**  
Dallas, TX  
(800) 477-8924, ext 3500  
**Circle No. 325**

### VOTE . . .

Please also use the Information Retrieval Service card to rate this article (circle one):

**High Interest 586**  
**Medium Interest 587**  
**Low Interest 588**

### Super Circle Number

For more information on the IC products available from the vendors listed in this box, you need only circle one number on the postage-paid reader service card.

**Circle No. 326**



# Don't Let EMI Be A DragOn Your Design



If you design microprocessor-based boards, or systems, you know that high emissions—EMI—can eat you alive. Your designs could be affected. Or even rejected. And redesigns for clock schemes take time. And cost money.

## Don't Lose Another Knight Redesigning Your Boards


AMCC clock and timing products are famous for their low emissions. They'll shield you from certification problems. And, your designs will use fewer components, cost less, and run faster.

## You Can Live Happily Ever After


Our SC3500 family of clock drivers provide:

- ◆ Patented low-noise outputs. To eliminate ringing and ground bounce. Fast edges rates without EMI-generating noise.
- ◆ On-chip termination eliminates extra components.

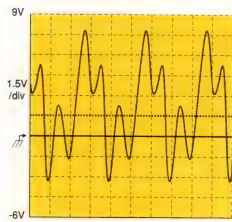- ◆ Low skew. As low as 250 ps.
- ◆ High speed. Up to 80 MHz for your Power PC, Pentium, Alpha, and other RISC-based applications.
- ◆ The SC3300 family provide a 3.3V I/O-compatible solution.



Theirs Unterminated

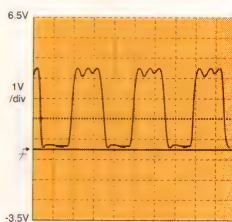

Ours Unterminated

## Contact AMCC Today

We won't tell you a fairy tale. Ask for a copy of our new Computer Products Databook.

FAX us at (619) 450-9885.

Or write to us: MarCom, AMCC,  
6195 Lusk Blvd., San Diego, CA 92121-2793.



Call (800) 755-2622



## HIGH-SPEED CLOCKS

for termination resistors when interfacing TTL, PECL, and CMOS with various supply rails.

### Calling for help can't hurt

In this specialty area of clock-timing and -distribution ICs, where "perfect" digital signals meet the real analog world, take advantage of IC vendors' application departments. Their experience can shorten your design cycle and minimize your following paths that lead to nowhere. Some vendor-independent consultants also specialize in design, analysis, and verification of high-speed clock-generation and -distribution subsystems.

You must also decide whether to fine-tune each system. Adjusting each unit in production to minimize error sources and assure operation can save on parts cost and up-front design time—a viable alternative if you are building only a few units. It can be a costly decision in a higher volume environment, however. Besides the sophisticated test and adjustment effort in the production cycle, it means that units in the field may be unreliable if they ever have a component or sub-section replaced—unless the field-repair site can also do a tune-up, which

is unlikely. Your products may develop a reputation for being difficult to fix if replacing a part induces new errors or soft failures or requires a complex procedure.

However, such per-unit tuning shouldn't be necessary. If you properly and thoroughly perform your analysis and take no short cuts, you should be able to produce and verify a reliable system that works by design rather than individual unit adjustment (see **box**, "Verifying your results").

### References

1. Williams, Michael K and Andreas MR Pfaff, "Clock design and measurement issues in Pentium systems," *Hewlett-Packard Journal*, December 1994.
2. Strassberg, Dan, "Signal-integrity tools don't yet replace EEs' intelligence," *EDN*, Jan 19, 1995, pg 61.
3. Duehren, Derrick, Will Hobbs, Arpad Muranyi, and Robin Rosenbaum, "I/O-buffer modeling spec simplifies simulation for high-speed systems," *EDN*, March 16, 1995, pg 65.
4. Gallant, John, "High-speed clock drivers catch up with  $\mu$ Ps," *EDN*, June 24, 1993, pg 87.
5. Bogatin, Dr Eric, "Multiple coupled transmission line properties

revealed by TDR," presented at Design SuperCon '95, sponsored by Hewlett-Packard and *EDN*.

6. Gibbs, W Wayt, "Turning back the clock," *Scientific American*, June 1995, pg 40.

### Acknowledgments

Thanks to Michael Williams, Amherst Systems Corp; Piyush Sevalia, Cypress Semiconductor Corp; Raju Shah and Victor Herrick, Integrated Circuit Systems Inc; Rick Walther, Integrated Device Technology Inc; Kelly Coffey, Ken McBride, and Roger Brockenbrough, Micro Linear Systems Corp; Todd Pearson, Motorola Inc; and Bernard Ta and Milton Schwartz, National Semiconductor Corp, for their assistance.



You can reach Technical Editor Bill Schweber at (617) 558-4484; fax (617) 558-4470.

### VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High  
Interest  
586

Medium  
Interest  
587

Low  
Interest  
588

## TOOLS AND MODELS OFFER HELP—WITH LIMITATIONS

Sending well-defined, absolutely periodic digital signals around a circuit board should be compatible with modeling and analysis tools. After all, you perform no "signal processing" on the clock signal, but simply pass along or recreate the signal. Although tools can help, they have limitations. Simple tools give you a good start: Even a spreadsheet is helpful as you investigate error budgets and tolerances for vendor parts and basic topology configurations.



The next step up from spreadsheets is to use Spice models. Virtually every vendor supplies these, and they are useful for a basic, first-level check. Most models represent the load with more fidelity than does an input capacitor, by using a  $\pi$  configuration of the input pin with a parallel capacitor, a series inductor, and another parallel capacitor. The models also assume you are using circuit-board-transmission microstrip or stripline as your signal conduit, which you can model simply, ignoring crosstalk, or with more complexity. If the device models reflect only typical operating specs, they are little better than using a spreadsheet, because jitter deviations and worst-case conditions are your true foe.

Your problem is not analysis of signal processing or signal content on pins of complex-function ICs, however. Focus instead on signal timing and integrity on those paths related to that function. Tools for this application can help if you accept their limitations (**Ref 3**). If Spice models are unavailable or insufficient, consider using models developed under the I/O-buffer information specification (IBIS) standard (**Ref 4**). IBIS concentrates on current-vs-voltage characteristics, rise and fall times, and similar behavioral modeling. Spice models, on the other hand, are summaries of transistor-level models and may reveal proprietary internal details that vendors don't want outsiders to know.

Don't worry if you can't model the signal path as fully as you may think is necessary, taking into account crosstalk and signal reflection. Following the guidelines for good design will take you and your signal a long way toward the goal (**Ref 5**). For example, 50 $\Omega$  microstrip lines have less than 3% coupled near-end noise when the spacing to the next adjacent track is equal to the trace width; for striplines, the corresponding rule is that spacing should be at least 1.5 times the trace width.


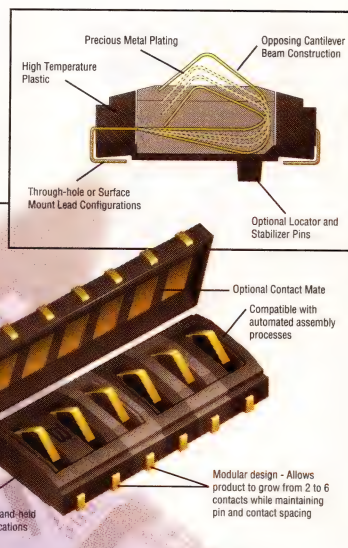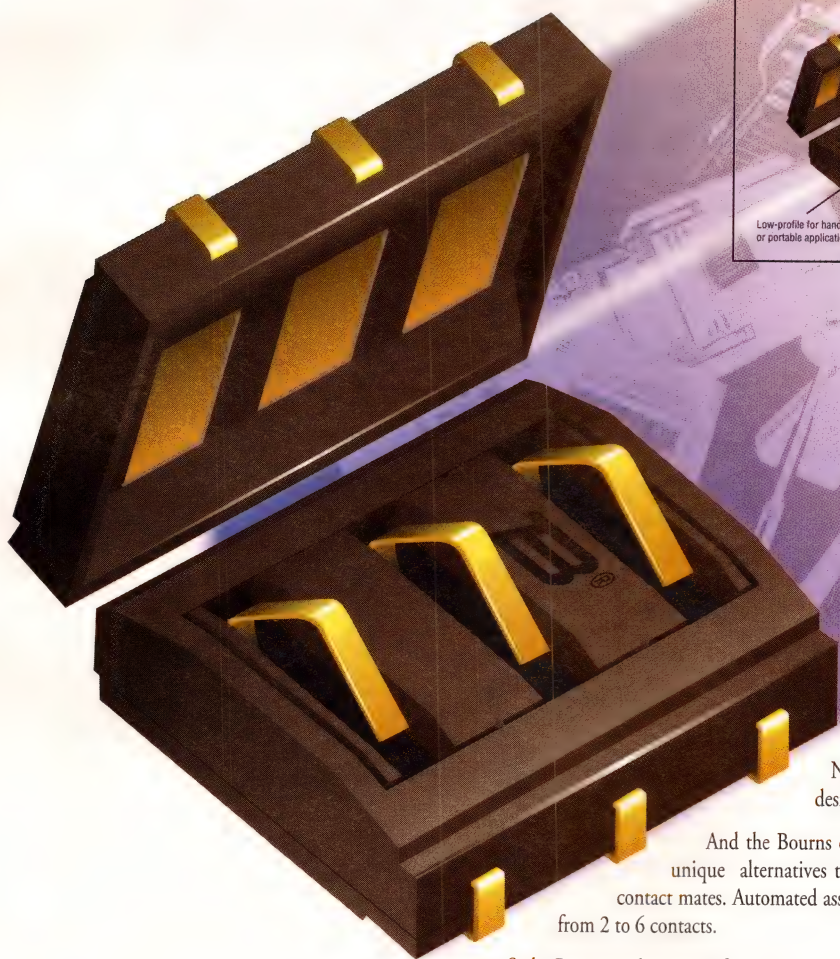
# Modular Contact for Portable Flexibility. It's Standard.



Now your most custom portable, hand-held designs have a standard battery contact solution.

And the Bourns offering of battery contacts provides simple, unique alternatives too. Like low profile packaging. Optional contact mates. Automated assembly compatibility. Plus a modular design from 2 to 6 contacts.

So let Bourns make contact for you.



**FAX**  
LIBRARY

Call 818 837-4341, account 411  
and request document 70235.



*Expanding Your Design Horizons*

For applications assistance call: North America: (909) 781-5050; Europe: 353-021-357001; Asia: 81-3-3980-3313

CIRCLE NO. 138

EDN JULY 6, 1995 ■ 45



# **OVER THE PAST 40 YEARS EDN HAS DELIVERED THE INFORMATION YOU NEED TO DO YOUR JOB MORE EFFECTIVELY.**

- 1st publication to discuss semicustom ICs as a design alternative.
- 1st publication to research and document surface-mount technology (SMT) with "hands-on" coverage actually designing and manufacturing a surface-mount PC board
- 1st publication to write about the implications of digital signal processing (DSP) which led to six DSP Directories
- 1st publication to actually design, fabricate and test a semicustom IC and describe the process
- Only publication to explore comprehensive tools and technology of the future through the Decade 90 series
- Only publication to provide readers with a free Bulletin Board
- Only publication to publish an annual microprocessor directory – 21 and counting
- Only publication to regularly complete hands-on projects – 16 and counting
- Only publication to exclusively employ engineers as technical editors
- Only publication to sponsor an annual awards competition for excellence and innovation in the electronics industry: the EDN Innovation Awards – 5 years and counting



# SO WHAT HAS EDN DONE FOR YOU LATELY?

- *Cooling Hot Microprocessors*  
by Dan Strassberg, January 20, 1994
- "Electromagnetic Compatibility Special Supplement"  
January 20, 1994
- *Wiring the World with ATM*  
by Richard A. Quinnell, March 3, 1994
- *Probing the Limits of Logic Synthesis*  
by Ray Weiss, March 17, 1994
- *New Chips Give PCs TV-Quality Video*  
by Gary Legg, March 31, 1994
- *Power ICs: Weighing the Benefits of Integration*  
by Anne Watson Swager, July 7, 1994
- *Fuzzy Logic Design Tools Help Build Embedded Systems*  
by Gary Legg, July 21, 1994
- *Synchronous Memories*  
by Richard A. Quinnell, August 4, 1994
- "Project Ploughshare: Putting Military Technology to Other  
Uses", August 18, 1994
- *CDPD Network*  
by John Gallant, October 13, 1994
- *Shooting-Down the True Lies in FPGA Benchmarking*  
by John Cooley, October 27, 1994
- "Green Design Issue", November 10, 1994
- "Hot 100 Products 1994", December 8, 1994
- *DRAM Annual Report*  
by Markus Levy, January 5, 1995
- *Cache Memory Special Report*  
by Markus Levy, January 19, 1995
- *Plug 'n Play*  
by Dan Strassberg, March 2, 1995

## EDN

What engineering is *really* all about.



**SIEMENS**

# System and Costs under Control

Always start adding up your system costs with a look at the performance of our C500 family of powerful 8-bit microcontrollers. It gives you fast processing speed, low supply voltage, minimal power drain, plus full 8051 compatibility.



C165: With its superior price/performance ratio, it's truly the reference class for 16-bit controllers with an 80 ns instruction cycle time and an unbeaten 40 ns reaction time to interrupts.

Up in the 16-bit class don't decide without first sizing up the C166 family with superb computing performance combined with unmatched real-time response, making it the reference class worldwide – whatever the competition.

And because both families are modular and come with an established and reliable mix

of intelligent peripherals, you can forget all the expensive extras and overheads.

Naturally, fast results count too. So you always get first class service and support all-round – from us and our selected partners. From 'C' compilers through debuggers to optimized realtime emulation we give you the kind of technical back-up that really makes the difference in your application.

So, add up all the benefits and only one name will show through clearly.

Just fax us on +49-911-300 12 38 quoting "Info Service HL 9144" and we'll put you in the picture.

**Global PartnerChip  
for Systems on Silicon.  
Siemens**







# First




## In Fast SCSI Terminators ...Again

Long SCSI connections were a problem until we began developing active terminators to satisfy just about any SCSI termination concern.

Take a look at our latest, the **UCC5606/5614** family of 9-Line 3-5V SCSI Active Terminators. The UCC5606 and UCC5614 are ideal for high speed fast 20 and battery powered systems with their ultra-low channel capacitance of 1.8pF and a supply current of 1mA. During disconnect, the UCC5606 and UCC5614 supply currents are only 0.5µA - keeping it really low!

For free samples of our latest SCSI terminators give us a call today. You name the number of lines, and we'll provide the application information to meet your design's requirements.

CIRCLE NO. 8

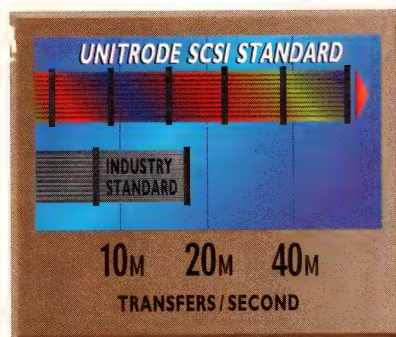

 **INTEGRATED  
CIRCUITS**  
**UNITRODE**

**TEL: (603) 429-8610**

FAX: (603) 424-3460

7 Continental Boulevard • Merrimack, NH 03054

### *The UCC5606 and UCC5614*

- ◆ Low Voltage Operation, 2.7V – 7V
- ◆ 110 Ohm/2.5k Programmable Termination
- ◆ Complies with SCSI, SCSI-2, SCSI-3 Fast 20
- ◆ Supports Hot Swap
- ◆ 400mA Sink/Source Regulator
- ◆ Adaptive Termination
- ◆ Logic Disconnect UCC5614
- ◆ Logic Disconnect UCC5606
- ◆ 9-Line Termination



# PORTABLE HARDWARE MAKES EXPERIMENTS INTERACTIVE

Bringing the data-acquisition system to the experiment can provide useful results in a hurry. But, if you're not careful, subtle flaws in what should be invisible software can stymie your hardware installation.

**DAN STRASSBERG, SENIOR TECHNICAL EDITOR**

Using a notebook PC for data acquisition can alter your whole concept of experimentation. What was a tedious, iterative process becomes a dynamic, interactive one. When the same PC that controls data acquisition reduces the data and displays the results, you can learn immediately what happens when you change test conditions.

Until recently, though, bringing a PC to an experiment more than a few feet from your lab bench was, at best, inconvenient. Despite the existence of notebook PCs, virtually the only portable PCs that could acquire data at speeds faster than about 5k samples/sec were "luggable" ac-powered units weighing over 20 lb.

Data-acquisition products designed for notebook PCs began to appear about two years ago. Some of these products are external units about equal in size to the PCs themselves; others are credit-card-sized PCMCIA

cards that plug into slots on the side of most modern notebooks.

Software kinks plagued early PCMCIA data-acquisition cards. Vendors have resolved many of the problems, and data-acquisition is preparing to join the portable-electronics revolution. Competition is heating up; different companies' products often look quite similar. But don't be fooled. To find hardware and software that play together well, ask pointed questions and pick vendors that supply good answers. (See box, "PCMCIA: A little caution saves a lot of grief.")

Nearly all PCMCIA data-acquisition cards are the 5-mm-thick Type II size. Most notebooks accept two Type II cards. Generally, the specs of PCMCIA data-acquisition cards don't quite equal those of similarly priced boards for desktop PCs, but many cards compare well with portable data loggers that lack the processing power to reduce



Signal termination and conditioning are as much a part of data acquisition as A/D and D/A conversion and translation of relay-contact status into logic levels. Strawberry Tree's DataShuttles (from \$995) represent a class of parallel-port attachments that handle the full spectrum of data-acquisition-system functions.



## NOTEBOOK-PC DATA ACQUISITION

data. The "For free information..." box lists vendors of PCMCIA data-acquisition cards and of external data-acquisition attachments that connect to notebook-PC parallel ports.

### Small size, big features

Most analog-input PCMCIA cards have 16 single-ended inputs (eight dif-

ferential) with software-programmable gain and four unipolar or bipolar full-scale ranges from ~1 to 10V. Resolution is 12 bits. Triggering can come from software or from an external source. The cards usually also offer four to eight digital I/O lines and a counter/timer. A/D-conversion speeds start at 30k samples/sec. Most vendors offer

models that take 100k samples/sec, although a few run faster; the top speed is currently 140k samples/sec. A few cards provide 16-bit resolution. Some cards accept low-level (10-mV full-scale) inputs. Some even provide cold-junction compensation for thermocouples.

Only a few analog-input cards also

## PCMCIA: A LITTLE CAUTION SAVES A LOT OF GRIEF

When you plug a PCMCIA card into a PC, you set in motion a chain of events that you aren't even supposed to notice. Indeed, if everything works as intended, you won't be aware of the complex drama that the PC's hardware and software are playing out. Unfortunately, the script is quite complex, and its many plot twists and subplots can confuse the actors. Sometimes, they forget their lines. However, if you think of yourself as the director and exercise a little care at the outset, you can keep the finale from resembling the last act of *Hamlet*.

Begin by becoming acquainted with the cast of characters. Among the key players are software modules called "socket services" (SSs) and "card services" (CSs), which reside on the PC's hard disk and load into RAM at boot time. Most notebooks shipped in the past 18 months have PCMCIA V2.0 or 2.1 SSs and CSs on their hard disks. SSs act as a driver for the ICs on the motherboard that interface with the PCMCIA sockets. CSs begin to act when you plug in a PCMCIA card (or when you power up a system with a PCMCIA card plugged in), but CSs do not work alone.

Another member of the cast is a software module called a "generic enabler" (GE), or "super client." The company that supplies the GE, usually the PC manufacturer, customizes the GE for the PC's hardware. GEs for similar but not identical PCs from the same manufacturer can differ from each other.

Most vendors of PCMCIA data-acquisition cards provide a hardware-specific driver for each card. You install this driver by running an installation program that the card vendor supplies. Sometimes, this driver is part of a set of drivers constituting a dynamic-link library (DLL) that one or more Windows-based data-acquisition application packages use. This is the case, for

example, with the NI-DAQ driver set that National Instruments furnishes with LabWindows/CVI and LabView. Sometimes, the DOS Autoexec.bat file installs the driver each time you boot the PC.

### The application contains a driver, too

In most cases, there is yet another driver. It is part of the data-acquisition application or application-development package. Examples of such packages are TestPoint from Capital Equipment Corp (Burlington, MA), DT-VEE from Data Translation, Snap-Master from HEM Data (Southfield, MI), Visual Designer from Intelligent Instrumentation, Labtech Notebook from Laboratory Technologies (Wilmington, MA), LabView from National Instruments, and DasyLab from NewWorld Resources (Amherst, NH).

Often, the application driver is not specific to a card but is general enough that an application you write for, say, an ISA bus board can run unmodified on a PCMCIA card. However, to get an application to run with specific hardware, you must configure the application to talk to the correct hardware-specific driver or the correct portion of a DLL driver set.

The proponents of PCMCIA describe the bus as "plug-and-play," which it is if everything works correctly. But, even when everything works correctly, a PCMCIA data-acquisition card doesn't necessarily work in

both of a notebook PC's PCMCIA slots (or *all* slots on units that have more than the usual two Type II slots). Usually, you must configure the application software to look for the card in the correct slot. Data Translation has gone to great lengths to make sure that the software that supports its PCMCIA cards automatically recognizes the cards and properly supports them wherever you plug them in.



**Suppliers of PCMCIA data-acquisition cards offer a variety of devices for terminating the field wiring from transducers and other signal sources found in data-acquisition setups. This unit from Intelligent Instrumentation includes cold-junction compensation for up to seven thermocouples.**



provide DAC outputs. You can buy cards whose primary function is DAC output, however. Some of these cards combine DACs and digital I/O lines. Other cards that lack analog inputs offer several counter/timers and digital I/O lines (24 are typical). Prices range from under \$200 for purely digital cards to almost \$700 for a 16-bit, eight-

channel, 50k-sample/sec, analog-input card. Prices of 12-bit cards range from just under \$300 to almost \$600.

Although PCMCIA cards represent the current state of the art in miniaturization of PC-based data-acquisition hardware, other types of notebook-PC data-acquisition equipment do exist. Units that connect to RS-232C ports

date back to the days of minicomputers. There are scores of vendors and models, but no RS-232C unit operates any faster than the serial port to which you connect it. At 115.2 kbps—very fast for an RS-232C port—a unit can transmit no more than 7.66k 12-bit samples/sec. Most units are much slower, although a few capture data bursts at

Now that we've met the players, we can try to follow the action. When you plug in a PCMCIA card or power up a PC with a card already plugged in, the GE, working in conjunction with CSs, attempts to identify the card. Identification consists of determining the manufacturer, the card function, the specific card type, and the resource requirements. These requirements include interrupt lines as well as the base address and the range of addresses in the PC's I/O space that the card uses to communicate. In most cases, after properly determining the resource needs, the GE and CSs leave the scene and let the card manufacturer's hardware-specific driver interface with SSs.

#### A case of mistaken identity

Complications often arise, though. In many cases, the GE causes CSs to misidentify the PCMCIA card. In such cases, the card vendor's driver must try to persuade CSs to determine the resource requirements again—this time, correctly. The alternative is to override the GE and use resources designated in the hardware-specific driver. The problem with this approach is that it can lead to some of the difficulties that were common with card-specific enablers (CSEs), the predecessors of CSs and SSs.

CSEs, which came from either card or PC vendors, allowed you to run one or a few types of PCMCIA card. CSEs' most notable problem was that their installation often caused some PCMCIA cards that once worked to stop working. Particularly under DOS (which, unless modified, does not support memory beyond 640 kbytes), CSEs would sometimes use so much memory they could keep you from running applications that ran before you installed the CSE.

The last part of the drama unfolds when you unplug a card. Whenever a PCMCIA card is in a PCMCIA socket, it connects several pins, thereby holding one of the I/O lines at ground potential. When you remove the card, a resistor pulls this line toward  $V_{CC}$ . The support chips in the PC detect when this line goes high and generate a signal indicating that the card is no longer in place. SSs then start a sequence that informs the operating system and any running applications that the card is no longer present.

#### Before you buy, do this...

To improve the chances that a PCMCIA card will work as advertised in your PC, do the following before purchasing a card:

- Find out if the card vendor *knows* that the card works in

your PC. Knowing involves more than just guessing. If you haven't yet purchased the PC, see if you can get the card vendor to provide a list of PCs known to work with the card vendor's cards.

- Remember that the PC vendor's name and model name may *not* adequately identify the PC to the PCMCIA card vendor. Be prepared to supply the card vendor with additional information, such as whether the PC vendor preinstalled SSs and CSs on the PC.

- Know the name of the BIOS vendor, the BIOS revision number or revision date, and the name of the vendor of the PC's PCMCIA chip set. If the PC's documentation doesn't provide this information, you may have to get it from the PC manufacturer's technical-support department.

- Use a version of SS that supports your chip set. Because PC vendors customize SSs for PCMCIA chip sets, turn first to the PC's manufacturer (not to the publisher of CSs and SSs) to obtain CSs and SSs.

- See if the card vendor will send you software to test the PC for compatibility if the card vendor isn't sure that the card and the PC are compatible. Ideally, you shouldn't have to pay for this software. Data Translation provides such software free.

- Alternatively, see if the card vendor will sell you the card with a money-back guarantee. That is, if you can't make the card work, the vendor provides a return-material authorization, you return the card, and the card vendor does not bill you.

- When you unpack the card and complete the software installation, make sure that applications that ran previously still run and that other PCMCIA cards that worked previously still work.

- Make sure that the driver in your data-acquisition application or application-development package interfaces correctly to the PCMCIA card vendor's hardware-specific driver. If you buy the card and the application software separately, make sure that each of the vendors *knows* that the drivers are compatible.

- Don't assume that using a "name-brand" PC precludes problems or that using a little-known brand of PC invites trouble. One PCMCIA data-acquisition-card vendor supplied *EDN* with a list of over 140 PCs. The list includes PCs known to work with the vendor's cards, PCs that don't work, PCs that probably work (but haven't yet been tested), and PCs that may not work. The size of a PC's manufacturer appears unrelated to the PC's degree of compatibility with this vendor's cards.



## NOTEBOOK-PC DATA ACQUISITION

high speed and store them internally for serial transmission to the host PC.

Table 1 compares the speed of several buses and ports that can connect data-acquisition devices to PCs. The table indicates the bus or port speed, not the speed of the data-acquisition hardware (the ADC, for example). Moreover, most data-acquisition units resolve 12 or 16 bits. Transferring a single reading usually takes 2 bytes. (A 12-bit unit *could* transfer two readings in 3 bytes, but few do so.)

Many PCs introduced in the past year have an enhanced parallel port (EPP) rather than a standard (Centronics) port. Data-acquisition units designed to connect to Centronics ports work equally well with EPPs. The EPP is backward-compatible with the two-decades-old Centronics standard but offers better two-way communication and is faster when operating with equipment designed to take advantage of its speed.

### Faster than a speeding ADC

The speeds of the EPP, the IEEE-488 bus, and the PCMCIA bus fall in a range of about 3:1. Unlike RS-232C and Centronics ports, these ports and buses are faster than most of the data-acquisition units you can connect. For example,

despite the PCMCIA bus's 2.5-Mbyte/sec maximum transfer rate, only a few PCMCIA ADC cards acquire more than 100k samples/sec.

Similarly, when connected to EPPs, nearly all parallel-port data-acquisition units that were designed to take advantage of EPP speed run only as fast as their ADCs allow. The EPP is faster than 12- or 16-bit ADCs with a top speed below 350k to 400k samples/sec. When you use a Centronics port to connect a unit designed for the EPP, the unit functions but runs more slowly than it does on an EPP.

Many parallel-port units replicate the PC's printer port. Therefore, you

don't have to disconnect the data-acquisition unit to connect a printer. The data-acquisition-unit driver intercepts messages intended for the printer. Before passing those messages to the PC's parallel port, the driver sends signals through the port. These signals stop data acquisition and make the external unit echo to the printer any signal from the PC and echo to the PC any signal from the printer.

Vendors of parallel-port data-acquisition attachments include Dataq, Iotech, Intelligent Instrumentation, National Instruments, Omega, and Strawberry Tree. Prices for units with eight differential analog inputs and 12-

### TABLE 1—BUS AND PORT SPEEDS

<b>RS-232C</b>	11.5 kbytes/sec
<b>Standard parallel port</b>	180 kbytes/sec
<b>EPP</b>	800 kbytes/sec
<b>IEEE-488</b>	1 Mbyte/sec (faster with short cables or special implementations)
<b>PCMCIA</b>	1.5 to 2.5 Mbytes/sec
<b>ISA bus</b>	2 to 2.5 Mbytes/sec (depends strongly on the PC)

**Note:** Most cards use 12- or 16-bit ADCs, so one reading usually takes 2 bytes, although it is technically feasible for software to pack two 12-bit readings into 3 bytes. (Data courtesy of Iotech)

## FOR FREE INFORMATION...

For free information on the notebook-PC data-acquisition products discussed in this article, circle the appropriate numbers on the postage-paid Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following companies directly, please let them know you read about them in EDN.

#### Notes:

C=Supplies PCMCIA data-acquisition cards.  
E=Supplies external data-acquisition units—in all cases for parallel ports, and in several cases, for the IEEE-488 bus as well.

**American Advantech Corp<sup>C</sup>**  
Sunnyvale, CA  
(408) 245-6678  
**Circle No. 301**

**Computer Boards Inc<sup>C</sup>**  
Mansfield, MA  
(508) 261-1123  
**Circle No. 302**

**Data Translation Inc<sup>C</sup>**  
Marlborough, MA  
(508) 481-3700  
**Circle No. 303**

**Dataq Instruments<sup>E</sup>**  
Akron, OH  
(216) 668-1444  
**Circle No. 304**

**Intelligent Instrumentation<sup>C,E</sup>**  
Tucson, AZ  
(520) 573-0887  
**Circle No. 305**

**Iotech Inc<sup>C,E</sup>**  
Cleveland, OH  
(216) 439-4091  
**Circle No. 306**

**Keithley Metrabyte<sup>C,E</sup>**  
Taunton, MA  
(508) 880-3000  
**Circle No. 307**

**National Instruments Corp<sup>E</sup>**  
Austin, TX  
(512) 794-0100  
**Circle No. 308**

**Omega Engineering Inc<sup>E</sup>**  
Stamford, CT  
(203) 359-1660  
**Circle No. 309**

**Quatech Inc<sup>C</sup>**  
Akron, OH  
(216) 434-3154  
**Circle No. 310**

**Soltec Corp<sup>C</sup>**  
San Fernando, CA  
(818) 365-0800  
**Circle No. 311**

**Strawberry Tree Inc<sup>E</sup>**  
Sunnyvale, CA  
(408) 736-8800  
**Circle No. 312**

#### VOTE...

Please also use the Information Retrieval Service card to rate this article (circle one):

**High Interest 590**  
**Medium Interest 591**  
**Low Interest 592**

### Super Circle Number


For more information on notebook-PC data-acquisition products available from all of the vendors listed in this box, you need only circle one number on the postage-paid reader service card.

**Circle No. 313**



**It's got to be simpler.  
It's got to be faster.  
It's got to be more highly integrated.**

**CRYSTAL**  
A Cirrus Logic Company

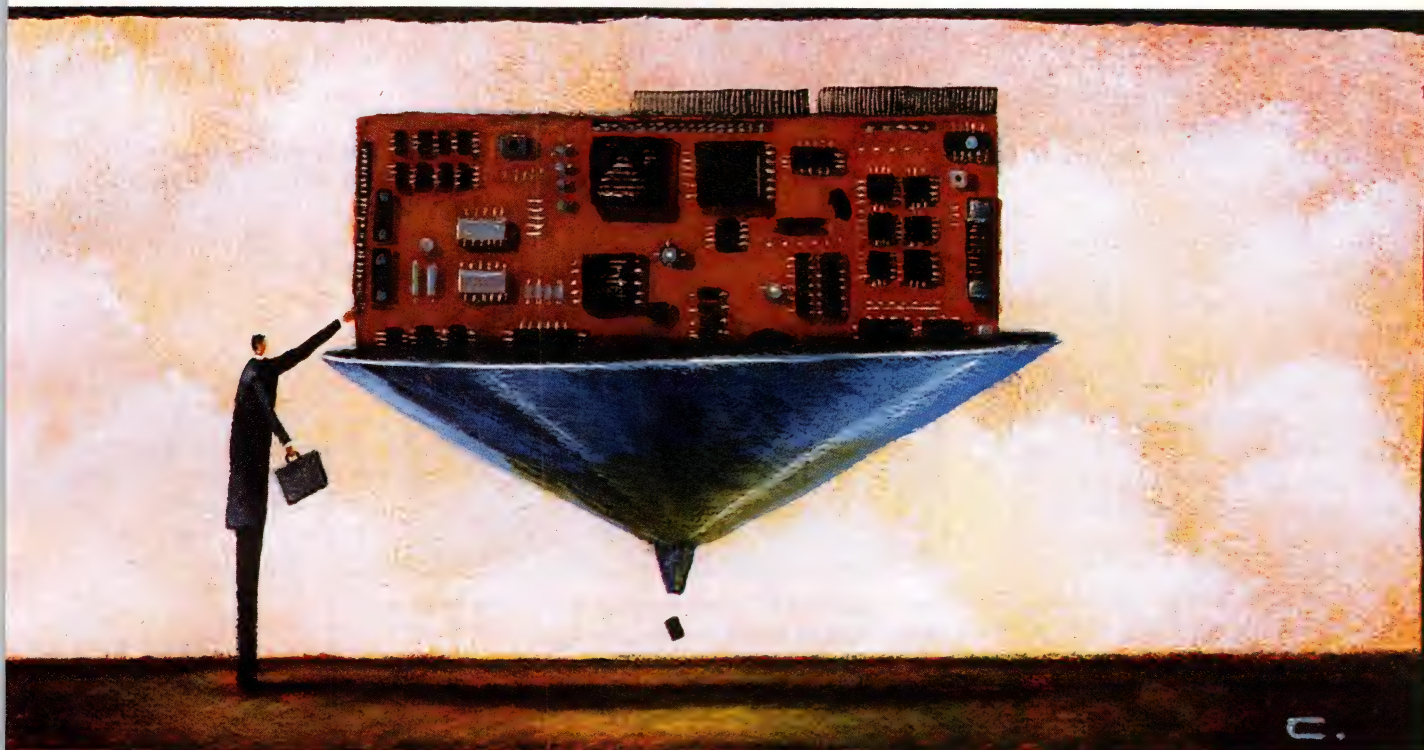

REMOTE DATA LOGGING POWER METERING PROCESS CONTROL HANDHELD INSTRUMENTATION PORTABLE MEDICAL DIAGNOSTICS

## It's got to be Crystal.

Crystal's SMART Analog™ ADCs mean simpler, faster designs—crucial parameters when your system has to master real-world applications today.

Specifically, Crystal Semiconductor's 5504 series of delta-sigma A/D converters has revolutionized the data acquisition industry. These highly integrated chips are

key to reducing design time, increasing performance, lowering costs and still getting to market first.

The 5504 series features Crystal's proven SMART Analog approach to delta-sigma technology,

which reduces external component requirements to near zero. On-chip digital filtering delivers clean signal processing. And the 16- or 20-bit resolution delivers higher accuracy. Much higher.

There's a full range of solutions, including on-chip

instrumentation amplifier and multiplexers allowing up to 200 samples/second per channel. And the lowest power, smallest package, lowest cost 16-bit chip.

Call now for more information on the 5504 series and evaluation kit: 1-800-888-5016 (or 1-512-445-7222). See why it's got to be Crystal's ADCs for your data acquisition design project.

### For real-world demands, it's got to be the 5504 series.

	Resolution (bits)	Number of Channels	Output Update Rate (samples/sec.)
CS5504	20	2	20/200
CS5505	16	4	20/100
CS5506	20	4	20/60
CS5507	16	1	20/100
CS5508	20	1	20/60
CS5509	16	1	20/200

Crystal Semiconductor (UK) Ltd.  
Spectrum Point, 297 Farnborough Road  
Farnborough, Hampshire GU14 7LS  
Ph: +44 (0) 1252 372762  
Fax: +44 (0) 1252 372763

Crystal Semiconductor  
Muhlfelder-Strasse 2  
D-82211 Herrsching, Germany  
Ph: +49 (8152) 40088  
Fax: +49 (8152) 40077



## NOTEBOOK-PC DATA ACQUISITION

bit, 100k-sample/sec ADCs begin at about \$700. Although PCMCIA cards that offer similar performance are smaller and less expensive, external units can appear attractive when you consider their expansion capabilities and the cost and size of the signal-conditioning and -termination panels you often need with the cards.

Several vendors, such as IOtech, have developed instrument-sized data-acquisition units that connect to the IEEE-488 bus. PCMCIA IEEE-488 interfaces now let you attach such units to notebook PCs. A PCMCIA IEEE-488 interface adds roughly \$200 to such a data-acquisition unit's cost. Despite that cost, you may prefer IEEE-488 if, in addition to doing data acquisition, you are also controlling one or more instruments. Today, most test-application-development packages let you treat IEEE-488 instruments just like other data-acquisition hardware. However, you can still program IEEE-488 devices with ASCII strings. People devoted to that approach may prefer IEEE-488.

### ISA—still the standard

The ISA bus appears in the table mainly for reference; ISA is the standard for desktop-PC data-acquisition boards. Standard notebook PCs don't accept ISA bus boards, but external attachments (from Keithley Metrabyte, among others) let notebooks use such boards. The speed of the port that connects to the external unit determines how fast the cards can run. Keithley's DacPacs connect to the high-speed ports that several popular notebooks normally use to attach to desktop docking stations. This arrangement lets the cards run at full speed. A unit that costs \$1199 holds two two-thirds-length boards; a unit that costs \$1499 holds two full-size boards. Both units include NiCd batteries.

Keithley Metrabyte also sells ruggedized FieldPCs that accept ISA bus boards internally and run them at full speed. These PCs resemble notebooks, but are both larger and heavier. Still, you may find these computers (from \$9869) more convenient to carry than notebooks with separate data-acquisition units.



**This industrial PC from Keithley Metrabyte withstands hostile environments. Though larger, heavier, and more costly than typical notebooks, it includes many features lacking in a standard notebook—for example, the ability to mount ISA bus data-acquisition cards inside and to run them at full speed.**

Because PCMCIA data-acquisition cards operate from notebook PCs' battery power supplies, the cards simplify data acquisition where no ac power source is handy. Vendors of PCMCIA data-acquisition cards sometimes heavily promote a card's low power consumption. When acquiring data, some analog-input cards draw almost five

times as much power as others do. (In standby mode, all cards draw reduced power, but even standby power drain varies.)

The differences among cards' power drains aren't as significant as they might seem, however. The highest power cards draw less than 0.5W. A typical notebook draws about 10W. Hence, a battery charge lasts almost as long with a high-power card as with a low-power one. But, when you evaluate notebook PCs, make sure that power dissipated within the PC does not excessively warm the PCMCIA slots. High temperatures can cause leakage and drift that degrade data-acquisition cards' performance.

Unlike PCMCIA cards, not all external data-acquisition units run from batteries. Of those that do, some use separate battery packs

that increase the number of items and the weight you must carry.

External units offer considerably more flexibility than do PCMCIA data-acquisition cards, however. External units often run faster and accommodate more channels, and many units provide DAC outputs in addition to

*(continued on pg 61)*


## LOOKING AHEAD

Like so many other parts of electronics, PC-based data acquisition has changed for the better and forever because of miniaturization. The demand will only accelerate for portable data-acquisition hardware that is more capable, rugged, and cost-effective. Although PCMCIA data-acquisition cards will form a significant part of the market, such cards won't supplant more conventionally packaged hardware in the near future.


Even when PCMCIA's "teething" problems are only unpleasant memories, many users will demand more ruggedness than the diminutive cards can supply. For these users, a growing list of companies will provide small, light, high-performance equipment in somewhat larger packages. Some of these units will perform functions unlikely to appear on PCMCIA cards for several years. A product that seems to offer a glimpse of such things is IOtech's \$2495, eight-channel Wavebook/512, a DSP-based, external unit that takes 1M samples/sec. Meanwhile, PCMCIA cards' performance will continue to improve, so that users who can take advantage of the cards' size will have a growing array of options.


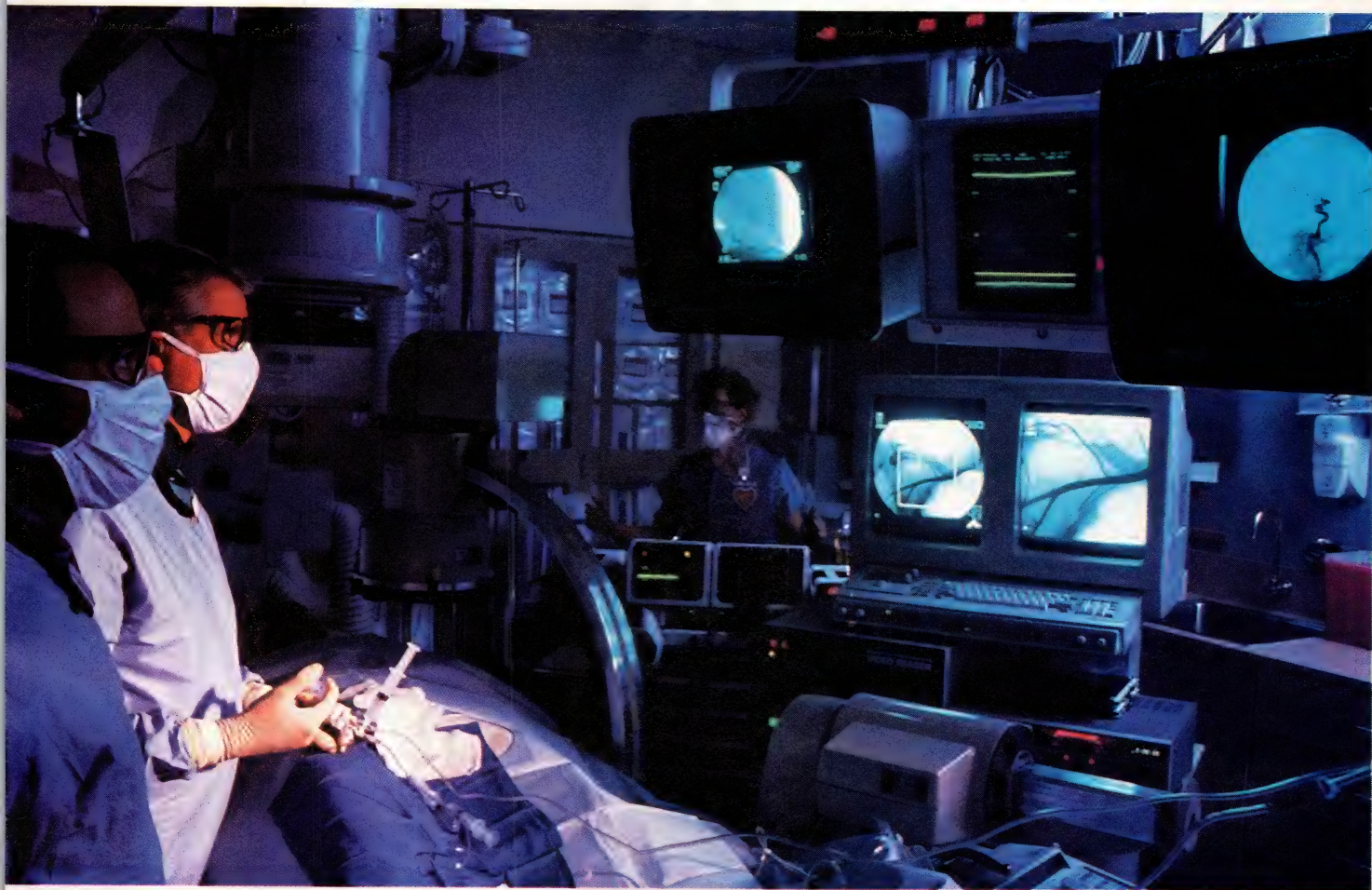
# ***When reliability counts, we have the power supplies you need.***



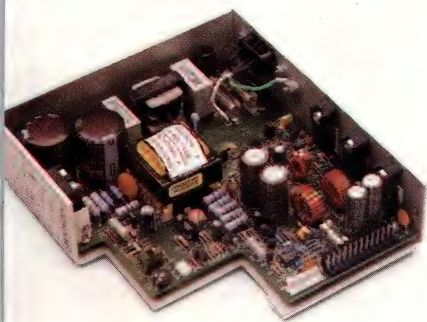***Condor's medical D.C.  
power supplies meet  
the world's toughest  
safety standards.***



Our medical switchers and linears meet every international safety requirement, including IEC601, VDE0750, UL544 CSA1402-3 and CSA22.2 No. 125. Only Condor combines full agency approvals with so many great features, including:

- 38 single- and multiple-output linears
- 44 multiple-output switchers
- More than 200 modified and custom medical designs (with all agency approvals)
- Leakage current less than 60 $\mu$ A (switchers) or 8 $\mu$ A (linears)
- Meet FCC20870, Class B and VDE0871, Class B with patented low-leakage filter
- Worldwide AC input ranges

- Industry-standard packages
- 100% burn-in/2-year warranty (switchers)
- 100% burn-in/3-year warranty (linears)
- Tested I.C.'s and 105 °C capacitors used throughout

Condor also offers complete design and manufacturing capabilities for custom medical units, with 100% success in obtaining required worldwide agency approvals. For safety, quality and reliability, look to the world leader in medical D.C. power supplies—Condor!

**WORLD CLASS RELIABILITY**  
***CONDOR***

Condor D.C. Power Supplies, Inc. • 2311 Statham Parkway, Oxnard, CA 93033 • (805) 486-4565 • 1-800-235-5929 (outside CA)  
FAX (805) 487-8911 • Send for our catalog, or see us in EEM.

CIRCLE NO. 144

EDN JULY 6, 1995 • 59



# Challenge Your Next FPGA To...

...do what never could be done before...

*Always* route your design... and do it automatically while holding fixed pinout and path timing.

With QuickLogic's 100% routability guarantee, development dollars don't go to waste on costly board spins. Abundant use of the small, metal-layer ViaLink® antifuse ensures we can provide more interconnect wire than you'll need to hold a pinout during design exploration.

Path timing fluctuations are minimized by this high-speed, ultra-low impedance ViaLink antifuse, which implements a Datapath benchmark at over 160 MHz.

Combine this fast, flexible routing capability with our superior QuickWorks™ tool suite to create a better product and get it to market faster than ever before. Call us for a \$99 QuickWorks eval kit, complete with all the tools needed to enter, analyze and synthesize your design.

Challenge us to get your product to market faster. Call 1-800-842-FPGA (3742) or email: [info@qlogic.com](mailto:info@qlogic.com) for a Quick response.

In Europe, call +49 (89) 899 143 28 or Fax +49 (89) 857 77 16.



QuickLogic's new fully PCI compliant 8,000 usable gate device outperforms so called "10,000 gate" devices!



## QUICKLOGIC

*Leading The Revolution in FPGAs*

©1995 QuickLogic Corporation. QuickLogic and ViaLink are registered trademarks and QuickWorks is a trademark of QuickLogic Corp. All other trademarks are properties of their respective companies. Synthesis by Synplicity, Inc.

CIRCLE NO. 218





## NOTEBOOK-PC DATA ACQUISITION

analog inputs and digital I/O points. (The DAC outputs, a standard feature of ISA bus analog-input boards, are uncommon on PCMCIA versions.) Often, too, external units' counter/timer and triggering facilities are more flexible than those of PCMCIA cards.

Many external units also accept signal-conditioning circuits that convert the low-level outputs of popular transducers to the high levels that most data-acquisition cards' analog inputs need. In some cases, the signal-conditioning circuits also provide transducer excitation and input-to-output ohmic isolation.

Some external units incorporate signal-termination blocks. Most users of data-acquisition equipment find soldering or crimping of connectors onto transducer wiring (field wiring) impractical. These users prefer screw-terminal blocks or other connection hardware that accepts individual wires. With some of these wiring devices, you don't even need to use a screwdriver.

PCMCIA cards are much too tiny and thin to accept field wiring directly. All vendors offer separate signal-termination units (STUs) for field wiring. A prewired cable runs from the STU to a miniature connector that forms the outer edge of the PCMCIA card. STUs vary considerably in size and in the range of wire sizes they accept. Some vendors include the price of one STU in the price of a card, but you are likely to want extra STUs, which cost from under \$50 to over \$200 each. Differences among STUs justify this wide price range.

STUs can be handy if the transducers' signals are directly compatible with the data-acquisition system's inputs. You may want to wire several STUs to different parts of your test setup and take advantage of the data-acquisition system's portability. You can carry a notebook PC around the setup and plug each of the STU cables in turn onto the PCMCIA data-acquisition card, gathering a few seconds or a few minutes of data at each stop.

When signals require conditioning to make them compatible with data-acquisition-system inputs, a PCMCIA data-acquisition card's advantages over an external data-acquisition unit are

less clear. One way to use a PCMCIA ADC card in such situations is to deploy manifolds of signal conditioners around the test setup in place of STUs. The manifolds of signal conditioners cost much more than STUs, however, so this approach isn't necessarily economical.

Alternatively, you can move a manifold of signal conditioners around with the notebook PC. To connect the transducers to the manifold, you probably should use an STU that you can plug into the manifold. Such an arrangement avoids the need to shut down the experiment to connect the data-acquisition system. However, when you carry around a setup that includes a signal-conditioner manifold, you're transporting a system that's about as large and heavy as one based on an external data-acquisition unit. Moreover, if both systems use plug-in STUs, the systems are equally easy to connect.

Compared with personal computing, and especially with notebook PCs, the pace of change in data acquisition—at least on the hardware side—appears glacial. But the marriage of portable computing and data acquisition has permanently changed data acquisition. PCMCIA data-acquisition cards are a stunning development. External units for notebook PCs, though lacking in some of the tiny cards' futuristic flavor, can be equally useful. When all questions require answers yesterday, portable data-acquisition equipment often offers the only hope of getting the necessary information on time.

EDN



You can reach Senior Technical Editor Dan Strassberg at (617) 558-4205, fax (617) 928-4205, e-mail: ednstrassberg@cahners.com

## VOTE

Please use the Information Retrieval Service card to rate this article (circle one):


High  
Interest  
590

Medium  
Interest  
591

Low  
Interest  
592

DAQValue

## Portable Data Acquisition

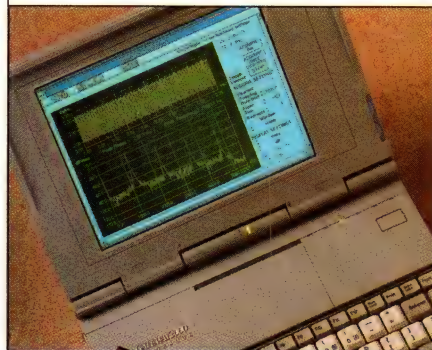

## Performance and Portability – We Give You Both.

## DAQPad™-1200

- Parallel port interface
- 100 ksamples/s
- 8 analog inputs, 2 analog outputs, 24 digital I/O lines, 3 counter/timers
- DC power, optional battery pack




## DAQCards™

- Type II PCMCIA cards
- 100 ksamples/s
- 16 analog inputs
- 24 digital I/O lines
- 2 counter/timers


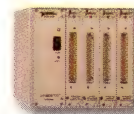
## SCXI

- Parallel port or PCMCIA interface
- Signal conditioning and data acquisition
- Expandable to 128 channels
- DC power, optional battery pack



## Software

- NI-DAQ® driver software for:
  - LabVIEW®
  - LabWindows®/CVI
  - Basic, C/C++, Visual Basic, Pascal, and many more



## Call for FREE

## DAQ Designer™ Software

(800) 433-3488 (U.S. and Canada)

**NATIONAL INSTRUMENTS™**  
The Software is the Instrument®

Tel: (512) 794-0100

Fax: (512) 794-8411


Come to NI Week, July 23-28

© Copyright 1995 National Instruments Corporation. All rights reserved. Product and company names listed are trademarks or trade names of their respective companies.


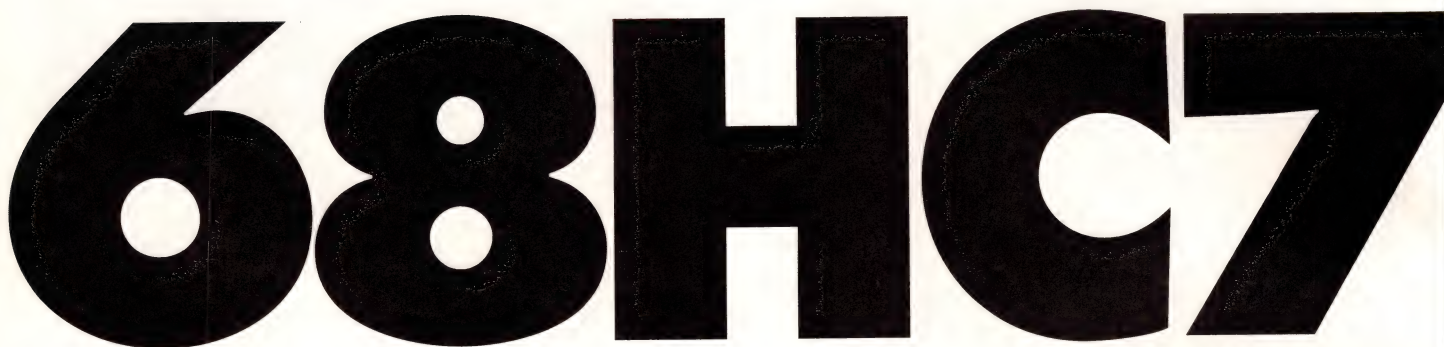
## [ WHAT'S IN A NAME? ]

This device's High-Density Complementary Metal Oxide (HCMOS) manufacturing process provides speed, low power consumption and a wide variety of operating voltage ranges.



# 68HC7

The number that got things rolling. Motorola's industry standard, microcontroller/microprocessor family architecture.

When you seek an EPROM device with One Time Programmable (OTP) memory technology, 7 is your lucky number. The OTP emulates the ROM version.

Meeting customer needs is the name of the game for Motorola's Customer-Specified Integrated Circuit (CSIC) design methodology.

Our new 8-bit OTP device, the 68HC705J1A, is a prime example.

The 68HC705J1A has it all. Code security, keyboard interrupt, a Computer Operating Properly

(COP) watchdog system, and a price of less than \$1.00 when ordered in high volume.

There's even a 68HC705J1A development kit to get you started. Introductory-priced at \$99\*. And available only at your local distributor. Plus, as an extra incentive, we're having a customer design contest that



The first device in the J-series. A proven low cost and low power consuming solution in a 20-pin package with 14 bi-directional I/O lines, 1.2K bytes of EPROM and 64 bytes of RAM. This one's enhanced CPU core has a 15-stage multifunctional timer. A real winner for 8-bit applications.



# 5J1A

A 68HC05 family member, a.k.a. the world's most popular line of 8-bit microcontrollers, with more than 180 versions.

Loaded with special "Grade A" enhancements, including outputs that directly drive LEDs, and software programmable pulldowns on all I/O pins.

gives you an opportunity to be awarded a brand new Ford Explorer\*\*.

The versatile 68HC705J1A. The perfect device for logic and mechanical replacement in industrial, communications, computer, automotive applications, and more.

And remember, for all your microcontroller needs, we offer more than

180 CSIC-based 68HC05 solutions. Or we'll design a custom derivative to meet the specific needs of your high-volume design. Quickly. Efficiently. And cost-effectively.

World-class microcontroller solutions. By any other name, they're just not Motorola.

To reserve your development kit

and to receive an entry form, rules and details about the design contest, contact your local Motorola distributor. Or for more information on the 68HC705J1A, contact us at 1-800-765-7795, ext. 813 or by FAX at 1-800-765-9753, or write us at P.O. Box 13206, Austin, Texas 78711-9855.

## The world's leading 8-bit solutions.



**MOTOROLA**



# Video fader preserves synchronization

FRANK COX, LINEAR TECHNOLOGY CORP, MILPITAS, CA

The common video effect "fade to black" is usually accomplished by increasing video signal attenuation to the point where the picture disappears, leaving a black screen. As the composite signal is attenuated, the signal's sync amplitude becomes too small to synchronize the picture properly, and the picture rolls and tears. One solution is to run a separate sync line to the monitor, but this is not a viable choice in composite systems.

Fig 1 shows a simple video "volume control" that operates on the picture but leaves the sync unchanged, allowing a smooth fade to black while maintaining video fidelity. High-speed op-amp IC<sub>1</sub> and its associated components form a basic sync separator. C<sub>1</sub>, R<sub>1</sub>, and D<sub>1</sub> clamp and clip composite video. D<sub>2</sub> biases the input of IC<sub>1</sub> to compensate for the voltage drop across D<sub>1</sub>. When D<sub>1</sub> conducts, IC<sub>1</sub> amplifies the most negative portion of the waveform (containing the sync information). Clamp-network D<sub>4</sub> through D<sub>7</sub> in the feedback of IC<sub>1</sub> prevents the amplifier from saturating and, thus, from


slowing the response. D<sub>3</sub> and a CMOS inverter complete the shaping of the sync waveform. The sync separator works with most video signals that have a minimum sync amplitude of 0.3V and are not excessively noisy or distorted.

Video-fader IC<sub>2</sub> is configured to fade between the original video and the sync stripped from that video. A voltage reference and a potentiometer generate a control voltage. This node (pin 3 of IC<sub>2</sub>) should be bypassed if the control is mounted a significant distance from the circuit or if the control generates any noise when adjusted. As the control voltage nears the lower 2% of its range, IC<sub>2</sub> automatically shuts off the channel with the active video (pin 1) and fully turns on the channel with the sync (pin 14). This feature makes the circuit more tolerant of offset or gain errors in the control signal. (DI #1724)

EDN

To Vote For This Design, Circle No. 390

FIGURE 1

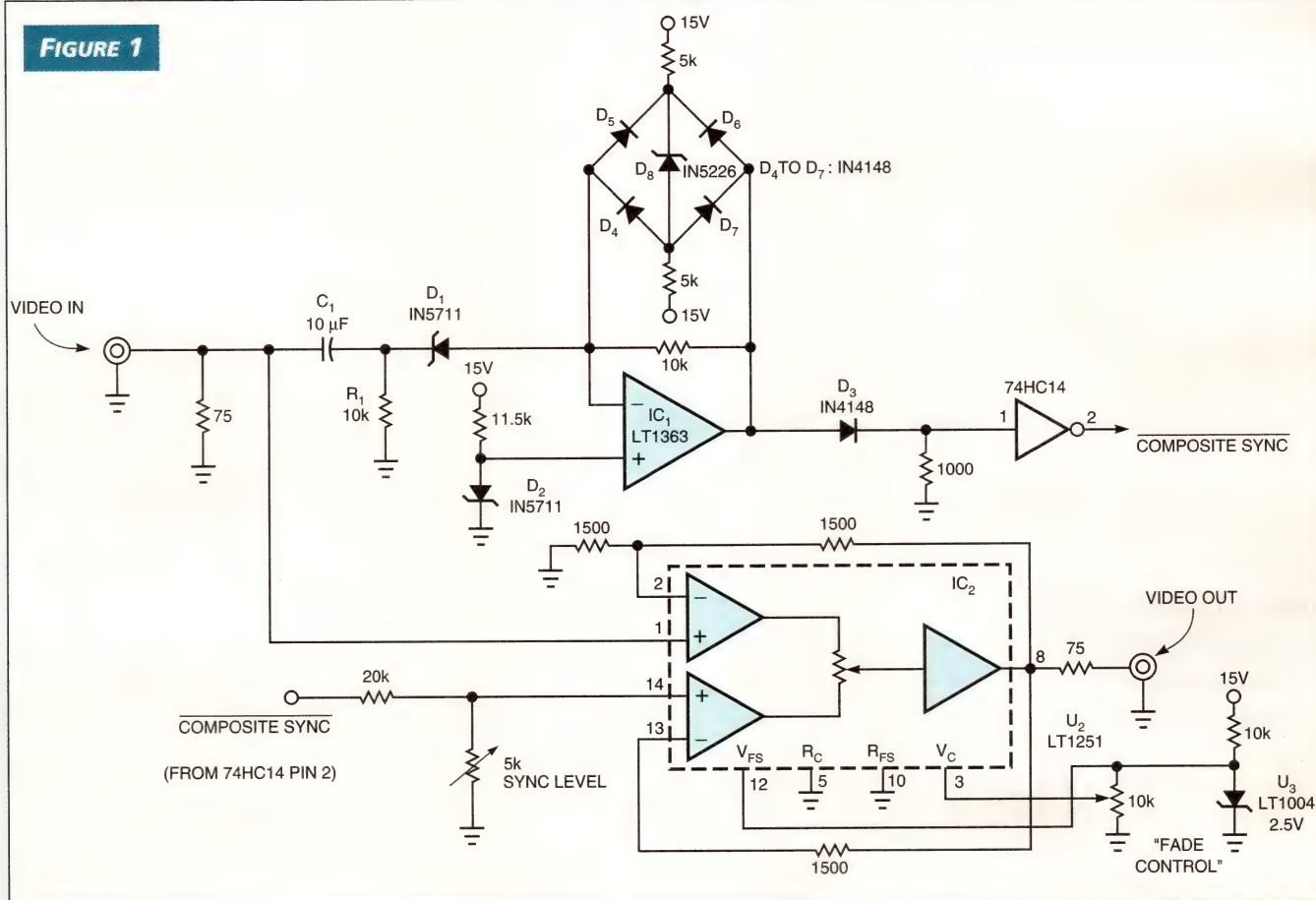

This circuit allows you to maintain sync amplitude while fading a composite-video signal.



# Behavioral Spice model emulates VCO

DR BASHIR AL-HASHIMI, STAFFORDSHIRE UNIVERSITY, STAFFORD, UK

A behavioral model treats a circuit as a black box, which you can describe using an equation or table. Listing 1 is a Microsim PSpice behavioral model that simulates the operation of a voltage-controlled oscillator (VCO). The output signal of a VCO is  $V_o = A \cdot \sin(2\pi f_o t)$ , where  $A$  is the amplitude,  $t$  is the time variable, and  $f_o$  is the output frequency. This fre-

quency is  $f_o = f_c + KV$ , where  $f_c$  is the center frequency,  $K$  is the sensitivity of the VCO in Hz/V, and  $V$  is the control-input signal.

The model expresses these equations using a VALUE description of a voltage-controlled voltage source. Note that the parameter TIME in the model represents the PSpice internal sweep variable used in transient analysis. To simplify use of the model, describe it as a parameterized subcircuit called VCO, whose input is at node 1 and whose output is at node 2. Describe the model function using the three parameters  $A$ ,  $f_c$ , and  $K$ . You must give the subcircuit parameters initial values to satisfy the .SUBCKT statement requirement. In this example, I arbitrarily set them to one; you'll change them to the required values when the program calls the subcircuit.

To use the model to simulate a VCO circuit, specify the parameters  $A$ ,  $f_c$ , and  $K$ . For example, if  $A=2V$ ,  $f_c=10$  kHz,  $K=5$  kHz/V, and the input control voltage ranges from +1 to -1V, the output frequency changes from 15 to 5 kHz, as Fig 1 shows. Listing 2 gives the PSpice netlist of the VCO circuit. (DI #1726) **EDN**

To Vote For This Design, Circle No. 391


## LISTING 1—VCO BEHAVIORAL MODEL

```
.SUBCKT VCO 1 2 PARAMS:A=1, Fc=1, K=1
E 2 0 VALUE={A*SIN(6.283*TIME*(Fc+K*V(1,0)))}
.ENDS VCO
```

## LISTING 2—VCO-CIRCUIT PSpice NETLIST

```
.LIB C:\PSPICE\MODELS ;VCO model location
V 1 0 PULSE(-1 1 0 10ns 10ns 0.5ms 1ms) ;control input signal
.TRAN 0.01m 2ms 0m 0.01m ;transient analysis range
X 1 2 VCO PARAMS:A=1, Fc=10K,K=5K ;call VCO subcircuit
.PROBE V(1),V(2) ;graphic input & output signals
.END ;end of netlist
```

FIGURE 1

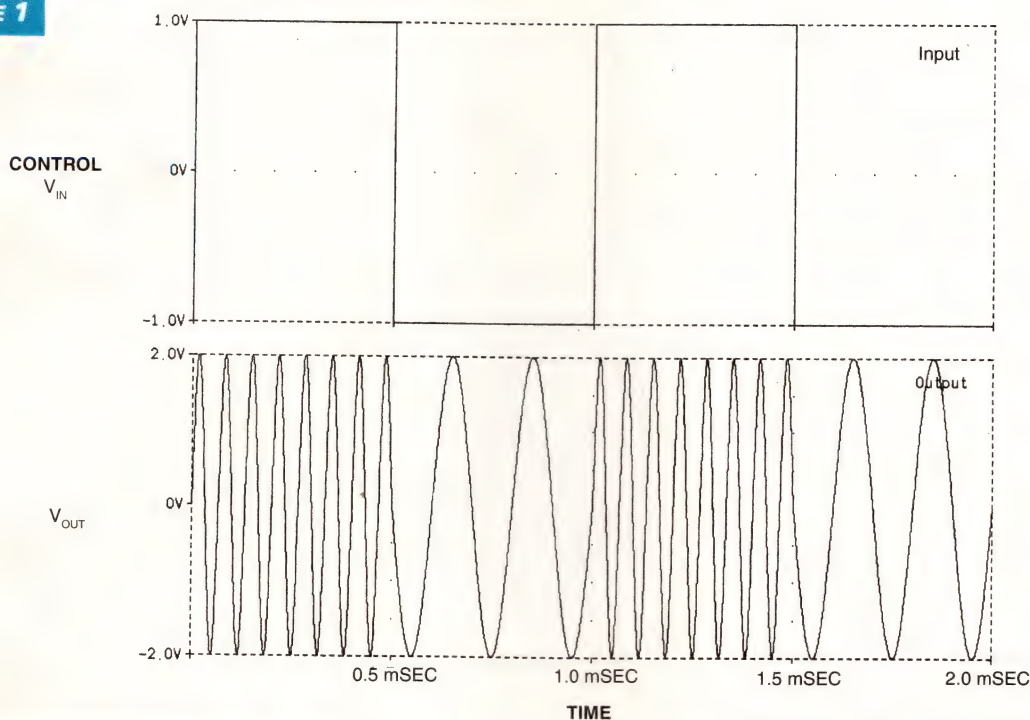

The bottom plot shows the result of a PSpice simulation of a VCO. When the control-input voltage changes from +1 to -1V, the output frequency changes from 15 to 5 kHz.



# Circuit guards against battery reversal

DANA DAVIS, MAXIM INTEGRATED PRODUCTS, SUNNYVALE, CA

The circuit in Fig 1 protects a battery-operated system in two ways:  $Q_1$  prevents damage from the flow of reverse current that could occur if you install the battery backward, and  $Q_3$  prevents the excessive current flow that could occur with a sudden load increase or a short circuit. A properly installed battery fully enhances  $Q_1$  by pulling its gate voltage more than 5V below the source voltage. If you install the battery backward,  $Q_1$  stays off because the gate voltage is positive with respect to the source voltage. Regardless of battery polarity, the orientation of the body diodes of  $Q_1$  and  $Q_3$  ensures that no current can flow when either device is off.

$IC_2$  is a current-sensing amplifier that senses the load current flowing between its  $RS^+$  and  $RS^-$  terminals.  $IC_2$ 's output is a proportional but smaller (1.5 mA max) current at the OUT pin, which develops a voltage across  $R_8$  proportional to the load current. During normal operation, both comparator outputs are high, and  $Q_3$  remains on.

When the load current exceeds a limit set by  $R_8$  ( $I_{LIMIT} = 2000V_{TH}/R_8$ ), where 2000 is the sense amplifier's gain, and


$V_{TH}$  is the comparator's input threshold of  $1.182V \pm 2\%$ , the B-comparator output switches low and turns off  $Q_4$ , which turns off  $Q_3$  and disconnects the battery from its load. At the same time,  $Q_6$  provides positive feedback by pulling the comparator input to the level of the collapsing supply rail, latching  $Q_3$  off as the supply voltage drops.

An output short circuit turns off  $IC_2$  by removing the voltage at pins 6 and 7 (3V is the minimum for proper operation). Control via the B comparator disappears because the  $R_8$  voltage goes to zero for this short-circuit condition, but comparator A then shuts off  $Q_5$  by turning off  $Q_5$ .  $Q_2$  speeds the  $Q_3$  turn-off time to about 10  $\mu$ sec. When  $Q_3$  is off, the circuit draws about 2  $\mu$ A. During normal operation, the battery current varies with its terminal voltage: 200  $\mu$ A at 5V, 230  $\mu$ A at 6V, 300  $\mu$ A at 8V, and 310  $\mu$ A at 10V. To restore power, press  $S_1$ . (DI #1730)

EDN

To Vote For This Design, Circle No. 392

FIGURE 1

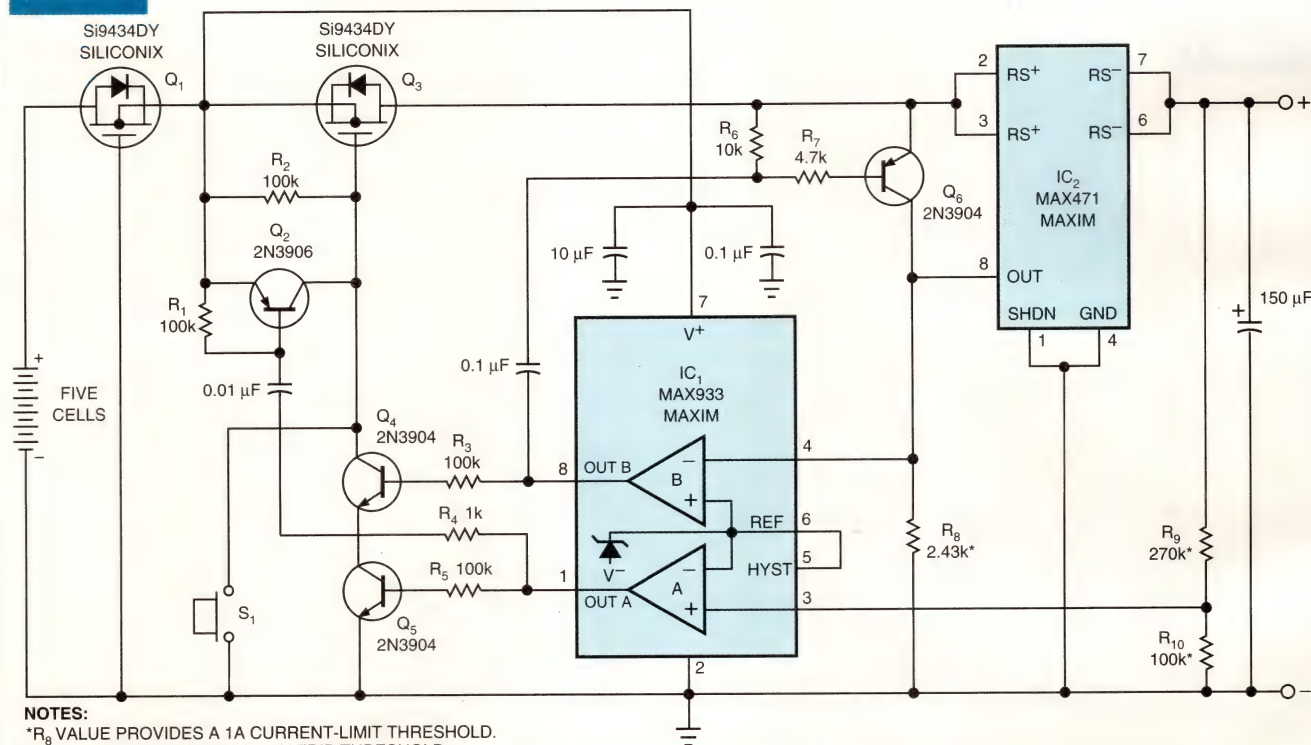

This circuit prevents damage from reverse current that flows when a battery is installed backward. The circuit also prevents excessive current flow that arises from a sudden load step or short circuit.



# Keep it light with **VoiceChip**<sup>TM</sup>

## and fly right by the competition to success!

**VoiceChip** is the new, highly-integrated controller chip for voice recording and playback. **VoiceChip** provides a comprehensive solution to your design needs on one very efficient, cost-sensitive chip. Combined with external flash memory, **VoiceChip** delivers the solid-state recording capabilities that are particularly useful for mobile products.

**VoiceChip** enables you to achieve very competitively priced, highly-reliable voice recording, storage and playback equipment.

Don't pack excess device count into your product. Specify **VoiceChip** by EUROM.

### *VoiceChip incorporates:*

- Built-in A/D and D/A channels
- Up to 20 minutes of voice storage in 1 Mbyte of external flash memory
- On-chip controller for audio compression algorithms
- Embedded voice sampling and playback interfaces
- Integrated keyboard support
- Built-in LCD display driver
- Variable voice compression per message
- Real time clock
- Alarm capability
- Built in filing system



sadna/graphic design

Call or fax:



- **Headquarters: EUROM FlashWare Solutions Ltd.**  
Atidim Industrial Park Bldg. 1, P.O.B 58032, Tel Aviv 61580, Israel  
Tel: +972-3-490 920 Fax: +972-3-490 922
- **USA Office: EUROM FlashWare Solutions Inc.**  
4655 Old Ironsides Drive, Suite 290, Santa Clara, CA 95054  
Tel: 408-748-9995 Fax: 408-748-8408



# Measure inductance with dc superimposed

HB FARENSBACH, CONSULTANT, ALBANO, ITALY

In some applications, magnetic components are difficult to characterize when steady-state current is flowing. Bridges having the necessary dc capability are expensive. If you don't need extreme precision (for example, 2% or better), other measurement methods exist. The method in Fig 1 is universally applicable over a range of inductances and frequencies. The basis for the inductance measurement is to determine the ac impedance at the frequency (f), ideally the inductor's working frequency of interest. In Fig 1, the ac voltages across the inductor and the reference resistor  $R_R$  are  $V_{LAC}$  and  $V_{RAC}$ , respectively, and the circulating alternating current is  $I_{AC}$ .

You need the following two components for proper operation: 1. The dc isolation transformer with a gap that prevents saturation at the maximum rated dc. In this example, for 25A current, use an EI-configured core of 0.014-in. grain-oriented silicon steel. The primary winding uses 160 turns of AWG 30 double-covered magnet wire. The secondary winding consists of 32 turns of AWG 14 magnet wire wound in two steps: 16 turns, followed by the primary winding, followed by the final 16 turns. 2. The reference resistor, which must have four terminals (two for forcing current, two for sensing voltage) if its value is lower than  $3\Omega$ . It also must have negligible inductance and skin effect at the frequency of interest. One way to make a resistor with such characteristics is to connect several (maybe five to 10) metal-film resistors in parallel.

To keep errors low, ensure that  $3V_{RAC}$  is less than  $V_{LAC}$ . Check oscilloscope photos to be sure the waveforms are rea-

sonably sinusoidal, denoting that the flux density is below the saturation level. You can also measure the dc  $I_{DC}$  by using the same DVM or the oscilloscope in dc mode. To determine the impedance,  $Z_L$ , use the following equations:

$$Z_L = \frac{V_{LAC}}{I_{LAC}} = \frac{V_{LAC} \times R_R}{V_{RAC}}$$

$$L = \frac{Z_L}{2\pi f} = \frac{V_{LAC} \times R_R}{2\pi f V_{RAC}}$$

The error in  $V_{LAC}$  from  $V_{RAC}$  is negligible because these two quantities are  $90^\circ$  out of phase. Measure both  $V_{LAC}$  and  $V_{RAC}$  the same way—by using the oscilloscope's p-p value, the DVM's average value, or the DVM's rms value. The power supply should have 3 to 5% maximum ripple and a constant-current setting for ease of making repeated measurements. The zener diodes across the primary winding protect the frequency generator against spikes that occur when you instantaneously apply or cut off the dc.

An example uses a 50- $\mu$ H inductor operating at 100 kHz, with a 100-m $\Omega$  reference resistor,  $R_R$ . Measurements yield  $V_{RDC}=1V$  (10A),  $V_{LAC}=1.2V$ , and  $V_{RAC}=38$  mV.


$$L = \frac{V_{LAC} R_R}{2\pi f V_{RAC}} = \frac{1.2V \times 0.100\Omega}{6.28 \times 100,000 \text{ Hz} \times 0.038V} = 5.03 \mu\text{H}$$

(DI #1729)

EDN

To Vote For This Design, Circle No. 393

FIGURE 1

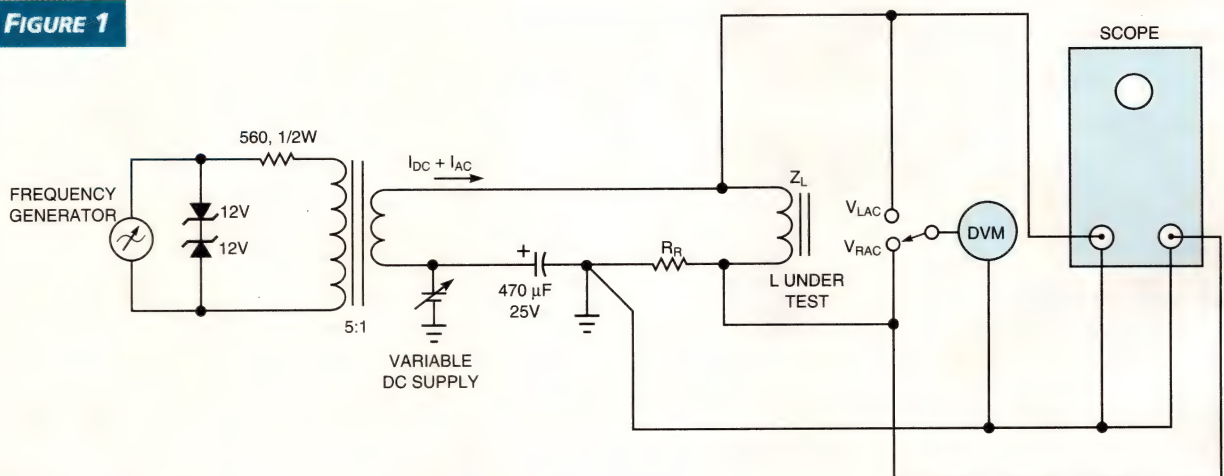


Using this circuit, you can measure inductance with any amount of direct current superimposed.


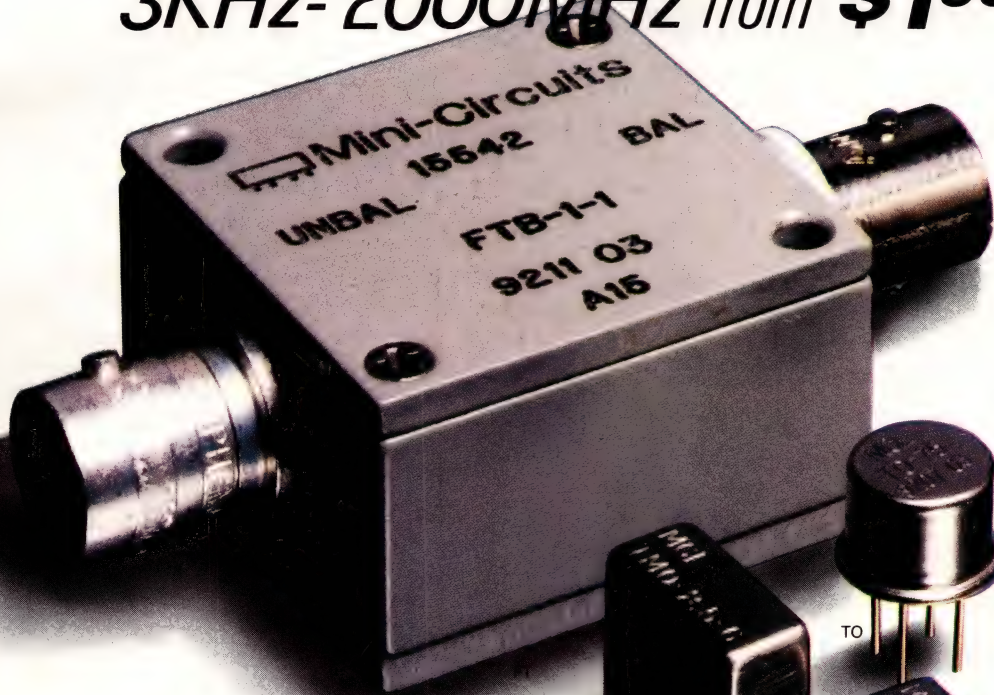
# RF TRANSFORMERS

Over 80 off-the-shelf models...  
3KHz- 2000MHz from **\$1<sup>95</sup>**




Having difficulty locating RF or pulse transformers with low droop, fast risetime or a particular impedance ratio over a specified frequency range?... Mini-Circuits offers a solution.

Choose impedance ratios from 1:1 to 36:1, in connector, TO-, flatpack, surface-mount, or pin versions (plastic or metal case built to meet MIL-T-21038 and MIL-T-55631 requirements\*). Coaxial connector models are offered with 50 and 75 ohm impedance; BNC standard, other types on request.

Ultra-wideband response achieves low droop and fast risetime for pulse applications. Ratings up to 1000M ohms insulation resistance and up to 1000V dielectric voltage. For wide dynamic range applications involving up to 100mA primary current, use the T-H series. Fully detailed data appear in our 740-pg RF/IF Designer's Handbook.

Need units in a hurry?... all models are covered by our exclusive one-week shipment guarantee. Only from Mini-Circuits.

\*units are not QPL listed.

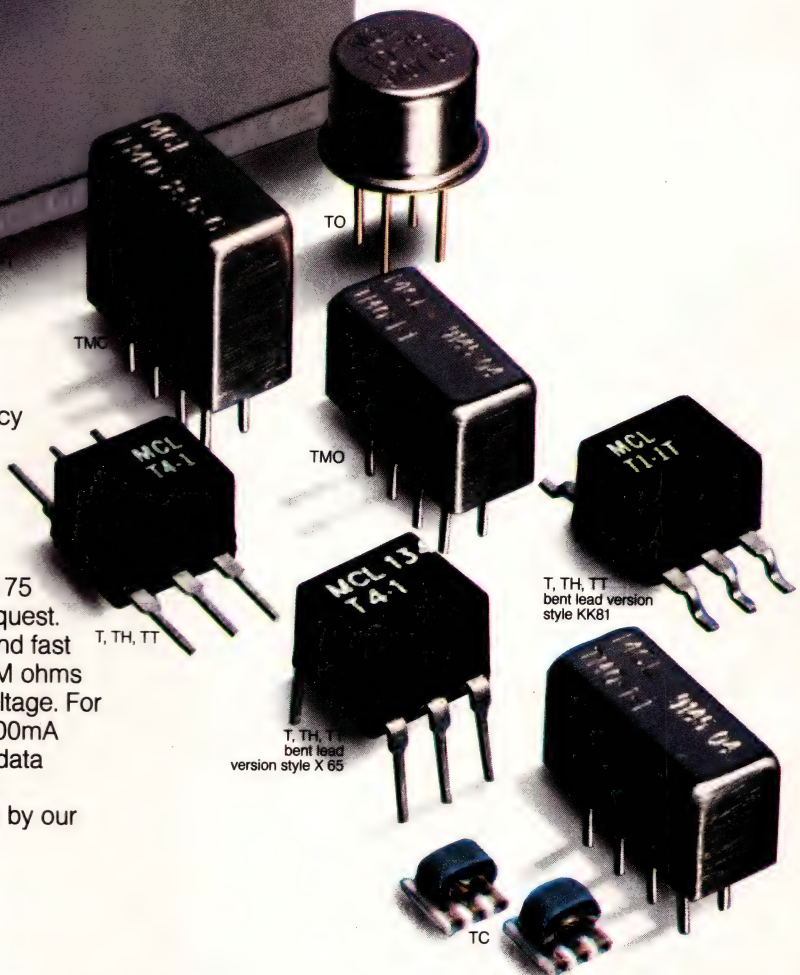

**Mini-Circuits®**

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER • MICROWAVE PRODUCT DATA DIRECTORY • EEM • MINI-CIRCUITS' 740-pg. HANDBOOK.

*CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.*

F 71 Rev F



# "Zero-power" A/D converter uses printer port

DHANANJAY GADRE, IUCAA INSTRUMENTATION LAB, PUNE, INDIA



You can use a desktop or laptop PC to monitor physical variables such as temperature or pressure. A convenient way to do this is to connect an A/D converter through the ubiquitous Centronics printer port (Fig 1). The current requirement of the ADC0804LCN used here is less than 1.5 mA at 5V supply voltage with a 640-kHz clock. Tristate-buffer 74HC244 multiplexes 8 bits of A/D-converter data through 4 bits (54 through 57) of the status port of the printer adapter.

This design does not require an external power supply, because it uses the RS-232C port of the PC to satisfy its meager power requirements. Most RS-232C ports are capable of delivering a current of about 10 mA. Of this current budget, the circuit shown here consumes about 3 mA. You could use the remaining available current to power additional circuitry. The 5V for the A/D converter and the tristate switch derives from the RS-232C port's DTR and RTS signal lines.

Because the power requirement is low, you can use a pair of LM-336-2.5V reference diodes to set the voltage and to generate the 2.5V reference for the A/D converter.


Control-port bits C0 and C1 control the tristate switch, IC<sub>2</sub>. The power-on reset level of C0 and C1 is logic one, so you run no risk of shorting IC<sub>2</sub>'s outputs. The other 2 control bits, C2 and C3, generate the read and write strobes for the A/D converter. The INTR pin of the A/D converter, which status-port bit S3 monitors, indicates end of conversion for the converter. With the component values shown, the converter has a 200-μsec conversion time on a 16-MHz AT, running the C code in Listing 1. A Turbo C version 2.01 compiler compiled this source code. (DI #1728) **EDN**

To Vote For This Design, Circle No. 394

(Listing 1 on pg 72)

FIGURE 1

REGISTER/DB-25 PIN/CENTRONICS PIN

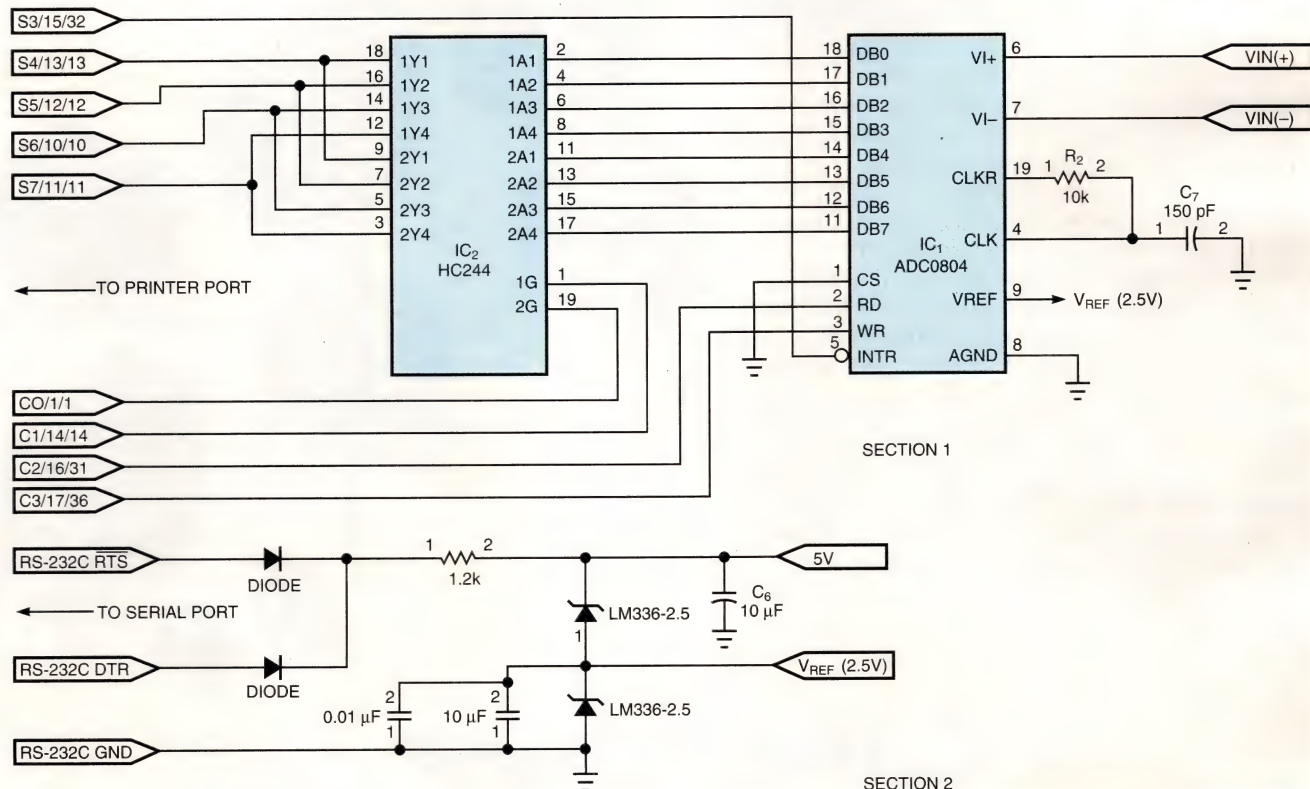

This A/D converter takes its power from the PC's RS-232C port and thus needs no external power source.



# μP SUPERVISOR AND LITHIUM BATTERY IN ONE SPACE-SAVING PACKAGE


## Low-Cost, Complete Package with MAX691A & 125mAh Battery

The new MAX1691A μP supervisor module contains a MAX691A and 125mAh lithium battery. It provides complete μP supervisory functions, as well as backup power for CMOS memory and real-time clocks. The 700 x 875-mil package reduces board space and saves design time.

### COMPLETE μP SUPERVISION AND MEMORY BACKUP IN 700 x 875 mil PACKAGE



MAX1691CHE

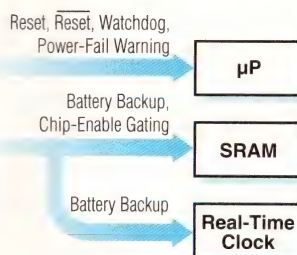

The MAX1691 provides complete μP supervision with battery backup for memory and real-time clocks.

- ◆ Complete solution:
  - MAX691ACSE + 125mAh Lithium Battery
- ◆ RST and  $\overline{\text{RST}}$  Outputs
- ◆ 4.65V Reset Threshold
- ◆ Battery Backup Switchover
- ◆ Watchdog Timer
- ◆ 10ns Max Chip-Enable Gate Delay
- ◆ Power-Fail Warning
- ◆ Output Current:
  - 250mA Operating
  - 50mA Standby
- ◆ Supply Current:
  - 35μA Operating
  - 1μA Standby



**FREE μP Supervisory Design Guide—Sent Within 24 Hours!**  
Includes: Data Sheets and Cards for Free Samples

**CALL TOLL FREE 1-800-998-8800**  
**For a Design Guide or Free Sample**

MasterCard® and Visa® are accepted for evaluation kits and small-quantity orders.

**MAXIM**



Distributed by Arrow, Bell, CAM RPC, Digi-Key, Elmo, Hamilton Hallmark, Nu Horizons, and Zeus. Authorized Maxim Representatives: **AL**, EnVision; **AZ**, Techni Source Inc.; **CA**, (Northern California) Maxim Integrated Products, (Southern California) Mesa, Infinity Sales, Inc.; **CO**, Component Sales; **CT**, Comp Rep Associates; **DE**, TAI Corporation; **FL**, Sales Engineering Concepts; **GA**, EnVision; **ID**, E.S. Chase; **IL**, Industrial Representatives, Inc.; **IN**, Technology Marketing Corp; **IA**, JR Sales Engineering, Inc.; **KS**, Delltron; **KY**, Technology Marketing Corp; **LA**, Maxim Integrated Products, Inc.; **MD**, Micro-Comp, Inc.; **MA**, Comp Rep Associates; **MI**, Micro Tech Sales; **MN**, Hanna Lind; **MO**, Delltron; **MT**, E.S. Chase; **NE**, Delltron; **NH**, Comp Rep Associates; **NJ**, Parallax, TAI Corporation; **NM**, Techni Source Inc.; **NY**, Parallax, Reagan/Compar; **NC**, EnVision; **OH**, Lyons Corporation; **OK**, Maxim Integrated Products, Inc.; **OR**, E.S. Chase; **PA** (Pittsburgh area) Lyons Corporation, (Philadelphia area) TAI Corporation; **SC**, EnVision; **TX**, Hamilton Hallmark; **UT**, Luscombe Engineering Co.; **VA**, Micro-Comp, Inc.; **WA**, E.S. Chase; **WI**, Industrial Representatives, Inc.

Distributed in Canada by Arrow. Authorized Maxim Representative in Canada: Tech Trek.

**Austria**, Maxim GmbH (Deutschland); **Belgium**, Master Chips; **Denmark**, Arrow-Exatec A/S; **Finland**, Yleiselektronikka Oy; **France**, Maxim France, Distributors: Maxim France, ASAP; **Germany**, Maxim GmbH, Distributors: Maxim GmbH, Spezial Electronic KG; **Ireland**, FMG Electronics; **Italy**, Consystem S.r.l., Distributor: Esco Italiana Electronics Supply; **Netherlands**, Koning En Hartman; **Norway**, Berendsen Electronics; **Poland**, Unipro, Ltd.; **Portugal**, ADM Electronics, S.A.; **Spain**, ADM Electronics S.A.; **Sweden**, Egevo AB; **Switzerland**, Laser & Electronics AG; **Turkey**, Interex (U.S.A.); **U.K.**, Maxim Integrated Products (U.K.), Ltd., Distributors: Maxim Integrated Products (U.K.), Ltd., 2001 Electronic Components, HB Electronics.

MAXIM is a registered trademark of Maxim Integrated Products. © 1995 Maxim Integrated Products.

North American inquiries, Circle No. 92

European inquiries, Circle No. 93

EDN JULY 6, 1995 ■ 71



## LISTING 1—SOURCE CODE FOR ZERO-POWER A/D CONVERTER

```

#include <stdio.h>
#include <dos.h>
#include <conio.h>
#include <process.h>

#define RESET_VALUE      0X04          /* C3* C2 C1* C0* */
#define START_ADC_CONV   0X0c          /* 0 1 0 0 */
#define READ_UPPER_NIBBLE 0X01          /* 1 1 0 0 */
#define READ_LOWER_NIBBLE 0X02          /* 0 0 0 1 */
/* 0 0 1 0 */

void main(void)
{
    int modem_control_reg, dport_lpt1, cport_lpt1, sport_lpt1;
    unsigned char adc_status, adc_val, upper_nib, lower_nib, intr_status;

    /* Sign ON */
    clrscr();
    printf("Zero power (well almost) ADC for printer port, Version 1.0");
    printf("\nD.V.GADRE");

    /* Get COM1 register address */
    modem_control_reg = peek(0x40,0)+4;
    if(modem_control_reg == 4)
        printf("\n\nCOM1 not available... aborting\n\n\n");
        exit(1);

    printf("\n\nCOM1 address = %X",peek(0x40,0) );

    /*Get LPT1 port addresses */
    dport_lpt1 = peek(0x40,0x08);
    if(dport_lpt1 ==0)
        printf("\n\nLPT1 not available... aborting\n\n\n");
        exit(1);

    printf("\n\nLPT1 address = %X", dport_lpt1);
    cport_lpt1 = dport_lpt1 +2; /* control port address */
    sport_lpt1 = dport_lpt1 +1; /* status port address */

    /* put power On on COM1 */
    outportb(modem_control_reg, 03);
    printf("\nPutting Power ON...");

    /* check if ADC is connected & working */
    /* start ADC conversion & wait for 1 ms, this puts INTR to logic '0' */
    /* reset the control port */
    outportb(cport_lpt1, RESET_VALUE);
    sleep(1);

    /* start conversion */
    outportb(cport_lpt1, START_ADC_CONV);
    outportb(cport_lpt1, RESET_VALUE);
    sleep(1);

    /* hopefully the conversion is over, so read the INTR status */
    /* if everything is OK, INTR should be '0' */
    adc_status = inportb(sport_lpt1) & 0x08;
    outportb(cport_lpt1, READ_LOWER_NIBBLE);
    outportb(cport_lpt1, RESET_VALUE);

    /* read the INTR status again */
    /* if everything is OK, INTR should be '1' */
    intr_status = inportb(sport_lpt1) & 0x08;
    if( !( (adc_status == 0) && (intr_status == 0x08) ) )
        printf("\n\nADC not connected... aborting\n\n\n");
        exit(1);

    /* acquire ADC sample */
    while(!kbhit())
    {
        outportb(cport_lpt1, RESET_VALUE);
        outportb(cport_lpt1, START_ADC_CONV);
        outportb(cport_lpt1, RESET_VALUE);
        wait_for_conv:
        adc_status = inportb(sport_lpt1) & 0x08;
        while(adc_status)
        {
            adc_status = inportb(sport_lpt1) & 0x08;
        }
        read_upper_nibble:
        outportb(cport_lpt1, READ_UPPER_NIBBLE);
        upper_nib = inportb(sport_lpt1) & 0x0f0;
        outportb(cport_lpt1, RESET_VALUE);
        read_lower_nibble:
        outportb(cport_lpt1, READ_LOWER_NIBBLE);
        lower_nib = inportb(sport_lpt1) >> 4;
        outportb(cport_lpt1, RESET_VALUE);
        adc_val = (lower_nib | upper_nib) ^ 0x88;
        delay(10);
        printf("sample = %X ", adc_val);
    }
}

```

## Serial-interface IC supplies bipolar voltages

GARY SELLANI, MAXIM INTEGRATED PRODUCTS, SUNNYVALE, CA

Some available ICs for serial-data interface not only operate from low supply-rail voltages (5 or 3.3V) but also generate bipolar dc voltages ( $\pm 6.5$  to  $\pm 10$ V) to meet minimum driver-output levels specified by EIA/TIA-232. With care, you can "steal" useful amounts of power from these rails without interfering with the IC's operation.

In Fig 1, switch-mode-controller IC<sub>1</sub> operates with an external inductor, two diodes, and two capacitors to produce  $\pm 6.5$ V. FETs Q<sub>1</sub> and Q<sub>2</sub> ensure start-up for the circuit by disconnecting the load until these switch-mode supply voltages are present. Q<sub>1</sub> must be a logic-level device.


Unlike ICs designed to generate supply voltages, an interface IC generally doesn't specify how much current you can draw from its internally generated supply rails. The amount

available depends almost entirely on loads connected to the driver outputs. For example, IC<sub>1</sub> guarantees that one transmitter can drive a parallel combination of 1 k $\Omega$  and 1000 pF at 250 kbps, and the other two transmitters can maintain dc outputs across 3-k $\Omega$  loads.

To calculate the maximum output current available, superimpose the ac and dc components. Output current flows alternately from each rail as the NRZ output waveform swings between the guaranteed-minimum-output levels ( $\pm 5$ V). Assuming the output requires one whole data period (4  $\mu$ sec at 250 kbps) to slew from  $-5$  to  $+5$ V, the ac component equals  $C_{LOAD}(dV/dt)=1000$  pF (10V/4  $\mu$ sec)=2.5 mA. For the dc component, Ohm's law gives  $I=E/R=5$ V/3 k $\Omega$ =1.67 mA from one transmitter, so the three transmitters together



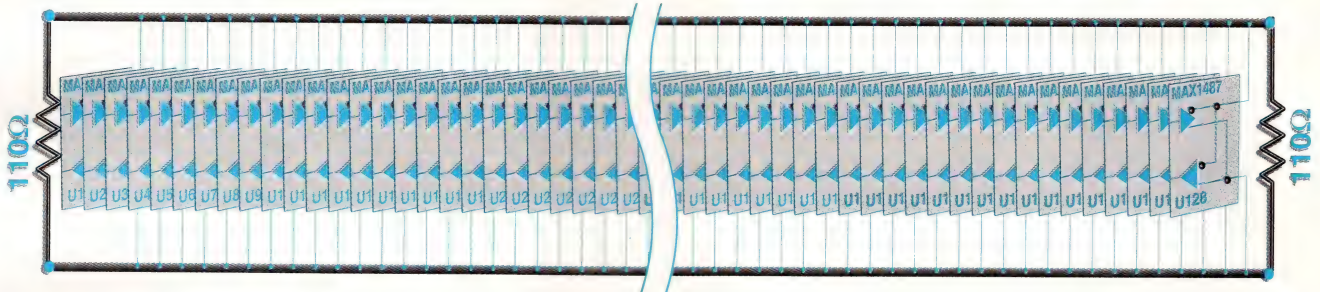
# PUT 128 RS-485 TRANSCEIVERS ON ONE PAIR OF WIRES!


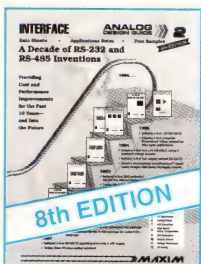
## New MAX1487 Runs at 2.5Mbps, Guaranteed!

Thanks to a 1/4-unit-load receiver, Maxim's new MAX1487 and the MAX487 are guaranteed to allow up to 128 RS-485 transceivers on one pair of wires—four times more than what other RS-485 transceivers allow.

- ◆ 120μA Supply Current—MAX487
- ◆ 230μA Supply Current—MAX1487
- ◆ Slew-Rate Limited to Reduce EMI and Reflections—MAX487
- ◆ 0.1μA Shutdown Mode
- ◆ Available in 8-Pin μMAX (the Smallest 8-Pin SO)
- ◆ Pin-Compatible with Industry-Standard 75176
- ◆ \$1.25 for 1000 Pieces\*



**FREE Interface Design Guide—Sent Within 24 Hours!**  
Includes: Data Sheets and Cards for Free Samples

**CALL TOLL FREE 1-800-998-8800**  
**For a Design Guide or Free Sample**

MasterCard® and Visa® are accepted for evaluation kits and small-quantity orders.

**MAXIM**



Distributed by **Arrow, Bell, CAM RPC, Digi-Key, Elmo, Hamilton Hallmark, Nu Horizons, and Zeus**. Authorized Maxim Representatives: **AL**, EnVision; **AZ**, Techni Source Inc.; **CA**, (Northern California) Maxim Integrated Products, (Southern California) Mesa, Infinity Sales, Inc.; **CO**, Component Sales; **CT**, Comp Rep Associates; **DE**, TAI Corporation; **FL**, Sales Engineering Concepts; **GA**, EnVision; **ID**, E.S. Chase; **IL**, Industrial Representatives, Inc.; **IN**, Technology Marketing Corp; **IA**, JR Sales Engineering, Inc.; **KS**, Delltron; **KY**, Technology Marketing Corp; **LA**, Maxim Integrated Products, Inc.; **MD**, Micro-Comp, Inc.; **MA**, Comp Rep Associates; **MI**, Micro Tech Sales; **MN**, Hanna Lind; **MO**, Delltron; **MT**, E.S. Chase; **NE**, Delltron; **NH**, Comp Rep Associates; **NJ**, Parallax, TAI Corporation; **NM**, Techni Source Inc.; **NY**, Parallax, Reagan/Compar; **NC**, EnVision; **OH**, Lyons Corporation; **OK**, Maxim Integrated Products, Inc.; **OR**, E.S. Chase; **PA** (Pittsburgh area) Lyons Corporation, (Philadelphia area) TAI Corporation; **SC**, EnVision; **TX**, Hamilton Hallmark; **UT**, Luscombe Engineering Co.; **VA**, Micro-Comp, Inc.; **WA**, E.S. Chase; **WI**, Industrial Representatives, Inc.  
Distributed in Canada by **Arrow**. Authorized Maxim Representative in Canada: **Tech Trek**.

**Austria**, Maxim GmbH (Deutschland); **Belgium**, Master Chips; **Denmark**, Arrow-Exatex A/S; **Finland**, Yleiselektronikka Oy; **France**, Maxim France, *Distributors*: Maxim France, ASAP; **Germany**, Maxim GmbH, *Distributors*: Maxim GmbH, Spezial Electronic KG; **Ireland**, FMG Electronics; **Italy**, Consystem S.r.l., *Distributor*: Esco Italiana Electronics Supply; **Netherlands**, Koning En Hartman; **Norway**, Berendsen Electronics; **Poland**, Uniprod, Ltd.; **Portugal**, ADM Electronics, S.A.; **Spain**, ADM Electronics S.A.; **Sweden**, Egevo AB; **Switzerland**, Laser & Electronics AG; **Turkey**, Interex (U.S.A.); **U.K.**, Maxim Integrated Products (U.K.), Ltd., *Distributors*: Maxim Integrated Products (U.K.), Ltd., 2001 Electronic Components, HB Electronics.

\* 1000-up Recommended Resale, FOB USA

**MAXIM** is a registered trademark of Maxim Integrated Products. © 1995 Maxim Integrated Products.

North American inquiries, Circle No. 94

European inquiries, Circle No. 95

EDN JULY 6, 1995 ■ 73



# Test Our Free Sample In Your Own Application.

## INRUSH CURRENT SUPPRESSOR



If you need a standard Inrush Current Suppressor sample that you can use for testing, call us today. We'll send you one on the double. When it comes to current suppressors for switch-mode power supplies, trust Therm-O-Disc with your application requirements.

**THERMODISC®**  
MIDWEST COMPONENTS PRODUCT GROUP

P.O. BOX 3303, MUSKEGON, MI 49443 • (616) 777-4100 • FAX (616) 773-4214


## For Technical Support Assistance...

Call our experienced staff of Sales Engineers for help with application requirements, custom capabilities, or spec data sheets of other Therm-O-Disc products.

**(616) 777-4100**

CIRCLE NO. 4
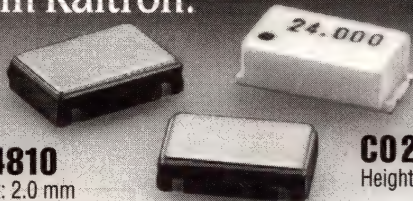
## The Smaller, The Better. Ultra Miniature SMD Crystal Clock Oscillators from Raltron.



### CO4810

Height: 2.0 mm  
(1.6 mm max. available)

### CO2300

Height: 2.3 mm

### CO4910

Height: 2.0 mm  
(1.6 mm max. available)

- SMD miniature package
- High stability/ reliability
- 3.3V version for battery applications

### Frequency Range:

1.8432 to 67 MHz

### Frequency Stability:

± 50, ±100 ppm  
(-10° to 70° C)

### Dimensions:

(CO4810 / CO4910)  
7.5 mm length  
5.0 mm width  
2.0 mm height  
(1.6 mm max. available)

Call or fax your specs to:

**RALTRON**

ELECTRONICS CORP.

2315 NW 107 AVENUE  
MIAMI, FLORIDA 33172 U.S.A.  
FAX (305) 594-3973  
(305) 593-6033

## ONLY RALTRON HAS IT ALL.

Crystals / Crystal Oscillators  
Crystal Filters / Ceramic Resonators

CIRCLE NO. 9

EDN

DESIGN IDEAS

represent a dc load of 5 mA. Adding the ac and dc components gives a conservative maximum rating of 2.5 mA+5 mA=7.5 mA.


The 3-kΩ load is an EIA-232 requirement, but the data rate and load capacitance are application-dependent parameters. Lower values for these parameters make more current available for external use. A remote-sensing system, for instance, might operate at 2400 bps with a load of 3 kΩ in parallel with 1000 pF (50 ft of cable at 20 pF/ft). For three transmitters, the load is 5 mA, and the ac load for one transmitter (72 μA) is almost negligible in this low-data-rate application. The available current in this case is calculated as 7.5 mA-(5 mA+72 μA)=2.428 mA.

These calculations are conservative: With  $V_{CC}$  at 2.7V and the three transmitters loaded with 3 kΩ/1000 pF while transmitting valid EIA-232 levels at 2400 bps, the circuit actually delivers 6.7 mA to an external load. As noted,  $Q_1$  and  $Q_2$  allow the circuit to start under these conditions. If you disconnect the transmitter loads, the maximum external load current that allows start-up is 11.5 mA; with  $Q_1$  and  $Q_2$  removed, the maximum current is only 5.7 mA. (DI #1725)

EDN

To Vote For This Design, Circle No. 395

FIGURE 1

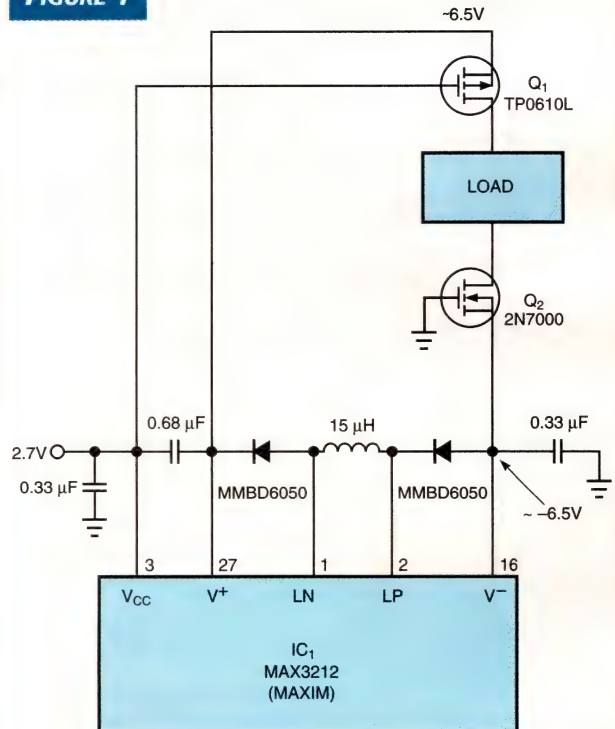


For data rates and driver-output loads less than the maximum allowed, the positive and negative voltage outputs of this serial-interface IC can supply modest amounts of current to an external circuit.



# IMPROVED DG400 SERIES GUARANTEES $3\Omega$ MATCHING & $4\Omega$ $R_{ON}$ FLATNESS, FOR FREE!
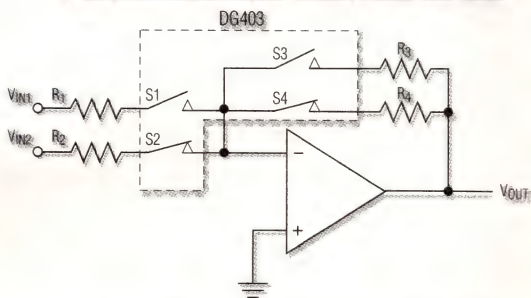
## The Only DG400s with Guaranteed Charge Injection PROGRAMMABLE GAIN AMPLIFIER



Switching into a virtual ground reduces distortion caused by  $R_{DS(ON)}$  variation over the analog signal range. Guaranteed  $R_{DS(ON)}$  matching (typically  $0.5\Omega$ ) ensures gain accuracy of  $<0.01\%$  when  $R1$  through  $R4$  are greater than  $10k\Omega$ .

Maxim's improved DG400 series switches upgrade the industry-standard DG400 devices. These new devices meet all original DG400 specifications. Their tested parameters for  $R_{ON}$  matching and flatness have never before been guaranteed. These new specifications assure lower distortion and improved linearity and accuracy for attenuators, tuned filters, sample-and-hold, and programmable-gain amplifiers. All switches operate over a wide supply voltage range of  $+10V$  to  $+30V$  or  $\pm 4.5V$  to  $\pm 20V$ .

### ONLY MAXIM OFFERS IMPROVED PARAMETERS FOR ALL DG400 FAMILY PARTS

IMPROVED PRODUCT	$R_{ON}$ MATCH ( $\Omega$ )	$R_{ON}$ FLATNESS ( $\Omega$ )	$Q_1$ (pC)	OFF LEAKAGE at $+85^\circ C$ (nA)	ON LEAKAGE at $+85^\circ C$ (nA)
DG401/3/5	2	3	15	5	10
DG411/2/3	3	4	10	5	10
DG417/8/9	3	4	10	5	10
DG421/3/5	3	4	15	5	10
DG441/2/4/5	3	9	10	5	10


- ◆ Guaranteed On-Resistance Match Between Channels ( $3\Omega$ )
- ◆ On-Resistance Flatness ( $4\Omega$ ) Over Signal Range
- ◆ Guaranteed Low Charge Injection (as low as  $10pC$ )
- ◆ 4-Times Less Leakage Over Temp. (less than  $5nA$  at  $+85^\circ C$ )
- ◆ Guaranteed ESD Protection ( $>2kV$ ) per MIL-STD-3015.7

**FREE Mux & Switch Design Guide—Sent Within 24 Hours!**  
Includes: Data Sheets and Cards for Free Samples

CALL TOLL FREE 1-800-998-8800  
For a Design Guide or Free Sample

MasterCard® and Visa® are accepted for evaluation kits and small-quantity orders.

**MAXIM**

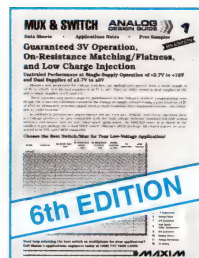

Distributed by Arrow, Bell, CAM RPC, Digi-Key, Elmo, Hamilton Hallmark, Nu Horizons, and Zeus. Authorized Maxim Representatives: **AL**, EnVision; **AZ**, Techni Source Inc.; **CA**, (Northern California) Maxim Integrated Products, (Southern California) Mesa, Infinity Sales, Inc.; **CO**, Component Sales; **CT**, Comp Rep Associates; **DE**, TAI Corporation; **FL**, Sales Engineering Concepts; **GA**, EnVision; **ID**, E.S. Chase; **IL**, Industrial Representatives, Inc.; **IN**, Technology Marketing Corp; **IA**, JR Sales Engineering, Inc.; **KS**, Delltron; **KY**, Technology Marketing Corp; **LA**, Maxim Integrated Products, Inc.; **MD**, Micro-Comp, Inc.; **MA**, Comp Rep Associates; **MI**, Micro Tech Sales; **MN**, Hanna Lind; **MO**, Delltron; **MT**, E.S. Chase; **NE**, Delltron; **NH**, Comp Rep Associates; **NJ**, Parallax, TAI Corporation; **NM**, Techni Source Inc.; **NY**, Parallax, Reagan/Compar; **NC**, EnVision; **OH**, Lyons Corporation; **OK**, Maxim Integrated Products, Inc.; **OR**, E.S. Chase; **PA** (Pittsburgh area) Lyons Corporation, (Philadelphia area) TAI Corporation; **SC**, EnVision; **TX**, Hamilton Hallmark; **UT**, Luscombe Engineering Co.; **VA**, Micro-Comp, Inc.; **WA**, E.S. Chase; **WI**, Industrial Representatives, Inc.  
Distributed in Canada by Arrow. Authorized Maxim Representative in Canada: Tech Trek.

**Austria**, Maxim GmbH (Deutschland); **Belgium**, Master Chips; **Denmark**, Arrow-Exatec A/S; **Finland**, Yleiselektronikka Oy; **France**, Maxim France, Distributors: Maxim France, ASAP; **Germany**, Maxim GmbH, Distributors: Maxim GmbH, Spezial Electronic KG; **Ireland**, FMG Electronics; **Italy**, Consystem S.r.l., Distributor: Esco Italiana Electronics Supply; **Netherlands**, Koning En Hartman; **Norway**, Berendsen Electronics; **Poland**, Uniproduct, Ltd.; **Portugal**, ADM Electronics, S.A.; **Spain**, ADM Electronics S.A.; **Sweden**, Egevo AB; **Switzerland**, Laser & Electronics AG; **Turkey**, Interex (U.S.A.); **U.K.**, Maxim Integrated Products (U.K.), Ltd., Distributors: Maxim Integrated Products (U.K.), Ltd., 2001 Electronic Components, HB Electronics.

MAXIM is a registered trademark of Maxim Integrated Products. © 1995 Maxim Integrated Products.

North American inquiries, Circle No. 96

European inquiries, Circle No. 97





SOLID STATE IS OUR BUSINESS

# OUR SOLID STATE RELAYS ARE SOLID IN EVERY WAY



**25 years of solid state relay experience – commercial/industrial experience since 1968. All of our products contain that know-how. Our price/performance ratios are better than ever. Here is an example:**

Housed in a 6 pin mini-DIP, the C60 Series is a family of bi-directional FET output solid state relays capable of controlling ac, bi-directional or dc loads. The optically coupled C60 handles a broad range of switched voltages (up to  $\pm 400$  Vdc) and currents (up to 1.25 Arms / 2.5Adc). The unique three terminal output allows the user to parallel the output FET's externally for dc operation ensuring low on resistance down to 0.07 ohms.

## **TELEDYNE RELAYS** **Solid State Products**

Innovations In Solid State Switching Technology

See these products in EEM 1995, Vol. B, Pages B. 1602-1605



Home Office: 12525 Daphne Avenue, Hawthorne, CA 90250.

Telephone: 213-777-0077 • FAX 213-779-9161

OVERSEAS: GERMANY +49 (0) 611-763-6147; ENGLAND +44 (0) 181-571-9596;  
BELGIUM +32 (0) 2-721-5252; JAPAN +81 (03) 3423-1051

## Design Idea Entry Blank

**Entry blank must accompany all entries. \$100 Cash Award for all published Design Ideas. An additional \$100 Cash Award for the winning design of each issue, determined by vote of readers. Additional \$1500 Cash Award for annual Grand Prize Design, selected among biweekly winners by vote of editors.**

To: Design Ideas Editor, EDN Magazine  
275 Washington St, Newton, MA 02158

I hereby submit my Design Ideas entry.

Name \_\_\_\_\_

Title \_\_\_\_\_

Phone \_\_\_\_\_

E-mail \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

Country \_\_\_\_\_ ZIP \_\_\_\_\_

Design Idea Title \_\_\_\_\_

Social Security Number \_\_\_\_\_  
(US authors only)

**Entry blank must accompany all entries.** (A separate entry blank for each author must accompany every entry). Design entered must be submitted exclusively to EDN, must not be patented, and must have no patent pending. Design must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested. Fully annotate all circuit diagrams. Please submit software listings and all other computer-readable documentation on a IBM PC disk in plain ASCII.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author, or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed \_\_\_\_\_


Date \_\_\_\_\_

**Your vote determines this issue's winner. Vote now, by circling the appropriate number on the reader inquiry card.**
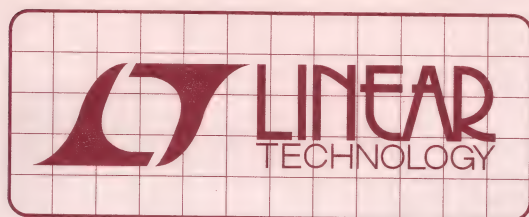
### How to use our bulletin board

This icon identifies those Design Ideas that have computer-readable material posted on EDN's bulletin-board system (BBS). Call our free BBS at (617) 558-4241, 2400 8,N,1 (V.32bis (617) 558-4580). Not every Design Idea has downloadable material, but each one does have a BBS number printed at the end of it. If you'd like to comment on any Design Idea, include the number in the subject field of your message.





# DESIGN NOTES

## C-Load™ Op Amps Conquer Instabilities – Design Note 107


Kevin R. Hoskins

### Introduction

Linear Technology Corporation has taken advantage of advances in process technology and circuit innovations to create a series of C-Load operational amplifiers that are tolerant of capacitive loading, including the ultimate, amplifiers that remain stable driving any capacitive load. This series of amplifiers have a bandwidth that ranges from 160kHz to 140MHz. These amplifiers are appropriate for a wide range of applications from coaxial cable drivers to analog-to-digital converter (ADC) input buffer/amplifiers.

### Driving ADCs

Most contemporary ADCs incorporate a sample-and-hold (S/H). A typical S/H circuit is shown in Figure 1. The hold capacitor's (C1) size varies with the ADC's resolution but is generally in the range of 5pF to 20pF, 10pF to 30pF and 10pF to 50pF for 8-, 10- and 12-bit ADCs, respectively.

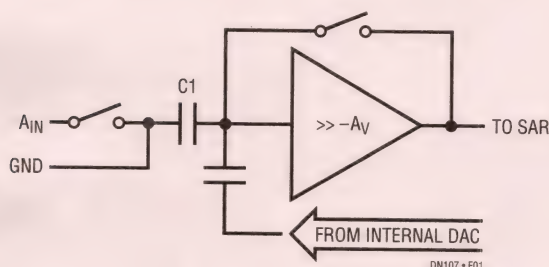

**Figure 1. Typical ADC Input Stage Showing Input Capacitors**

At the beginning of a conversion cycle, this circuit samples the applied signal's voltage magnitude and stores it on its hold capacitor. Each time the switch opens or closes, the amplifier driving the S/H's input faces a dynamically changing capacitive load. This condition generates current spikes on the input signal. This capacitive load and the spikes produced when they are switched constitutes a very challenging load that can potentially produce instabilities in an amplifier driving the ADC's input. These instabilities make it difficult for an amplifier to quickly settle. If the output of an amplifier has not settled to a value that falls within the

error band of the ADC, conversion errors will result. That is unless the amplifier is designed to gracefully and accurately drive capacitive loads, such as Linear Technology's C-Load line of monolithic amplifiers. Table 1 lists Linear Technology's unconditionally stable voltage feedback C-Load amplifiers. Table 2 lists other voltage feedback C-Load amplifiers that are stable with loads up to 10,000pF.

**Table 1. Unity-Gain Stable C-Load Amplifiers Stable with All Capacitive Loads**

SINGLES	DUALS	QUADS	GBW (MHz)	I <sub>S</sub> /AMP (mA)
—	LT®1368	LT1369	0.16	0.375
LT1200	LT1201	LT1202	11	1
LT1220	—	—	45	8
LT1224	LT1208	LT1209	45	7
LT1354	LT1355	LT1356	12	1
LT1357	LT1358	LT1359	25	2
LT1360	LT1361	LT1362	50	4
LT1363	LT1364	LT1365	70	6

**Table 2. Unity-Gain Stable C-Load Amplifiers Stable with C<sub>L</sub> ≤ 10,000pF**

SINGLES	DUALS	QUADS	GBW (MHz)	I <sub>S</sub> /AMP (mA)
LT1012	—	—	0.6	0.4
—	LT1112	LT1114	0.65	0.32
LT1097	—	—	0.7	0.35
—	LT1457	—	2	1.6


### Remaining Stable in the Face of Difficult Loads

As can be seen in Figure 2, an amplifier whose design is not optimized for handling a large capacitive load, has some trouble driving the hold capacitor of the LTC®1410's S/H. While the LT1006 has other very desirable characteristics such as very low V<sub>OS</sub>, very low offset drift, and low


LT, LTC and LT are registered trademarks of Linear Technology Corporation.  
C-Load is a trademark of Linear Technology Corporation.



power dissipation, it has difficulty accurately responding to dynamically changing capacitive loads and the current glitches and transients they produce (as indicated by the instabilities that appear in the lower trace of Figure 2a).

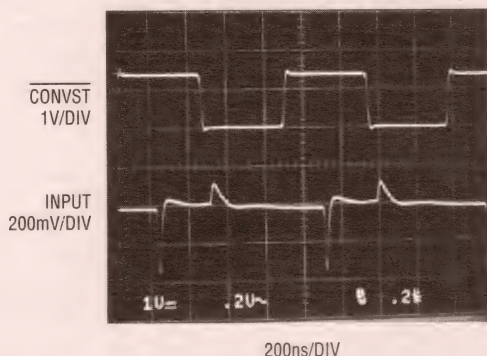

**Figure 2a. Input Signal Applied to an LTC1410 Driven by an LT1006**

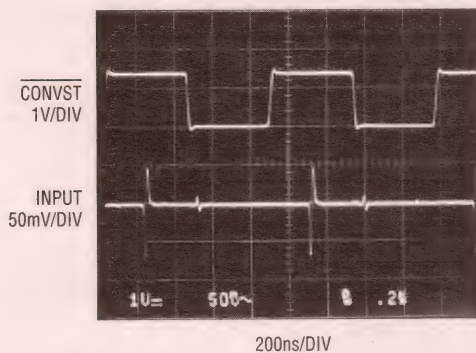


**Figure 2b. Input Signal Applied to an LTC1410 Driven by an LT1360**

By contrast, Figure 2b shows the LTC1360 C-Load op amp driving the same LTC1410 input. The photo shows that the LTC1360 is an ideal solution for driving the ADC's input capacitor quickly and cleanly with excellent stability. Its wide 50MHz gain-bandwidth and 800V/ $\mu$ s slew rate very adequately complement the LTC1410's 20MHz full power bandwidth. The LTC1360 is specified for  $\pm 5$ V operation.

Figure 3 shows the circuit used to test the performance of op amps driving the LTC1410's input and measure the input waveforms.

### Conclusion

Linear Technology's C-Load amplifiers meet the challenging and difficult capacitive loads of contemporary ADC analog inputs by remaining stable and settling quickly.

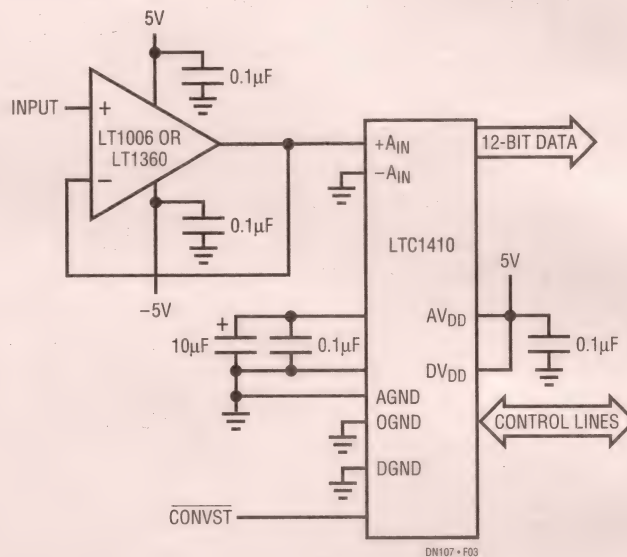

**Figure 3. Test Circuit Used to Measure LTC1410 Input Signal Waveform**

For literature on our Operational Amplifiers, call **1-800-4-LINEAR**. For applications help, call (408) 432-1900, Ext. 456



**It's No Accident**  
**Digi-Key Rates #1 for**  
**Overall Performance**



**Three Years in a Row!**  
**Mainline or Catalog Distributors**

*Results based on the percentage of Digi-Key customers rating it highest on a six point scale in recent "Engineering & Distribution" surveys conducted by Electronic Engineering Times*

**Call, write or fax for your FREE CATALOG today!**

**Digi-Key<sup>®</sup>**  
CORPORATION

**1-800-344-4539**

**701 Brooks Ave. South, Thief River Falls, MN 56701**

**Fax: 218-681-3380**






© 1995 FUJITSU LIMITED

**CIRCLE NO. 125**

**FAX HOTLINE INFORMATION:**

Germany (49) 89-291-3603, U.K. (44) 1959-562800, France (33) 1-60-46-0071, Italy (39) 2-8246-189, Sweden (46) 8-6266711, Benelux (31) 40-444158





# We knew where multimedia was going before *it* did.

You know where multimedia is going, too.

Into most everything you're designing. From networking products, desktop PCs and telecommunications systems to home computers, interactive TV, public information display systems and kiosks.

At Fujitsu Microelectronics, we saw all this coming years ago and have been investing in multimedia technology ever since. Which means we have a considerable lead over our competitors. A lead you can turn into a lead of your own.

Fujitsu, for instance, has developed a family of ATM chips (with chip sets for a variety of applications) that enable your products to transfer massive amounts of multimedia data at speeds up to 155 Mb per second. Many times faster than Ethernet.

To provide high performance graphics and audio in workstations and supercomputers, we've developed a new generation of SDRAM including the world's first 64Mb SDRAM.\*

To get a completely different view of multimedia, take a look at our brilliant new color plasma display. It's a 21-inch (larger formats are on the way), 640 x 480 resolution, flicker-free display that's a mere 35mm thick. It's already being used in selected corporate applications. And we're sure you can think of others (wall-mounted TV and public information display systems may come to mind).

So if you're working with multimedia, perhaps you should be working with Fujitsu, too. And wherever multimedia goes, we'll both get there first.




**FUJITSU**

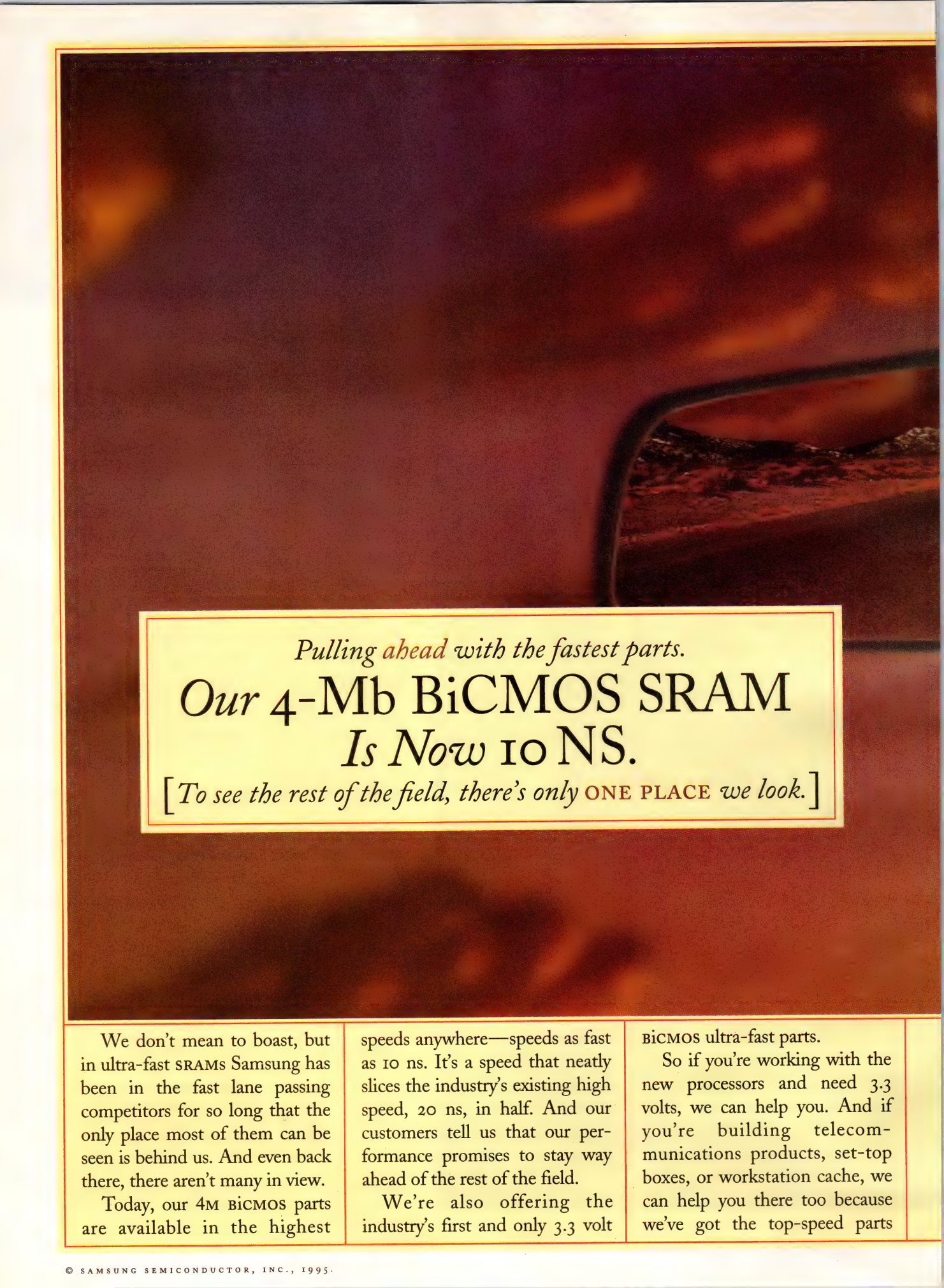**COMPUTERS, COMMUNICATIONS, MICROELECTRONICS**

\*Announcement of the development of the 64 Mb SDRAM was made at ISSCC '91.

FUJITSU LIMITED (Electronic Devices Sales Promotion & Marketing Dept.):  
Tokyo MI Bldg. 2-2-4 Higashi-Shinagawa, Shinagawa-ku, Tokyo 140, Japan Phone: (81) 3-5479-7616, Fax: (81) 3-5479-8528/8529





*Pulling **ahead** with the fastest parts.*

# **Our 4-Mb BiCMOS SRAM Is Now 10 NS.**

*[To see the rest of the field, there's only **ONE PLACE** we look.]*

We don't mean to boast, but in ultra-fast SRAMs Samsung has been in the fast lane passing competitors for so long that the only place most of them can be seen is behind us. And even back there, there aren't many in view.

Today, our 4M BiCMOS parts are available in the highest

speeds anywhere—speeds as fast as 10 ns. It's a speed that neatly slices the industry's existing high speed, 20 ns, in half. And our customers tell us that our performance promises to stay way ahead of the rest of the field.

We're also offering the industry's first and only 3.3 volt

BiCMOS ultra-fast parts.

So if you're working with the new processors and need 3.3 volts, we can help you. And if you're building telecommunications products, set-top boxes, or workstation cache, we can help you there too because we've got the top-speed parts



*The 4-Mb BiCMOS SRAM*

PART	ORG.	SPEED	VOLTAGE
KM616B4002	256K X 16	10, 12, 15 ns	5 V
KM68B4002	512K X 8	10, 12, 15 ns	5 V
KM64B4002	1M X 4	10, 12, 15 ns	5 V
KM616BV4002	256K X 16	12, 15, 20 ns	3.3 V
KM68BV4002	512K X 8	12, 15, 20 ns	3.3 V
KM64BV4002	1M X 4	12, 15, 20 ns	3.3 V

*All parts sampling now; mass production Q4.*



you're absolutely going to require.

These BiCMOS parts mean that Samsung offers designers the most complete range of 4M SRAM options out there—with parts ranging in speeds from 70 on down to 10 ns.

Our SRAMs are just one of many things that are making

Samsung the leader in memories worldwide. And it's a leadership we have every intention of sustaining.

For information on SRAMs from the one who's in front, please call Samsung at 1-800-446-2760 today. Or write to SRAM Marketing, Samsung

Semiconductor Inc., 3655 North First Street, San Jose, California 95134.



**SEMICONDUCTOR**

*STILL A Generation AHEAD.*



# EMUL<sup>TM</sup> 16/300

Pull-down Menus

Microsoft Windows 3.1  
based user interface

Speed bar  
(point and click)

Disassembly  
Window  
with in-line  
assembler

Shadow RAM  
shows data  
changes in real-  
time. This data  
can be trans-  
ported to other  
Windows  
programs  
through DDE


Register  
Window

## EMUL16/300-PC FEATURES:

- Supports both the 68HC16 and 683xx families.
- Hosted on PC's and Workstations.
- Modular hardware: low cost (BDM) to full feature.
- Real-time emulation at maximum chip speed.
- High-level C, C++ support for HIWARE, Intermetrics, Introl, Microtec, SDS, Sierra and more.
- In-line assembler and disassembler.
- Hardware and software breakpoints.
- Up to 4 Mbytes of emulation RAM.
- Trace board up to 512K deep, 104 bits wide, 40 bit timestamp.
- Triggering and filtering with full pipeline decoding.
- Code coverage. Program performance analysis.
- Memory contents available in real-time (Shadow RAM).
- DDE support to transfer Shadow RAM to other Windows applications.


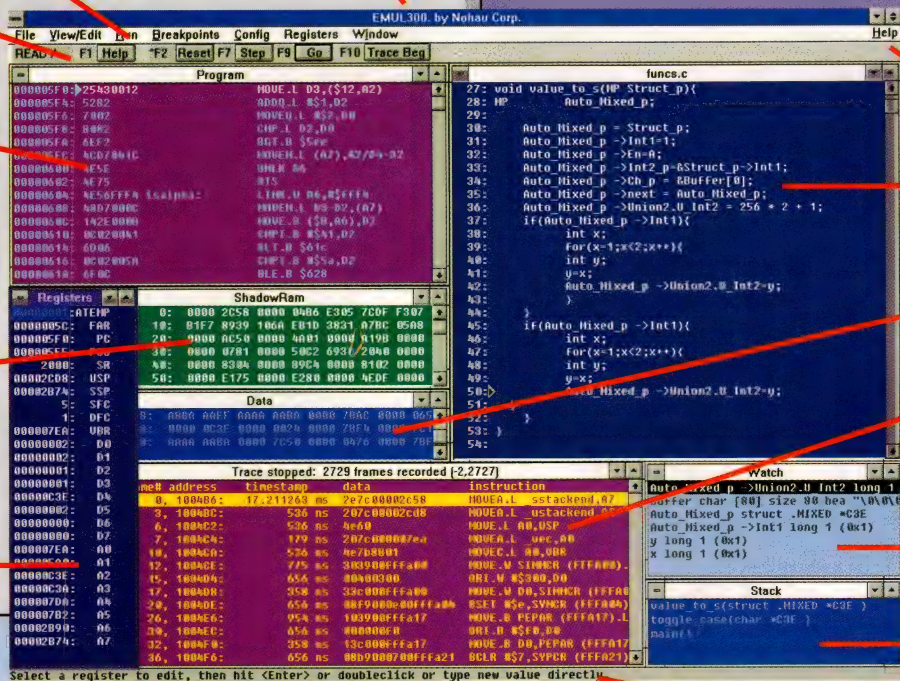
# 68HC16 683xx In-Circuit Emulators & Background Debuggers



On line help

Source  
Window

Data  
Window

Trace Buffer  
Window

Watch  
Window  
for high level  
variables

C Call Stack

Context sensitive help line

Support  
also  
available  
for:

## 8051 68HC11 80C196

To learn more, please  
call (408) 866-1820  
for a product brochure  
and a FREE Demo Disk.



For more information  
via your Fax, call our  
24-hour Fax Center at  
(408) 378-2912.

## NOHAU CORPORATION

51 E. Campbell Avenue  
Campbell, CA 95008-2053  
Fax. (408) 378-7869  
Tel. (408) 866-1820

### NOHAU INTERNATIONAL

Argentina 541 312-1079/9103, Australia (02) 654 1873, Austria 0222 277 20-0, Brazil (011) 453-5588, Canada 514-689-5889, Czech Republic 0202-2683, Denmark 45 43 44 60 10, Finland 90 777 571, France (1) 69 41 28 01, Germany 07043/40247, Great Britain 0962-733 140, Greece +30-1-924 20 72, India (0212) 422164, Israel 03-491202, Italy (011) 437 15 51, Japan (03) 3405-0511, Korea (02) 784-7841, Netherlands (01858) 16133, New Zealand 09-3092464, Norway (+47) 22-67 40 20, Portugal 01-80 95 18, Romania 056 130078, Singapore +65 749-0870, S. Africa (021) 23-4943, Spain (93) 276 22 69, Sweden 040-92 24 25, Switzerland 01-745 18 18, Taiwan 02 7640215, Thailand (02) 281-9596.



# Optimize sensor systems using fixed components

ERIC JACOBSEN AND JEFF BAUM, MOTOROLA SENSOR PRODUCTS DIVISION

A circuit design for a sensor system with fixed-value components is easier and less costly to produce in high volume. The alternatives to using fixed-value circuitry—laser-trimming resistors, manually calibrating potentiometers, or measuring and selecting specific component values—are labor-intensive.

Fixed-value components combine with a design procedure to optimize the performance of a sensor system using standard components. The method considers device-to-device, temperature, and other circuit variations that can create alterations in the amplified sensor output.

The method starts with a desired performance and set parameters. The design then considers each type of variation in a worst-case analysis to determine if the system can attain the desired performance. Every sensor type has device-to-device variations in the output offset voltage, the full-scale output voltage, and the dynamic output-voltage range. (Span is the difference between full-scale and zero-scale output voltage.) These parameters vary with temperature, according to the temperature coefficients (TCs) of offset,  $TCV_{OFF}$ , and full-scale span,  $TCV_{FSS}$ . The fixed-value circuit comprising the sensor has variations. For example, the voltage or current regulator and resistors have specified tolerances and TCs.

Because modern, unamplified solid-state sensors typically have output voltages of 10s of millivolts, a gain stage is a major part of the fixed-value circuitry. The gain stage amplifies the signal to a level large enough for additional processing. One such sensor, Motorola's MPX10 10-kPa pressure sensor, has a typical full-scale span of 58 mV at 5V excitation. The additional processing typically requires using an A/D converter to digitize the amplified analog sensor signal.

The ADC window is the difference between its high and low reference voltages. To obtain the best signal resolution from an ADC, the sensor's


**A design method that uses device-to-device variations, temperature effects, and component tolerances allows you to configure optimum amplifier and ADC circuitry for sensor systems.**

amplified dynamic output-voltage range should fill as much of the ADC's window as possible without extending beyond the reference voltages. The zero-pressure offset voltage must be greater than or equal to the low reference voltage, and the full-scale output voltage must be less than or equal to

the high reference voltage. In any case, the device-to-device, temperature, and circuit variations create a problem.

With a fixed-value amplifier circuit, the gain and any dc level shift inherent in the amplifier design are fixed. If the variation of any sensor parameters is too large, the amplified sensor output may saturate the amplifier near either its high or its low supply rail. The output may also extend beyond the high or low reference voltages of the ADC. In either case, nonlinearity errors occur in the system. To avoid such errors, you should design a fixed-value circuit that optimizes performance in terms of signal resolution and takes all types of sensor-output variation into account.

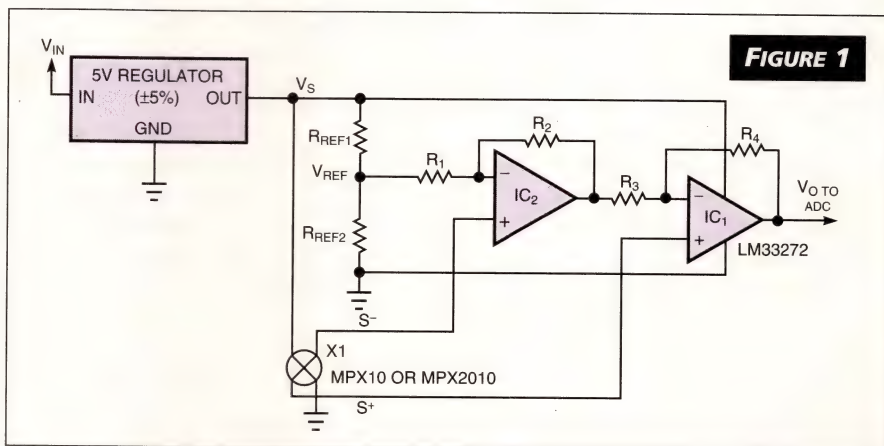The goal of the fixed-value sensor system is to obtain the best performance possible. The system's design needs to ensure that the sensor's amplified output is always within the saturation levels of the amplifier and reference levels of



**This amplifier circuit scales up the low-level output voltage of an IC pressure sensor for processing by an ADC.**



## FIXED-VALUE SENSOR SYSTEMS

the ADC, regardless of any system variation. Satisfying these tenets makes effecting an accurate software calibration of the sensor's output possible. By sampling the sensor's output voltage at a few points (such as, zero and full-scale output) at room temperature, a software calibration can nullify all the room-temperature, device-to-device, and circuit variations. Temperature variations in the sensor's output can create errors in the system, but careful design can ensure that the output remains within the ADC's valid range.

### Applying the method

Fig 1 shows how you can apply the method using Motorola's MPX10 and MPX2010 pressure sensors. Both sensors have a full-scale rated pressure of 10 kPa. The MPX2010 also has on-chip circuitry for calibration and temperature compensation of the zero-pressure offset voltage and span. Comparing these devices emphasizes how dramatically device-to-device and temperature variations, if not compensated, can affect a system's overall performance.

Both pressure sensors interface to the same amplifier-circuit topology. Tables 1 and 2 give the device-to-device and temperature variations for the MPX10 and MPX2010, respectively. Additional factors to consider in the method are the voltage-regulator and resistor tolerances. The voltage regulator's device-to-device tolerance is  $\pm 5\%$ , and each resistor's tolerance is  $\pm 1\%$ .

The amplifier topology in Fig 1 is a two-stage operational-amplifier gain block that has the desirable characteristics of a differential-input instrumentation amplifier:


- High input impedance,
- Low output impedance,
- Differential-to-single-ended signal conversion,
- High gain, and
- Level-shifting capability.

For good common-mode rejection, the ratio of  $R_4$  to  $R_3$  should equal the ratio of  $R_1$  to  $R_2$ . With this simplification, the transfer function of the amplifier is

$$V_o = \left( \frac{R_4}{R_3} + 1 \right) (S^+ - S^-) + V_{REF}$$

where the gain is  $R_4/R_3 + 1$ , and the pressure sensor's differential output voltage is  $S^+ - S^-$ . The positive dc voltage-level shift, which the voltage divider comprising  $R_{REF1}$  and  $R_{REF2}$  creates, is  $V_{REF}$ . You should use the cited resistor-ratio equal-

**FIGURE 2**

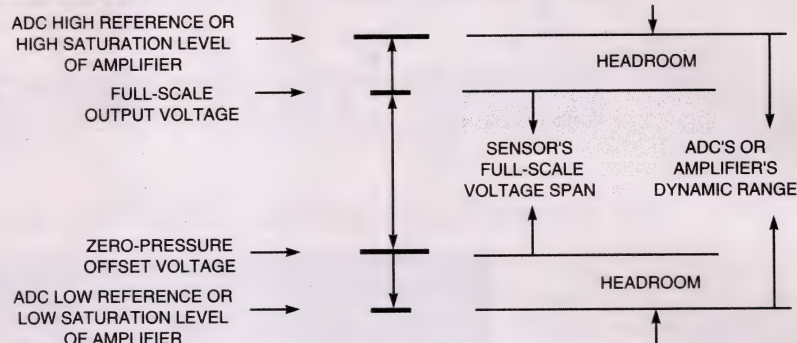

The difference between the offset and full-scale span of the sensor and the dynamic range of the amplifier or ADC is headroom.

**TABLE 1—MPX10 PRESSURE-SENSOR VARIATION CHARACTERISTICS**

Characteristic ( $V_s=5V$ )	Symbol	Minimum	Typical	Maximum	Unit
Pressure range	$P_{OP}$	0		10	kPa
Full-scale span	$V_{FSS}$	33	58	83	mV
Zero-pressure offset	$V_{OFF}$	0	33	58	mV
TC of full-scale span (Note 1)	$TCV_{FSS}$	-0.22	-0.19	-0.16	%/ $^{\circ}C$
TC of zero-pressure offset (Note 2)	$TCV_{OFF}$		$\pm 15$		$\mu V/^{\circ}C$

**Notes:**

1. Slope of endpoint straight line fits to full-scale span at  $-40$  and  $125^{\circ}C$ , relative to  $25^{\circ}C$ .
2. Slope of endpoint straight line fits to zero-pressure offset at  $-40$  and  $125^{\circ}C$ , relative to  $25^{\circ}C$ .

ity to preserve the common-mode rejection. Also, make sure that the effective resistance of the parallel combination of  $R_{REF1}$  and  $R_{REF2}$  presents a low impedance to ground, relative to the value of  $R_1$ .

### Factors affecting resolution

Performance of a pressure-sensor system relates directly to its resolution. Resolution is the smallest increment of pressure the system can resolve. For example, a system that measures pressure as high as 10 kPa with 1% resolution can resolve pressure increments of 0.1 kPa. The voltage resolution of an 8-bit ADC with a 5V window (5V high reference voltage and 0V low reference voltage) is  $5V/255$ , or 19.6 mV. Many pressure-sensor systems have ADC interfaces. If the 8-bit system requires 1% resolution, the pressure sensor's span must be at least  $19.6 mV \div 1\%$ , or 1.96V. For 0.5% resolution, the span must be 3.92V.

The greater the resolution the system requires, the greater the sensor's amplified span must be. A pressure sensor's



unamplified span is only 10s of millivolts. Therefore, you must design an amplifier to provide the minimum span that yields the desired resolution. If the amplifier has a fixed gain, any device-to-device variation in the sensor's unamplified span results in variation in the amplified span. For example, if the sensor's span variation results in an amplified span that's smaller than the system requires, the system resolution is not as high as desired.

If the sensor's span variation results in an amplified span that's larger than the system requires, the resolution is better than desired. However, the amplified span might saturate the amplifier near its supply rails. The span might also extend beyond the reference levels of the ADC. The ADC converts voltages above the high reference as  $255_{10}$  for an 8-bit ADC and converts voltages below the low reference as  $0_{10}$ . This digital clipping creates nonlinearities in the A/D conversion and in the overall system-transfer function.

A problem occurs if you want to design a fixed-gain amplifier that gives the desired resolution, does not violate the limits of the linear ranges of the op amps and ADC, and also accommodates the complete distribution of possible sensor spans. The same problem occurs with additional sources of variation: device-to-device variation, temperature effects in the sensor's span, and zero-pressure offset voltage. You must also consider any component tolerances for the voltage regulator and resistors.

Designing a system that has only one source of variation is not difficult. However, the design becomes complicated when all the cited variations are interacting. This design method considers all the variations and interactions and uses worst-case limits to design a fixed-value system.

### Resolution vs headroom

The amplified span of the sensor must fit within the high and low references of an ADC to avoid any nonlinearity errors. The span must be large enough to provide the resolution the application requires. Headroom is any part of the ADC's window that's not used for the sensor's dynamic signal range. Headroom functions as a cushion between the high and low reference voltages and the sensor's dynamic output range. This cushion allows the sensor's dynamic range to move, or vary, within the ADC's window.

Fig 2 shows the relationship among the sensor's output span, the headroom, and the ADC's (or amplifier's) window. The total amount of sensor output-signal variation is from temperature effects, device-to-device variation, and interface-circuit component tolerances. This variation must not exceed the headroom available for the requisite system resolution. A large sensor span that uses more available bits for signal resolution results in a smaller amount of headroom to accommodate sensor-parameter and interface-circuit varia-


**TABLE 2—MPX2010 PRESSURE-SENSOR VARIATION CHARACTERISTICS**

Characteristic ( $V_s=5V$ )	Symbol	Minimum	Typical	Maximum	Unit
Pressure range	$P_{OP}$	0		10	kPa
Full-scale span	$V_{FSS}$	12	12.5	13	mV
Zero-pressure offset	$V_{OFF}$	-0.5		0.5	mV
Temperature effect on full-scale span (Note 1)	$TCV_{FSS}$	-1		1	%FSS
TC on zero-pressure offset (Note 2)	$TCV_{OFF}$	-0.5		0.5	mV

**Notes:**

1. Maximum change in full-scale span at 0 and 85°C, relative to 25°C.
2. Maximum change in offset at 0 and 85°C, relative to 25°C.

**FIGURE 3**

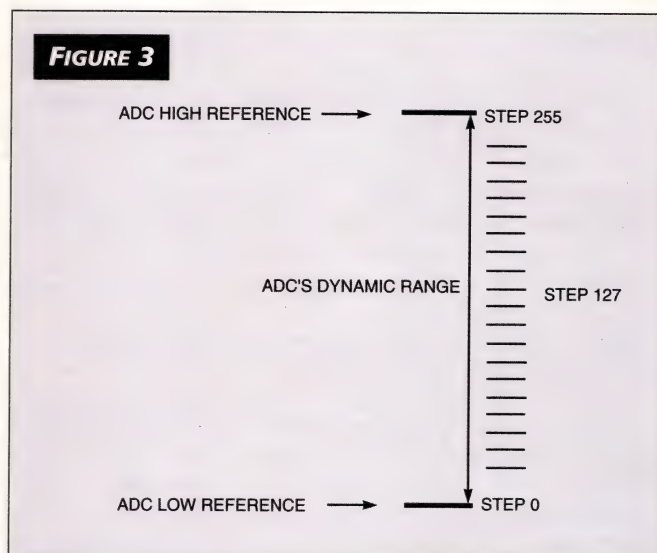

**An 8-bit ADC produces digital outputs in 255 discrete steps.**

tions. A trade-off exists between resolution and variations. The more variation in the system, the more headroom the system requires for the variation. Consequently, less of the ADC's window is available for the sensor's true-signal span. Less span results in poorer resolution—fewer bits for resolving the sensor's output signal.

The method starts by defining all the known parameters. Parameters with an asterisk (\*) are specified at 25°C. The parameters are

**Resolution**

**MaxFSS\***

**MinFSS\***

**$TCV_{FSS}$**

Desired system resolution

Maximum full-scale voltage span of the pressure sensor,

Minimum full-scale voltage span of the pressure sensor,

Maximum TC of the sensor's full-scale voltage span



## FIXED-VALUE SENSOR SYSTEMS

MaxSensOff*	Maximum zero-pressure offset voltage of the pressure sensor
MinSensOff*	Minimum zero-pressure offset voltage of the pressure sensor
TCV <sub>OFF</sub>	Maximum TC of the offset voltage of the pressure sensor
V <sub>LO</sub>	Low saturation level of the amplifier or low reference voltage of an ADC (whichever is more limiting)
V <sub>HI</sub>	High saturation level of the amplifier or high reference voltage of an ADC (whichever is more limiting)
V <sub>REF</sub>	Reference voltage for positive dc-voltage level shifting
V <sub>TOL</sub>	Voltage-regulator tolerance
MinTemp	Minimum operating temperature
MaxTemp	Maximum operating temperature.

These parameters are either specific to the application, such as system resolution, or appear in the sensor's data sheet. Tables 1 and 2 provide the parameters for the two designs. The data in Tables 1 and 2 represent a 5V supply voltage. The data sheets for the MPX10 and MPX2010 give specs for 3 and 10V supplies, respectively.

Apply the following steps to the MPX10 (example 1) and MPX2010 (example 2):

**Step 1.** Determine the required resolution in percent of full-scale output for the system.

**Step 2.** Calculate the number of steps the chosen resolution requires. The resolution sets the number of steps into which to break the pressure signal. (Note Fig 3, which assumes an 8-bit ADC with 255 steps of resolution.) A conservative way to determine the number of steps is to assume that for an ADC the digital quantization of the pressure signal can be within plus or minus one step. Therefore, assume that you need twice the number of steps previously determined to resolve a given minimum incremental signal. Thus, the number of steps for the chosen resolution is  $2 \cdot 100 \div \text{resolution}$ . The scaling factor of 100 in the numerator converts the resolution from a percentage to a decimal.

**Step 3.** Evaluate the minimum amplified-sensor span. (The minimum required span is the minimum span that satisfies the resolution requirement (Fig 4).) Assuming the use of an 8-bit ADC with a 5V window, in which one step equals 19.6 mV with nominal regulator voltage, the minimum amplified sensor span equals the number of steps times 19.6 mV.

**Step 4.** Compute the amplifier's gain. The gain must be high enough over the entire distribution of sensor spans to achieve the minimum required span. Therefore, you calculate this gain using the smallest pressure-sensor voltage span, MinFSS. Using the smallest, worst-case sensor-voltage span to calculate the gain guarantees the minimum required span for the entire distribution of sensor spans. The worst-case minimum full-scale sensor span occurs at the highest tem-

TABLE 3—THE MPX10 PRESSURE SENSOR

Given parameters	Performance parameters	Headroom parameters
MaxFSS 83 mV at 25°C	[1]Resolution (%FSS) 4.5	[7]Maximum temp effect on offset 0.03V
MinFSS 33 mV at 25°C	[2]Number of steps 44	[8]Maximum offset variation 1.76V
TCV <sub>FSS</sub> -0.22 %FSS/°C	[3]Minimum required span 0.87V	[9]Minimum offset -0.03V
MaxSensOff 58 mV at 25°C	[4]Gain 29	[10]Maximum offset 1.73V
MinSensOff 0 mV at 25°C	[5]Maximum span 2.57V	[13]V <sub>REF</sub> 0.23V
TCV <sub>OFF</sub> ±15 μV/°C		
V <sub>S</sub> 5V	[6]Calculated headroom 1.78V	[11]Required headroom 1.75V
V <sub>HI</sub> 4.8V		
V <sub>LO</sub> 0.2V		[12]Is calculated headroom ≥ required headroom?
V <sub>TOL</sub> 5%		
MaxTemp 70°C		
MinTemp 0°C		

perature, MaxTemp, because the span decreases with increasing temperature (TCV<sub>FSS</sub> is negative). The following equation shows the worst-case minimum:

$$\text{Gain} = \frac{\text{Minimum required span}}{\left[ \text{MinFSS} \right] \cdot \left[ 1 + \text{TCV}_{\text{FSS}} \cdot (\text{MaxTemp} - 25) \right]}$$

where the term  $[1 + \text{TCV}_{\text{FSS}} \cdot (\text{MaxTemp} - 25)]$  is the temperature effect on the span.

In Steps 1 through 4, the calculations reflect a minimum desired resolution. The resolution requirement determines the number of steps into which to break the signal. This number of steps, multiplied by the number of millivolts per step, equals a minimum voltage range, or minimum required span. Finally, to ensure that you obtain this minimum required span over the entire distribution of sensor spans, calculate the gain using the worst-case smallest sensor span. (The gain varies because of resistor tolerances in the amplifier circuit. To ensure that tolerance-induced system variation is negligible in comparison with other sources of variation, you should design the system with resistors of 1% tolerance or better.)



# Congratulations to the EDN Innovation of the Year Award Winners

*Honoring excellence and innovation in the electronics industry since 1990*

## 1994 Innovator of the Year Award Recipient

Robert C. Dobkin,  
Linear Technology Corp.

## 1994 Innovation of the Year Award Recipients

### ICs & Semiconductors

TrueGauge MTA11200 Battery-Management IC, Microchip Technology, Inc.

V.flex High-Speed Modem Chipset, AT&T Microelectronics

### Microprocessors

NLX220 Fuzzy-Logic  $\mu$ C, American Neuralogix, Inc.

68060  $\mu$ P, Motorola, Inc.

### Test & Measurement

TDS 700A Series DSOs, Tektronix, Inc.

### Embedded Systems

DiskOnChip Flash-Memory Module, M-Systems, Inc.

### Power Sources

3C050M Powerdex Lithium Battery, Gould, Inc.

### EDA

Behavioral Compiler, Synopsys, Inc.

### Computers & Peripherals

Cardio-486 Motherboard, Epson America, Inc.

### Components, Hardware & Interconnects

Model PPF21C8060UA Plasma Display Panel, Fujitsu Microelectronics, Inc.

## 1990-1993 Award Recipients

### Innovator of the Year

1990 - Dr. Klas Eklund, founder and VP of Engineering, Power Integrations Inc.

1991 - Paul Gulick and Arlie Conner,

In Focus Systems Inc.

1992 - Jim Williams, Linear Technology Corp.

1993 - A. Paul Brokaw, Analog Devices Inc., Jerald Graeme, Burr-Brown Corp.

### Innovation of the Year

#### Integrated Circuits

1990 - PWR SMP-3 switching-power-supply IC, Power Integrations Inc.

1991 - ISD 10xx Analog Storage ICs, Information Storage Devices Inc.

1992 - ADXL50

Acceleration Sensor, Analog Devices Inc.

1993 - LTC1145 and LTC1146 Isolator ICs, Linear Technology Corp.

### Test & Measurement

1990 - Crosscheck Test Technology, Crosscheck Technology Inc.

1991 - HP54600A 100-MHz Digital Storage Oscilloscope, Hewlett-Packard Co.

1992 - 90-Series Scopometers, John Fluke Mfg Co Inc./Philips Test and Measurement

1993 - TDS 544A Digitizing Oscilloscope, Tektronix Inc.

### CAE/CAD

1990 - Analog Fasttrack design system, Harris Semiconductor

1991 - Falcon Framework For Concurrent Design, Mentor Graphics Corp.

1992 - DESP Station Software, Mentor Graphics Corp.

1993 - Analog Model Synthesis, Analog Inc.

### Computers and Peripherals

1990 - Hp 48SX scientific calculator, Hewlett-Packard

1991 - Color LCD Technology, In Focus Systems Inc.

1992 - Stingray 1842 1.8-in. Disk Drive, Integral Peripherals Inc.

1993 - Touchmate Touch-Sensing Peripherals, Visage Inc.

### Components, Hardware and Interconnects

1990 - EL 1C-C000 VGA display, Cherry Corp.

1991 - Isocon Interconnection System, Rogers Corp.

1992 - AX1024 Programmable Interconnect Device, Aptix Corp.

1993 - Cro-Bar Electrostatic-Discharge Protective Device, Polaroid Corp.

### Software

1990 - Tekcolor CMS, Tektronix Inc.

1991 - IRMX For Windows, Intel Corp.

1992 - Gabor Spectrogram, National Instruments

1993 - Visual C++ Development System For Windows, Microsoft Corp.

### Power Sources

1990 - 78SR/79SR

switching regulators,

Power Trends Inc.

1991 - Genesis High-Power-Density Battery,

Gates Energy Products Inc.

1992 - 3D-PCB

Transformer, Philips Industrial Activities SA

1993 - P Series Power Modules, Lambda Electronics Inc.



# EDN

What engineering is really all about.



## FIXED-VALUE SENSOR SYSTEMS

**Step 5.** Calculate the maximum span—the largest possible span (Fig 4). You calculate the span by using the maximum full-scale sensor span, MaxFSS, and the gain. The worst-case maximum full-scale sensor span occurs at the lowest temperature, MinTemp. After you calculate the maximum span, the remaining dynamic range within the ADC's window or the saturation levels of the amplifier is the lowest number of bits (most limiting case) available for headroom. The following equation defines the maximum span:

$$[\text{Gain}] \cdot [\text{MaxFSS}] \cdot [1 + \text{TCV}_{\text{FSS}} \cdot (\text{MinTemp} - 25)],$$

where  $[1 + \text{TCV}_{\text{FSS}} \cdot (\text{MinTemp} - 25)]$  is the temperature effect on the span.

**Step 6.** Compute the calculated headroom (Fig 5), which reserves bits in the ADC's dynamic range only for the variation arising from the sensor's zero-pressure offset voltage. In general, headroom is reserved for all sources of variation: system components, resistor tolerances (if significant), and the sensor. However, you should reserve the largest part of the headroom for the device-to-device variations and temperature effects on the sensor's zero-pressure offset voltage.

The sources of variation from the other system components subtract immediately from the headroom so you can focus on the sensor-related variations. (This subset of the total headroom is the calculated headroom.) The following expression gives the calculated headroom:

$$5 \cdot \left( 1 - \frac{V_{\text{TOL}}}{100} \right) - 2 \cdot V_{\text{LO}} - \text{Maximum span}.$$

This equation assumes the difference between  $V_{\text{HI}}$  and the high supply rail, or high reference of the ADC, equals the difference between  $V_{\text{LO}}$  and the low supply rail, or the low reference of the ADC; thus, the term:  $2 \cdot V_{\text{LO}}$ .


Step 6 is pivotal because it makes the transition from the performance requirements to the headroom requirements. Before Step 6, the method considered only the span of the sensor to guarantee a minimum resolution, despite device-to-device variation, component tolerances, and temperature effects. After determining the calculated headroom, the remaining steps consider the offset variations from device-to-device differences and temperature effects.

These offset variations add to form the required headroom (Fig 6). The required headroom is the number of bits the ADC's dynamic range needs to accommodate the offset variations. You compare this required headroom

with the calculated headroom to determine if the calculated headroom can allow for the offset variations. The calculated headroom must be greater than or equal to the required headroom. If not, you must relax the resolution requirement or reduce the variations rising from offset, span, or component tolerances (or all three).


**Step 7.** Calculate the maximum offset drift, the maximum temperature effect on offset in Fig 6, rising from temperature fluctuations. A conservative approach is to determine the maximum total voltage change over the entire operating-temperature range. This maximum offset change is the product of the amplifier gain,  $\text{TCV}_{\text{OFF}}$ , and the entire operating-temperature range, from MaxTemp to MinTemp. Because the TC of offset can be positive or negative, the offset may increase or decrease with increasing temperature. Although this step considers only the maximum magnitude of the temperature-induced change in offset, a segment in the required headroom is reserved for both possibilities: a positive or negative TC offset (Fig 6). The maximum temperature effect on offset is

**FIGURE 4**

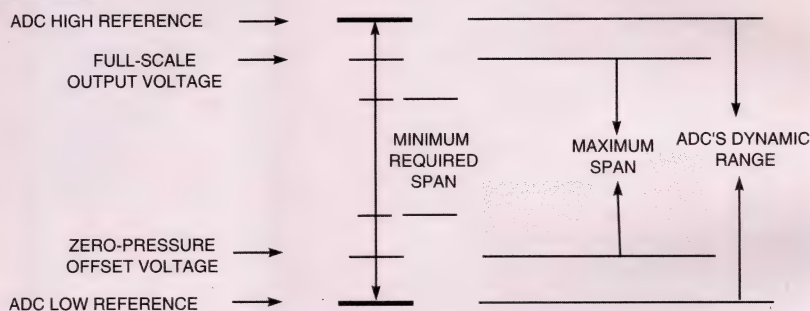

**The ADC's resolution and dynamic range determine the minimum required amplified sensor span.**

**FIGURE 5**

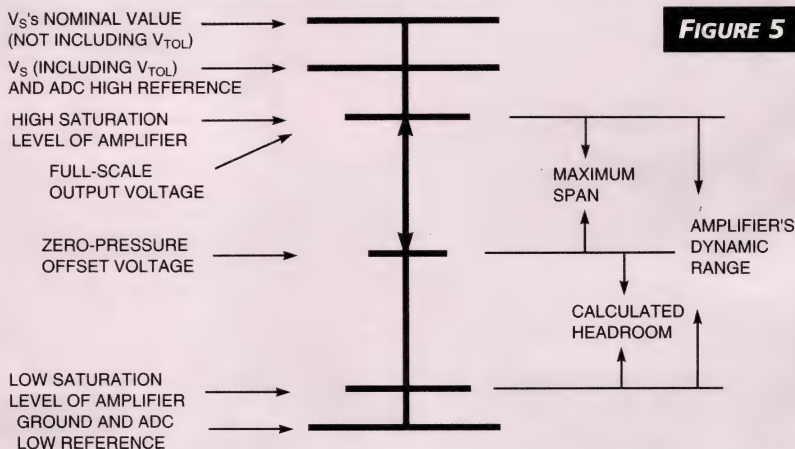

**You must reserve a section of voltage for each source of variation from ground to the supply voltage.**



# How do you replace a surface mount fuse in under 5-seconds?



AN ISO 9001  
FACILITY

Wouldn't it be great if you could replace a surface mount fuse without desoldering and resoldering?

The Littelfuse NANO<sup>2</sup>™ fuse and fuseholder makes that possible. Makes assembly and repairs easier.

Makes space-saving circuit protection more reliable and affordable than resettable devices.

We're ready to send you all the facts today, by fax, on the NANO<sup>2</sup> fuse and surface mount fuseholder, or on any of these other Littelfuse surface mount Slo-Blo<sup>®</sup> and fast-acting fuses.



**Littelfuse<sup>®</sup>**  
Electronic Products

## Get all the facts by FAX: 1-708-391-0894

Check the surface mount fuses you're interested in and fax us this ad and the following information. In minutes, we'll fax you back the information you want.



☐ NANO<sup>2</sup> and Fuseholder  
3/8-5A  
125V

☐ PICO<sup>®</sup> SMF  
3/8-5A  
125V

☐ 1206 Case SMF  
Fast-Acting  
2/10-2A  
32V

☐ Nanofuse™  
1/16-15A  
125V, 60V, 32V

☐ 250 Volt Flat Pak™  
¼-5A  
250V

I'd like information on other Littelfuse Surface Mount products.

Name: \_\_\_\_\_

Company Name: \_\_\_\_\_

Company Address: \_\_\_\_\_

City: \_\_\_\_\_ State: \_\_\_\_\_ Zip: \_\_\_\_\_

Your return FAX: \_\_\_\_\_

Company phone #: \_\_\_\_\_

Application needs: \_\_\_\_\_



## FIXED-VALUE SENSOR SYSTEMS

$$[\text{Gain}] \cdot [\text{TCV}_{\text{OFF}}] \cdot [\text{MaxTemp} - \text{MinTemp}]$$

**Step 8.** Determine the maximum offset variation (Fig 7). This parameter is the total amount of required headroom that you must reserve for the entire distribution of sensor offsets at room temperature. To determine the maximum offset variation

$$[\text{Gain}] \cdot [\text{MaxSensOff} - \text{MinSensOff}],$$

where the largest offset is Gain·MaxSensOff and the smallest offset is Gain·MinSensOff.

**Step 9.** Calculate the worst-case minimum offset (Fig 7). This parameter uses both temperature effects from Step 7 and device-to-device variations from Step 8 to determine the smallest possible offset over the entire distribution of sensor offsets and the operating-temperature range. This worst-case minimum offset occurs when a sensor has a nominal room-temperature offset of MinSensOff and a negative TC, so that the offset decreases with increasing temperature. MinSensOff is the smallest offset in the sensor-offset distribution. The following expression defines the minimum offset:

$$[\text{Gain}] \cdot [\text{MinSensOff}] - \text{maximum temperature effect on offset.}$$

**Step 10.** Compute the worst-case maximum offset (Fig 7). This parameter uses both temperature effects from Step 7 and device-to-device variations from Step 8 to determine the largest possible offset over the entire distribution of sensor offsets and the operating-temperature range. This worst-case maximum offset occurs when a sensor has a nominal room-temperature offset of MaxSensOff and a positive TC, so that the offset increases with increasing temperature. MaxSensOff is the largest offset in the sensor-offset distribution. The following expression defines the maximum offset:

$$[\text{Gain}] \cdot [\text{MaxSensOff}] + \text{maximum temperature effect on offset.}$$

**Step 11.** Determine the required headroom (Fig 7), which is the difference between the maximum and the minimum offset. This parameter is also the amount of voltage range (in bits of the ADC) the system requires to allow for device-to-device and temperature variations of the sensor's offset. The equation for the required headroom is

$$\text{Maximum offset} - \text{Minimum offset.}$$

**Step 12.** Compare the required headroom of Step 11 with the calculated headroom of Step 6. The calculated headroom is the absolute amount of offset variation rising from device-to-device variations and temperature effects that the system can allow for the desired resolution. If the required headroom is greater than the calculated headroom, the desired resolution is not attainable for all worst-case variations from temperature effects, component tolerances, and device-to-device variations. The requirement to attain the desired system resolution is:

$$\text{Calculated headroom} \geq \text{Required headroom.}$$

If your system does not meet this requirement, you can take the following actions:


- Relax the resolution requirement, and repeat the method;

(continued on pg 95)

**TABLE 4—THE MPX2010 PRESSURE SENSOR**

Given parameters	Performance parameters	Headroom parameters
MaxFSS 13 mV at 25°C	[1]Resolution (%FSS) 1.2	[7]Maximum temp effect on offset 0.14V
MinFSS 12 mV at 25°C	[2]Number of steps 167	[8]Maximum offset variation 0.55V
$\text{TCV}_{\text{FSS}}$ ±1 %FSS/°C	[3]Minimum required span 3.27V	[9]Minimum offset -0.27V
MaxSensOff 0.5 mV at 25°C	[4]Gain 275	[10]Maximum offset 0.27V
MinSensOff -0.5 mV at 25°C	[5]Maximum span 3.61V	[13] $V_{\text{REF}}$ 0.47V
$\text{TCV}_{\text{OFF}}$ ±0.5 mV, 0 to 85°C		
$V_S$ 5V	[6]Calculated headroom 0.74V	[11]Required headroom 0.55V
$V_{\text{HI}}$ 4.8V		
$V_{\text{LO}}$ 0.2V		[12]Is calculated headroom ≥ required headroom?
$V_{\text{TOL}}$ 5%		
MaxTemp 85°C		
MinTemp 0°C		

**FIGURE 6**

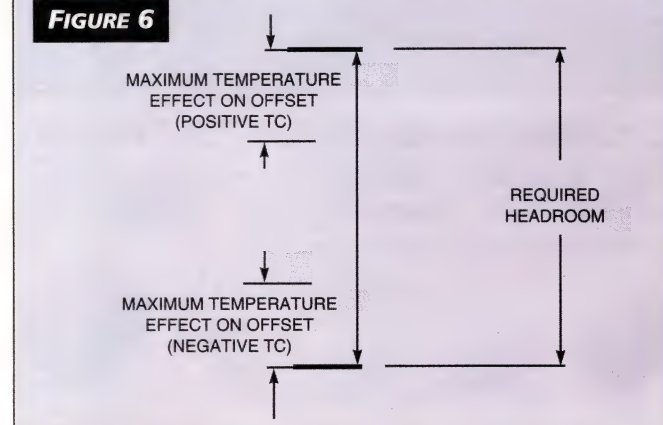

**You must reserve segments in the required headroom for both positive and negative TCs of zero-pressure offset.**



# The potential of the 1 Gigabit DRAM.

(an analysis, in three words...)







# → Kick some byte.

**The One Gigabit DRAM** With it will come the power to inspire your imagination. And the design "elbow room" to realize your dreams. In other words, Mitsubishi is designing a 1 Gb DRAM (0.15 $\mu$ m design rule) that will give design engineers some serious byte-kicking capability.

In the meantime, our 64 Mb (0.3 $\mu$ m design rule), and soon, 256 Mb (0.25 $\mu$ m design rule) EDO and synchronous memories will kick higher density and wider bandwidth designs into motion.

Mitsubishi's complete family of DRAMs, from 4 Mb to 256 Mb, EDO to synchronous, cache DRAM to 3D-RAM™ provide solutions for virtually any application.

To score big with your next design, call 1-800-987-9653, ext. A or 408-774-3189.

 **MITSUBISHI**  
ELECTRONIC DEVICE GROUP



This logo is representative of Mitsubishi Electric's environmental protection activities.

©1995 Mitsubishi Electronics America, Inc., Electronic Device Group, a wholly owned subsidiary of Mitsubishi Electric Corporation. Products subject to availability.

CIRCLE NO. 164



## FIXED-VALUE SENSOR SYSTEMS

- Reduce (tighten) the span or offset (or both), and repeat the method;
- Reduce the TCs, and repeat the process;
- Reduce the component tolerances, and repeat the method; or
- Perform a combination of the above actions, and repeat the method.

**Step 13.** You need a dc offset,  $V_{REF}$ , to position the sensor's span within the ADC's window. This offset ensures that no device-to-device, temperature variation, or component tolerances cause the sensor's output to fall outside the window. Therefore, calculate the  $V_{REF}$  required to ensure that the sensor's smallest zero-pressure offset voltage (minimum offset) is greater than or equal to  $V_{LO}$  (Figs 5 and 7). The sum of the reference voltage and minimum offset must be greater than or equal to the amplifier's low saturation voltage, as the following equation shows:

$$V_{REF} + \text{Minimum offset} \geq V_{LO}$$

To solve for  $V_{REF}$

$$V_{REF} \geq V_{LO} - \text{Minimum offset.}$$


The reference voltage,  $V_{REF}$ , has variations from the tolerances of the resistors in the divider that create  $V_{REF}$ . To ensure that the system variation from resistor tolerances is negligible in comparison with other sources of variation, you should design the system using resistors having 1% tolerances or better.

### Executing the method

Tables 3 and 4 contain designs using the MPX10 and MPX2010 pressure sensors, respectively. The cell headings in the tables correspond to the designs in the text. In addition, the bracketed numbers next to the cell headings are the steps in the method. The first column lists the parameters that should be available in, or derived from, the data sheets for the appropriate components: sensor, amplifier, voltage regulator, and resistors.

The second column lists the performance requirements of the sensor system. This column lists the calculations for a minimum sensor span that you need to obtain the desired resolution, despite device-to-device variations, temperature effects, and component tolerances. The third column lists the calculations that determine the headroom for the system, the given component tolerances, the sensor-offset device-to-device variations, and the temperature effects. You can easily implement the table and design equations into a spreadsheet to efficiently perform the required calculations.

Tables 3 and 4 show how sources of variation can affect the overall system resolution. The MPX2010 has on-chip temperature-compensation and calibration circuitry to reduce device-to-device variations and temperature effects. Consequently, when you design the fixed-value amplifier system, the possible resolution with the MPX2010 is almost four times greater than the resolution from the amplifier circuit using an MPX10. In each example, the method optimizes the system resolution, taking account of the sensor

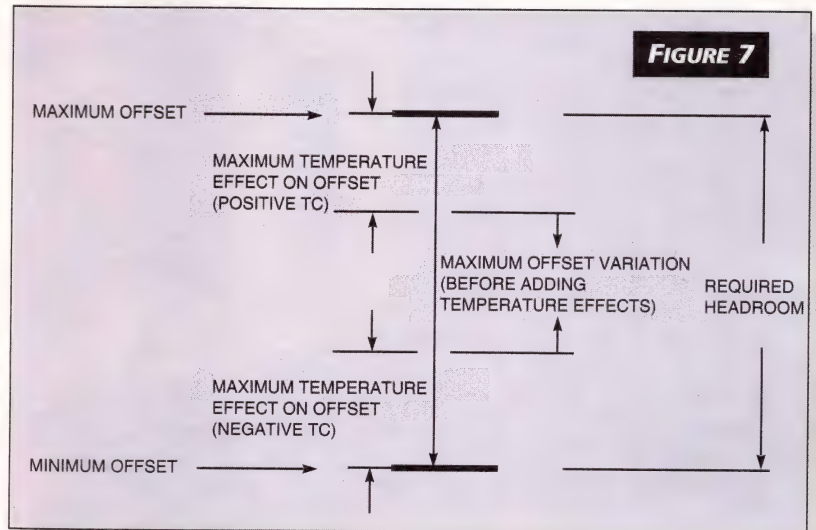

**The temperature effects of Fig 6 combine with device-to-device variations to determine the worst-case offset conditions.**

device variations and other component variations.

This method does not address how to obtain the best performance from a single sensor system. Instead, the focus is on obtaining the best possible system performance while considering the distribution of device parameters that result from manufacturing and other sources of variation. By considering the sources of variation, you can mass-produce the system without individually calibrating the sensor-system hardware. If the system's calculations show that the sensor's signal is within the dynamic range of the amplifier and the ADC, you can implement a software calibration to nullify any room-temperature device-to-device and component variations.

EDN

### Authors' biographies

*Eric Jacobsen is a systems and applications engineer for Motorola's Sensor Products Division, Phoenix, where he has worked on product and system design and customer support for three years. He holds a BSEE from the University of Illinois, Urbana/Champaign, and is pursuing an MSEE at Arizona State University, Tempe, AZ. His hobbies include music and audio equipment.*

*Jeff Baum is a systems-engineering manager at Motorola's Sensor Products Division, Phoenix, where he's worked for five years. He defines new products, develops system-level sensor circuitry, and designs new-product prototypes. A member of Eta Kappa Nu, Baum holds a BSEE from the University of Illinois, Urbana/Champaign, and an MSEE from the University of Arizona, Tucson, AZ. His hobbies include travel, studying Japanese, and combat-pistol shooting.*

### VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High Interest  
578

Medium Interest  
579

Low Interest  
580





# 0.35µm

## Scale new performance peaks with deep submicron technology

### CMOS-9 offers 2 million gates and 155MHz speed

Our 0.35µm gate arrays can take your system to higher levels of speed, integration and energy efficiency. And they can do it now. NEC is the first in the industry to offer immediate availability of deep submicron ASICs. We've tested, proven and perfected our 0.35µm process during production of 64Mb DRAMs.

#### HIGHER INTEGRATION

If you're designing high-end computer, communication or networking products, the CMOS-9 family gives you four competitive advantages. The first is higher integration.

The family offers 20 base arrays. They range from 190,000 to two million raw gates (1.2 million usable).

#### FASTER GATES

CMOS-9 also offers more speed. A 2-input NAND gate operates at 119 picoseconds (F/O=2, L=0.5mm). That's fast enough to support high-end systems operating at clock speeds up to 155MHz.

#### LOWER POWER CONSUMPTION

CMOS-9 consumes less power and generates less heat. Operating at 3.3V, the new arrays dissipate only 0.9µW/

**For fast answers, call us at:** **USA** Tel:1-800-366-9782,Fax:1-800-729-9288. **Germany** Tel:0211-650302,Fax:0211-6503490.  
**The Netherlands** Tel:040-445-845,Fax:040-444-580. **Sweden** Tel:08-753-6020,Fax:08-755-3506. **France** Tel:1-3067-5800,Fax:1-3946-3663.  
**Spain** Tel:1-504-2787,Fax:1-504-2860. **Italy** Tel:02-6709108,Fax:02-66981329. **UK** Tel:0908-691133,Fax:0908-670290. **Ireland** Tel:01-6794200.  
**Hong Kong** Tel:2886-9318,Fax:2886-9022. **Taiwan** Tel:02-719-2377,Fax:02-719-5951. **Korea** Tel:02-551-0450,Fax:02-551-0451.  
**Singapore** Tel:253-8311,Fax:250-3583. **Australia** Tel:03-8878012,Fax:03-8878014. **Japan** Tel:03-3454-1111,Fax:03-3798-6059.





# ASIC

MHz/gate. That's 30% less than our 0.5 $\mu$ m family, also known for low power consumption.

## MORE FEATURES

To meet your needs for high-speed system design, CMOS-9 features Digital Phase-Locked Loop (to minimize chip-to-chip clock skew) and Clock Tree Synthesis (to minimize on-chip clock skew). The family supports a wide variety of I/O functions, including PCI and 5V interfaces. Package options are PQFP, Tape BGA and PGA. Pin counts range from 160 to 696.

Base arrays (3-layer metal)	$\mu$ PD65926	$\mu$ PD65927	$\mu$ PD65928	$\mu$ PD65929	$\mu$ PD65930	$\mu$ PD65931	$\mu$ PD65933	$\mu$ PD65935	$\mu$ PD65937	$\mu$ PD65939
Raw gates	190,152	249,948	317,904	376,740	462,088	629,824	805,580	1,076,032	1,545,240	1,990,600
Usable gates	114,091	149,968	190,742	226,044	277,252	377,894	483,348	645,619	927,144	1,194,360
Signal pads	388	444	500	540	596	692	772	892	1,060	1,204

*NEC also offers 10 base arrays for 2-layer metal.*

## AVAILABLE NOW


CMOS-9 not only speeds up your system. It also shortens your design cycle. Available now, the family is fully supported by our OpenCAD<sup>®</sup> Design System. OpenCAD is a seamless environment that lets you mix-and-match popular third-party programs with our proprietary tools.

For immediate answers on how to raise system performance with 0.35 $\mu$ m ASICs, call NEC today.



# The *FLIP* *Century* Series

## A New Era in VF Displays

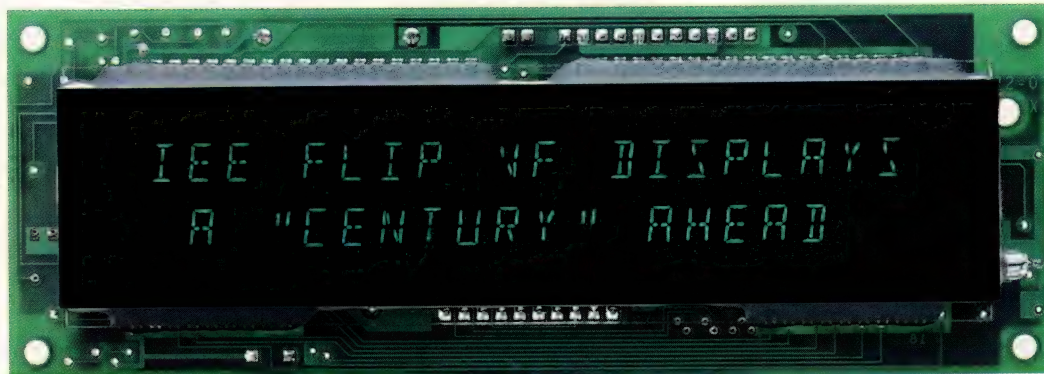

03702-020-05220

(Displays Shown Actual Size)

### Key Features


- Interface to Intel or Motorola host processors.
- Emulate Hitachi 44780 data input.†
- Parallel 8-bit or serial EIA-232 data to 19.2Kb.
- Low 5Vdc power.
- 100% surface mount technology.
- Standard temperature range -20° to +70°C. Extended range available -40° to +85°C.
- Hardware and software self-test modes.

03602-100-05420

### Software Control Features

- Selectable character sets: ASCII, European, Katakana, Cyrillic and Hebrew.†
- Segmented displays have standard ASCII 64-character set.
- Ten (10) user-defined, downloadable characters.†
- Vertical and horizontal scroll modes.
- Eight (8) software and hardware controlled dimming levels.
- Variable blink fields and rates.
- Screen saver control mode for increased tube life.
- Bell alarm output.†

† Dot matrix units only

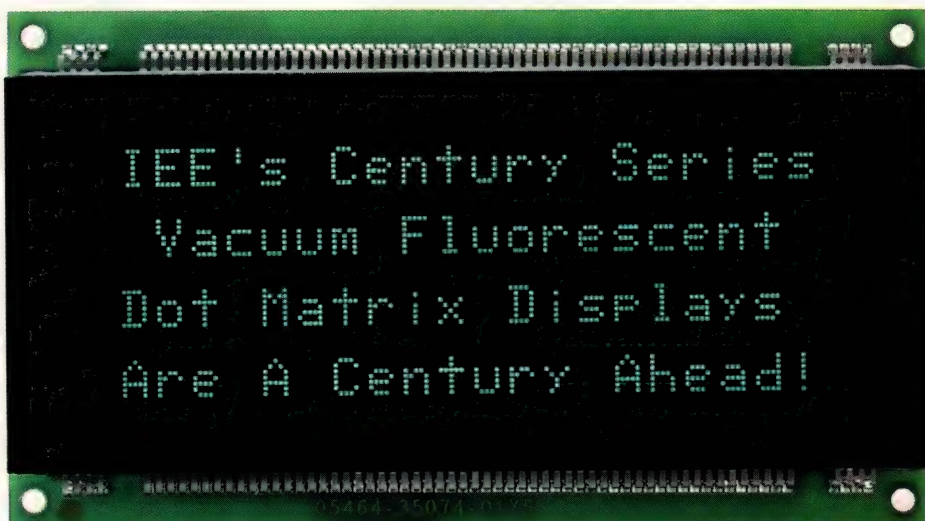

IEE is a sustaining member of **SOD**

## Versatile, Compact, High-Performance...Value Priced!

Model	Character Format	Display Format	Character Height	Package Size:			Max. Current
				Length	Width	Depth	
03602-100-05420	5x7 dot matrix	4x20	5mm	5.00"	2.78"	0.92"	890mA
03602-105-05220	5x7 dot matrix	2x20	5mm	5.00"	2.25"	0.88"	405mA
03602-122-09220	5x7 dot matrix	2x20	9mm	7.75"	2.58"	1.00"	675mA
03602-124-09420	5x7 dot matrix	4x20	9mm	7.75"	3.40"	1.00"	1300mA
03702-020-05220	14-segment	2x20	5mm	5.65"	1.98"	0.82"	270mA
03702-021-08110	14-segment	1x10	8mm	5.00"	1.60"	0.90"	140mA
03702-022-13112	14-segment	1x12	13mm	7.20"	2.40"	0.90"	323mA
03702-024-09116	14-segment	1x16	9mm	6.70"	2.30"	0.90"	360mA
03702-026-09120	14-segment	1x20	9mm	8.30"	2.35"	0.95"	390mA
03702-029-13120	14-segment	1x20	13mm	10.20"	1.93"	0.96"	526mA



**DISPLAYS  
KEYBOARDS  
INTEGRATED PANELS**

**INDUSTRIAL ELECTRONIC ENGINEERS, INC.**  
7740 Lemona Avenue  
Van Nuys, California 91409-9234  
Tel 818-787-0311 ext. 418 • Fax 818-901-9046



# Cryptography is key to securing proprietary information

ANTONY WATTS, SGS-THOMSON MICROELECTRONICS

It's no secret that digital information has become a hot commodity. Because of increased demands for electronic information and the corresponding growth in value of this data, companies are stepping up security efforts. Telephone companies have deemed simple security mechanisms, such as fuses and transport codes, sufficient for applications such as prepaid telephone cards. But consumers and retailers are demanding more sophisticated security for applications involving credit cards, electronic mail, electronic cash, and home banking. "Cryptography" technology, which is the science of encoding and decoding messages, makes new levels of electronic security now viable for mass-market applications.

Cryptography is not a new subject for the semiconductor industry; microprocessors have implemented schemes such as DES (Data Encryption Standard) for more than 20 years. However, the secret-key cryptographic technique upon which DES is based is now being challenged by public-key cryptography, which offers major advantages in many applications.

Growing interest in smart bank cards, "electronic purses," and home-banking systems also raises security concerns. For example, a customer can use a home terminal to instruct the bank to pay bills by transferring money from one account to another. In this transaction, electronic security involves ensuring that the customer's message will not be intercepted—and the identity of the payee altered. Similarly, the bank must be able to prove that the payment request was indeed sent by the customer (and that the message was not altered during transmission). A security system must also protect against a technique known as "replay," where a genuine message (for example, one that instructs the bank to pay a certain sum into an account) is recorded and sent again and again.

Computer and communications technologies are converging. Satellite and cable TV, electronic mail, and smart bank cards are among the slew of applications involved. Some applications routinely risk transmitting valuable information over low-security channels. By using cryptography, however, you can encode proprietary data and prevent its misuse.

The most common security threats include the following:

- **Interception**—passive eavesdropping
  - **Replay**—genuine messages that are recorded and resent
  - **Masquerade**—receiving a message from a source other than the source the message claims
  - **Repudiation**—receiving a message that the sender later denies sending
  - **Manipulation**—intercepting and modifying messages for fraud or industrial sabotage.
- To protect against these threats, a cryptographic system must offer three features:
- **Secrecy**—to protect message privacy from anyone without an appropriate key to decipher encrypted messages
  - **Integrity**—to allow detection of whether a message has been altered
  - **Signature**—to establish sender identity and prove that an individual sent the message.

## Cryptographic systems

All practical cryptographic systems operate in the same basic way. An encryption algorithm and key convert an original message, "plain text," into a coded message, "cipher text." A decryption algorithm and key are necessary to decode the cipher text. Security and secrecy normally reside in the keys, not in the algorithms, because using standard algorithms has clear commercial benefits. In fact, cryptographers usually act on a worst-case assumption that the entire mechanism of encryption is known to all parties, which is called Kerckhoff's Assumption.

Cryptographic schemes fall into two distinct groups: secret-key and public-key methods. Fig 1 illustrates the secret-key system. The secret-key algorithm is fully reversible



## CRYPTOGRAPHY

and symmetric; decrypting the cipher text yields the original plain text.

The most widely used scheme of this kind is DES, which breaks plain text into 64-bit blocks and encrypts each block using a 56-bit secret key to generate a 64-bit block of cipher text. You must use the same key to recover the original text from the cipher text.

Encoding data is sufficiently complex to ensure that even the most powerful computers currently available would take more than 100 years to break the code. Unfortunately, anyone who knows the key can decode the message. In addition, there is no way of ascertaining whether the decoder is supposed to know the key. Similarly, although it is possible to use hash functions to add integrity checks to the message, the value of this move is undermined by the lack of a signature facility.

### Scoring high marks

Secret-key systems score high marks in secrecy but perform poorly in other applications. These systems are also impractical in situations where many potential pairs of senders and receivers need to agree on a unique key to communicate. The unique key is not a problem in banking applications, because the bank can issue the keys in the same way as conventional PINs (personal-identification numbers). In e-mail systems, on the other hand, the number of keys can approach the number of users squared.

**FIGURE 1**

### HOW A SECRET-KEY SYSTEM WORKS:



Public-key systems (Fig 2) are asymmetric; the encryption and decryption algorithms are different, so passing the cipher text through the encryption stage again does not yield the original message. For public-key systems, you need one key for encryption and another key for decryption. Although these keys are mathematically related, it is possible not only to devise algorithms that allow the encryption key to be distributed publicly, but also to prevent discovery of the decryption key from this knowledge (Ref 1).

To send a message using a public-key system, the sender looks up the recipient's encryption key in a public directory and uses this to encrypt the message. He can then send the

# Lost Time.



If you're measuring literature request response time with a calendar, start using a stop-watch. With a click of your mouse, you are seconds away from [Marshall on the Internet](#) and just about every type of information on Texas Instruments products you need. Information to find solutions and make critical decisions about your design. All on your PC.

■ [View & Print Data Sheets](#)

■ [Request Samples](#)

■ [Order Products](#)




cipher text using an insecure communications method, such as the public-telephone system. The recipient then decodes the message using his secret decryption key.

Public-key systems have two important benefits. The first is that you have to remember only your own decryption key, which greatly simplifies key distribution and management. The second benefit is that public-key systems offer the ability to implement "electronic signatures," a particularly important feature in applications such as home banking and electronic mail.
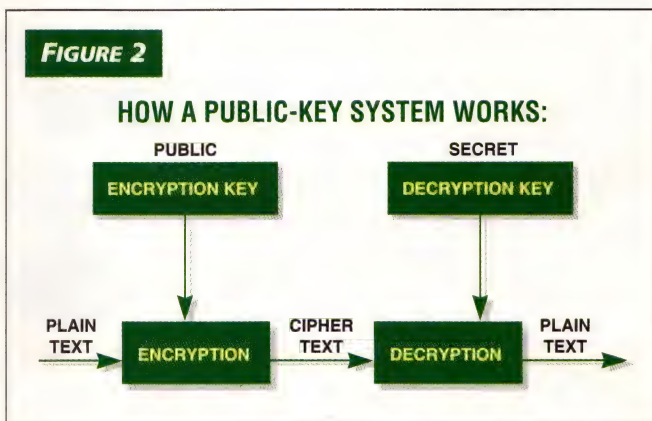
#### De facto standards

Although there are no international standards for public-key cryptosystems, de facto standards, such as RSA (named after Rivest, Shamir, and Adelman, who published their algorithm in 1977), have emerged. You can use public-key systems without knowledge of the underlying mathematics, but the following simplified description of the RSA method illustrates the encryption and decryption processes. For this example, the message is a 512-bit number, equivalent to a block of 64 conventional 8-bit ASCII characters. Longer messages are encrypted in 512-bit blocks.

Suppose you choose two very large prime numbers,  $P$  and  $Q$ , and another very large number,  $d$ , which is relatively prime to  $(P-1)*(Q-1)$ . Then calculate  $e$ , the unique number that satisfies the equation  $e*d=1 \text{ [mod } ((P-1)*(Q-1))]$ . The pair of numbers  $(e, N)$ , where  $N$  is congruent to  $P*Q$ , is the



encryption key; the number pair  $(d, N)$  is the decryption key.

The encryption algorithm consists of raising the message to the power of  $e$  and taking the remainder when the result is divided by  $N$ . The result is the cipher text. Note that the same algorithm operating on the cipher text as the input and  $d$  instead of  $e$  as the exponent yields the original message (Ref 2).

Although the encryption key  $(e, N)$  uniquely determines the decryption key  $(d, N)$ , potential hackers can compute  $d$  only if they know the prime factors,  $P$  and  $Q$ , of  $N$ . Breaking the code is equivalent to finding the prime factors of the



No phone calls. No voice mail. No waiting for returned calls. Right this minute, 24-hours a day, Marshall can deliver information to your PC on DSP Solutions, Mixed-Signal, Advanced Logic and Memory products from Texas Instruments, and other manufacturers. For a \*FREE Web browser, make time and call Marshall at 800/877-9839 ext 3028.



**Marshall**

■ [Download Software](#)

■ [Register for Seminars](#)

■ [Technical Support](#)

\*While supplies last, one per customer. Offer ends 9/30/95.



## CRYPTOGRAPHY

number  $N$ ; you can make the time required to do this arbitrarily large by a suitable choice of  $P$  and  $Q$ . Typical public-key systems use prime numbers with 100 digits or more; with numbers of this size, the chance of success using any known factoring algorithm is effectively zero. At the same time, readily available computer algorithms can rapidly calculate suitable values for  $P$ ,  $Q$ ,  $d$ , and  $e$ .

### Electronic signatures

One immediate advantage of public-key cryptography is that it eliminates key-management problems; a new member of a public-key system needs only to obtain a copy of the public directory and to distribute his chosen encryption key. However, you may opt to attach an electronic signature to a message.

Electronic signatures are possible in a public-key system because the distinction between encryption and decryption keys and algorithms is arbitrary. Provided that the equation  $e \cdot d = 1 \pmod{(P-1)(Q-1)}$  is satisfied, it makes no difference whether you chose  $e$  or  $d$  as the encryption key. This means that you can encode a message using the secret key that is normally used for decryption and decode the cipher text using the public key normally used for encryption.

As Fig 3 shows, you can sign an electronic message using a two-stage encryption. First, encode the message using your secret key,  $SD$ , to generate an intermediate cipher text,  $C1$ . This step provides no protection by itself because the decryption key is freely available in the public directory. Following the first encryption by a second encryption using the receiver's public key,  $RE$ , to generate the cipher text allows you to transmit the encrypted and safe data over an open communications channel.

On receipt of the cipher text, the receiver can use his secret key to decrypt the message. However, instead of the message, decryption yields the intermediate cipher text. The receiver can then decrypt the message with the public key. As a result, the receiver has the original message and the sender's signature. This method protects against masquerade and repudiation threats. The signature exists because you created a signed message by encoding with your secret key.


### Additional safety features

A third party can send a message purporting to be from you only if that party knows your secret key. If the third party uses any other key, the final decryption stage using  $SE$  will generate gibberish. Similarly, you cannot deny having sent the message because a message that decodes successfully with your public key must have been originally encoded with your secret key.

By using hash functions and adding date and time data to messages before encrypting, you can provide complete protection against replay and manipulation threats. Public-key systems thus satisfy all of the major cryptographic require-

**FIGURE 3**
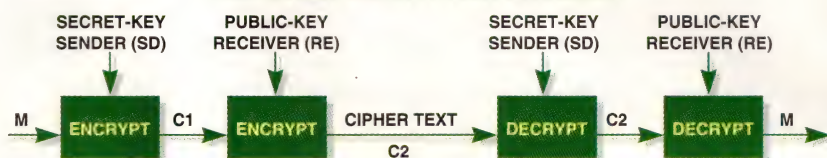
### "SIGNING" MESSAGES USING A TWO-STAGE ENCRYPTION PROCESS:



ments; many organizations, including the US National Institute of Standards and Technology, the American Bankers Association, and the French Banking Association, have accepted the technique.

Despite the significant advantages available with public-key cryptography, secret-key systems have enjoyed far greater use. Public-key algorithms require considerably more computational resources to match the encryption/decryption speeds of secret-key systems. These resource requirements have led to unacceptably high costs.

Secret-key cryptography requires a CPU to perform modular exponentiation in the equation:  $M$  is congruent to  $Cd \pmod{N}$ . Traditionally, this operation involves multiplying a number by itself, dividing the result by  $N$  to give a quotient, subtracting  $N \cdot \text{quotient}$  from the number squared, and repeating the sequence  $d$  times. The division operation is particularly undesirable because it is the slowest of the basic arithmetical operations.

With the discovery of algorithms that perform modular exponentiation without division (Ref 3), CPUs can speed computations.

EDN

## References

1. Diffie, W, and M Hellman, "New Directions in Cryptography," *IEEE Transactions on Information Theory*, November 1976, pg 644.
2. Rivest RL, A Shamir, and L Adelman, "A Method for Obtaining Digital Signatures and Public-Key Cryptosystems," MIT Laboratory for Computer Science, Technical Memo LCS/TM82, August 1977.
3. Montgomery, PL, "Modular Multiplication without Trial Division," *Mathematics of Computation*, Volume 44, 1985, pg 519.

## Author's biography

Antony Watts holds a degree in Solid State Physics from London University. He currently works as communication director for the Memory Products Group of SGS-Thomson Microelectronics.

## VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High Interest  
598

Medium Interest  
599

Low Interest  
600



# Power Op Amps Made Easy

## The Hard Way




## The Easy Way

### Hassle-Free "Monolithic" Solutions

**OPA544** is your hassle-free solution to power amp requirements. It's a monolithic high current, high voltage op amp that delivers  $\pm 2A$  while operating on up to  $\pm 35V$  supplies. No messy, time-consuming, and expensive discrete designs—just drop it in and power up a wide range of electro-mechanical devices including motors, valves, and speakers. It's also ideal for programmable power supplies, automatic test equipment, and audio applications. **OPA544** is easily your choice for simple, hassle-free power op amps.
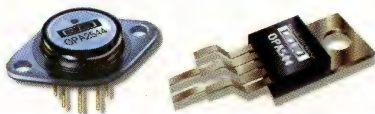
### Low Cost Power Options

**OPA544's** 5-pin TO-220 package saves money—it's your low cost solution. It's also available with stagger-formed leads. Need a dual? Try our **OPA2544**—two high performance FET op amps with output stages on a single chip. For all your power needs—use **OPA544** or **OPA2544**—the power op amp solutions for every application.




### OPA544 & OPA2544 Key Specifications

- Output current .....2A
- Quiescent current (per amplifier).....12mA
- Power supply range ..... $\pm 10V$  to  $\pm 35V$
- Slew rate .....8V/ $\mu s$
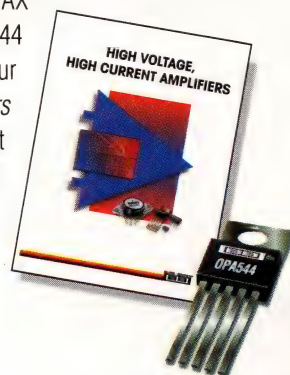
### FREE Sample and Selection Guide

Add power to your next design—FAX (602) 741-3895 for a **FREE** OPA544 sample. And, ask for a **FREE** copy of our new *High Voltage, High Current Amplifiers* guide. It describes the industry's most complete line of power op amps and buffers. Or, call your local sales rep for more information.



**ISO9001 CERTIFIED**

**BURR - BROWN®**  
**BB**

International Subsidiary Offices: France (33) 1 39 54 35 58, Germany (49) 711 77040, Italy (02) 5801 05 04, Japan (81) 33 586 8141, Netherlands (31) 3465 50204, Switzerland (41) 1 724 09 28, United Kingdom (44) 923 233837.

CIRCLE NO. 139

EDN JULY 6, 1995 ■ 103



# When you're the leader in 80C51 microcontrollers...



Philips' family of 80C51 derivatives is the world's largest. And most popular.

With over 75 derivatives based on the 80C51, Philips offers you the broadest range and richest



feature set available. But innovators never rest. Now, Philips is extending the power of the 80C51 family with a smooth migration path to 16-bit. The XA™ (eXtended Architecture) is a high-performance 16-bit

**Philips  
Semiconductors**





**...you keep things moving.**

architecture that also delivers superior code density. Source level code compatibility lets you run existing 80C51 source code through new assemblers without modification. The result is unmatched price/performance. In short, moving from 8-bit to 16-bit couldn't be easier. Exactly what

you'd expect from the world's leading supplier of 80C51 microcontrollers. Push your designs to the leading edge and beyond. With the growing power of Philips 80C51 microcontrollers. Call Philips today.

**1-800-447-1500 ext. 1181**



**PHILIPS**





# HOW HP AND SYNOPSYS GOT THE HP LASERJET PRINTER TO MARKET FASTER.

The HP Boise Printer Division needed to develop the key ASIC for a new HP LaserJet® Printer design — fast! So they took an Empowered Engineering approach and created a world-class design environment complete with HP 9000 workstations, Synopsys' high-level design software and Logic Modeling SmartModels® — all in an integrated environment with a common database.

Synopsys' VHDL System Simulator™ (VSS) and SmartModels® let HP simulate the ASIC with the major components surrounding it — pins-out verification — to verify its performance for production. Plus, Synopsys' synthesis and VHDL code reuse capabilities will save HP

redesign time in the future. HP's designers can choose from 250 target silicon libraries and port code for the same chip to more than one vendor. This demanding process was expedited thanks to the great performance of HP's powerful 9000 workstations. Propel your products to market — with Synopsys and HP. Call 1-800-388-9125, email [designinfo@synopsys.com](mailto:designinfo@synopsys.com) or see us on the WWW at <http://www.synopsys.com>



**SYNOPSYS®**



**HEWLETT  
PACKARD**



# Options dot the programmable-logic landscape

RICHARD KAPUSTA, CYPRESS SEMICONDUCTOR CORP

PLDs have emerged as indispensable tools for system designers. They have evolved from fast prototyping tools into production devices that quickly get your designs to market, when anticipated volumes don't justify the cost of a full ASIC design.

When contemplating the use of PLDs, you face an array of options. Each PLD type has a unique set of characteristics that bring advantages and disadvantages to any design. Knowing how to sort out these differences is essential to creating efficient, cost-effective designs that wring the highest possible performance out of the devices.


Three major PLD types are in use, each with a distinct architecture, capacity, and performance capability:

- A simple PLD comprises a single logic block. It is restricted in the amount of logic that can be implemented. The industry-standard 22V10 is such a device. It has 12 dedicated inputs, a product-term array, a product-term allocation scheme, 10 macrocells, and 10 I/O cells.
- A complex PLD (CPLD) comprises multiple logic blocks that communicate with one another through a global interconnect (Fig 1). Each logic block in a CPLD is similar to a simple PLD, containing inputs, a product-term array, a product-term

allocation function, macrocells, and I/O cells. These elements connect to build desired logic functions. The number of macrocells and inputs and the method of allocating product terms vary with vendors' product families.

- A field-programmable gate array (FPGA) is a collection of logic cells that communicate with each other and with I/O pins via horizontal and vertical routing channels (Fig 2). Functions are built by connecting the logic cells. The logic contained within FPGAs is typically more versatile or fine-grained than that of simple PLDs or CPLDs. However, the flexibility of FPGAs comes at a price; FPGAs cannot provide fixed delays, so they are more complicated to use.

FIGURE 1

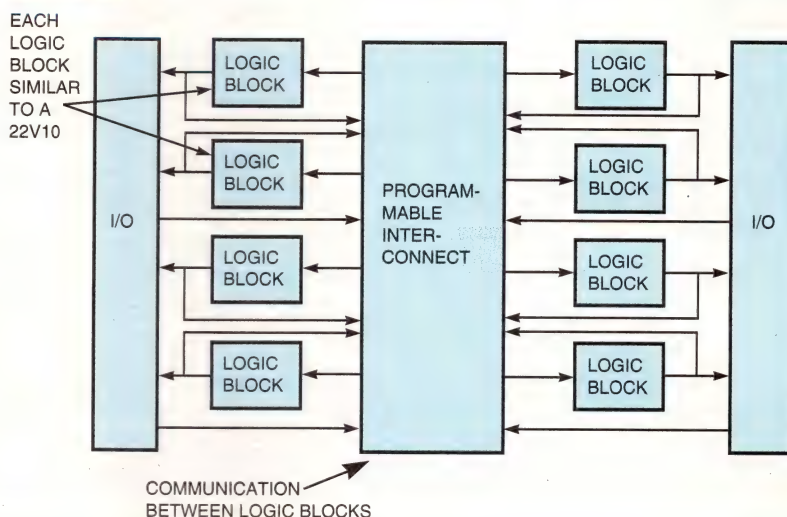

In a CPLD such as the Flash370, logic blocks and I/O pins communicate with each other through the programmable interconnect.



## PROGRAMMABLE LOGIC DEVICES

- A PLD's capability depends on resources such as its approach to interconnect—the way in which it routes signals between logic blocks and I/O pins. In CPLDs, interconnects can occur in two ways:
- In a full crosspoint switch configuration, typified by the Cypress MAX340 family. Such an interconnect is completely routable; that is, any combination of simultaneous signals can be routed to or from any logic block through the global interconnect. However, this arrangement is slow and large: The 100% crosspoint-switch-based interconnect sacrifices speed and die size for maximum flexibility of signal placement and design modification.
- A multiplexer-based approach, typified by the Cypress Flash370 CPLD family and used by many vendors. Distributing all signals through multiplexers instead of a crosspoint-switch system reduces interconnect size and enhances speed. There are many implementations of multiplexer-based interconnects, and the ultimate routability of a multiplexer-based scheme varies from vendor to vendor. The Cypress Flash370 CPLD family provides much higher performance than CPLDs based on the crosspoint switch and provides a highly routable interconnect.

Routability involves two aspects. First is the number of signals the global interconnect provides into each logic block. If the maximum number of signals that can be routed to a logic block is smaller than the required number for a particular logic function, then the design will not fit or will have to be partitioned among multiple logic blocks.

The second aspect is the routability within the interconnect itself; that is, the probability of finding an interconnect that routes all the required signals into the appropriate logic blocks.

Two factors make finding such an interconnect difficult.

First, as the number of signals that must be routed into a logic block approaches the maximum, it becomes much more difficult to find a way to interconnect the signals. Second, as you begin to fix the input location of these signals, it becomes harder to route them to the appropriate logic blocks.

Additional problems can arise in some CPLDs if their design requires logic changes after a pinout produces a successful route. With the changes, the design may no longer fit with the same pinout. Some architectures feature better interconnect routability than others, and you should carefully consider routability as you select your device.

After interconnect, the second major resource to consider in evaluating a PLD is the characteristics of the logic blocks themselves, such as their ability to perform logic on a given number of inputs. Logic-block capabilities have evolved since the introduction of the now-ubiquitous simple PLD, the 22V10. This device has a fixed number of product terms available to each macrocell, designated by the numbers 10, 12, 14, and so on. If you use fewer product terms than the designated capacity of a macrocell, you lose the rest because you cannot steer them to another macrocell. Furthermore, multiple macrocells cannot share a product term, so you must duplicate this logic at every macrocell that requires it. The concepts of steering and sharing are important because they permit more efficient utilization of device resources and enhance performance.


As CPLDs emerged, vendors attempted to implement product-term steering and sharing. With product-term steering in many early CPLDs, designers moved a group of logic from an adjacent macrocell when a function required more product terms than those allocated to a macrocell. This movement increases the amount of logic available to that macrocell, but it also strands the adjacent macrocell with no logic, reducing the overall utilization of the CPLD and resulting in wasted resources because no logic is available for them.

The product-term sharing that many CPLDs use allows you to implement logic once and use it multiple times in generating other more complex functions. The basic problem in most implementations of this scheme is the added signal delay using these shared resources incurs.

The most advanced CPLDs employ a method in which software steers and shares single product terms as needed without stranding macrocells or incurring any extra delay (Fig 3).
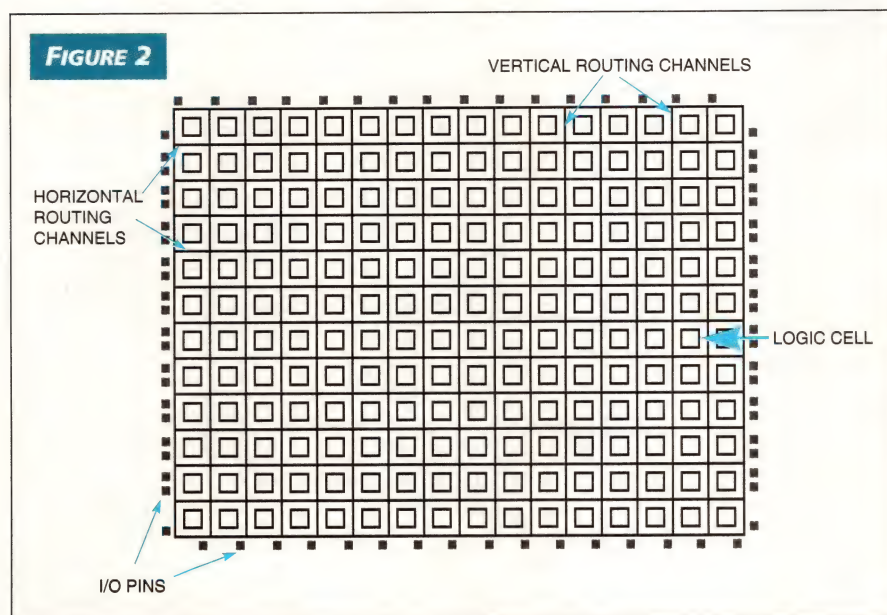
### Capabilities of FPGAs

The architecture of an FPGA differs widely from that of a CPLD. Instead of a global interconnect matrix, the logic cells of an FPGA communicate with one another via vertical and horizontal routing channels. A typical FPGA logic cell is smaller and less complex than



**Horizontal and vertical routing channels and I/O pins appear along the periphery of this ASIC380 FPGA.**



that of a CPLD. The cell usually comprises a register with associated logic and has multiple inputs and outputs (Fig 4).

An FPGA design typically employs an I/O pin, one or more logic cells, an optional register, and another I/O pin leading off the chip. The delays imposed by the wire and programmable elements, the number of cascaded logic cells, and the propagation delay of each logic cell determine the ultimate design performance. The capacity depends upon the flexibility inherent in the logic cells and the routability of the interconnect.

An FPGA's technology impacts both the interconnect delay and the routability. The two major types of FPGA technologies are SRAM- and antifuse-based. The smaller size of the antifuse interconnect permits many more programmable elements to fit on a chip of comparable size and density. An SRAM-based FPGA, with fewer possible interconnects, is more restricted in its routability than an antifuse-based FPGA. On the other hand, an SRAM-based FPGA has the advantage of reconfigurability, a feature that some applications require.

SRAM- and antifuse-based FPGAs also differ in their logic-cell architecture. Although no logic-cell configuration is inherently better than another, the two architectures are distinguished by whether they are fine- or coarse-grained. Antifuse FPGAs typically use the fine-grained approach, which involves quite small and relatively simple logic cells. You have to use more logic cells to implement a function than you would to implement an equivalent function with a coarse-grained FPGA. Thus, a fine-grained approach relies more heavily on the interconnect and multiple cascaded cells, which may slow performance.


However, if the interconnect and logic cells are inherently fast, delays aren't a problem. Alternatively, with SRAM-based FPGAs, you must minimize interconnect because of the higher delay and fewer fuses available, thereby limiting your routing choices.

### Selecting the right device

Your choice of PLD may involve several trade-offs. For example, the smallest PLDs are usually the fastest. However, they are also the least dense and may not be able to accommodate your design in one device. The maximum rating of a 22V10 can vary from vendor to vendor, but the leading edge today is approximately 175 MHz, corresponding to about a 4-nsec delay from input to output. A CPLD works better in more complex designs because it is somewhat like having many smaller PLDs on one chip.

For a 7.5-nsec delay, CPLDs can reach approximately 150 MHz. For some CPLD families, taking advantage of various architectural features affects design performance, and the

FIGURE 3

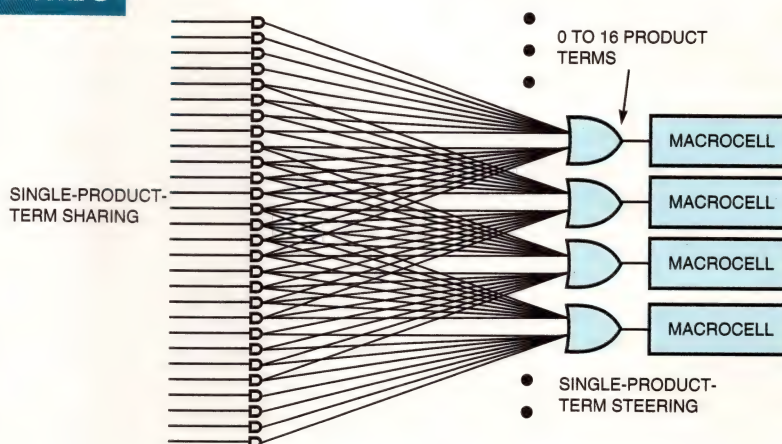

**Product terms go to macrocells on an individual basis as the software requires in this Flash370 CPLD product-term allocator. As many as four macrocells can share a product term without performance penalty, eliminating the need to duplicate logic.**

maximum performance rating of a device applies only to the simplest of designs. In other words, make sure that a CPLD with a 7.5-nsec input-to-output delay in its data sheet will perform your design at that speed before you make your decision.

The story is different for FPGAs. It is difficult to provide specifications for parameters such as propagation delay and maximum frequency because they depend completely on the placement and routing of the design. An absolute timing prediction is, therefore, impossible. An FPGA is generally slower than a CPLD or simple PLD, depending on the application. In terms of density, FPGAs are the largest devices in the PLD spectrum.

The ease of predicting design performance based on the manufacturer's data-book specifications is also an important concern. Predictability is tied closely to the general ease of use of each PLD family. As a rule of thumb, the smaller the device, the more predictable it is. With a 22V10, you typically know in advance exactly what the performance will be.

CPLDs are somewhat less predictable but vary from family to family. Some CPLD families have specifications for timing delays that depend on factors like fan-out or the number of product terms. The software compiler ultimately makes these implementation decisions, forcing you to implement the entire design before knowing what the performance will be. Other CPLD families have more straightforward timing specifications and are, thus, much easier to use. Finally, FPGAs are the least predictable of PLDs: You must implement the design before knowing what the final performance will be.

To determine which device will meet your performance requirements, you can use the benchmarks provided by the Programmable Electronics Performance Corp (PREP) (see box, "Using the PREP benchmarks"). In addition to performance, though, consider the tools available for implementing the design (see box, "Design-tool considerations").



## PROGRAMMABLE LOGIC DEVICES

Choosing a PLD based on density is a cut-and-dried decision. If your design calls for a certain capacity, your choice is circumscribed. The problem lies in determining the true capacity of a device. Two FPGA vendors may offer products listed as 4000-gate devices, but the actual densities they provide might differ widely.

The real question is, "How many gates are usable?" In a CPLD application, if your design contains signals with very complex logic, it may borrow logic from other macrocells, thus stranding macrocells throughout the device. The actual density available might be much smaller than the vendor-specified density. One way to get reasonable assurance of the actual density and whether your design will fit is to use the PREP benchmarks.

Power consumption is an important consideration in any design, especially with the current rapid growth of mobile communications and portable computers. Because the power a PLD consumes depends on the speed of operation and varies from vendor to vendor, it's difficult to create a guideline based on power alone. As a rule, for the same application, a CPLD consumes more power than does an FPGA. Typically, flash- or EEPROM-based PLDs require more

power than SRAM- or antifuse-based devices.

State machines are among the most popular applications for programmable logic. Because CPLDs and FPGAs differ in architecture, the optimal state-machine implementation also differs. FPGAs have a register-intensive architecture, and the amount of logic per register is less than that of a CPLD.

(continued on pg 114)

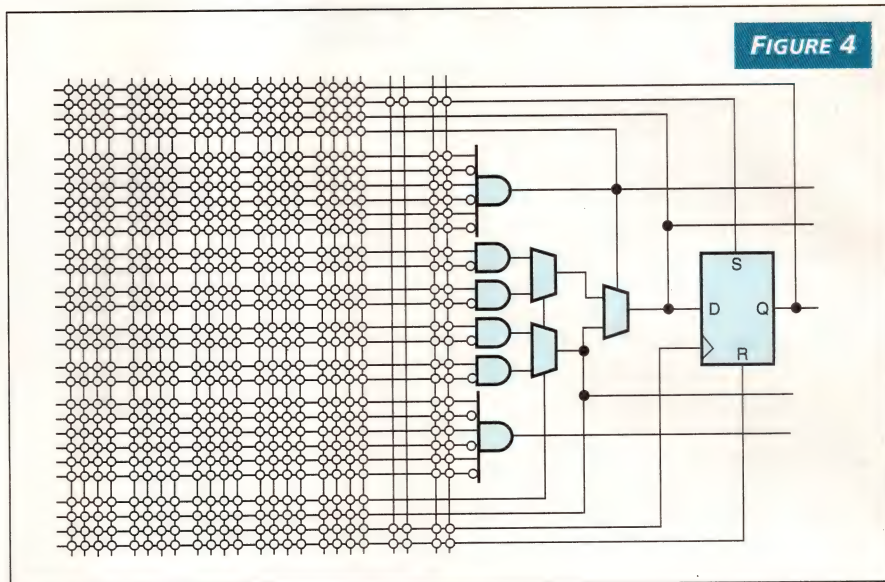


FIGURE 4

**This fine-grained pASIC380 logic cell accommodates 23 inputs from routing channels and provides five outputs.**

## USING THE PREP BENCHMARKS

In 1991, eight PLD vendors in association with programmable-logic users formed the Programmable Electronics Performance Corp (PREP) to provide a comparison standard for the relative capacity and performance of field-programmable gate arrays (FPGAs) and complex PLDs (CPLDs). The PREP members developed a suite of nine benchmark circuits to objectively evaluate the relative performance and capacity of the various devices in a design.

These benchmarks provide a means for comparing the relative impact of device architecture and technology implementation on performance and capacity. The actual implementation of each circuit is left to the device vendor, which implies that the reported results are the absolute best for each device. The functionality of each implementation must exactly match the PREP benchmark specification, and any user must be reproducible by any user.

The benchmark data quantifies the speed and logical capacity of the PLDs. You measure the capacity by instantiating the benchmark circuit multiple times in a single device until the device is filled. You calculate the performance by measuring the instance-to-instance performance for each repetition of the benchmark and then reporting the best, worst, and arithmetic mean of the internal clock-to-clock maximum

frequency based on worst-case guaranteed device specifications. The external frequency also uses the clock-to-output specification and the external pin-setup time between the last instance and the first.

Each PREP member seeking PREP certification for a device must report benchmark data for all nine benchmarks in a standard format and submit them for verification and certification by a third party before publication of certified results. PREP itself cautions that, although benchmarks are important, they are not a substitute for data sheets, and they provide a limited view of device capabilities.

The benchmarks can be useful as a first-level, coarse screening in selecting a device, but keep benchmark limitations in mind. In most cases, the interconnection of multiple instances in a benchmark circuit is unlike the interconnections in real designs. As a result, the reported capacities for a device may be higher than actually available in a real design, and real design may exhibit slower performance than the benchmark because of denser interconnection.

Further, PREP does not endorse averaging data for a device across all nine benchmarks. Such averages in vendor data sheets can be misleading. In general, you cannot use the benchmarks to predict system design performance.



# WHAT MAKES THE POWERPC BOARDS FROM MOTOROLA SO FAST?

## THE POWERPC BOARD FAMILY.

Motorola's leading-edge board technology brings you leading-edge PowerPC™ boards. These boards will speed up your product development, your system performance, and more than likely, your heartbeat.

## DESIGNED TO SHRINK YOUR DESIGN TIME.

Slice weeks or even months off your product development time. Our PowerPC boards are ready today, so you can get right to work on your systems. Development software is also ready to go. Right now.

## A WARRANTY AS AMAZING AS THE BOARD.

Developing this fast has never been this safe. All of our PowerPC boards are backed by the industry's first Five-Year Warranty. Call today for complete information about our PowerPC boards.



**MOTOROLA**  
Your Source for POWER Computing™



Available  
in VME  
and Non-VME  
Platforms.  
Ethernet and  
SCSI-2  
Interfaces.  
SVGA Graphics.  
Low Profile  
Desktop Form  
Factors.

66 MHz PowerPC 603.

100 MHz PowerPC 604.

Parallel and Serial I/O.

Floppy and IDE

Interfaces.

8 to 128MB DRAM.

33 MHz PCI Local Bus

with PCI and

ISA Expansion Slots.

PowerPC Reference

Platform

Compatible.

Development

Software Available

for PowerPC

Reference Platform

Compatible Software

Environments.

© Copyright 1993 Motorola, Inc. Motorola and the Motorola logo are registered trademarks of Motorola, Inc. Your Source for Power Computing is a trademark of Motorola, Inc. The PowerPC name and the PowerPC logo are trademarks of International Business Machines Corporation, used under license herefrom. All other products mentioned are trademarks or registered trademarks of their respective holders.

Australia 61-2-906-3855 Belgium 32-2-718-5582 China (PRC) 86-1-843-7222 France 33-1-4674-3560 Germany 49-40-236204-0 Hong Kong 852-966-3210 Italy 39-2-8220-239 Japan 81-3-3280-8461 Korea 82-2-720-0653 Netherlands 31-30-870857 Scandinavia 46-8-734-8800 Spain 34-1-329-0461 Taiwan 886-2-717-7089 UK 44-628-39121



## PROGRAMMABLE LOGIC DEVICES

Thus, you can take advantage of the inherent architectural edge of CPLDs by minimizing the number of registers your design requires.

In sequential state encoding, you assign each state a binary value starting with zero and progressing sequentially. In some very complex state machines, the amount of transition logic for a sequentially encoded state machine exceeds the maximum logic available in even the most sophisticated CPLDs, and you should use another state-encoding scheme.

Another architectural advantage that some CPLDs have over FPGAs is the programmable, T-type register. For some state-machine designs, such devices can significantly reduce the amount of required logic, producing a compact and fast implementation. Counters implemented in CPLDs using T-type registers usually use fewer product terms than those implemented in CPLDs that use D-type registers. As the width of the counter increases, the number of product terms saved also increases. Furthermore, the addition of features such as load, enable, reset, and preset does not add significant logic requirements, and you can implement these features at the maximum rated frequency of the device. However, vendors of some CPLD families rate the maximum performance of a device differently for T- and D-type devices (Ref 1).

When targeting a state-machine application into an FPGA, choose a state-encoding technique that minimizes the logic between each state transition. One example of this type of state encoding is called "one-hot" state encoding, which uses one register per state. Thus, a one-hot-encoded state machine with 12 states would require 12 registers. Such a machine can take advantage of the more register-intensive architecture of an FPGA. The ultimate goal is to reduce the state-transition logic to a single logic cell.

Just like in CPLDs, for simple state machines, one-hot encoding may be too simplistic and require more registers than an alternative approach that would employ fewer registers but more transition logic between each register. You would have to base this decision on the synthesis-tool and place-and-route results.

When deciding between an FPGA and a CPLD for a state-machine application, consider the performance requirements along with the logic complexity required for each state transition. CPLDs are inherently faster than FPGAs in state-machine applications, as PREP benchmarks 3 and 4 show (Table 1). However, if performance is not the overriding concern, base your choice on state transition-logic requirements. Furthermore, other functions the application requires might weigh the decision in favor of an FPGA or a

## DESIGN-TOOL CONSIDERATIONS

The decision on which design tool to use to describe, synthesize, and optimize a PLD design is as important as your selection of a PLD device. Frequently, an architecture might appear to have the appropriate resources for solving a design problem, but the actual result may fall short of your goal because the tool did not efficiently use those resources.

In selecting a tool, you can use a tool from the PLD vendor and tailored for the vendor's products or a tool from a third-party tool vendor. PLD vendors' tools support a given architecture, so they can perform architecture-specific synthesis at the front end and are usually more efficient than are third-party tools. PLD vendors deliver more efficient optimization and mapping capability earlier than do third-party tool vendors. Third-party vendors must serve a broad range of users, and survival does not depend on supporting one vendor.

On the other hand, you may already have a design environment built around a third-party vendor's tools and want to incorporate PLD design into your design process. You may also prefer a tool that supports a broad range of PLDs so you don't have to learn a new tool every time you use a different vendor's devices.

In the short term, a PLD vendor's tool can get you started easily, provide good optimization and mapping for the target architecture, and is usually low-cost. Some PLD vendors' tools support a wide range of devices. For example, Cypress's Warp3 tools support PLDs, complex PLDs (CPLDs), and field-programmable gate arrays (FPGAs). In the long term, the ongoing integration of PLD vendors' synthesis and place-and-

route engines into third-party tools will continue to improve the tools' efficiency and effectiveness.

CPLDs historically have been more amenable to traditional third-party approaches that generally synthesize a product's logic into a standard format. Getting a tool to map to the widely varying FPGA architectures requires different synthesis and optimization strategies. The ultimate consideration may be one of design style: whether to use a hardware-description language, such as VHDL, or a schematic-capture approach. The schematic-capture approach lets you tailor your design to the idiosyncrasies of an architecture. This typically library-based design, and some tools even provide users with a VHDL-based version of the library components.

However, using VHDL or another HDL lets you quickly run your design through one or more tools to see how they map to the target device. Doing your own benchmarking of various synthesis tools is a good idea. Programmable Electronics Performance Corp (PREP) is considering undertaking such an activity, which should users should support.


The PREP benchmarks are useful as rough performance and capacity indicators, but be aware of their limitations. You might interpret the benchmark results to indicate that one device gets twice as many instances as any other in building a state machine. But the tool you use or the design style you employ may not give you the same level of efficiency. The synthesis to the target device affects the resulting design. It is, therefore, important to understand what kind of special or architecture-specific synthesis and optimization techniques are available in the tool to get the most efficient design.



# When Your World Enters Ours...
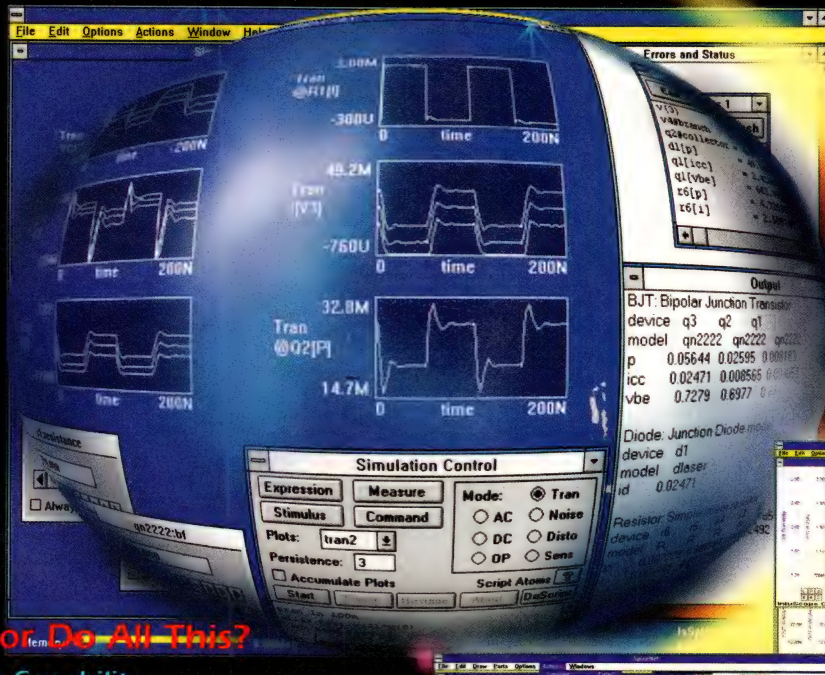
## Look At All That You Can Do!

With ICAP/4, The Virtual Circuit Design Lab, you can tackle the toughest System, IC, and Board-level designs.



### Can Your Simulator Do All This?

#### \* Powerful Simulation Capability

Simulate all types of designs: Power, ASIC, RF, Mixed Mode, System-Level, Mixed Technologies (Electrical, Mechanical, and Thermal) and Mixed Environment (Hardware/Software).

#### \* IsSPICE 4 Gives You More

The First and Only Truly Interactive Native Mixed Mode SPICE 3F based simulator with UNLIMITED circuit size. Combine analog, digital, behavioral, procedural, and sampled-data elements with state machines, array processing algorithms (wavelet transforms, FFT), and hardware (fast equipment, microphones, speakers etc.) WOW!! Can Your SPICE Do That?

#### \* Completely Integrated System

Systems include Schematic Entry, Interactive SPICE Simulation, Extensive Model Libraries (over 6000 models), and Graphical Data Processing.

#### \* HDL Model Development


Develop analog, digital, mixed mode, and non-electrical models, using a C based high level description language.

#### \* Platform and Product Support

Windows (32s), Windows NT(x86, Alpha, Mips), DOS, Macintosh and Power Macintosh, FREE Modeling Service.
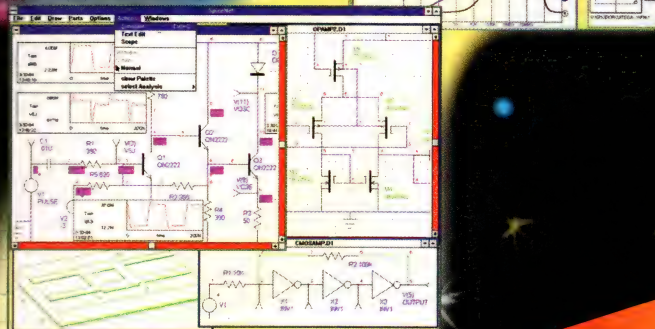
#### \* Affordable Prices

Complete systems are available for \$595 - \$2595.



**New Keyless  
Network Version**

**Call, Write, or e-mail for your FREE  
Working IsSpice Simulation Kit**

**intusoft**

P.O. Box 710 San Pedro, CA 90733-0710  
Tel. 310-833-0710 • Fax 310-833-9658  
e-mail 74774.2023 © compuserve.com  
FTP Site - ftp.iee.ufrgs.br

**The Future is Interactive!**



## PROGRAMMABLE LOGIC DEVICES

CPLD. Alternatively, you could explore both FPGA and CPLD options after synthesis and place-and-route and base your decision on actual simulated performance in the application. In this case, choose state-encoding methods separately for each target architecture to take advantage of the device's inherent architectural characteristics.

### Arithmetic functions

In general, FPGA architectures are more adaptable to arithmetic applications than are CPLD architectures. The simplest type of arithmetic application is an accumulator. The 16-bit accumulator circuit is one of the PREP benchmarks, and you can take advantage of the PREP benchmark data when deciding which type of architecture to use. Using the official PREP benchmark numbers, according to PREP PLD Benchmark Suite 1, Versions 1.2 and 1.3 for Benchmark 6, you can average the internal frequency for all the certified CPLDs. Then, average the same parameter for all of the certified FPGAs. (PREP does not endorse the averaging of PREP benchmarks.) Comparing these values shows that, for the accumulator circuit, FPGAs typically operate faster than do CPLDs.

Most FPGAs have a much finer-grained architecture than that of CPLDs. The granularity also varies even among FPGA devices. The finer the grain of an architecture, the more flexibility it offers in implementing the logic associated with arithmetic circuitry. For example, the Cypress pASIC380 FPGA devices employ a multiplexer-based, logic-cell architecture that allows the implementation of efficient carry-select accumulator circuits. FPGAs that are not multiplexer-based excel in arithmetic applications because of dedicated carry calculation and passing circuitry built into the devices themselves.

Whatever your application, try many target architectures before choosing the device to use. This approach can be time-consuming and costly, however. Intelligently using the PREP benchmarks helps make your job easier and more satisfying.

EDN


### Reference

1. Jones, Christopher, "Knowing your CPLD maximizes its resources," *EDN*, Jan 5, 1995, pg 117.

**TABLE 1—CPLDs vs FPGAs in PREP BENCHMARKS 3, 4, AND 6**

Device	Internal frequency	BM3	BM4	BM6
<b>CPLDs</b>				
Altera EPM7032-6		152	70	51
Altera EPM7064-7		125	78	43
Altera EPM7096-7		125	78	43
Altera EPM7128-10		100	59	32
Altera EPM7160E-10		100	63	32
Altera EPM7192-12		91	53	31
Altera EPM7256E-12		91	53	31
AMD MACH230-15		67	33	22
Cypress CY7C371-143		143	87	50
Cypress CY7C374-100		100	56	39
Cypress CY7C375-100		100	45	39
Lattice pLSI1048-80		78	43	30
Lattice pLSI2032-135		135	61	19
Xilinx XC7272A-16		62	62	32
Xilinx XC73108-10		62	62	42
<b>Average CPLD performance</b>		102.07	60.93	35.73
<b>FPGAs</b>				
Actel A1225-1		34	21	24
Actel A1240A-2		39	24	29
Actel A1280-1		29	17	21
Actel A1425		46	28	36
Actel A1240		29	18	22
Altera EPF81188-2		45	17	59
Altera EPF8282-2		49	20	60
Altera EPF8452-2		45	17	58
Altera EPF8820-2		45	18	57
Altera EPF81500-2		41	18	57
Altera EPF81500-2		41	18	57
AT&T AT&T1C07-2		30	18	50
AT&T AT&T1C07-3		38	22	62
Quicklogic QL12X16-2		57	33	39
Quicklogic QL8X12A-3		62	38	45
<b>Average FPGA performance</b>		43.07	22.80	43.87

### Author's biography

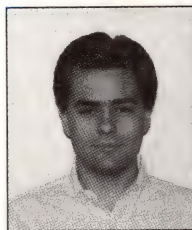

Richard Kapusta is PLD software applications manager at Cypress Semiconductor (San Jose, CA), where he has worked for three years. At Cypress, he's engaged in product planning and working with third-party tool vendors and customers. He holds a BS in computer engineering from the University of Illinois, Urbana/Champaign. He enjoys skiing and music.

### VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High Interest  
582

Medium Interest  
583

Low Interest  
584





# 200W MIL-STD 1/2 the space

interpoint

## MK200

dc-dc converter

Made in U.S.A.

V in: 28  
V out: 15  
Output: 200W  
Model: MK200-2815

MK200 shown actual size.

Introducing Interpoint's new high-density, high-performance MK200 dc-dc converter.

If you're designing power supplies into military or aerospace systems, the new MK200 Series will put uncompromising performance on your board.

SINGLE			DUAL		
Vout Single	Output Current	Ripple mVp-p	Vout Dual	Output Current	Ripple mVp-p
5	30A	10	±12	±7.1A	50
12	14.1A	20	±15	±6.7A	60
15	13.3A	25			

1 MHz operating frequency (fixed) • 500V, 100 Mohm isolation • 150 grams weight • 2.4 x 2.28 x 0.45 in. (61.0 X 57.9 X 11.4 mm) • 16 to 40 or 19 to 40 Vdc input • Wide range output trim

They provide the industry's highest usable power density: 80W/in<sup>3</sup>, from -55° to +125° C with no external components. That's up to a full 200 watts of output power in a low-profile, standard-pinout part half the size of "the brick". Internal filtering and low noise levels eliminate external filters. Efficiencies up to 90% drastically reduce heat sink requirements.

These high reliability dc-dc converters are packaged in six-sided sealed metal cases and utilize hermetically sealed silicon. They meet MIL-STD-810 environmental standards, and are tested to the stringent thermal shock conditions of MIL-STD-202.

To order samples and complete specifications, call Interpoint today at **1-800-822-8782** and power up your board in half the space.



## interpoint

### Corporate Headquarters

P.O. Box 97005 Redmond, WA (USA) 98073-9705  
(206) 882-3100 Fax: (206) 882-1990  
Internet: power@intp.com

### International Headquarters

Fleet, Hampshire (UK)  
Ph: 44-1252-815511 Fax: 44-1252-815577  
Internet: poweruk@intp.com

### Interpoint France

Paris  
Ph: 33-1-34285455 Fax: 33-1-34282387  
Internet: powerfr@intp.com

CIRCLE NO. 157



# THE ART OF THE SMALL

Precision capacitors for small spaces and a broad range of applications




The growing demand for smaller end products calls for fresh, challenging designs. Now, TOKIN is meeting this challenge with a newly expanded lineup of compact capacitors that makes it easier than ever to satisfy exacting miniaturization needs.

Capacitance ranges from 1 to 22 FμF, and all models feature low impedance, excellent

frequency characteristics, exceptional reliability and convenient surface mounting.

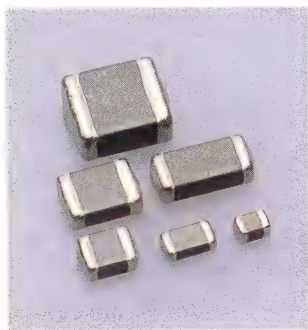So whatever you have in mind—switching power supplies or DC-DC converters, drive circuits or LCD module controllers—check out the TOKIN lineup. You'll find the ideal capacitor to fit your needs, with plenty of room to spare.




Product lineup and dimension "T"

Rated voltage (V DC)	10V.DC	16V.DC	25V.DC	50V.DC	100V.DC
Capacitance (μF)					
0.1					
0.15					
0.22					
0.33					
0.47					
0.68					
1					
1.5					
2.2					
3.3					
4.7					
6.8					
10					
15					
18					
22					

CL Series (Y5V) CL Series (X5T) CT Series (Y5V) CU Series (Y5U)

Temperature vs. DC bias characteristics

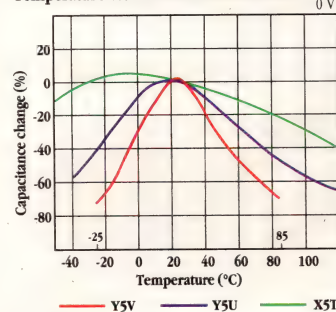

## TOKIN

### Tokin Corporation

**Head Office**  
7-1, Koriyama 6-chome, Taihaku-ku, Sendai, Miyagi-ken 982 Japan  
**International Sales Department**  
Sumitomo Seimei Sendai Chuo Bldg., 6-1, Chuo 4-chome, Aoba-ku, Sendai 980, Japan  
Phone: 022-211-1281 Fax: 022-211-0975  
**Seoul Representative Office**  
#602, Champs-Elysees Bldg., 889-5, Daechi-Dong, Kangnam-gu, Seoul, Korea  
Phone: (2) 569-2582~5 Fax: (2) 554-7087

### Tokin America Inc.

155 Nicholson Lane, San Jose, California 95134, U.S.A.  
Phone: 408-432-8020 Fax: 408-434-0375  
**Chicago Branch**  
9935 Capitol Drive, Wheeling, Illinois 60090, U.S.A.  
Phone: 708-215-8802 Fax: 708-215-8804

### Tokin Electronics (HK) Ltd.

Unit 705-707, Chiwan Tower, Park Lane Square, 1 Kimberly Rd., Tsim Sha Tsui, Kowloon, Hong Kong  
Phone: 730-0028 Fax: 375-2508  
**Taiwan Liaison Office**  
Phone: (02) 7728852 Fax: (02) 7114260  
**Singapore Branch**  
Phone: 2237076 Fax: 2236093, 2278772  
**Shanghai Liaison Office**  
Phone: 21-433-4488 Ext. 80809 Fax: 21-433-3265 Ext. 80809

### Tokin Europe GmbH


Hellersberg, Str. 14, 41460 Neuss, Düsseldorf, Germany  
Phone: 2131-1866-0 Fax: 2131-1866-18



# COMPONENTS

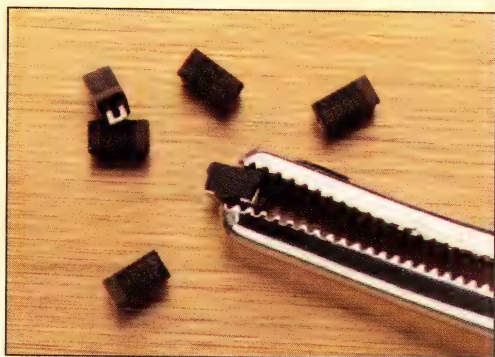
## SHOWCASE

- ▶ RESISTORS
- ▶ CAPACITORS
- ▶ INDUCTORS


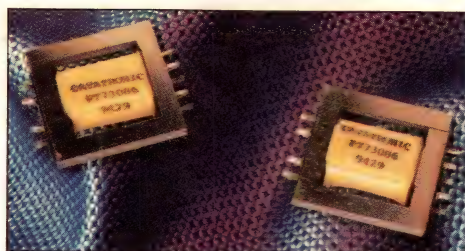
### TANTALUM CHIP CAPACITOR WITH FUSE.

The TCF Series of tantalum chip capacitors includes a built-in fuse to protect against the possibility of fire if the polarized device is mounted incorrectly. The capacitors are available in values from 1 to 10  $\mu\text{F}$  in the A (3216) case size and up to 33  $\mu\text{F}$  in the B (3528) case size. Rated voltages range from 4 to 35V. Tests on the TCF devices after soldering show 4 $\Omega$  equivalent series resistance. Prices range from \$0.085 to \$0.105 (1,000,000). **Rohm Corp, Electronics Div,** Nashville, TN. (615) 641-2020. **Circle No. 425**




### LINE-MATCHING TRANSFORMER FITS PCMCIA CARDS.

The PT73086 surface-mount line-matching transformer has a maximum height of 0.172 in. and a footprint of 0.790 $\times$ 0.670 in. The device meets the V.32 and V.32bis standards for modem applications. Key specifications include a nominal impedance of 600 $\Omega$ , -76-dB distortion, and an insertion loss of 3.15 dB at 1 kHz. The device costs \$1.05 (100,000). **Datatronics Inc,** Romoland, CA. (909) 928-7700. **Circle No. 426**

### LOW-PROFILE TANTALUM CHIP CAPACITOR.

The Type 592D tantalum chip capacitor measures 0.047 in. above the board. The conformally coated device fits standard molded chip-mounting-pad dimensions. The 12 capacitance values are available from 1.0 to 100  $\mu\text{F}$  with voltage ranges from 4 to 35V at 85°C. Typical performance ratings for a 22- $\mu\text{F}$ , 16V dc device at 25°C include an ESR of 1.85 $\Omega$  at 100 kHz, a dc-leakage current of 0.01  $\mu\text{A}/\text{CV}$ , and a dissipation factor of 6% at 120 Hz. Typical price for a 10- $\mu\text{F}$  capacitor with a 10W-Vdc rating and a  $\pm 20\%$  tolerance is \$0.336 (1000).

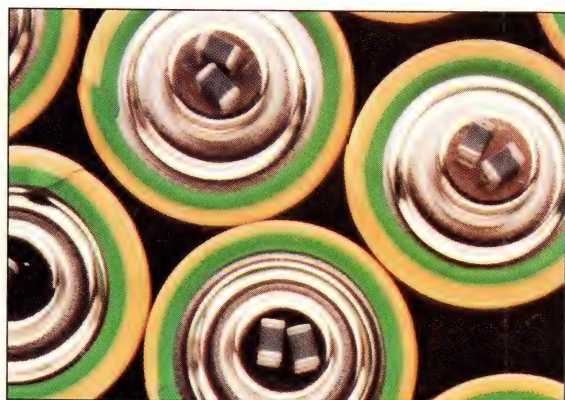**Sprague,** Columbus, NE. (402) 563-6350. **Circle No. 427**



### SURFACE-MOUNT CHIPS SUPPRESS EMI.

The LCB-0805 EMI suppressor has a standard 0805 footprint, 600 $\Omega$  impedance, and a dc resistance of 1.0 $\Omega$ . The JCB-0805 has a 300 $\Omega$  impedance and a dc resistance of 0.5 $\Omega$ . The KCB-0805 has a 120 $\Omega$  impedance and a dc resistance of 0.6 $\Omega$ . Maximum current for all devices is 200 mA. Operating temperatures are from -55 to +125°C. The devices cost \$0.11 (100,000). **Associated Components Technology,** Garden Grove, CA. (714) 636-2645. **Circle No. 428**

(continued on pg 120)




- ▶ RESISTORS
- ▶ CAPACITORS
- ▶ INDUCTORS
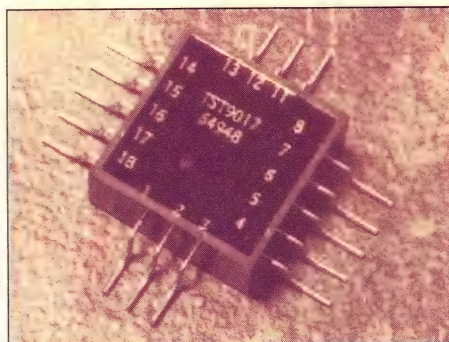
### ISOLATION TRANSFORMERS.

DU and SU series isolation transformers accommodate international input voltages and are available in models from 250 VA to 10 kVA, with the VA rating doubled for autotransformer connections. The transformers feature 2500V-rms HIPOT, Class A insulation (105°C) and a grounded 2-mil-thick copper-foil electrostatic shield. They are designed with dual primaries (DU Series) and secondaries (SU Series). Windings are identically rated at 0/104/110/120V ac or 0/208/220/240V ac, letting you




connect primary and secondary windings in series or in parallel. Prices range from \$53.50 to \$480 (100). **Signal Transformer Company Inc.**, Inwood, NY. (516) 239-5777. **Circle No. 429**


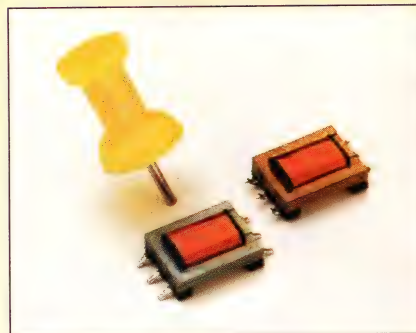
### DUAL MIL-STD-1553 TRANSFORMER HAS SMALL FOOTPRINT.

The TST-9000 has a case measuring  $0.625 \times 0.625 \times 0.28$  in. high. The dual transformer has a 10,000-hr life expectancy and meets the MIL-STD-1553 requirements for component isolation and common-mode rejection ratio. The transformers are encapsulated in a diallyl phthalate case and tested in compliance with MIL-T-21038 and MIL-STD-202. All models have center-tapped primaries and multi-tapped secondaries to accommodate existing systems. The transformers cost \$90 (10). **Beta Transformer Technology Corp.**, Bohemia, NY. (516) 244-7393. **Circle No. 430**



### SURFACE-MOUNT TRANSFORMERS FOR PCMCIA MODEM APPLICATIONS.

The transformers meet the voice, data, and facsimile requirements of the V.34bis 28,800-bps protocol. The transformer-mounting footprint measures  $0.33 \times 0.40$  in., and the height measures 0.164 in. It has a turn ratio of 1:1 and a frequency response of 0.15 to 0.35 dB from 300 to 3500 Hz. Insertion loss is 2.7 dB  $\pm 0.4$  dB, and return loss is 25 dB minimum at 300 to 3500 Hz. Total harmonic distortion is 82 dB typical and 89 dB maximum at 600 Hz and -10 dBm. These transformers meet the telecommunications requirements of FCC Part 68. The TTC-103SL is for surface mounting with board cutout; the TTC-203SL is for surface mount; and the TTC-303SL has a through-hole mounting. The transformers cost \$3.52 (5000). **Tamura Corp of America**, Temecula, CA. (909) 699-1270. **Circle No. 431**

(continued on pg 123)



## Fast Async FIFOs



IDT offers a variety of high-speed 3.3V FIFOs, with configurations ranging from  $512 \times 9$  to  $8K \times 9$ , all operating as fast as 25ns! These FIFOs are ideal for achieving fast data throughput in high-performance 3.3V systems.

**Kit Code 0341**

## 32- and 64-bit RISC Microprocessors



IDT's family of RISC CPUs meet the price/performance needs of a full spectrum of applications. 3.3V offerings include the 32-bit RV3041™, RV3071™, and RV3081™ RISCControllers™, as well as the 64-bit 3.3V RV4400™ and RV4600™, RV4650™, and RV4700™ Orion™ CPUs.

**Kit Code 0341**

## High-Speed SRAMs and Modules



IDT is the only vendor to offer complete cache solutions for the highest-performance 3.3V systems. From the 15ns 3.3V IDT71V256  $32K \times 8$  SRAM to 3.3V Pentium™, chipset-specific 256KB and 512KB modules, IDT has what you need to enter the 3.3V world now!

**Kit Code 0341**

# Comin' At Ya!



## 3.3V Solutions from IDT

### High-Performance at 3.3V

IDT opens up a new world of opportunity by offering 3.3V devices with 5V performance and much lower power. Now you get the highest performance in a variety of 3.3V applications, such as PCs, notebook computers, PCMCIA cards, data communications, cellular phones, and handheld instruments.

### True 3.3V Technology

IDT's 3.3V products are built using a true 3.3V process technology that is in volume production now. This leadership technology provides much higher performance than recharacterized 5V ICs.

### We've Got What You Need

IDT has a full complement of high-performance 3.3V components on-hand, including **9 high-speed SRAMs and modules**, **65 octal and Double-Density FCT3 Logic devices**, **7 32-/64-bit RISC microprocessors**, **7 high-density dual-port memories**, and **5 fast asynchronous FIFOs** to meet your design and production needs.

**(800) 345-7015 • FAX: 408-492-8674**

**ASK FOR KIT CODE 0341**

FAX-On-Demand Document #0341

### 3.3V Devices Available Now


Contact us now and receive IDT's new **CD-ROM Data Book**, containing technical specs and application notes, and a 3.3V sample request form so you can start designing today!



**Integrated  
Device  
Technology, Inc.**
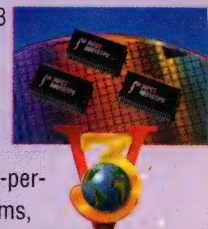
## Octal and Double-Density™ FCT3 Logic

IDT's 3.3V FCT3 Logic family includes all the 5V-equivalent functions needed to build high-performance systems, including Pentium-based PCs, and offers several speed grades from a single family to meet a range of price/performance requirements. One qual does it all.



**Kit Code 0341**

## Cost-Effective, High-Density Dual-Ports

IDT has cut the costs of dual port memories, giving designers viable alternatives to multiplexed SRAM implementations, and providing lower-cost-per-bit options for shared memory while maintaining high levels of performance.





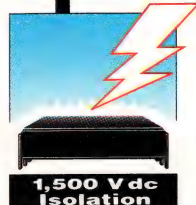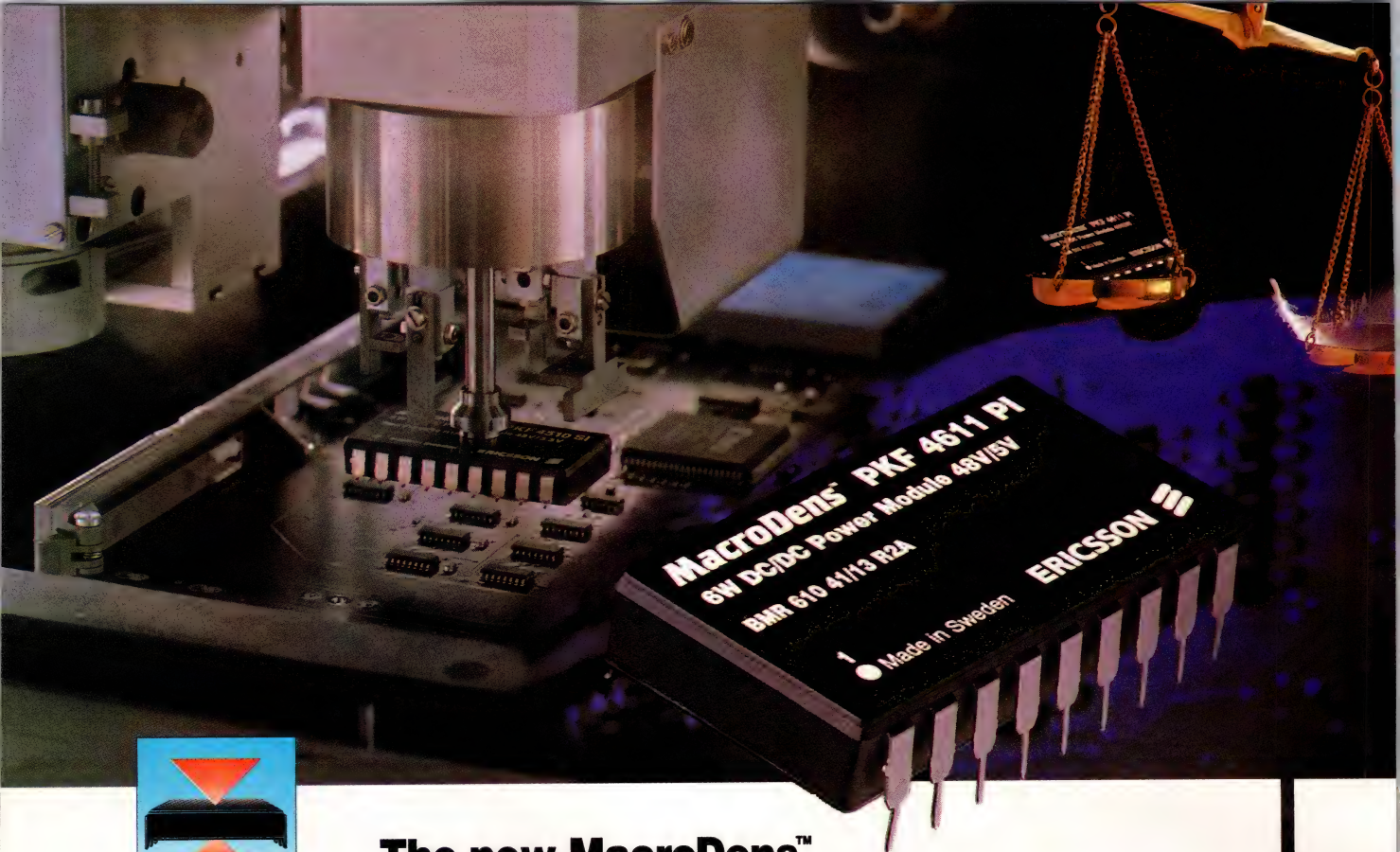**Kit Code 0341**

The IDT logo is a registered trademark and Double-Density, Orion, RV3041, RV3071, RV3081, RV4600, RV4650, RV4700, and RISCController are trademarks of Integrated Device Technology, Inc. All others are trademarks of their respective owner.







## The new MacroDens™ DC/DC converter. So small it's bound to make a big impression.

The latest in a long line of DC/DC converter innovations for distributed power from Ericsson, the MacroDens™ is unlike any other 3-7 watt device on the market. In a remarkably small 18-pin DIL package measuring just 48mm x 24mm x 8mm (1.89" x 0.94" x 0.31"), the different versions weigh only 15-20 grams (0.52 - 0.71oz). This makes it the first device of its type suitable for automatic placement. And there's a choice of through-hole or surface mount versions.

The size of the MacroDens™ does not limit its specification: 38 to 72 Vdc input range; a choice of 2, 3.3, 5 or 12 V outputs; and 1,500 Vdc isolation. And thanks to its optimized flyback circuitry, smart power chip, and highly integrated design, the MTBF is more than 400 years!

If you need more power, simply parallel MacroDens™ converters together. You don't even need load sharing components.

In short, the MacroDens™ is certainly the world's most advanced miniature DC/DC converter, so it's bound to make a big impression. Call us for the full specification.

Sweden	Stockholm, Tel: +46-8-721 6356 Fax: +46-8-721 7001
Brazil	Sao Bernardo do Campo, Tel: +55-11-759 6622 Fax: +55-11-759 5208
Denmark	København, Tel: +45-33 88 31 00 Fax: +45-33 88 31 05
Finland	Helsinki, Tel: +358-0-299 4189 Fax: +358-0-299 4188
France	Guyancourt, Tel: +33-1-30 64 85 00 Fax: +33-1-30 64 11 46
Germany	Düsseldorf, Tel: +49-211-534 0 Fax: +49-211-534 1514
Great Britain	Swindon, Tel: +44-1793-48 83 00 Fax: +44-1793-48 83 01
Hong Kong	Hong Kong, Tel: +852-2590 2388 Fax: +852-2590 7152
Italy	Milano, Tel: +39-2-55 21 26 16 Fax: +39-2-55 21 30 36
Norway	Oslo, Tel: +47-66 84 18 10 Fax: +47-66 84 19 09
Spain	Madrid, Tel: +34-1-339 2035 Fax: +34-1-339 3145
United States	Richardson, TX, Tel: +1-214-997-6561 Fax: +1-214-680-1059

**ERICSSON**






## LOW-PROFILE TRANSFORMERS HAVE HEIGHTS RANGING FROM 0.65 TO 1.375 IN.

Flathead low-profile transformers operate in the 2- to 48-VA range. The transformers feature 1500V rms HIPOT, Class B insulation (130°C), dual primaries (115/230V at 50/60 Hz), and series or parallel secondaries. They use semitoroidal construction to minimize radiated magnetic fields. Split-bobbin construction eliminates the need for an electrostatic shield. The transformers are recognized to UL 506, and they are CSA certified to C22.2. Prices range from \$5.08 to \$9.68 (100). **Signal Transformer Co Inc**, Inwood, NY. (516) 239-5777.

**Circle No. 432**
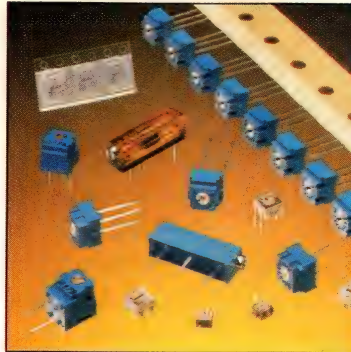
## SEALED CERMET TRIMMING POTENTIOMETERS.

The TR Series trimming potentiometers are sealed to withstand automated soldering and cleaning processes. The cermet resistive elements provide setting accuracy and



stability over a wide temperature range. Single-turn surface-mount models include the TR03 (3 mm square) and TR04 (4 mm square). In addition, 15 through-hole models are available with versions having single-turn, double-turn, and 12-turn operation. Resistance values range from 10Ω to 2 MΩ. Prices start at \$0.39 (1000).

**C&K Components Inc**, Watertown, MA. (617) 926-6400.

**Circle No. 433**

- ▶ RESISTORS
- ▶ CAPACITORS
- ▶ INDUCTORS

## POWER TOROIDAL INDUCTOR FOR DC/DC CONVERTERS.

The LPT-4545 provides high efficiency and low EMI radiation for dc/dc converter applications. The inductor has two separate windings, letting you connect them in series for higher inductance or in parallel for low dc resistance. The standard series includes 14 values ranging from 10 to 1200 μH. Current ratings range to 4A. The case measures 0.45 in. in diameter and 0.25 in. high. Typical price for a 10-μH device with a 4A current rating is \$2.20 (5000). **Dale Electronics Inc**, Yankton, SD. (605) 665-9301.

**Circle No. 434**

## SNUBBER CAPACITORS FOR IGBT MODULES.

The PMB Series capacitors feature mounting lugs that attach directly to the terminals of IGBT modules. In addition to ease of mounting, the new design also provides higher reliability in vibration- or shock-prone applications. The capacitors are constructed in a rectangular-box package and are available in ranges from 0.1 to 2.5 μF and voltage ratings from 850 to 2000W Vdc. \$3.50 (1000). **Illinois Capacitor Inc**, Lincolnwood, IL. (708) 675-1760.

**Circle No. 435**



(continued on pg 124)




- ▶ RESISTORS
- ▶ CAPACITORS
- ▶ INDUCTORS



### SURFACE-MOUNT TOROIDS.

KM Series toroids use molypermalloy powder cores, giving them a flat frequency response between 0 and 1 MHz. The toroids are designed for use as in-line noise filters in applications where the inductor must support 110 or 220V ac without core saturation. Inductances range from 10 to 250  $\mu$ H, and dc resistance is between 0.04 and 0.7 $\Omega$ . A 2A version can store 8  $\mu$ J, and a 0.25A version can store 20  $\mu$ J. The inductors have a 0.40 $\times$ 0.38-in. footprint and cost \$1.60 (1000). **Associated Components Technology**, Garden Grove, CA. (714) 636-2645.

**Circle No. 436**

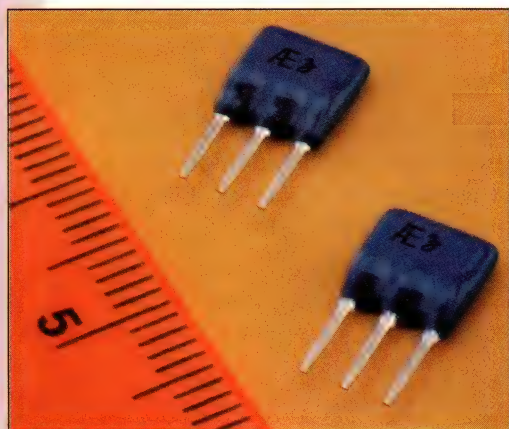

### TWO PRECISION RESISTORS IN THREE-TERMINAL NETWORK.

The SLD series resistor networks have a 0.25W power rating and values ranging from 50 $\Omega$  to 30 k $\Omega$ . Absolute-resistance tolerances range from 0.05 to 1%; matching tolerances range from 0.02 to 1%. The resistors' temperature coefficient of resistance equals 0.4 ppm/ $^{\circ}$ C with either  $\pm$ 2.5- or  $\pm$ 5-ppm tolerance. Temperature-coefficient tracking depends on the resistance ratio and ranges from  $\pm$ 0.5 ppm/ $^{\circ}$ C to  $\pm$ 3 ppm/ $^{\circ}$ C. A 1-k $\Omega$ /10-k $\Omega$  resistor combination with 0.4-ppm/ $^{\circ}$ C  $\pm$ 5-ppm tolerance costs \$4.15 (1000). **Isotek Corp**, Swansea, MA. (508) 673-2900.


**Circle No. 439**

### MAGNETIC MODULES FOR ATM 155-MBPS TRANSMISSION.

PE-6850X Series magnetic modules are designed for 155-Mbps transmission rates over data-grade unshielded-twisted-pair (UTP) copper wire. The new series also conforms to the proposed Fast Ethernet 100Base-TX standard and has been tested for interoperability with 100Base-TX hardware.

The modules are designed to minimize the inherent problems of electromagnetic interference (EMI) and noise susceptibility encountered in 100/155-Mbit transmission over UTP cable. The modules provide 1500V rms isolation, wide bandwidth, and rise times of 2.5 nsec. Single-channel modules cost \$3.28 (1000); dual-channel modules cost \$4.32 (1000). **Pulse Engineering Inc**, San Diego, CA. (619) 674-8100.

**Circle No. 437**

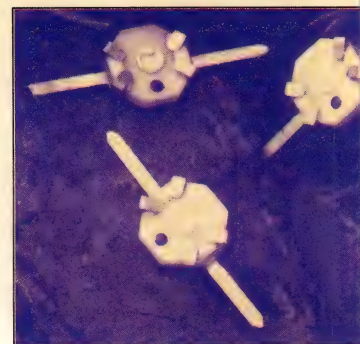

### 2-GHZ MINIATURE TRIMMER CAPACITORS.

The Series 9401 Thin-Trim capacitors have a capacitance range of 0.25 to 0.7 pF through 1.5 to 4.0 pF and a Q>100 at 2 GHz. The trimmer capacitors have an operating temperature range of  $-55$  to  $+125^{\circ}$ C and are rated for 250V dc. Capacitor dimensions are 0.140 in. long $\times$ 0.125 in. wide $\times$ 0.040 in. high. They cost \$1.02 (25,000). **Johanson Manufacturing Corp**, Boonton, NJ. (201) 334-2676.

**Circle No. 438**



New Titles in the **EDN** Series for Design Engineers

# Books that work the way you work

FREE  
Trial Offer!

The latest one-stop guide from this highly-respected author

## □ Simplified Design of Switching Power Supplies

John D. Lenk

An essential volume for students and experimenters as well as for design professionals, *Simplified Design of Switching Power Supplies* concentrates on the use of IC regulators, offering an all-inclusive, one-stop guide to switching power supply design. All popular forms of switching supplies are described in detail.

©1995 221 pp Hardcover 0-7506-9507-2 \$39.95



The second compilation of articles from EDN Magazine!

## □ EDN Designer's Companion

Edited by Bill Travis and Ian Hickman

This fully up-to-date collection of articles covers a broad variety of subjects, including analog and digital circuits, test and measurement, software and algorithms. Fully annotated, indexed, and cross-referenced!

©1994 254 pp Hardcover 0-7506-1721-7 \$29.95




Covers all popular forms of linear supplies in detail, including zener, three-terminal, feedback, current foldback, op-amp, series, shunt, and IC package

## □ Simplified Design of Linear Power Supplies

John D. Lenk

*Simplified Design of Linear Power Supplies* is an all-inclusive, one-stop guide to linear power supply design that enables even those with no previous design experience to use the techniques described. Includes design examples that can be put to immediate use as is, or modified to meet specific design goals.

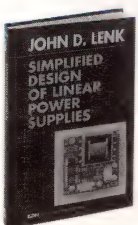©1994 218 pp Hardcover 0-7506-9506-4 \$34.95




Enables technicians or engineers to complete a complex schematic for a state-of-the-art power supply in less than one day

## □ Power Supply Cookbook

Marty Brown

Written to serve as a practical reference on power supplies during the design process, the *Power Supply Cookbook* provides easy-to-follow, step-by-step design procedures for every phase of power supply design. It offers common industry approaches along with relevant explanations that facilitate implementation. Many easily modified design examples are provided as design templates to help the reader.

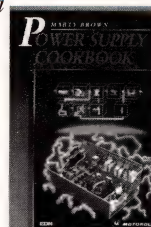©1994 248 pp Hardcover 0-7506-9442-4 \$39.95



Emphasizes today's modular approach to analog circuit design using low-cost integrated circuits


## □ Operational Amplifier Circuits

### Analysis and Design

John C.C. Nelson

This book, a revised and updated version of the author's *Basic Operational Amplifiers* (Butterworths 1986), enables the non-specialist to make effective use of readily available integrated circuit operational amplifiers for a range of applications, including instrumentation, signal generation and processing (it is assumed the reader has a background in the basic techniques of circuit analysis).

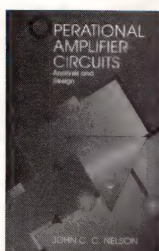©1995 175 pp Paperback 0-7506-9468-8 \$22.95



For Faster Service, call Toll Free 1-800-366-2665  
or 617-928-2500 (outside U.S. and Canada)  
M-F, 8:00-6:00 EST

### FREE trial offer, with 3 easy ways to order in the U.S.!

□ **YES!** Please send me the book(s) indicated for a FREE 30-day examination. After 30 days, if I decide to keep the book(s), I will honor your invoice for the price of the book(s) plus applicable sales tax and handling. Otherwise I will return the book(s) and owe nothing.

1. **CALL** toll-free 1-800-366-2665 weekdays between 8:00 and 6:00 EST
2. **MAIL** Check the title(s) you want, provide the information requested below, and mail this page to Butterworth-Heinemann, 225 Wildwood Ave., Woburn, MA 01801
3. **FAX** Provide the information requested below and fax this page to (800) 446-6520 (Fax anytime, 24 hours a day)

- Simplified Design of Switching Power Supplies/Lenk (0-7506-9507-2)
- Simplified Design of Linear Power Supplies/Lenk (0-7506-9506-4)
- Operational Amplifier Circuits/Nelson (0-7506-9468-8)
- EDN Designer's Companion/Travis & Hickman (0-7506-1721-7)
- Power Supply Cookbook/Brown (0-7506-9442-4)

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Tel: \_\_\_\_\_  
Signature \_\_\_\_\_

TS105

European orders must be prepaid with a credit card and specify preferred shipping. All others will ship via surface mail.

**B**UTTERWORTH  
**H**EINEMANN

225 Wildwood Avenue  
Woburn, MA 01801

Prices subject to change.




# *Our Power Module is Dual... theirs is only single output!*
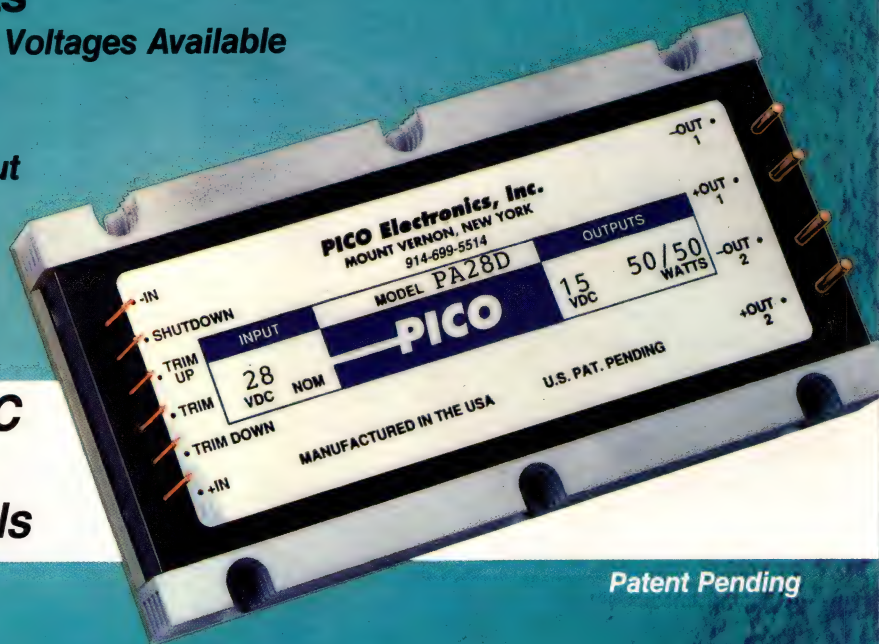
## **Now—75, 100 and 200 Watt Models**

- **Low Cost DC-DC Converters**  
*Single Outputs \$104 / Dual Outputs \$149*
- **Dual Isolated Outputs**  
*28 Standard Models / Special Voltages Available*
- **Wide Input Voltage**  
*Four Series / 18-380 VDC Input*
- **Parallel Operation**  
*Fixed Frequency 100kHz  
True Redundancy Operation*

**New 3.3 VDC to 100 VDC  
standard in Industrial,  
COTS and Military Models**



**Patent Pending**

The availability of DUAL ISOLATED OUTPUTS creates cost and space savings in many applications.

Fully safeguarded for over voltage, over temperature and continuous short circuit protection, these FIXED Hi-Frequency units minimize technical problems.

With output voltages from 3.3VDC to 100VDC, four distinct input ranges and the choice of single or dual outputs plus the capability of Parallel Operation, as standard features, your circuit designs can be optimized.

Assembled in the U.S.A. with PICO quality components, these hi density units allow the most stringent mechanical, electrical and environmental requirements.

FAX or call today for immediate engineering assistance, product information or FREE catalog.

# **PICO Electronics, Inc.**

453 N. MacQuesten Pkwy., Mt. Vernon, N.Y. 10552

**Call Toll Free**

# **800-431-1064**


**in New York Phone 914-699-5514  
FAX 914-699-5565**



**FREE INFO, FREE POSTAGE**

Use our postage-paid reader-service cards to get more information on any of these products.

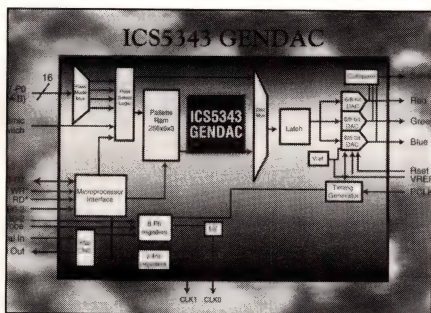**Memories for military and high-reliability applications offer SRAM, flash, and EEPROM versions.** The family of 128k×32-bit memories is available in 68-pin J-lead packages. The EDI8C32128 SRAM is available with access times from 20 to 55 nsec. A low-power version provides data retention at 2V. The devices start at \$652 (100). The EDI7C32128 flash memory comes with access times of 120 to 200 nsec; prices start at \$652 (100). The EDI5C32128 EEPROM device offers 120- to 200-nsec access times and costs \$2002 (1000). Electronic Designs Inc, Westborough, MA. (508) 366-5151. **Circle No. 328**



**Integrated RAMDAC and programmable video-timing generator support 1600×1200-pixel resolution.** The ICS5343 operates at pixel speeds to 170 MHz and supports a standard 16-bit pixel port that is compatible with most DRAM-based graphics controllers. The chip has a 256×six-color look-up-table palate RAM, a programmable-pixel clock-timing generator, and a programmable-memory clock-timing generator. The device comes in a 68-pin PLCC and costs \$6.50 (10,000). Integrated Circuit Systems Inc, San Jose, CA. (408) 297-1201. **Circle No. 329**

**PCMCIA controller chip for PCI bus supports two PCMCIA slots.** The M5235 PCMCIA controller chip meets PCMCIA 2.1 and JEIDA 4.0 specifications. It works with 3.3 and 5V PC cards. The device comes in 208-pin TQFPs and PQFPs and costs \$10.50. Acer Laboratories Inc, Pacific Technology Group, Santa Clara, CA. (408) 764-0644. **Circle No. 330**

**Flash-memory cards have up to 20-Mbyte capacity.** The D-Series flash-memory cards are PCMCIA Type I cards operating from a 5V supply. The cards have a low-power standby mode that requires <1 mA. Memory is organized into 64-kbyte sectors, each with a guaranteed minimum of 100,000 write/erase cycles. The 4-Mbyte AmC004-DFLKA costs \$131 (1000), the 8-Mbyte AmC008DFLKA costs \$219 (1000), and

the 20-Mbyte Am020DFLKA costs \$494 (1000). Advanced Micro Devices Inc, Sunnyvale, CA. (408) 749-5703.


**Circle No. 331**

**256k×16-bit DRAM has 50-nsec row-address-strobe access time and 22-nsec EDO page-mode cycle time.** The 4-Mbit V53C16258H extended-data-out (EDO) suits applica-

HCMOS/TTL & Sinewave • Surface Mount & Thru-Hole

# WE'VE GOT A LOT TO SAY ABOUT TCXOs...

# BUT THIS AD HAS LIMITED BANDWIDTH.

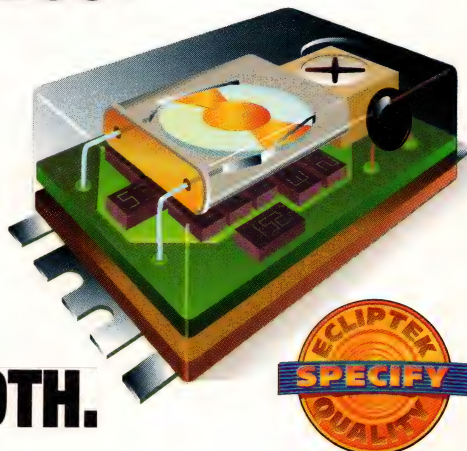

When it comes to TCXOs, you've got more options now than ever before. Logic. Packaging. Frequency stability. Temperature range.

We'd like to tell you everything you need to know, but there's not enough room here. Design specs. Quality stats. Availability. Pricing. You've got questions. We've got answers. If you're wired to the Internet, come visit our web site or **e-mail any questions to [ecliptek-sales@ecliptek.com](mailto:ecliptek-sales@ecliptek.com)**

If you like the human touch, our customer support team has all the bandwidth you'll ever need. They're knowledgeable, responsive, flexible and reliable. Committed to making Ecliptek your TCXO supplier.

**Dial 1-800-ECLIPTEK for accurate answers,** guaranteed quality and on-time delivery. Data sheets available 24-hours by fax-on-demand.



1-800-ECLIPTEK • (714) 433-1200 • (714) 433-1234 Fax

<http://www.ecliptek.com/ecliptek/>



## books that work the way you work

*Specific design examples of circuits!*

### Radio Frequency Transistors:

#### Principles and Practical Applications

**Norman E. Dye and Helge O. Granberg,**  
**Motorola**

Written by two experienced RF design engineers, this new book discusses the selection of solid state devices for specific applications. For the most part, it is devoted to specific design examples of circuits.  
Sept. 1992 288pp. cloth 0 7506 9059 3 \$39.95 (£40.00)

*Achieve acceptable EMC performance at minimal cost!*

### EMC for Product Designers

**Tim Williams**

Electromagnetic compatibility is becoming increasingly important in the design of electronic products. In the absence of comprehensive U.S. standards, the Europeans are leading the way in this field. This book examines the European Commission's standards on EMC and, most importantly, outlines how EMC design principles need to be incorporated from the beginning to avoid cost and performance penalties.

October 1992 272pp cloth 0750612649 \$42.95 (£24.95 paper)

*Loaded with practical information*

### Rechargeable Batteries Applications Handbook

**Technical Staff, Gates Energy Products**

In order to obtain the best performance from rechargeable batteries, it is essential that they be applied correctly. This is a comprehensive reference on proper selection, specification and application guidelines from one of the world's largest sealed-cell manufacturers.

May 1992 290pp. cloth 0 7506 9227 8 \$49.95 (£38.50)

In the U.S.



**1-800-366-2665**



M-F 8:30-4:30 E.T.

**Fax 617-438-1479**

**BUTTERWORTH-HEINEMANN**

80 Montvale Ave., Stoneham, MA 02180

**The EDN Series  
for Design Engineers**

*In the U.K. and Europe, order from:*

**REED BOOK SERVICES LTD.**

Special Sales Department

P.O. Box 5 Rushden, Northants NN10 9YZ U.K.

*To order by phone:*

TEL. 0933 58521 FAX 0933 50284 **SS018**

CAHNS 12.89

**EDN**

**INTEGRATED CIRCUITS**

tions such as graphics accelerators, set-top boxes, disk drives, laser printers, and communications buffers. The memory comes in a 40-pin SOJ package and costs \$22 (10,000). **Mosel Vitelic**, San Jose, CA. (408) 433-6000. **Circle No. 332**


**Dual-channel, 14-bit, correlated-double-sampling, CCD analog processor.** The ET4265 provides 14-bit resolution at throughput rates to 2 MHz. The device has 0.3-LSB-rms noise, an 84-dB dynamic range, and a  $\pm 0.5$  LSB differential nonlinearity. Power consumption is 2.8W for the  $2.5 \times 2.5 \times 0.4$ -in. module. The ET4265 costs \$694 (100), and the ET426501, with a digitally controlled dark-current offset, costs \$796 (100). **Edge Technology Inc**, Waltham, MA. (617) 899-7900. **Circle No. 333**

**4-Mbit flash memory available with 55-nsec access time.** The Am29F040 is organized as  $512k \times 8$  bits. The memory is divided into 64-kbyte sectors and is in-system programmable from a 5V supply. The device features the company's Embedded Program and Embedded Erase algorithms to simplify flash operations and free the host CPU from dedicated control of the device. The company guarantees the device for a minimum of 100,000 program/erase cycles. Available in 32-pin TSOP, PLCC/LCC, and DIP packages, the device costs \$18 (1000). **Advanced Micro Devices Inc**, Sunnyvale, CA. (408) 749-5703.

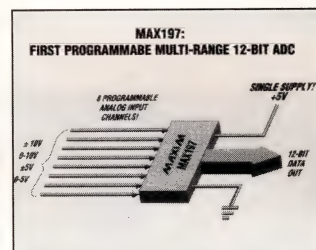**Circle No. 334**

**64-kbit parallel EEPROM has access times down to 100 nsec.** The M28C64 has a page-write feature that lets you latch 64 consecutive bytes into memory and then program all 64 locations in

one 2-msec program cycle. Organized as an  $8k \times 8$ -bit device, the memory has a write/erase endurance of at least 100,000 cycles. The device features standard JEDEC byte-wide pinouts and has a minimum data retention of 10 years. Operating from a single 5V supply, the device draws 30-mA current while active and 100  $\mu$ A in standby mode. It is available in 28-pin DIP, TSOP, SO28, and 32-lead PLCC packages. It costs \$3.80 (10,000). **SGS-Thomson Microelectronics**, Lincoln, MA. (617) 259-0300. **Circle No. 335**



**12-bit, 100k-sample/sec ADC has eight input channels with software-programmable ranges.** The MAX197's eight input channels are independently software programmable to accept 0 to 5, 0 to 10,  $\pm 5$ , and  $\pm 10$ V signals. The device operates from a 5V supply and tolerates  $\pm 16.5$ V on any input channel without affecting the conversion results on other channels. The overvoltage tolerance makes the device suitable for interfacing to  $\pm 15$ V-powered sensors without additional circuit protection. A byte-wide digital output provides data in an 8+4-bit format. The converter includes a 5-MHz bandwidth track/hold amplifier. The device uses an internal 4.096V reference or an external reference. The device comes in a 28-pin DIP, SO, and SSOP packages, and prices start at \$9.90 (1000). **Maxim Integrated Products**, Sunnyvale, CA. (408) 737-7600, ext 6087. **Circle No. 336**



# Lower Dropout Rating Gets Semtech an EZ 'A'

**Power your Pentium® Processor and other low voltage microprocessor applications knowing that Semtech's designers have done their homework!**

■ **First**, Semtech introduced the EZ1083/4/5/6 family of low dropout linear regulators with 1.3V maximum dropout voltage and outstanding transient response at an economical price.

■ **Then**, Semtech offered the EZ1584/5/7 family also with guaranteed 1.3V maximum dropout voltage, even at full load current.

■ **Now**, Semtech offers the 'A' versions of the EZ108x and EZ158x families— 1.2V maximum dropout at full load current, suitable for powering even the VRE version of the Pentium Processor.

CIRCLE NO. 11

LT is a registered trademark of Linear Technology.  
Pentium is a registered trademark of Intel Corporation.

**FAX BACK TO: 805.498.3804 SEMTECH, CA**

- ☐ Yes, please send more information about Semtech's "EZ" Low Dropout regulators.  
☐ Please send me a quotation on: \_\_\_\_\_

DATE \_\_\_\_\_  
FROM \_\_\_\_\_  
COMPANY \_\_\_\_\_  
TITLE \_\_\_\_\_  
PHONE \_\_\_\_\_  
FAX \_\_\_\_\_

ADDRESS \_\_\_\_\_  
M/S \_\_\_\_\_  
CITY \_\_\_\_\_  
STATE \_\_\_\_\_  
ZIP \_\_\_\_\_  
APPLICATION \_\_\_\_\_

**TEL: 805.498.2111**  
**e-mail: NPSMTCHAD@AOL.COM**

**SEMTECH**




# GET TOUGH


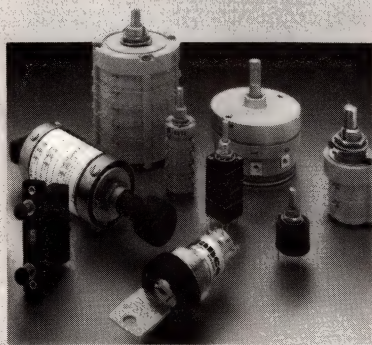
## MIL Spec QPL Rotary Switches & Switching Systems

Reliability... in even the toughest environments. It's why the world's military, aviation and aerospace contractors rely extensively on Janco switching technology to keep their programs flying high and trouble free. To put all the reliability of rotary to work for you—contact Janco today to discuss your application and for your free Engineering and Selector Guide.



# Janco

3111 Winona Avenue, Burbank, CA 91504.  
Phone: (818) 846-1800.

CIRCLE NO. 29

EDN

INTEGRATED CIRCUITS

### Video encoder converts RGB into luminance, chrominance, and composite video.

The AD722 video encoder generates National TV Systems Committee or phase-alternation-line standard video from red, green, and blue color-component signals. The device's composite- and S-video outputs have a typical differential gain of 0.1% and a typical differential phase of 0.1°. The device accepts a frequency subcarrier (FSC) or a 4FSC clock. When a clock is not available, the chip's internal oscillator and an external FSC crystal can create the FSC. The device also accepts the FSC clock from an external video source providing phase-locking, as required in Genlock applications. Operating from a single 5V supply, the device drives 75Ω reverse-terminated loads. The 16-pin SOIC costs \$3.55 (10,000). **Analog Devices Inc.**, Wilmington, MA. (617) 937-1428.

Circle No. 337

### High-speed coil drivers integrate logic, MOSFETs, and MOSFET drivers on single IC.

The EL7240C and EL7241 coil driver ICs have a 20-nsec propagation delay and a 2A pk drive current. The drivers have a 3Ω output impedance and operate at 4.5 to 16V. They are compatible with 3 and 5V logic inputs. The devices operate as coil drivers for computer-tape-drive-backup systems, but they are also useful for other applications requiring high-speed and high-current drive capabilities. Prices for the devices start at \$1.90 (1000). **Elantec Inc.**, Milpitas, CA. (408) 945-1323.

Circle No. 338

### Two-port isolated amplifier has instrumentation amplifier inputs.


The ISO213 is intended for applications with low signal levels needing galvanic isolation. It has a ±10 input-signal range, ±40V input-overvoltage protection, and a 0.5 to 5000 gain range. The device operates from a 12 to 15V supply and dissipates 45 mW. It is rated for continuous operation at 1500 or 2500V rms pulsed, and has nonlinearity specifications compatible with 12-bit conversion systems. The device comes in a low-profile, 38-pin ZIP package and costs \$29.65 (100). **Burr-Brown Corp.**, Tucson, AZ. (602) 746-1111.

Circle No. 339

### Low-cost isolation amplifiers are rated for 500V-rms input isolation.

The AD104 and AD102 use transformer-coupled galvanic isolation and have 100-dB common-mode rejection. The AD102 is a stand-alone device with 1.5-kHz, full-power bandwidth. It operates from a 15V supply and dissipates 75 mW. The AD104 for multichannel systems requiring input-to-input isolation has a 4-kHz bandwidth and requires a 25-kHz, 15V square-wave clock source. Both devices come in SIP-style packages measuring 2.08×0.26×0.625 in. The AD104 costs \$20.55 (1000), and the AD102 costs \$22 (1000). **Analog Devices Inc.**, Wilmington, MA. (617) 937-1428.

Circle No. 340

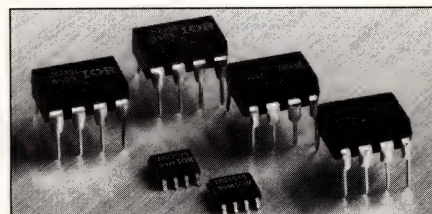

### Low-cost control ICs for driving power MOSFETs and insulated-gate bipolar transistors.

A family of eight 600V control ICs for specific applications costs \$1.20 for samples and \$0.75 for production volumes. For motor control, the IR2101 provides a high- and low-side drive. The IR2102 also provides a high- and low-side drive with inverted inputs. For power supplies, the IR2103 provides a high- and low-side drive with dead time and one inverted input. The IR2104 half-bridge driver has dead time and shutdown. For single-channel driver applications not requiring both high- and low-side drives, the IR2117 has a noninverted input, and the IR2118 has an inverted input. For electronic ballast, the IR2151 provides a self-oscillating half-bridge driver, and the IR2152 provides a self-oscillating half-bridge driver with inverted output phase. **International Rectifier Corp.**, El Segundo, CA. (310) 322-3331.

Circle No. 341

### Power-supply chip for switching power supplies of >1000W.

The ML4822 first-stage power-factor-correction chip converts ac-line voltages of 85 to 265V into a steady 400V regulated output with a power factor >0.99. The chip uses an active snubbing cir-



# 16-Bit

# 2-MHz

## Hybrid Sampling A/D Converter


### Only from Analogic... Who else?

Analogic takes precision high-performance technology to a *new level!* In addition to high speed and high resolution, the ADC4322, which is available *today*, features:

- Low power
- Low noise
- Low harmonic distortion
- Hermetic environment
- Small size
- High reliability

Call us today at **1-800-446-8936** to find out how you can take your application to a new level of performance... at surprisingly attractive OEM prices.

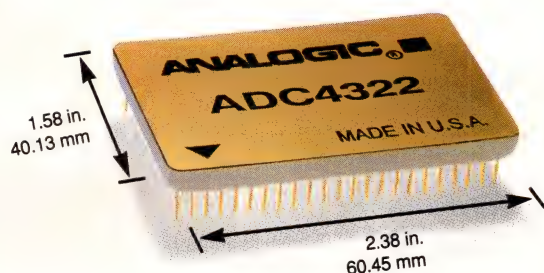Analogic Corporation, 360 Audubon Road, Wakefield, MA 01880  
1 (800) 446-8936, FAX: (617) 245-1274




**ANALOGIC** ■

*The World Resource  
for Precision Signal Technology*

CIRCLE NO. 212

133



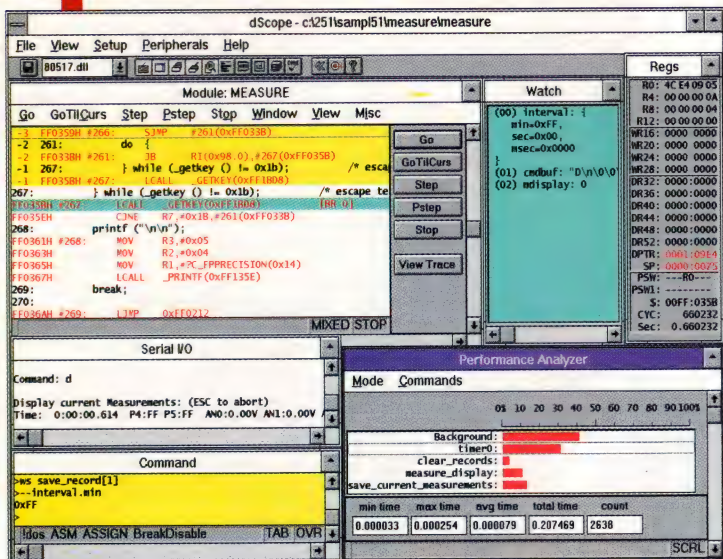


dScope-251: Windows™ based 8051 & 251 debugger

# C51 Version 5

## The best 8051 C compiler just got better...

- ✓ Compatible with the new Intel MCS® 251 architecture
- ✓ Faster 32-bit long and floating-point math operations
- ✓ MS Windows™ based development tools
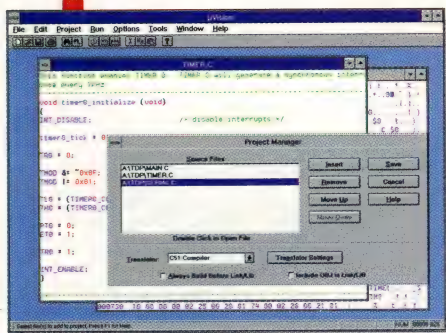
## ...and creating 8051 & 251 software has never been easier.




µVision/251 Windows™ IDE

The Keil C51 compiler, with over 15,000 installations worldwide, is the industry de-facto standard for 8051 software development. C51 is unsurpassed in code quality and flexibility and it supports all 8051 derivatives including the Dallas Semiconductor 80c320, the Siemens 80c517, and the Philips 80c751 family.

To better support our customers in the United States and Canada, **Keil Software, Inc.** has opened a new sales and support office in Dallas, Texas. Previously, the Keil 8051 development tools were marketed under the Franklin brand name. Now, customers can get upgrades and technical support directly from Keil Software.

## Whetstone Benchmark Results

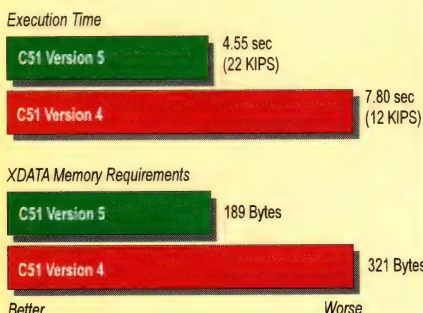

Call for complete benchmarks

## C51 Benchmark Comparison

## Call today for more information!

**USA & Canada:**  
Keil Software, Inc.  
16990 Dallas Parkway, Suite 120  
Dallas, Texas 75248  
Phone: (214) 735-8052  
Fax: (214) 735-8055

In the USA call  
**800-348-8051**

**Europe:**  
Keil Elektronik GmbH  
Bretonischer Ring 15  
85630 Grasbrunn - Germany  
Phone: ++49 89 / 46 50 57  
Fax: ++49 89 / 46 81 62

**US Distributors:** Franklin, Nohau, MetaLink, Hitex, Emulation Technology

**International Distributors:** Australia: Electro Optics 02/654 1873 A: Rekirsch 01/2597 2700  
B: Bytcom 010/223 455 Czech Rep: ComAp 2/684 8862 CH: Redacom 032/410 111, Thau 01/740 4105  
DK: Nohau 043/446 010 E: CAPEL 93/217 2340 F: Convergie 1/4904 9200 I: BRM 011/437 1551, NORD 02/6610 4160  
IRL: Ashling 061/33 44 66 Israel: ITEC 03/491 202 NL: Tritex 01858/16133 PL: WG 022/217 704  
S: Nohau 040/922 425 Singapore: Testtech 65/7492162 SLO: ASYST 061/445526 South Africa: Eagle (021) 23 4943  
Taiwan: Demmax 35/77272 Turkey: EMPA 1/599 3050 UK: Hitex 01203/692 066, Nohau 01962/733140


MCS® 251 is a registered trademark of Intel Corporation. MS Windows™ is a trademark of Microsoft Corporation.





## LINEAR SOLUTIONS DATA CONVERSION
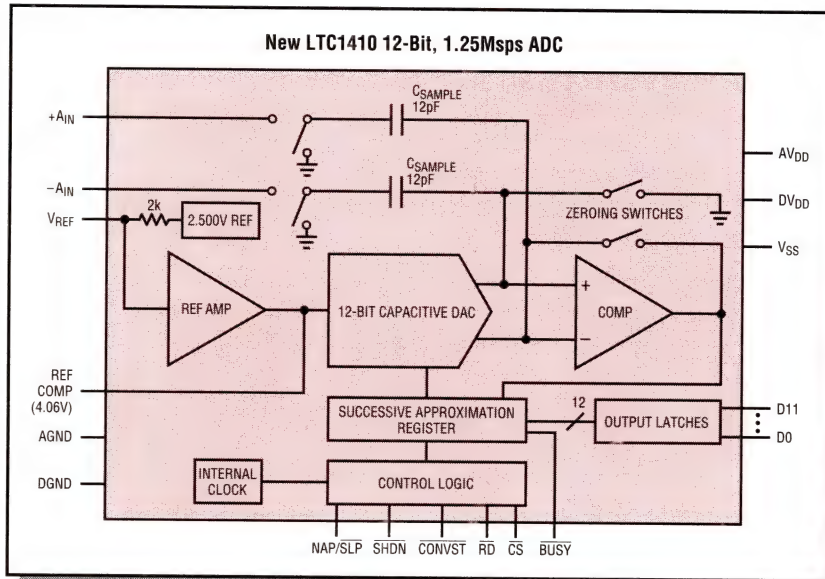
### LTC1410 Breaks 12-Bit, 1Mps Barrier with 71dB SINAD at Nyquist!



The LTC1410 is a 12-bit, 1.25Mps, sampling ADC designed for demanding telecom and signal analysis applications. It delivers true 12-bit performance from DC to Nyquist at unprecedented low cost and power dissipation.

Key features are:

- 1.25Mps throughput
- 71dB S/(N+D) at Nyquist
- 160mW typical power dissipation, 12mW nap mode, 100μW sleep mode
- Complete, sampling ADC
- True differential inputs reject common-mode noise

The LTC1410 contains a wideband sample-and-hold, precision voltage reference and

high speed, parallel interface to DSP and microprocessor ports. Two digitally selectable power-down modes allow optimal power saving and response time for low power systems. A unique differential input can acquire single-ended or differential signals while rejecting wideband, common-mode noise. Packaged in 28-pin SO the LTC1410 is available screened to the commercial and extended industrial temperature ranges. Pricing begins at \$23.00 in 1000-piece quantities.


Circle No. 102: Please send literature.

Circle No. 103: Call me. I'm interested.
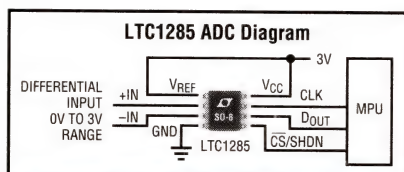
### Tiny 3V, 12-Bit ADCs Draw 160μA and Shut Down to 1nA


The LTC1285/LTC1288 are tiny 12-bit ADCs designed to operate on 3V supplies. They draw only 160μA of supply current and automatically power down to 1nA between conversions. Packaged in 8-pin DIP and SO the LTC1285/LTC1288 pricing begins at \$6.22 in 1000s, perfect for space and power sensitive applications such as pen screen interface, remote data acquisition and battery monitoring.

The LTC1285 features a differential input while the LTC1288 input is 2-channel multiplexed. Both devices have 3-wire serial I/O compatible with the SPI and Microwire™ interface standards and easily accommodate isolated applications. The LTC1285 is offered screened to the extended industrial temperature range.



Circle No. 104: Please send literature.

Circle No. 105: Call me. I'm interested.

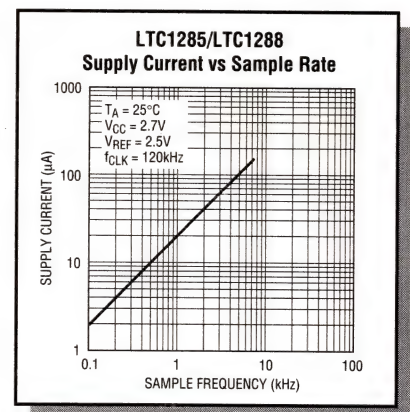




## Complete 12-Bit ADC Operates on Single 5V Supply at 500KSPS

The LTC1278 is a 12-bit, 500ksps ADC perfect for demanding low power applications such as telecom, vibration analysis and portable DSP.


Outstanding performance includes:

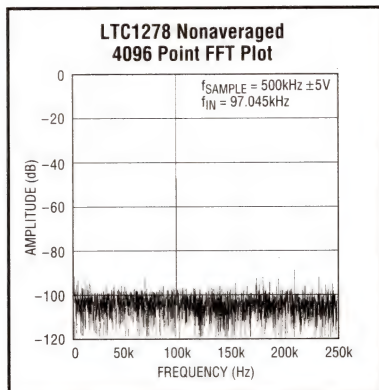- 400ksps (LTC1278-4) and 500ksps (LTC1278-5) throughput
- 70dB S/(N+D) at Nyquist
- 75mW power dissipation and 8.5mW power shutdown
- Complete ADC in small footprint
- Single 5V or  $\pm 5V$  supply



The LTC1278 contains a sample-and-hold, synchronized conversion clock, precision voltage reference and high speed, parallel interface to DSP and microprocessor ports.

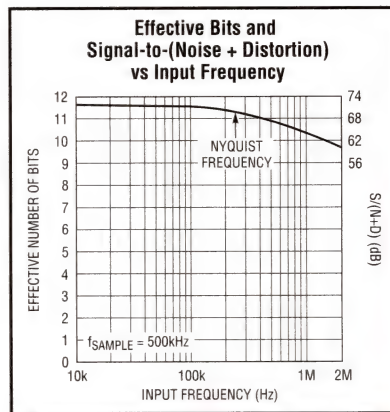The ADC features a 8.5mW power-down mode with instant wake-up for maximizing power savings. Input range is 0V to 5V on a single 5V supply and  $\pm 2.5V$  with  $\pm 5V$  supplies. For applications requiring additional throughput the LTC1279 provides a pin compatible 600ksps ADC. Pricing begins at \$12.00 in 1000-piece quantities.




Circle No. 106: Please send literature.

Circle No. 107: Call me. I'm interested.
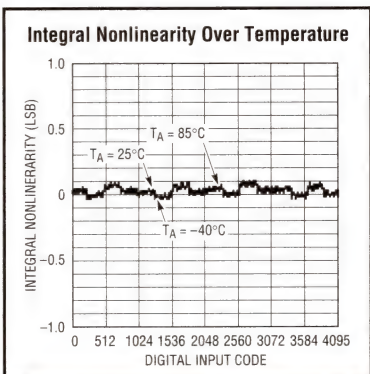
## Serial 4-Quadrant Multiplying 12-Bit DAC Available in SO-8

The LTC8043 is a serial input 12-bit multiplying DAC that is a superior pin compatible replacement for the DAC-8043.


Improvements include better accuracy, better stability over temperature and supply variations, lower sensitivity to output amplifier offset, tighter timing specifications and lower output capacitance.



Outstanding specifications include :

- Maximum DNL and INL over temperature  $\pm 0.5LSB$
- $\pm 1LSB$  maximum gain error
- 5 ppm/ $^\circ C$  maximum gain temperature coefficient
- Total Harmonic Distortion (THD): 108dB typical

The LTC8043 is extremely versatile. It can be used in a variety of 2- and 4-quadrant applications such as: programmable gain amps, digitally controlled filters and power supplies, process control and industrial automation. Packaged in 8-pin DIP or SO, the LTC8043 is available screened to the extended industrial temperature range of  $-40^\circ C$  to  $85^\circ C$ . Pricing begins at \$4.80 in 1000s.

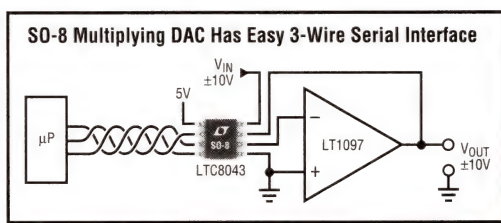


Circle No. 108: Please send literature.

Circle No. 109: Call me. I'm interested.


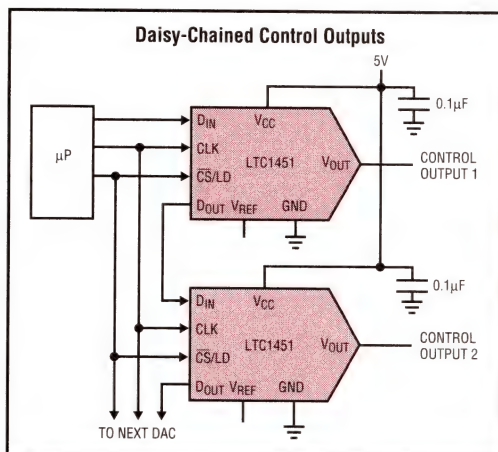
## Complete Voltage Output 12-Bit DACs Have Rail-to-Rail Swing in SO-8




The LTC1451/LTC1452/LTC1453 are micropower rail-to-rail voltage output 12-bit DACs in 8-pin DIP and SO. The devices have an easy-to-use, 3-wire serial interface that is cascadable, allowing multiple DACs on a single data I/O line.

Key features are:

- Single 3V or 5V supply
- Built-in reference: 2.048V (LTC1451), 1.220V (LTC1453)
- Multiplying version: LTC1452
- Power-on reset
- Maximum DNL  $< \pm 0.5\text{LSB}$

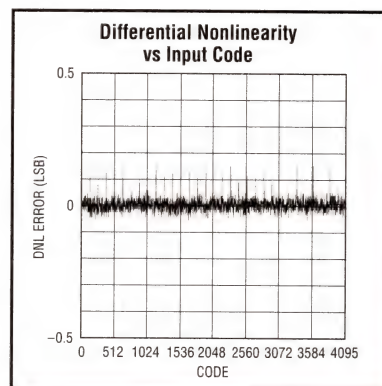The devices dissipate only 2mW on 5V supply and 750 $\mu$ W from 3V, making them ideal for



low power designs including: cellular telephony, POS systems, industrial process controls, wireless communications and general trim-pot applications. The output range includes both rails with improved capacitive load handling capability over competing solutions. Available screened to the commercial and industrial temperature ranges. Pricing begins at \$4.20 in 1000-piece quantities.

Circle No. 110: Please send literature.

Circle No. 111: Call me. I'm interested.



## Unique, Data Acquisition Device Provides a Variety of Environmental Monitoring Functions

The LTC1392 is a micropower, 10-bit data acquisition system designed to measure ambient temperature, on-chip supply voltage and differential common-mode rail-to-rail input signals. The device accomplishes these functions in a single SO-8 package and dissipates less than 2.5mW.

The LTC1392 features:

- 10-bit sampling ADC
- High accuracy bandgap reference
- 3-wire half-duplex serial interface
- On-chip temperature sensor
- A 3-channel multiplexer
- Rail-to-rail common-mode input

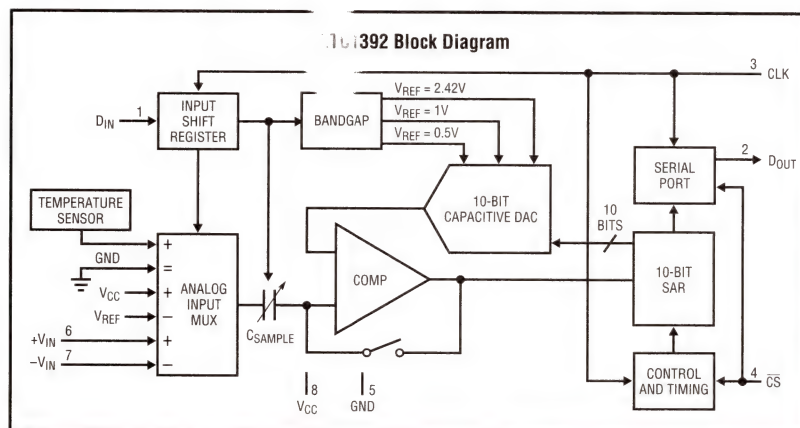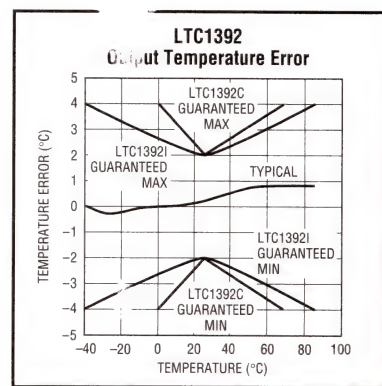The LTC1392 is suited for a wide variety of environmental monitoring applications including: power distribution systems, temperature measurement, airflow, relative humidity, pressure and weight measurement.



The LTC1392 is available screened to the commercial and industrial temperature ranges. Pricing begins at \$3.94 in 1000-piece quantities.

Circle No. 112: Please send literature.

Circle No. 113: Call me, I'm interested.



## Sampling A/D Converters

Part	Resolution (Bits)	F <sub>SAMPLE</sub> (ksps Max)	# of Inputs	V <sub>REF</sub>	Data* I/O	V <sub>CC</sub> (V)	P <sub>DISS</sub> ** (mW)	Features	Package†
LTC1096	8	33	1	Ext	Serial	2.7-9	0.6/0	Micropower SO-8 ADC	N8/S8
LTC1098	8	33	2	Ext	Serial	2.7-6	0.6/0	2-Channel LTC1096	N8/S8
LTC1196	8	1000	1	Ext	Serial	2.7-6	55	1Msps SO-8 ADC	N8/S8
LTC1198	8	750	2	Ext	Serial	2.7-6	55/0	2-Channel LTC1196	N8/S8
LTC1090	10	30	8	Ext	Serial	4-9	5	Low Power Multiplexed ADC	N20/S20
LTC1091	10	31	2	Ext	Serial	4-9	7.5	8-Pin 2-Channel ADC	N8
LTC1092	10	38	1	Ext	Serial	4-9	5	8-Pin 10-Bit ADC	N8
LTC1093	10	26	6	Ext	Serial	4-9	5	Low Power Multiplexed ADC	N16/S16
LTC1094	10	26	8	Ext	Serial	4-9	5	Low Power Multiplexed ADC	N20
LTC1095	10	26	6	+5.0	Serial	4-9	15	Complete 6-Channel ADC	N18
LTC1283	10	15	8	Ext	Serial	3-3.6	0.45	3V LTC1090	N20
LTC1285	12	7.5	1	Ext	Serial	2.7-6	0.48/0	3V LTC1286	N8/S8
LTC1286	12	12.5	1	Ext	Serial	4-9	1.25/0	Micropower SO-8 12-Bit ADC	N8/S8
LTC1288	12	6.6	2	Ext	Serial	2.7-6	0.63/0	3V LTC1298	N8/S8
LTC1298	12	11.1	2	Ext	Serial	4-6	1.25/0	2-Channel LTC1286	N8/S8
LTC1290	12	50	8	Ext	Serial	4-6	30/0.05	8-Channel ADC	N20/S20
LTC1291	12	54	2	Ext	Serial	4-6	30/0.05	8-Pin 2-Channel ADC	N8
LTC1292	12	60	1	Ext	Serial	4-6	30	8-Pin 12-Bit ADC	N8
LTC1293	12	46	6	Ext	Serial	4-6	30/0.05	6-Channel ADC	N16
LTC1294	12	46	8	Ext	Serial	4-6	30/0.05	8-Channel ADC	N20/S20
LTC1296	12	46	8	Ext	Serial	4-6	30/0.05	LTC1294 w/Shutdown Output	N20/S20
LTC1297	12	50	1	Ext	Serial	4-6	30/0.05	LTC1292 w/Auto-Shutdown	N8
LTC1287	12	30	1	Ext	Serial	2.7-6	3	3V LTC1292	N8
LTC1289	12	25	8	Ext	Serial	2.7-6	3/0.03	3V LTC1290	N20/S20
LTC1272-8	12	100	1	2.42	μP 8 or 12	+5	75	Sampling AD7572-12	N24/S24
LTC1272-3	12	250	1	2.42	μP 8 or 12	+5	75	Sampling AD7572 A-3	N24/S24
LTC1273	12	300	1	2.42	μP 8 or 12	+5	75	5V High Speed ADC w/Ref	N24/S24
LTC1274	12	150	1	2.42	12	5/±5	15/0.005	Low Power Sampling ADC w/Shutdown	S24
LTC1275	12	300	1	2.42	μP 8 or 12	±5	75	High Speed ADC w/Ref	N24/S24
LTC1276	12	300	1	2.42	μP 8 or 12	±5	75	High Speed ADC w/Ref	N24/S24
LTC1277	12	150	1	2.42	μP 8	5/±5	15/0.005	Low Power Sampling ADC w/Shutdown	S24
LTC1278-4	12	400	1	2.42	μP 12	3/±3	75/5	Sampling ADC w/Shutdown	N24/S24
LTC1278-5	12	500	1	2.42	μP 12	3/±3	75/5	Sampling ADC w/Shutdown	N24/S24
LTC1279	12	600	1	2.42	μP 12	3/±3	75/5	Sampling ADC w/Shutdown	N24/S24
LTC1282	12	140	1	1.20	μP 8 or 12	3/±3	12	3V Sampling ADC	N24/S24
LTC1410	12	1250	1	2.50	12	±5	160/0.01	Sampling ADC w/Shutdown	S28

\* Serial I/O is Microwire, SPI and QSPI compatible

\*\* Power dissipation is listed in the Active and Shutdown modes

† N8 = 8-pin DIP    N16 = 16-pin DIP    N18 = 18-pin DIP    N20 = 20-pin DIP    N24 = 24-pin DIP    N28 = 28-pin DIP  
S8 = 8-pin SOIC    S16 = 16-pin SOIC    S20 = 20-pin SOIC    S24 = 24-pin SOIC    S28 = 28-pin SOIC

## D/A Converters

Part	Resolution (Bits)	Output Type	V <sub>REF</sub>	Data I/O	V <sub>CC</sub> (V)	P <sub>DISS</sub> (mW)	Features	Package
LTC1257	12	V	Int	Serial	4.5-15	1.75	Single Supply V <sub>OUT</sub> DAC	N8/S8
LTC1451	12	V	Int	Serial	4.5-6.0	2.0	5V Rail-to-Rail V <sub>OUT</sub> DAC	N8/S8
LTC1452	12	V	Ext (MDAC)	Serial	3.0-6.0	1.12	Single Supply V <sub>OUT</sub> MDAC	N8/S8
LTC1453	12	V	Int	Serial	3.0-4.5	0.750	3V Rail-to-Rail V <sub>OUT</sub> DAC	N8/S8
LTC7541A	12	I	Ext (MDAC)	Parallel	5-16	15	Industry Standard MDAC	N18/S18
LTC7543	12	I	Ext (MDAC)	Serial	4.75-5.25	0.500	Industry Standard Serial MDAC	N16/S16
LTC8043	12	I	Ext (MDAC)	Serial	4.75-5.25	0.500	8-Pin SOIC MDAC	N8/S8
LTC8143	12	I	Ext (MDAC)	Serial	4.75-5.25	0.500	Industry Standard MDAC	N16/S16



**Linear Technology Corporation**  
1630 McCarthy Blvd.  
Milpitas, CA 95035-7487  
Phone: (408) 432-1900  
Fax: (408) 434-0507  
**For literature only: 1-800-4-LINEAR**




to redirect power normally lost in switching back to the output, providing efficiencies of 90 to 97%. The device comes in a 16-pin DIP or SOIC package and costs \$4.05. **Micro Linear Corp.**, San Jose, CA. (408) 433-5200.

**Circle No. 342**

**Tips for PCI-based multimedia applications.** The IIT 3304 Multimediate Encoder Processor (MEP) single-chip multimedia authoring and playback processor lets you author and edit multimedia publications in real time. The chip performs Moving Pictures Experts Group 1 video encoding and decoding in full-motion video capture. It comes in a 240-pin PQFP and costs \$450,000. The IIT 3501 Video PCI Interface Chip connects all members of the company's Multimedia Processor architecture family, including the MEP, directly to the PCI bus. The device comes in a 160-pin PQFP and costs \$180,000. **Integrated Information Technology Inc.**, Santa Clara, CA. (408) 7-1885.

**Circle No. 343**

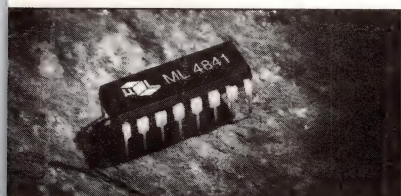

**Power-supply chip uses two-stage conversion for power-factor correction and conversion efficiency.** The ML4841 accepts an ac input voltage from 85 to 265V ac and converts it to standard dc voltages, such as  $\pm 3.3$  or  $\pm 5$  V. The chip provides power-factor correction  $>0.99$  and efficiencies  $>90\%$ . The chip uses a two-stage conversion process. The first stage is optimized for high power-factor rating on the ac line, and the second stage is optimized for high output efficiency. The chip powers power supplies to meet the C555 standard, which requires power-factor correction for products over 50W sold in Europe in 1996. Available in a 14-pin DIP or 16-pin SOIC package, the device costs \$3.08 (1000). **Micro Linear Corp.**, San Jose, CA. (408) 433-5200.

**Circle No. 344**

**Video line buffer operates at speeds to 50 MHz.** The LF9501 has a buffer length programmable from 2 to 31 words to match line lengths of

various video formats including National TV Systems Committee, phase-alternation-line, Systeme Electronique Couleur Avec Memoire, and other proprietary formats. The device accommodates a 10-bit word length. It comes in a 44-pin plastic J-lead chip carrier, and prices start at \$13.23 (500). **Logic Devices Inc.**, Sunnyvale, CA. (408) 737-3300.

**Circle No. 345**

**MPEG 1 audio and video decoder chip.** The CL480PC decodes Moving Pictures Experts Group (MPEG) 1 audio and video for portable and desktop computers. The chip features a host or CD interface for input of MPEG-1-system bit streams, the ability to load the microcode initializing the CL480PC via the host interface, 16-bit dithered video output; programmable output video timing and interpolation control, and advanced error concealment. The 128-pin PQFP dissipates  $<1$ W from a 3.3V supply while operating and  $<0.1$ W in stand-by mode. It costs \$31 (OEM). **C-Cube Microsystems Inc.**, Milpitas, CA. (408) 944-6300.

**Circle No. 346**

**FIFO for printer applications.** The GT-24002 PrintFIFO is a 32-bit-wide, 1104-location-deep, synchronous FIFO buffer. The device can output data 1 bit or 1 byte at a time. Input and output ports can operate at 33 MHz, providing an input bandwidth of 133 Mbytes/sec. The true dual-port device can simultaneously receive input data while outputting data. Additional features include margin counters and registers to support printer operations. The device comes in a 128-lead PQFP and costs \$49.95 (5000). **Galileo Technology Inc.**, San Jose, CA. (408) 451-1400.


**Circle No. 347**

**LPGA has >100,000 gates and one-day delivery.** The QYH600 family of laser-programmable gate arrays (LPGAs) offers densities of 17,000 to 120,000 available logic gates and supports system clock rates  $>120$  MHz. The initial members of the family include 70,000- and 100,000-gate devices that will be available in the third quarter of 1995. Two tested 100,000-gate LPGAs with a five-day turnaround cost \$70,000. **Chip Express Corp.**, Santa Clara, CA. (408) 988-2445.

**Circle No. 348**

# PICO

## SURFACE MOUNT DC-DC Converters

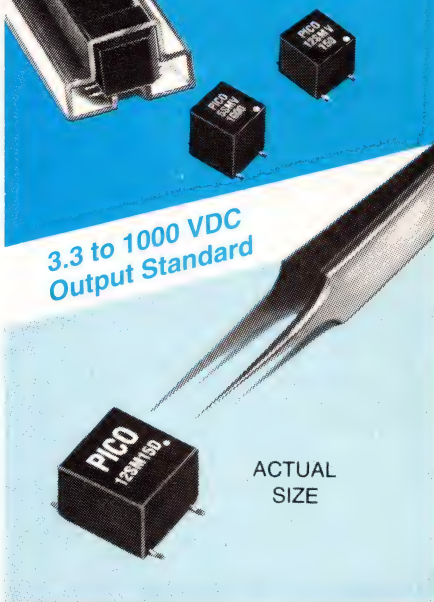

### PICO's SM and SMV Series

- 1.25 watt output at 70° ambient
- 140 standard models
- Ultra-miniature size .34 ht., 3.5 grams weight
- 5 input voltage ranges 5, 12, 24, 28 and 48 VDC
- Up to 1500 volts input/output isolation
- No heat sink or electrical derating required
- Up to 1000 volts DC output
- MIL-STD 883 options available
  - Expanded operating temp ( $-55^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$ )
  - Stabilization Bake ( $125^{\circ}\text{C}$  ambient)
  - Temperature Cycle ( $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$ )
  - Hi Temp, burn in
- Over 1400 standard DC-DC and AC-DC models up to 200 watts

Delivery—  
stock to one week

See EEM  
or send direct  
for **Free PICO Catalog.**  
Call toll free **800-431-1064**  
in NY call **914-699-5514**  
FAX **914-699-5565**

**PICO Electronics, Inc.**

453 N. MacQuesten Pkwy., Mt. Vernon, N.Y. 10552  
**CIRCLE NO. 30**



**FREE INFO, FREE POSTAGE**


Use our postage-paid reader-service cards to get more information on any of these products.

**Design environment automates high-speed system-design methodology.** The BoardQuest environment combines tools from the timing, signal-integrity, EMI, thermal, reliability, and manufacturing domains. The environment integrates with the company's Concept and Composer design-entry tools; the SigNoise, EMControl, Thermax, and Viable DesignFor analysis tools; and the Allegro correct-by-design layout system. Prices for BoardQuest start at \$19,000. Prices for DesignFor analysis tools range from \$18,000 to \$35,000. **Cadence Design Systems Inc**, San Jose, CA. (408) 943-1234. **Circle No. 409**

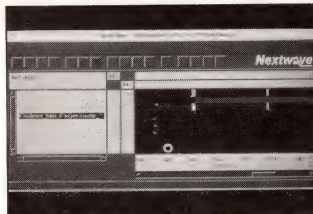**Multilevel simulation tool for submicron designs.** QuickVHDL Co-Lsim combines the QuickVHDL simulator with Lsim for transistor-level analysis of timing and power effects in deep-submicron designs. The co-simulation interface is based on the Precedence SimMatrix simulation backplane. A node-locked license costs \$16,000, and a floating license costs \$20,000. The tool requires Lsim and QuickVHDL. **Mentor Graphics**, Wilsonville, OR. (503) 685-8000. **Circle No. 410**

**Graphical state-machine-design tool adds Verilog to supported languages.** The StateCAD Verilog Edition translates bubble diagrams into synthesizable, Open Verilog International-compliant Verilog for tools

from FrontLine, Simucad, and Exemplar. The tool also helps you analyze your state designs for problems. Other versions of StateCAD generate code in Abel, VHDL, and C from the same diagram. The Verilog edition costs \$1495. **Visual Software Solutions**, Coral Springs, FL. (305) 346-8890. **Circle No. 411**



**Tool links graphical timing and HDL specification to create Verilog testbenches.** TesTech links the company's TDS, a graphical timing-specification tool, with its Visual HDL, a graph-

ical hardware-description language- (HDL)-specification tool, to create Verilog test benches. The tool checks conformance of circuit timing to design specifications throughout a design. It also simplifies stimulus capture by using a standard data-book format to describe timing requirements. The tool is available as an option to TDS and Visual HDL and costs \$20,000. **Summa Design Inc**, Beaverton, OR. (503) 643-9281. **Circle No. 412**

**Tool combines static-timing analysis and Verilog spread-delay simulation.** The Epilog-MX multitime timing-verification tool checks the timing of all parts of a design's logic in operation. Static-timing analysis quickly finds timing hazards for synchronous

## Wavetek's New Model 9100

### Performance and Portability... Unparalleled Calibration Quality

If your calibration needs are multiplying, Wavetek's new Model 9100 is just what you need.

The Model 9100 Universal Calibration System can fully exercise the performance limits of the most diverse calibration workload—from analog and digital multimeters to panel meters, clamp meters, electronic thermometers, chart recorders and data loggers. You can even configure the Model 9100 to calibrate analog and digital oscilloscopes, combination scope/multimeters and counters!

The Model 9100 is light enough to carry on-site to your instruments. With plug-in PCMCIA procedure cards, the Model 9100 is ready to guide even untrained operators through the entire calibration process, from connecting the leads to printing out an ISO9000 compliant calibration certificate.

So however diverse your calibration workload, and wherever you need to go on-site, the Model 9100 has the power and performance to make the task easy.



## Universal Calibration System



**For more information on the Model 9100 Universal Calibration System**

#### In the USA:

#### Wavetek Corporation

9045 Balboa Ave  
San Diego, CA 92123  
Tel 1-800-223-9885  
Fax (619) 450-0325

#### In Europe:

#### Wavetek Ltd

Hurricane Way  
Norwich Norfolk NR6 6JB, UK  
Tel +44 1603 404824  
Fax +44 1603 483670

# WAVETEK

WAVETEK and the Wavetek logo are registered trademarks of Wavetek Corp.  
© 1995 Wavetek Corporation

**CIRCLE NO. 31**



INTRODUCING VMIC'S

**New!**

## INDUSTRIAL DUAL PENTIUM WORKSTATION

### VMIC COMPUTER SYSTEMS FEATURES:

- Dual 90 or 100 MHz Pentium Central Processing Units (CPUs) with 16K Cache, 32-bit Architecture, and Built-In Math Coprocessor
- 512 Kbyte Synchronous Burst Write-Back Secondary Cache
  - At Least 32 Mbyte DRAM Expandable to 256 Mbyte Using Single In-Line Memory Modules (SIMMs)
- A 1 Gbyte or 2 Gbyte SCSI-2 System Disk with Expansion Capability for a Second 3.5-in. Hard Drive
- Peripheral Component Interconnect (PCI) Graphics with 2 Mbyte Video RAM (VRAM) Using High-Speed 64-bit Graphics Accelerator and Supporting High-Resolution Graphics and Color Standards
- Two Available Expansion Slots. The Second Expansion Slot has a PCI Connector, and the Lower Expansion Slot has both a PCI and an EISA/ISA Connector
- Fast SCSI-2 Quad-Speed CD-ROM Drive
- External Fast SCSI-2 Expansion Bus Supporting Up to Five External Devices. Four External Devices are Supported when the Optional Second Internal Hard Disk Drive is Installed in the System
- Two Asynchronous Serial Ports with Full Modem Controls
- Hardware Supporting a Multimode Bi-directional Parallel Port which provides Standard Mode, Enhanced Parallel Port (EPP) Mode, and Extended Capability Port (ECP) Mode
- On-Board Ethernet Supporting Either a 10Base-T or Attachment Unit Interface (AUI) Connector
- Operating System Software (Windows NT) Installed on the System Disk
- Rack Mount, Tower, Embedded VMEbus, and Desktop Solutions
- PCI to VME adapter available
- PCI expansion available



**TWO-YEAR WARRANTY  
24-HOUR SUPPORT**

**1-800-322-3616**

**CALL VMIC TOLL-FREE TODAY** For High Performance Industrial Workstation Solutions look to the world leader - VMIC. Tap into the power and performance of VMIC's new Dual Pentium Industrial Workstations.

**CIRCLE NO. 123**



VME MICROSYSTEMS  
INTERNATIONAL CORPORATION

12090 S. Memorial Parkway • Huntsville, AL 35803-3308  
(205) 880-0444 • FAX (205) 882-0859

World Wide Web Home Page: <http://www.industry.net/vmic>





logic. The Verilog gate spread-delay simulation finds timing problems for nonsynchronous parts of a design. Although not as fast as static-timing analysis, the spread-delay simulation is necessary for some parts of most designs. Using the simulation for only those portions of a design in which static-timing analysis is inadequate saves time over a full timing simulation of the complete design. A single node-

locked license costs \$35,000. **Nextwave Design Automation**, San Jose, CA. (408) 437-3939.

**Circle No. 413**

**PC-based semiconductor-device-simulation software.** The Device Wizard simulates semiconductor devices on PCs. According to the company, the software's simulation speed

and accuracy meets or exceeds that of Unix-based semiconductor-device simulators. The tool can simulate arbitrary 2-D semiconductor devices and includes predefined templates for >20 common semiconductor-device types. The base price is \$12,000. **Dawn Technologies Inc.**, Sunnyvale, CA. (408) 737-6181.

**Circle No. 414**

## books that work the way you work

### Analog Circuit Design: Art, Science, Personalities

**Jim Williams, Linear Technology Corp., Editor**

*"If you do any analog circuit design, buy this book!...The well-indexed volume ... provides a picture of analog design, in all its diversity, as a way of thinking and a way of approaching problems."*

**Dan Strassberg, EDN**

1991 352pp. cloth 0 7506 9166 2 \$44.95 (£30.00)

Based on the EDN Series, with 20% NEW material

### Troubleshooting Analog Circuits

**Robert Pease, National Semiconductor**

*"Here's a chance to take advantage of [Pease's] years of experience designing analog circuits--and working the bugs out of them. This book is for you whether you're designing analog circuits at the board, box, system, or IC level."* **Electronic Design**

1991 208pp. cloth 0 7506 9184 0 \$32.95 (£19.95)

Loaded with practical information

### Rechargeable Batteries Applications Handbook

**Technical Staff, Gates Energy Products**

This is a comprehensive reference on proper selection, specification and application guidelines from one of the world's largest sealed-cell manufacturers. May 1992 432pp. cloth 0 7506 9227 8 \$49.95 (£38.50)

### The EDN Series for Design Engineers

In the U.S.  
for more information  
or to place an order call  
**1-800-366-2665**  
M-F 8:30-4:30 E.T.  
Fax **617-279-4851**


In Europe, order from:  
Reed Book Services Ltd.  
Special Sales Department  
P.O. Box 5, Rushden  
Northants NN10 9YZ U.K.  
TEL. 0933 58521 FAX 0933 50284  
Please quote "Cahners 13.89"

**BUTTERWORTH-HEINEMANN**

80 Montvale Ave., Stoneham, MA 02180



CAHNERS 13.89

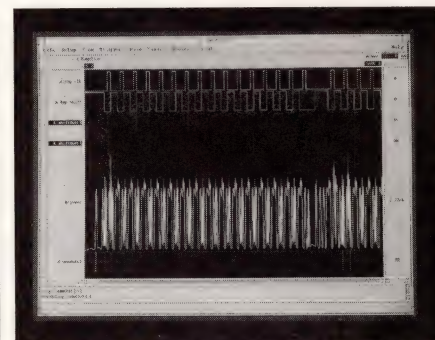

**Power-calculation tool for ICs can handle bus-contention and state-dependent currents.** PowerSim 2.0 performs power calculations on ICs described in Verilog HDL. It takes into account capacitive charging/discharging, slew effects, bus contention, state-dependent currents, leakage, and other power factors. According to the company, the tool operates at the cell level and runs at virtually the same speed as a gate-level simulation. The tool works with Verilog simulators and runs on SPARC, HP700, and DEC Alpha computers. It costs \$18,500. **System Science Inc.**, Palo Alto, CA. (415) 812-1800.

**Circle No. 415**

**PC-board-layout tool offers interface to Spectra autorouter.** The WinBoard pc-board-layout tool now has an interface to the Spectra autorouter from Cooper & Chyan Technology. The interface lets you partially route a board before launching the autorouter and edit the board after autorouting. WinBoard PCB layout costs \$995, and the interface costs \$295. **Ivex Design International**, Beaverton, OR. (503) 531-3555.

**Circle No. 416**

**New versions of analog and logic simulators.** T-Spice version 3.0 improves computational efficiency, robustness, reliability, and accuracy over previous versions. A source-stepping feature adjusts power-supply values until it converges on the dc operat-



ing conditions. The tool also offers a lossy transmission-line model for modeling high-frequency effects, mismatch, and coupling between elements. Prices for the software for PCs and workstations start at \$1245. Gate Sim version 2, a PC-based gate-level digital simulator, handles 250,000 gates and costs \$1295. **Tanner Research Inc**, Pasadena, CA. (818) 792-3000. **Circle No. 417**

(FPGA) logic modules, mapping to complex I/Os, and links to macro generators. The new release costs \$5000 to \$45,000. **Viewlogic Systems Inc**, Marlborough, MA. (508) 480-0881.


**Circle No. 420**

**Verilog simulator now runs under Windows and OS/2.** VeriWell 2.0 now is available for Windows, Windows NT,

Windows 95, and OS/2. According to the company, the simulator complies with Open Verilog International standards and offers Verilog XL compatibility and performance. The base module costs \$1495, the gates and timing-preference module cost \$895, and both modules together cost \$2390. **Well-spring Solutions Inc**, Sutton, MA. (508) 865-7271. **Circle No. 421**

**Spice library for power-supply designers.** The Spice model library for power-supply designers contains >20 PWM IC models for parts from Cherry Semiconductor, Linear Technology, Siliconix, and Unitrode. Some models offer multiple levels of complexity. The models use Spice 3, Boolean-logic, and HDL elements. The model library works with the company's IsSpice3 or IsSpice4 simulators. It costs \$395. **Intu-soft**, San Pedro, CA. (310) 833-0710.

**Circle No. 418**

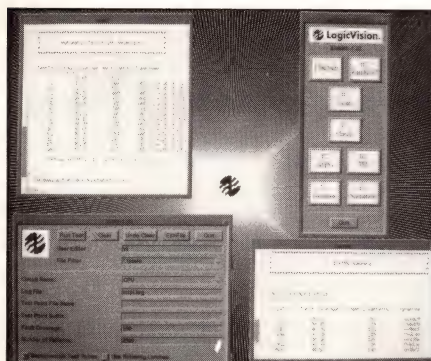

**BIST tool for ICs.** ICBIST couples front-end generation of synthesizable register-transfer-level code for logic built-in self-test (BIST), RAM BIST, and Joint Test Action Group/1149.x with back-end tools for BIST analysis and testability insertion. The tool suits complex ASICs and custom ICs. Prices start at \$140,000 per seat. **Logic Vision Software Inc**, San Jose, CA. (408) 453-0146. **Circle No. 419**

**Windows-based EDA-design environment offers improvements.** Workview Plus 5.2 offers a variety of improvements over earlier versions. The ViewDraw tool now supports bus rippers and net aliasing. ViewTrace includes faster database reads and refresh rates. The optimization engine for ViewFPGA includes direct mapping to field-programmable gate-array

# The Solution...

for your power supply EMI needs

# is within reach

**Whether your application involves**

- **Military** - (EMI suppression to MIL461 including CE01, CE03) or (Surge/spike protection to MIL704 or 1399 or 1275)
- **Airborne** - DO160 specifications
- **Rail & Transportation** - Wide range input requirements
- **Industrial Controls** - 40 year long life designs
- **Communications** - High Reliability

**Arnold Magnetics has standard high density power supply modules to meet your exacting system needs.**

- AC-DC Front ends, DC-DC multi outputs
- Auto Ranging inputs
- Power Factor Corrected designs
- -55°C to +100°C temperature ranges
- N+1 current sharing

## (800) 421-8181



*Power Supplies Since 1956*

4000 Via Pescador • Camarillo, CA 93012 • (805) 484-4221 • FAX (805) 484-4113

**CIRCLE NO. 32**



**FREE INFO, FREE POSTAGE**

Use our postage-paid reader-service cards to get more information on any of these products.

**Real-time executive for component-based real-time executive.**

The MQX version 2.31 real-time executive has a minimum size of 8 kbytes for a Motorola 68000 processor and a maximum size of about 23 kbytes if using all 15 components. The executive includes a component if an application references the component. The actual size of the kernel is determined at link time. The new release gives you better control over the size and functionality of the executive. It costs \$5000 on a per-project basis with a royalty-free source-code license. **Precise Software Technologies Inc.**, Nepean, ON, Canada. (613) 596-2251, ext 27. **Circle No. 397**

**PC/104 computers feature flat-panel displays.**

The DisplayPac-104 is available with 14-, 10.4-, and 8.4-in., VGA, color, thin-film-transistor (TFT) LCDs with up to 256,000 colors; 11.8-in., XGA, color TFT LCDs; dual-scan, passive-color LCDs; active-matrix, monochrome LCDs; electroluminescent displays; and monochrome LCDs. A complete system with a display, a 486 computer, a touchscreen, and a PC/104 expansion module is 2.5 in. thick. A 50-MHz system, including a touchscreen and 4 Mbytes of DRAM, costs \$3782 (50). **Computer Dynamics**, Greer, SC. (803) 877-8700.

**Circle No. 398**

**Tool lets you create and maintain graphical data models of PowerBuilder databases.** Database Engi-

neer for PowerBuilder lets you visually define systems for design specifications, documentation, and maintenance. The tool works with EasyCASE Professional 4.2 and PowerBuilder Desktop and Enterprise versions 3.0/4.0. The tool has an interface that imports, exports, and updates PowerBuilder table structures and extended attributes. It costs \$995. **Evergreen CASE Tools Inc.**, Redmond, WA. (206) 881-5149.

**Circle No. 399**

**16-bit embedded controllers.** The MQX16 real-time executive requires 3 kbytes or less of ROM. It is written in ANSI C, and can be extended by integrating real-time executive components from the company's standard MQX product. The executive provides func-

tions such as task switching, pre-emptive scheduling, memory management, time stamping, delaying, and interrupt management. The product is available for the Motorola 68HC11 and Intel 8088 and 80x86 processors. A project-based, royalty-free, source-code license, including one PC-based executable, costs \$3000. **Precise Software Technologies Inc.**, Nepean, ON, Canada. (613) 596-2251, ext 27.

**Circle No. 400**

**Embedded DOS runs Windows.** Embedded DOS 6-XL is compatible with Microsoft DOS 5.x and 6.x and provides real-time, fully pre-emptive, multitasking with 32-bit thread support. It comes with a set of 48 kernel services callable from C or assembly and includes threads, timers, events,

# EUREKA!

**Embedded software demos, pricing and product news!**

<http://www.archimedesinc.com/devtools>



**Archimedes Software, Inc.**

Phone 1-800-338-1453 • email: [devtools@archimedesinc.com](mailto:devtools@archimedesinc.com)  
FTP: <ftp:ftp.archimedesinc.com>

**CIRCLE NO. 33**

## New

## Bare Board Printed Circuit Design Manual

### Design for Manufacturability

A comprehensive manual, authored specifically for bare-board printed circuit design to meet today's demanding fine pitch surface mount requirements. Includes bare board costing. The **only** manual of its kind internationally!

This is a new publication, released in June, 1995, covering all of the necessary design parameters for a quality product at the best cost. The contents include: the complete tooling package; electrical testing; selection of materials; controlled impedance for high speed circuits; selecting a surface finish for coplanarity, solderability and shelf life; and design guidelines for manufacturability. All of the cost drivers are identified, with the last Chapter dedicated to calculating the vendors bare board pricing. This manual is a *must* for every designer, manufacturing engineer, quality manager and bare-board buyer.

Price: \$49.95  
(U.S. funds)

Add Shipping and Handling:  
\$4.00 inside the U.S.  
\$8.00 outside the U.S.

(Massachusetts Residents add 5% Sales Tax)

**Printed Circuit Technology**  
P.O. Box 334  
Burlington, MA 01803

Phone: (617) 938-1440  
Fax: (617) 932-8056

**CIRCLE NO. 34**




mutex semaphores, and memory pool. The operating system is available in binary and full-source adaptation kits for \$995 and \$2500, respectively. **General Software**, Bellevue, WA. (206) 454-5755.

**Circle No. 401**

**ICES for Motorola's MCF 5102.** The CodeICE system couples a full-featured in-circuit emulator (ICE) with a debugger. The MWX-ICE debugger operates on Sun 4, HP 9000, and Windows PC platforms. It supports popular compilers, including MRI and DIAB Data. The emulator is available with a run-control system, 4 Mbytes of overlay memory, a 32k-word trace system, and a multi-threaded event system. Prices start at \$21,950 for a PC-based system with 32k-word trace memory and no overlay memory. **Applied Microsystems Corp.**, Redmond, WA. (206) 882-2000.

**Circle No. 402**

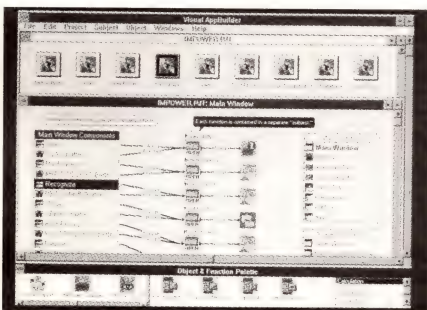

**Development tool simplifies the creation of imaging applications.** The ImPowerTools let you create imaging applications for deployment on Novell LANs and Windows-based PCs without writing code. The tool kit also includes AppWare loadable modules for scanner, viewer, ICR, OCR, index, store, retrieve, and print functions. According to the company, the tools let you create customized imaging applications in hours or days, instead of weeks or months. Prices for the tools start at \$7500 for a five-seat license. **Alta Technology Corp.**, Sandy, UT. (801) 562-1010.

**Circle No. 403**

**FDDI, LAN, SCSI, and ATM cards use PCI mezzanine-card architecture.** The new products using the Peripheral Component Interconnect (PCI) Mezzanine Card (PMC) architecture are: The MPMC221 fibre-distributed-data-interface (FDDI) adapter, the MPMC201 high-performance 100VG AnyLAN adapter, the MPMC101 high-end fast

and wide SCSI-2 communications controller, and the MPMC281 asynchronous-transfer-mode (ATM) adapter. Prices for the cards start at \$550. **Motorola Computer Group**, Tempe, AZ. (800) 624-6449.

**Circle No. 404**

**Programming environment for embedded systems has sophisticated editors for C and assembly.**


The Embedded Development Environment (EDE) is available for 8051, MCS 251, MCS 96, 68HC08, 80C166, and R3000 devices. The EDE shell provides a consistent interface to the tools for creating, editing, building, and debugging an embedded application. It includes a high-level C- and assembly-language editor, a C interface generator, a make tool, a librarian, object-code and cross-reference report writers, for-

# Let's play!

## Flash <sup>TrueFFS®</sup> Disks

*For embedded systems & mobile computers*

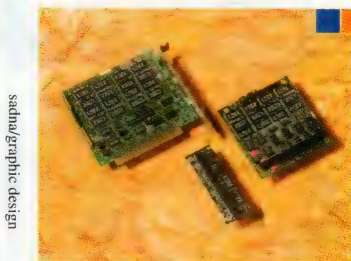
**M-Systems' current game plan includes:**



sadu/graphic design

**PC Flash Disk**  
For ISA and PC104 Bus

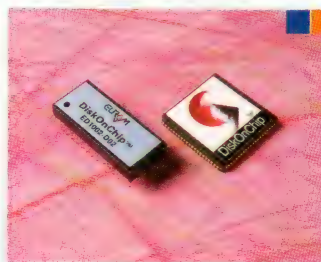- Up to 32 MBytes capacity
- ISA and PC104 Interfaces
- Embedded TrueFFS® (True Flash File System)
- DOS, Windows, QNX and VENIX compatibility
- Low Power Consumption
- Full Hard Disk Compatibility
- Easy to integrate - "Plug-'n-Play"
- Bootable Disk
- Extended temperature range option (-40°C + 85°C)



**DiskOnChip™**  
ED102/ED104, 1-4 MByte Flash Disk

- BIOS and Bootable Disk in one Package
- 1 to 4 MByte Capacity
- Embedded Flash Disk 100% Compatible with DOS
- Pin to Pin Compatible with EPROM BIOS
- Interleaving Support for Fast Write and Erase
- Low Power Consumption
- Single 5 Volt Supply
- Industry Standard Packaging
- No Battery Backup Required



USA Tel: 408-654-5820 Fax: 408-654-9107  
EUROPE Tel: 31-10-262-1144 Fax: 31-10-462-4855  
ISRAEL Tel: 972-3-647-7776 Fax: 972-3-647-6668

TrueFFS® is a registered trade mark of M-Systems and is protected by US patent #5404485

*Get in on the action*

**M-Systems**  
Flash Disk Pioneers



## TCP/IP



## Features

- Most powerful TCP/IP available for embedded systems
- All source code written in C
- Compatible with all C compilers
- "Drop in" Drivers for most ethernet and processor chip sets
- 100% RFC compliant
- Comes with powerful real time scheduler that accommodates most ports
- Compact design, code is Romable and re-entrant
- Routing services for WAN support
- Socket libraries are incorporated into TCP/IP stack for maximum performance
- All upper layer applications available

## Services

- Full porting services available at competitive rates
- Comprehensive porting guide and programmers reference manual
- Royalty free options available
- Monthly internal porting classes
- On-site consultation
- Unlimited porting support via telephone, fax, or internet
- Upgrade service, providing all the latest RFC changes and performance enhancements

WHEN "TIME TO MARKET" IS KEY USE FUSION: TCP/IP, SNMP, PPP DEVELOPER KITS

FUSION DEVELOPER KITS ARE THE MOST POWERFUL INTERNET PROTOCOLS DEVELOPED FOR EMBEDDED APPLICATIONS. OUR "TIME TO MARKET" PHILOSOPHY HAS MEANT WE'VE DEVELOPED PRODUCT WITH "DROP IN SUPPORT" FOR ETHERNET, AND PROCESSOR CHIPS AS WELL AS REAL TIME KERNELS. HIGH QUALITY, HIGH PERFORMANCE PROTOCOLS DEVELOPED WITH OVER 12 YEARS OF INTERNET PROTOCOL EXPERIENCE FOR YOUR SYSTEM DESIGNS.



Pacific Software

FOR MORE INFORMATION CALL:  
(800) 541-9508 within USA  
(805) 484-2128 outside USA  
(805) 484-3929 FAX

Internet: sales@pacificsw.com

World Wide Web <http://www.pacificsw.com>  
Offices in Europe & Japan

CIRCLE NO. 37

## PCMCIA SOLUTIONS

## Specializing in Industrial Applications

- **CARDS:** Flash ATA (1.8 MB to 175 MB), parallel port, synchronous serial, SRAM, LAN, 1.3" & 1.8" IDE (4 MB to 80 MB), & Type III hard disk drives (up to 260 MB)
- **CARD DRIVES:** Single/dual slot, PC 104, IDE, ISA, serial, parallel & SCSI card drives

**SunDisk**  
The Solid Advantage

**ADTRON**

ActionTec, Quatech...And More

**PRIMA**  
INTERNATIONAL



Call for information


**(800) 737-7462 ext. 10**

3350 SCOTT BLVD., BLDG. 7  
SANTA CLARA, CA 95054  
408-727-2600 • 800-737-7462  
Fax: 408-727-2435

CIRCLE NO. 38

matters, and converters. You can extend the tool set to include other tools from the company and interfaces to other company's tools. EDE costs \$229. **Boston Systems Office/Tasking**, Dedham, MA. (617) 320-9400.

**Circle No. 405**

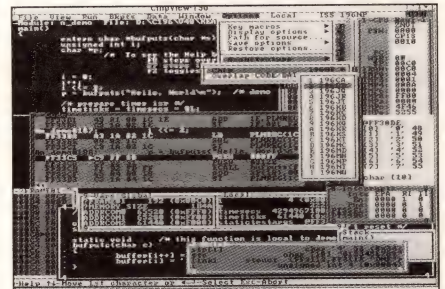

### High-level debugger for 80196 C compilers and assemblers.

ChipView-196 version 1.0 is derived from the company's ChipView-51 products and is compatible with Borland's Turbo Debugger. The debugger supports all phases of design and test with a single user interface. The system includes an instruction-set simulator/debugger, a high-level user interface for CheckMate Systems' 80196 emulator, and a reduced-instruction-set monitor (RISM) based on a ROM monitor debugger. The system costs \$795 for the instruction-set-simulator version and \$995 for the RISM-based ROM-monitor version. **ChipTools Inc.**, Mississauga, ON, Canada. (905) 274-6244.

**Circle No. 406**

**Real-time modular development system for 16- and 32-bit microcontroller families.** The MMDS1632 hardware- and software-development system provides real-time in-circuit emulation for the company's 68HC16 and 68300 microcontroller families. The modular system comprises a station module, a device-specific microcontroller personality board, package-specific personality and target boards, emulation software, and the necessary interfaces. The modular approach lets you configure the system for a range of applications at minimum cost, because you need to purchase only the modules necessary for your application. The MMDS1632 costs \$12,500, and prices for microcontroller personality boards start at \$500. **Motorola Microcontroller Technologies Group**, Austin, TX. (800) 765-7795, ext 912.


**Circle No. 407**



# High Profile. Low Tech.



# Low Profile. High Tech.

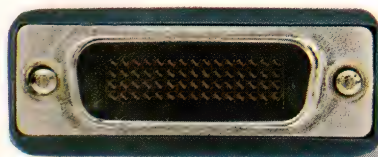

LFH™

High-Density

Interconnects

**Molex's LFH™ Interconnect - 60 Pins  
In A Standard 15-Pin D-Sub Shell, Saves  
Space And Lowers System Costs.**

It takes four of their 15-pin connectors to equal just one Molex LFH interconnect. Our unique 60-pin design in a standard 15-pin D-Sub shell saves space and lowers system costs.

Molex's LFH (Low Force Helix) connector also offers high cycle life reliability and low insertion force. The LFH connector's patented helix pins are thicker

and stronger than conventional pins, yet small enough to allow low insertion force and high-pin counts—on .075" or .050" centers.

A controlled contact finish and plating provides the best possible stamped contact interface, while also reducing the friction that causes the wear associated with

stutting and zippering. Testing confirms the LFH connector exceeds the industry's most stringent reliability standards.

For designs requiring small packages, high pin counts, and reliable performance, the LFH interconnect is the singular choice. Test one for yourself. Call Molex today at 1-800-78MOLEX for more information.



*Bringing People & Technology Together, Worldwide<sup>SM</sup>*


Corporate Headquarters: 2222 Wellington Ct., Lisle, IL 60532 U.S.A., Tel: (708)969-4550 • European Headquarters: Munich, Germany, Tel: 49-89-413092-0  
Far East North Headquarters: Tokyo, Japan, Tel: 81-427-21-5539 • Far East South Headquarters: Jurong Town, Singapore, Tel: 65-660-8555

©1995, Molex Incorporated

CIRCLE NO. 189


**EDN JULY 6, 1995 ■ 147**



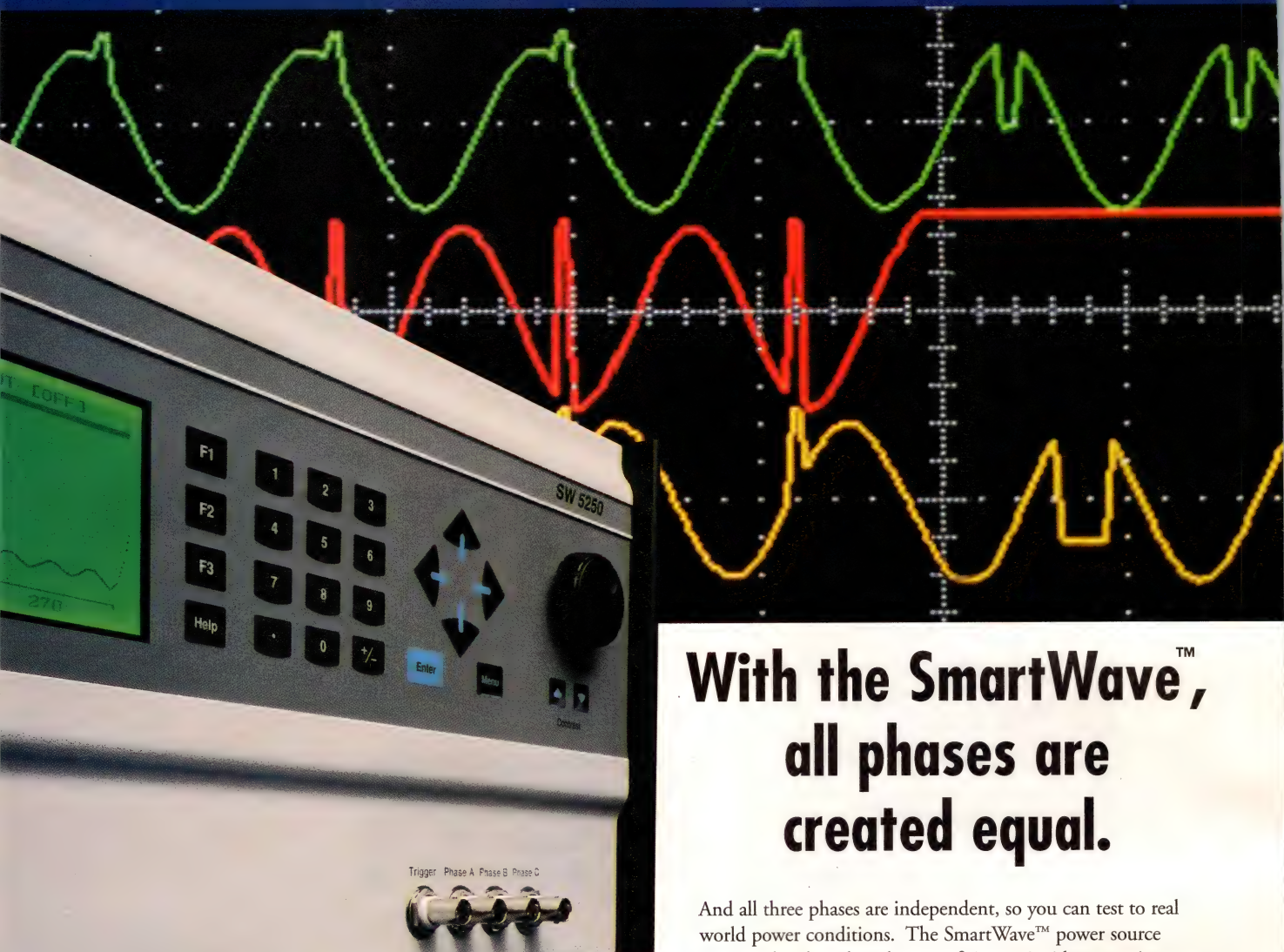

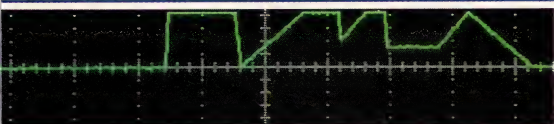
## With the SmartWave<sup>TM</sup>, all phases are created equal.

And all three phases are independent, so you can test to real world power conditions. The SmartWave<sup>TM</sup> power source can simulate line disturbances of time coincident transients on three phase power, create simultaneous AC and DC power plus seamlessly transition from one waveform to another. With three independent arbitrary waveform generators and AC plus DC output, the SmartWave 5250 solves the most demanding test problems.



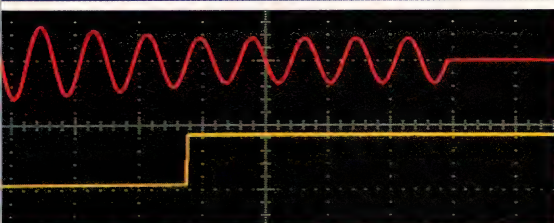Aerospace companies find the SmartWave perfect for simulating transients on a 28V DC bus. Voltage sags, surges and dropouts can be programmed in accordance with a variety of federal regulations. The 20 microsecond response time and 7 volts/microsecond slew rate allow the fastest transitions available for accurate simulation of real world conditions.



Uninterruptible power supply manufacturers use SmartWave to simulate both AC input and DC battery power at the same time. By simulating a wide range of AC line and DC battery conditions and measuring the results, the SmartWave provides all the necessary resources in a single instrument. The SmartWave saves time, space and money by replacing an AC source, a DC power supply, two voltmeters and two current meters.

Single and three phase power line simulation, standards testing and battery simulation are just a few of the many SmartWave applications. Call Elgar at **1-800-733-5427** or **619-450-0085**; our application engineers deliver solutions for all phases of test problems.

# ELGAR

POWERFUL SOLUTIONS  
**1-800-733-5427**



## FREE INFO, FREE POSTAGE

Use our postage-paid reader-service cards to get more information on any of these products.

**RISC processor provides glueless interface to memory and other improvements.** The MB86936 RISC processor is available in 30- and 60-MHz versions. It includes an 8-bit video interface to streamline rasterization and configurable bus sizing, so that the IC can accommodate 8-, 16-, and 32-bit memories. The processor also has a 4-kbyte instruction cache and a 2-kbyte, two-way set-associative data cache. Samples cost \$80. **Fujitsu Microelectronics Inc.**, San Jose, CA. (408) 922-9000. **Circle No. 363**

**μC based on 8051 offers expanded feature set.** The SABC509 8-bit μC has a 29-channel capture-compare unit, 3.3 kbytes of RAM, a 15-channel, 10-bit A/D converter with adjustable sampling and conversion times, a 60-kHz PWM unit, and up to 64 general I/O pins and 15 input-only pins. The device costs \$12.60 (10,000). Other versions offering less RAM start at \$2.37 (1000). **Siemens Components Inc.**, Integrated Circuits Division, Cupertino, CA. (408) 777-4500. **Circle No. 364**


**Communications processor for V.34 modem applications.** The 68DP356 combines a general-purpose μP core, a RISC communications engine, and a 24-bit DSP. It provides the hardware and software to perform data-pump functions for V.34 modem applications. The processor works with the ST7544 codec from SGS Thomson Microelectronics to perform data-pump and controller functions. The processor costs \$75.95 (10,000). **Motorola Microprocessor and Memory Technologies Group**, Austin, TX. (512) 891-2429. **Circle No. 365**

## What's Next in EDN

- ◆ Designing for speed with high-performance PLDs
- ◆ Technology promises free multimedia in PCs
- ◆ High-density FPGA synthesis

New!

## MT-Series DC/DC Converter

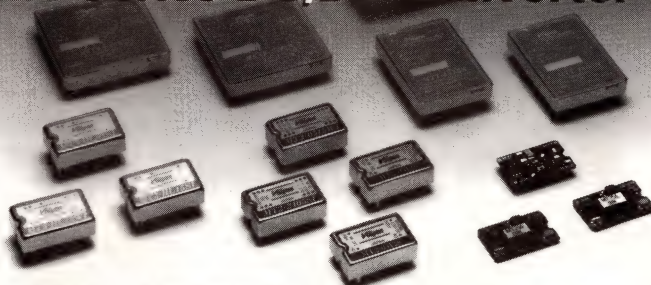

### Board Mount DC/DC Converters for Commercial, Industrial and Telecommunication Applications.

Single and Dual Output 2W, 3W, 7.5W, 15W and 100W DC/DC Converters.

**Wide Input Voltage Range  
High Efficiency  
High Power Density  
Low Profile  
Competitively Priced**

- Input: 5, 12, 24, 48 VDC
- Output: 3.3, 5, 12, 15 VDC
- Isolated Input / Output
- Metal Encapsulated
- Low Output Ripple and Noise

- Short-Circuit Protection
- Regulated Outputs
- High MTBF
- Remote On-Off
- Two Year Warranty

For Information Call:

Tel: (510) 429-7170 \* Fax: (510) 429-7173

**Volgen America**

QUALITY FIRST

32980 Alvarado-Niles Road • Union City, CA 94587  
Volgen — A Tokyo Keidenki Company

**CIRCLE NO. 39**

# SPEEDBOARD™

## LOW DIELECTRIC CONSTANT PREPREGS

**Faster signals, superior controlled impedance, standard PWB processing!**

Gore's low dielectric constant (2.6-3.1) **SPEEDBOARD** prepregs offers all this plus faster risetimes, lower parasitics and higher wiring densities. **SPEEDBOARD** prepregs use standard processing PWB techniques **so your costs stay down**. **SPEEDBOARD** materials combine a nonwoven fluoropolymer matrix with cyanate ester or epoxy resins providing an exceptionally low dielectric constant bonding layer. They can increase speeds by 20% while decreasing thickness by 29% when compared to FR-4 glass laminate prepregs. Yet you can use the same artwork, same image transfer process and materials, same etching and other steps in standard PWB processes. **SPEEDBOARD** prepregs offer a high performance PWB solution without the typically associated higher costs. For technical information call:

W. L. Gore & Associates, Inc.  
Elkton, MD Fax (410) 996-3879



**1-800-255-GORE**  
(1-800-255-4673)



**FREE INFO, FREE POSTAGE**

Use our postage-paid reader-service cards to get more information on any of these products.

**High-speed recording and real-time display package provides throughput rates to 400 kHz.**

This high-speed recording and real-time display package has throughput rates of 400 kHz to RAM disk and 330 kHz to a hard disk. The package provides triggered and continuous acquisition modes in 16-, 32-, or 64-channel configurations. From \$4000. RC Electronics Inc, Santa Barbara, CA. (805) 685-7770. **Circle No. 367**


**Portable SCSI performance and protocol analyzer attaches to PCMCIA socket.**

The SCSI-View Model SV-8020 measures 5.75×3.6×0.81 in. and attaches to a notebook PC via the PCMCIA socket. The instrument transfers captured SCSI phase-event information to the host computer for analysis with the software. The software can search captured files for phase times, incomplete commands, messages, status bytes, and data burst rates. The instrument includes reprogrammable field-programmable gate arrays, allowing the company to add analyzer features and other changes by software updates. The analyzer with software costs \$2995. Verisys Inc, Soquel, CA. (408) 464-4292. **Circle No. 368**

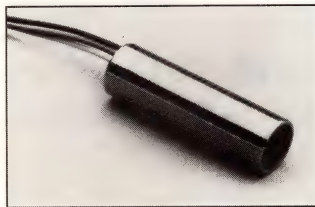**Low-cost data-acquisition device connects to serial port.**

The 232SDA10 has 11 channels of 10-bit A/D conversion with a 0 to 5V input range, three digital inputs with a ±30V range, and three digital outputs with a 0 to 5V range. The module uses three commands and has automatic

baud-rate detection from 1200 to 9600 baud. The 10-bit version costs \$49.95, and a 12-bit version costs \$59.95. RS-485-compatible modules are also available. B&B Electronics Manufacturing Inc, Ottawa, IL. (815) 434-0846. **Circle No. 369**



**Hall-effect sensor works over wide range of air gaps.**

The Model 427008-30 zero-speed noncontact sensor senses targets at speeds from 0 to 20,000 Hz. It operates over air gaps ranging from 0.010 in. for 44-pitch gears to 0.120 in. for eight-pitch gears. The 0.375-in.-diameter×1.4-in.-long sensor is available in a standard model rated for 105°C and a high-temperature model rated for 150°C. Samples cost \$75. Magnetic Sensors Corp, Anaheim, CA. (714) 630-8380. **Circle No. 370**

**I/O board provides interface between commercial test equipment and custom designs.**

The Interface Control Board (ICB) provides embedded  $\mu$ P control of custom circuitry across an IEEE-488.2 or RS-232C interface. The board comes with 72 digital I/O lines, programmable timers, an interrupt timer, DMA circuitry, and several system clocks to control hardware. You can install custom circuitry in a prototype area and interface it to test circuitry through three 96-pin DIN connectors. The ICB is designed around a Eurocard 6U form factor and fits into a VME-type chassis, B-sized slot. The board, including RS-232C cable, daughter-board, and software, costs

\$995. Advanced Designs Inc, Colorado Springs, CO. (719) 598-9224. **Circle No. 371**

**PCI bus analyzer performs 200-MHz timing and 66-MHz state analysis on all 96 PCI bus lines.**

The 64-bit PCI-BA+64 and the 32-bit PCI-BA+32 acquire and display timing or state information on all types of bus cycles for 64- and 32-bit PCI-based systems. The bus analyzers use the high-speed ECP parallel-port interface protocol to transfer data as fast as 2 Mbytes/sec to PCs running Windows. It stores as many as 256,000 samples for each of the 96 input lines. You can select the amount of pre-trigger and post-trigger information you want in the sample data. Eight external 200-MHz input channels are also available. The 64-bit board costs \$6995, and the 32-bit board costs \$4995. NewBus Co, Fremont, CA. (408) 929-9060. **Circle No. 372**

**Instrument-driver DLL simplifies instrument control for Visual Basic and C users.**

The Instrument Driver dynamic-link library includes >75 instrument drivers for controlling popular IEEE-488 test instruments from Fluke, HP, Tektronix, Wavetek, and other instrument suppliers. The library is available on CD-ROM and costs \$495. National Instruments, Austin, TX. (512) 794-0100. **Circle No. 373**


**10-MHz direct digital-synthesis function generator costs \$1269.**

The Model 29 function generator provides both standard and arbitrary waveform generation. Standard functions include sine, square, positive pulse, negative pulse, multi-

level square, triangle, ramp-up, ramp-down, sin x/x, dc, and pseudorandom noise. The instrument includes both RS-232C and IEEE-488 interfaces for remote programming. Battery-backed memory stores nine instrument setups. Wavetek Corp, San Diego, CA. (619) 279-2200. **Circle No. 374**

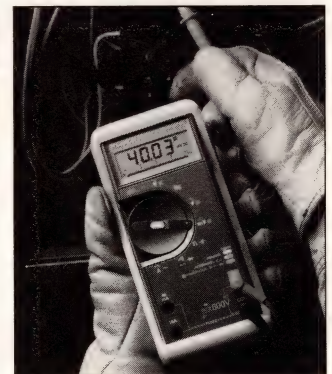**Passive bus analyzer adds support for SCAM protocol.**

The IPC-6500 bus analyzer now supports SCSI Configured AutoMagically (SCAM), which Windows 95 requires on SCSI systems. The bus analyzer features a single-ended and differential line connector, 20-nsec resolution for 16- and 8-bit SCSI, event filtering using transition masks, a 50-MHz programmable state machine, 16-level triggering, and multiple data display modes. The hardware comes with a full-length ISA-bus card with 68- and 50-pin connectors. It costs \$5100. I-Tech Corp, Edina, MN. (612) 941-5905. **Circle No. 375**



**True-rms DMM meets IEC-1010 Category III standards.**

The Model 76 DMM for overvoltage Category III requirements continuously withstands 600V ac or dc and has impulse withstand protection up to 6000V. The DMM is either certified to or has pending certification to the following agency approvals: UL, CSA, CE, and



# Traceable 10 MHz Calibration Standard with Cesium Stability

**\$4950** (U.S. list)

Atomic clocks have long been the recognized standard for applications requiring a highly accurate and stable frequency reference.

**Now there's a low cost alternative.**


The FS700 is a LORAN-C based frequency standard that provides the long-term stability of a Cesium clock ( $10^{-12}$ ) with NIST traceability. LORAN-C timing signals are transmitted by over 90 stations throughout the northern hemisphere, guaranteeing reception in North America, Europe and many parts of Asia.

Why use LORAN-C? The advantages are clear.

The FS700 delivers Cesium clock performance without the high price and maintenance costs of an atomic standard. Additionally, the FS700 provides dependable reception and higher stability than WWVB and GPS systems.

The FS700 LORAN-C Frequency Standard is the optimum, cost effective solution for all your frequency management and calibration needs. Contact SRS for more information on the FS700 and our complementary line of high resolution synthesizers and precision counters.

- **10 MHz NIST traceable standard**
- **Cesium long-term stability ( $10^{-12}$ )**
- **$10^{-10}$  short-term stability ( $10^{-11}$  optional)**
- **Four 10 MHz sinewave outputs**
- **Variable frequency output (TTL)**
- **Phase comparator for calibrating external timebases (0.01 Hz to 10 MHz)**

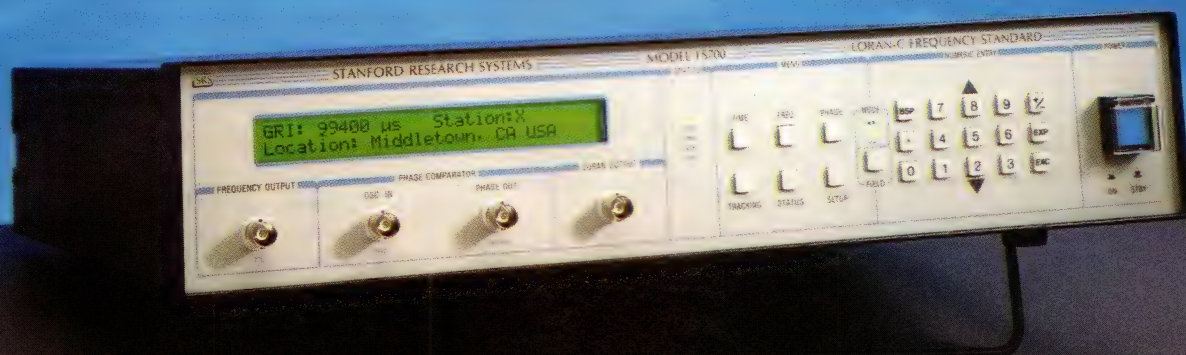

**FS700 - The Optimum Frequency Management System**



**STANFORD RESEARCH SYSTEMS**  
1290-D Reamwood Avenue, Sunnyvale, CA 94089  
TEL (408)744-9040 • FAX (408)744-9049

CIRCLE NO. 13



# CONTACT CLEANERS ARE NOT CREATED EQUAL


## ProGold™

### ADVANCED CONTACT TREATMENT

- Improves Conductivity
- Maintains Optimum Signal Quality
- Reduces RFI & Intermittents
- Seals & Protects Surfaces
- Reduces Wear & Abrasion

Even the finest equipment cannot guarantee noise-free/error-free operation. One "dirty" connection anywhere in the signal path can cause unwanted noise, distortion and signal loss. Considering the hundreds (if not thousands) of connections in electronic equipment today, it is only a matter of time before they begin to fail.

Use what the  
Manufacturers  
Use!

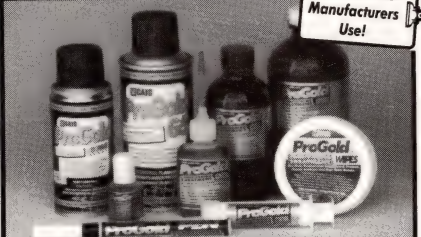

Environmentally-Safe/Non-Flammable Wipes, Pens & Precision Dispensers - Ideal for Service Techs


### How Does ProGold Actually Work?

ProGold outperforms all other contact cleaners, enhancers and lubricants. Due to its unique properties, it deoxidizes and cleans surface contamination, and penetrates plated surfaces and molecularly bonds to the base metals - **NO OTHER PRODUCT DOES THIS.** ProGold fills the gaps in the contact surfaces, increasing the effective surface area and current flow (conductivity).


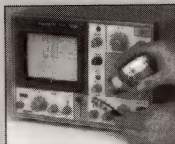
### Why Use ProGold?

ProGold increases the performance and reliability of all probes, connectors, switches & equipment. It improves conductivity for greater reliability, repeatability and reduces noise & interference and lowers distortion. Unlike other products, it also stabilizes connections between similar and dissimilar metals. ProGold is available in many convenient non-flammable and environmentally-safe applications that are ideal for use by service techs worldwide.



CAIG Products ... used by those who demand the best!

Beckman Inst.	Hewlett Packard	Johnson Controls	Texas Instruments
Diebold, Inc.	Honeywell	Motorola	Wayne-Dresser
E.I. DuPont	IDI, Inc.	Switchcraft	Xerox Corp.
General Electric	John Fluke Mfg.	Tektronix	... & many more!

Since 1956

**CAIG**  
LABORATORIES, INC.

16744 West Bernardo Drive  
San Diego, CA 92127-1904  
TEL: 619 / 451-1799  
FAX: 619 / 451-2799

**1-800-CAIG-123**

**CIRCLE NO. 47**

**EDN**

**TEST & MEASUREMENT**

TUV. The 3½-digit, 4000-count multi-meter measures true-rms ac voltage and current, dc voltage and current, resistance, frequency, capacitance, continuity, and diode test. It costs \$199. **Fluke Corp.**, Everett, WA. (206) 347-6100.

**Circle No. 376**

**16-bit data-acquisition boards for ISA bus have 10-μsec scanning per channel.** The DaqBoard/200A provides 16 channels, expandable to 256 while maintaining the 10-μsec per channel scanning speed. The board also provides a 512-position sequencer for selecting the analog channel sequence and gain value in any order. The board has two 12-bit analog output channels supporting sample rates to 500k samples/sec, a high-speed 16-channel digital I/O port, a 24-bit general-purpose digital I/O port, and five independent 16-bit counter/timers. The board costs \$1195. The DaqBoard/216A offers the same data-acquisition features without the digital I/O and counter/timers; it costs \$995. **IOtech Inc.**, Cleveland, OH. (216) 439-4091.

**Circle No. 377**

### Extenders for ISA bus provide hot-swap and other debug features.

The PC/AT150 extender for 8-bit ISA bus and the PC/AT200 for 16-bit ISA bus cards let you add and remove cards without turning off the system power. The feature adds a 250-psec propagation delay and a 4Ω on-resistance, causing minimal degradation in performance for the board under test. The extenders also provide short-circuit protection and current limiting to avoid motherboard damage. The extender generates a power-on reset signal whenever the extender board is turned off and on. DIP switches let you selectively isolate signals for debugging. The PC/AT150 costs \$295, and the PC/AT200 costs \$345. **Catalyst Enterprises Inc.**, San Jose, CA. (408) 268-4145.

**Circle No. 378**


**64-Mbyte oscilloscope-memory option accommodates waveform processing of long records.** The 930X-64 option for the company's 9300 series digital oscilloscopes lets you perform integration, differentiation, FFT, square, square-root, log, and exponential functions and use six selectable digital filters on data records up to 8 Mbytes long. The option costs \$3500 and can be retrofitted into pre-

viously delivered oscilloscopes. **LeCroy Corp.**, Chestnut Ridge, NY. (914) 425-2000.

**Circle No. 379**

**Pen-style DMM has 4200-count display.** The DM73A has a reading-hold feature to freeze a reading. It also automatically holds maximum voltage readings and minimum resistance readings. The meter has an automatic shut-off for extended battery life. It is designed to UL and EN (IEC) agency safety standards. \$69.95. **Wavetek Corp.**, San Diego, CA. (619) 279-2200.

**Circle No. 380**

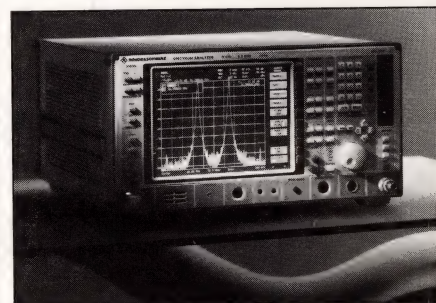

**Fast spectrum analyzers cover frequencies from 20 Hz to 3.5 GHz.** The FSEA 20 spectrum analyzer operates from 9 kHz to 3.5 GHz and costs \$29,995. The FSEA 30 spectrum analyzer covers frequencies from 20 Hz to 3.5 GHz and costs \$43,895. Specifications include a resolution bandwidth of 1 Hz to 10 MHz, an intermodulation-free dynamic range of 113 dB, a noise floor of -145 dB for a 10-Hz bandwidth, and a phase noise of -123 dBc/Hz at 10-kHz offset. The instruments evaluate the performance of mobile communications systems. **Rohde & Schwarz** developed the analyzers, which Tektronix market and support in the United States and Canada. **Tektronix Inc.**, Beaverton, OR. (800) 426-2200.

**Circle No. 381**

**Tool creates boundary-scan-description-language files from Verilog netlists.** BSDLMaker compiles structural Verilog netlists and package pin files, performs 1149.1 design-compliance checks, and generates a boundary-scan-description-language (BSDL) file. The tool also provides a warning- and error-message file and a debug file. You can configure the tool to accept primitives and macro-cells from multiple silicon vendors, such as LSI Logic, TI, VLSI, and others. The software costs \$6750 for PCs and



\$8100 for the Sun SPARC. **Intellitech Corp.**, Meredith, NH. (603) 279-6308.

**Circle No. 382**

**PC software lets you document, archive, analyze, and create waveforms for test instruments.** Any-Wave 2.0 is for the company's ScopeMeter, CombiScope oscilloscopes, and ARB generators. The software lets you create waveforms from scratch using a mouse or modify waveforms captured by an oscilloscope. You can use the waveforms in the PM 5150 arbitrary waveform generator or on the oscilloscopes for pass/fail testing. The software communicates to the instruments through RS-232C or IEEE-488 interfaces and costs \$295. **Fluke Corp.**, Everett, WA. (206) 347-6100.

**Circle No. 383**



**Cart holds logic analyzers and oscilloscopes.** The HP 1183 Testmobile holds the HP 54620A logic analyzer and the HP 54600 oscilloscopes. A locking system attaches the instrument to the cart. You can lock the tray holding the instrument into various positions. The tray also has a holder for scope probes. The cart costs \$495. **Hewlett-Packard Co.**, Santa Clara, CA. (800) 452-4844, ext 9422. **Circle No. 384**

**Computer-aided-experiment design package for Windows.** The Computer Aided Research and Development (CARD) software suits use by scientists and engineers working in product, process, and quality R&D. The tool helps you design experiments to

get the information you need from the experiment. It handles multilevel experiments with mixture variables and multiple constraints. The software costs \$495. **Westing Software**, Corte Madera, CA. (415) 945-3870.

**Circle No. 385**



**Compact power meter has wide power level and frequency coverage.** The Model 4220 power meter covers frequencies from 100 kHz to 100 GHz and measures power from -70 to +44 dBm. Dynamic range is up to 90 dB with diode sensors and 50 dB with thermocouple sensors. The meter fits into a half-rack panel, making it suitable for production automatic-test-equipment environments. It costs \$2150. **Boonton Electronics Corp.**, Parsippany, NJ. (201) 386-9696.

**Circle No. 386**

**Bus analyzer for IDE/ATA packet interface.** The ID-520 IDE/ATAPI bus analyzer has 32 ATbus-attachment (ATA) channels plus four general-purpose channels. It has a 50-MHz sampling frequency, a 1-million-event capture buffer, and the ability to capture continuously to disk. The board and Windows-based software cost \$6500. **Innotec Design Inc.**, Buena Park, CA. (714) 522-1469.

**Circle No. 387**

**Low-cost programmer for Xilinx EPLD devices.** The XPGM programmer for erasable PLD (EPLDs) and serial configuration PROMs (SPROMs) costs \$295. Xilinx certifies the programmer to meet the programming criteria for all of the current EPLD and SPROM product lines. The programmer is an ISA bus card that connects with an external programming socket via a 30-in. ribbon cable. It comes with adapters for 44-pin PLCC packages and eight-pin DIP packages. Adapters for other packages cost \$99 to \$199. **Deus Ex Machina Engineering**, St Paul, MN. (612) 645-8088.

**Circle No. 388**

## Plug and Play GPIB



### AT-GPIB/TNT (Plug and Play ISA)

- PC system configures hardware resources on boot up; no jumpers or DIP switches
- Maximum GPIB transfer rates
  - 1.5 Mbytes/s using IEEE 488.1 handshake
  - 3.4 Mbytes/s using HS488 (EISA)
- TNT4882C™ IEEE 488.2 Controller ASIC

### PCMCIA-GPIB

- Type II PCMCIA card
- Compliant with PCMCIA PC Card Standard 2.0 and above
- Hardware resources automatically configured when inserted
- TNT4882C IEEE 488.2 Controller ASIC for low-power operation



### Cross-Platform Software Compatibility

- Industry-standard NI-488.2™ software for DOS and Windows
- Configuration and development utilities
- Simple migration path to new Plug and Play operating systems

**For more information on Plug and Play GPIB and a FREE catalog, call (800) 433-3488**  
(U.S. and Canada)



**NATIONAL INSTRUMENTS™**  
*The Software is the Instrument®*

6504 Bridge Point Parkway • Austin, TX 78730-5039  
Tel: (512) 794-0100 • Fax: (512) 794-8411

E-mail: info@natinst.com

**Come to NI Week, July 23-28**

© Copyright 1995 National Instruments Corporation. All rights reserved. Product and company names listed are trademarks or trade names of their respective companies.



**FREE INFO, FREE POSTAGE**

Use our postage-paid reader-service cards to get more information on any of these products.

**Catalog for system-power products.** A catalog features technical information on a range of products, including alternate current sources, dc power supplies, and electronic loads. The 66-pg guide contains application information, dimension drawings, photos, and product specifications. **Hewlett-Packard Co**, Santa Clara, CA. **Circle No. 350**

**Brochure presents power supplies for displays.** A guide for a line of information-display power supplies includes dc/ac inverters for cold-cathode-fluorescent-tube, backlit LCDs. The brochure features a line of dc/dc converters for applica-

tions such as gas-plasma displays. **Endicott Research Group**, Endicott, NY.

**Circle No. 351**


**Interactive catalog on disk.** This interactive computer program guides users through the selection and configuration of a line of power supplies, including modular components and configurable systems. The catalog includes power-system accessories. **Vicor Corp**, Andover, MA. **Circle No. 352**

**Hypertext Markup Language pocket reference.**

A reference card details the Hypertext Markup Language, the language of the World Wide Web. The fold-out card shows how to format a Hypertext document for use with the World Wide Web, including how to lay

out text and how to set up headers, titles, and tables. The guide also describes the types of forms, how to set up a point-and-click mat, and how to include anchors, sounds, and images. \$4.50. **Specialized Systems Consultants Inc**, Seattle, WA.

**Circle No. 353**

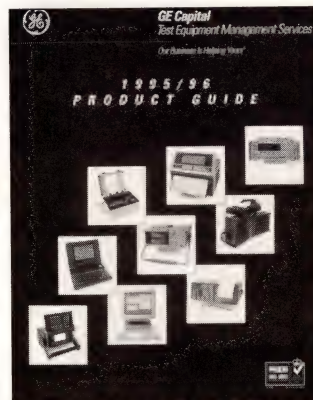

**Test-equipment product guide.** This catalog features rental equipment for testing power-transmission and distribution, communications, industrial-plant operations, and microwave/RF systems. The guide describes the company's one-source repair, calibration, and certification services. **GE Capital Test Equipment Management Services**, Norcross, GA.

**Circle No. 354**

**Trimmer-capacitor catalog.** This 34-pg catalog describes a line of glass, quartz, air, and trimmer capacitors. The guide details sample kits, tuning tools, and design capabilities. **Voltronics**, Denville, NJ.

**Circle No. 355**

**Catalog features components.** A detailed catalog offers specifications for a product line, including triacs, SCRs, rectifiers, and diacs. The guide provides diagrams, application notes, and a cross-reference guide. **Teccor Electronics Inc**, Irving, TX.

**Circle No. 356**

**Handbook covers Windows software.** This guide highlights software under DT-Open Layers for Microsoft Windows 95 Plug-and-Play. It covers numerous programming tools, a new high-level DSP language and compiler, and visual-programming applications. **Data Translation**, Marlborough, MA.

**Circle No. 357**

**Satellite-wire-and-cable guide.** This free guide highlights lightweight wire and cable for commercial, military, and NASA satellites. The brochure details a radiation-cross-linked insulation system. **Raychem**, Menlo Park, CA.

**Circle No. 358**

**Catalog details sensors.** This catalog provides diagrams, dimensions, and specifications for a line of photoelectric sensors. The guide includes a detailed accessories guide. **Aromat Corp**, New Providence, NJ.

**Circle No. 359**

**Guide for Teflon pc-board prototypes.** *What Does it Take to Get a Good Teflon Circuit Board Prototype Around Here?* is a guide to fabricating Teflon prototypes. The guide details a Teflon prototyping service for microwave and wireless-applied pc boards. **Southwest Circuits**, Tucson, AZ.


**Circle No. 360**

**Power-switches and regulators data book.** This catalog contains data sheets on more than 50 devices, including single- and dual-output linear regulators, switching regulators, and power-supply-control ICs. The guide features an expanded section of application notes on topics such as hysteretic mode control. **Cherry Semiconductor**, East Greenwich, RI.

**Circle No. 361**

# SCSI 1&2
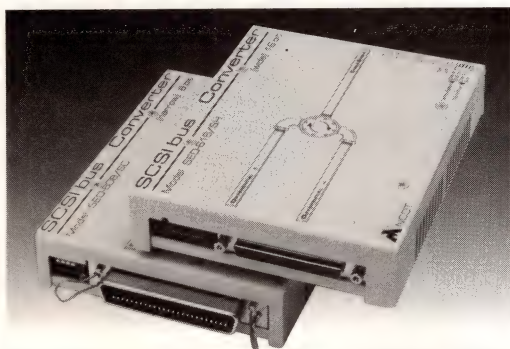
## SE-Diff CONVERTERS & SCSI bus EXTENDERS



Tel: (415)322-5322

Fax: (415)322-0455

**ANCOT**  
CORPORATION

115 Constitution Drive, Menlo Park, CA 94025

**CIRCLE NO. 49**



# EDN PRODUCT MART

This advertising is for new and current products.

Please circle Reader Service number  
for additional information from manufacturers.

## DECISION IS YOURS!

as to who gives you the best value?

**FR4 Multilayer Boards 1-5 Day Turn**

QUANTITY	2	5	10
15	\$186	\$245	\$310
30	210	280	352
60	248	330	415
90	285	380	486
120	305	415	519

QUANTITY	2	5	10
15	\$715	\$950	\$1175
30	795	1040	1350
60	890	1190	1425
90	995	1355	1710
120	1048	1480	1860

**SERVICES**

- Same day Prototype
- Hi-Volume Production Runs
- Instant Quotes
- Complete CAD/DFM Service
- Deep Tank Gold & Palladium
- 24 Hour Modems
- Gerber/AutoCad/HPGL/P-CAD
- SMT & Thru Hole Assembly
- Stencil


EXTRAS • Photoplotting  
• Gold \$50.00 • Testing

**Accutrace Inc.**

CALL US TODAY AT  
408-748-9600

CIRCLE NO. 250

## 486 Single Board Computer

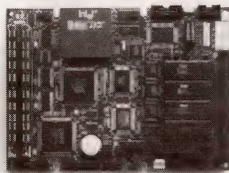


- All-In-One features and size only 5.75" x 8"
- 486DX2-66/486DX-33/486SX-33 CPU
- On board RAM/ROM disk sockets
- Built-in Ethernet, VGA/Flat Panel interface
- On board enhanced IDE, serial and parallel
- Watchdog timer, PS/2 mouse and K/B port
- PC/104 socket and Up to 32MB DRAM

**Ideal SBC for OEM  
Advantech, 800-800-6889**

750 East Arques Ave., Sunnyvale, CA 94086  
Tel: 408-245-6678, Fax: 408-245-8268

CIRCLE NO. 251

## UNIVERSAL/GANG PROGRAMMERS

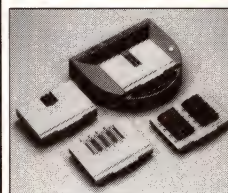

### FLEX-700

48 pin from \$945  
40 pin from \$845  
8 gang from \$845  
TUP-400 \$695  
TUP-300 \$545

Appreciated by over 70,000 users worldwide

- Supports Altera 7xxx, MACH 435, Xilinx, Intel FX7xxx, nearly all FPGA/CPLD/PLD...
- Support EPROM, 28/29F flash, serial PROM, PSD4XX/5XX, Intel/Motorola/NEC/Hitachi MPU devices. Over 3,000 devices supported.
- Test TTL 74/40/45 series, DRAM (SIP/SIMM), and SRAM. EPROM EMULATION option.
- Gang programming & stand alone option.
- Universal 44,68 pin PLCC modules.

## 8051 IN-CIRCUIT EMULATORS

### NICE-51 SYSTEMS FROM \$895

- Supports 87(C)51 and many derivatives.
- Fully supports emulation of internal and external memory with no intrusion on user memory, I/O, stack, INT...
- Supports Archimedes, Franklin, Intel, IAR, KEIL, 2500AD.... C compilers and most assemblers.
- Single step, go slow, run in real time, set break-points and much much more...
- Complex trigger and filter functions let you trace in real time all or any portion of program execution you desire (up to 16K 48bit words).

## ROM/RAM EMULATORS

### TRE/EML SYSTEMS FROM \$195


- Emulate up to two 27(C)64 - 27(C)1010 devices at one time in independent or 16 bit even/odd mode.
- Emulate one 27C020, 27C1024, 27C2048.

## EPROM PROGRAMMER FROM \$145



**Tribal Microsystems Inc.**  
44388 S. GRIMMER BLVD., FREMONT, CA 94538  
Tel: (510) 623-8859  
Fax: (510) 623-9925

CIRCLE NO. 255

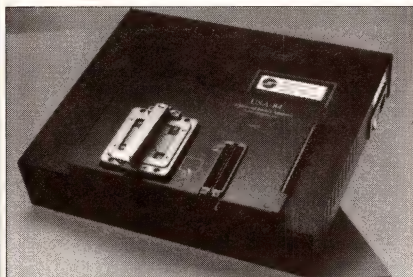

### PILOT-U84 Universal Programmer

#### #1 in New Device Support & Expandability

If Data I/O cannot support you or your devices, please call us. We support the newest devices from Altera, AMD, Atmel, Cypress, Intel, Lattice, NEC, Microchip, Motorola, NEC, Philips, WSI, Xilinx, etc.

All packages types: PLCC, PGA, QFP, TQFP, TSOP, SOIC, etc.  
800-627-2456, 408-243-7000, FAX: (408) 736-2503

CIRCLE NO. 253

## EXPRESS

Best Value in the World

**POLYIMIDE & FR4  
1 to 5 DAY TURN**  
1 to 12 Layers

PRINTED CIRCUIT PROTOTYPES

2 PIECE PRICES FOR FR4 .062 Th.						
LAYERS		1	2	3&4	5&6	7&8
SQUARE INCH UP TO	15	\$233	\$292	\$639	\$787	\$935
	30	264	330	724	891	1059
	60	311	389	853	1049	1137
	90	358	448	980	1207	1434
	120	385	486	1044	1311	1559

■ 5 PIECES x 1.34 ■ 5 DAY PRICES ABOVE  
■ 10 PIECES x 1.67 ■ UL LISTED

EXTRAS CAPABILITIES DISCOUNTS

- Photo Plotting
- Testing
- Gold Contacts - \$50
- 25% - Below 8 Mil Hole
- Below 15 Mil Hole
- SMOBC & LPI - \$50
- Buried & Blind Vias
- Polyimide Multilayer
- Full Body Gold
- Carbon Paste
- Tin nickel burn-in boards
- SMT-SMOBC
- Up to 22 layers
- Impedance control boards
- 5%
- COD
- 10%

FOR MORE INFORMATION CALL OR FAX

Ken Bahl ■ 1108 W. Evelyn Ave., Sunnyvale, CA 94086  
Phone (408) 735-7137 FAX (408) 735-1408 Modem (408) 735-9842


CIRCLE NO. 254

To advertise in Product Mart, call Joanne Dorian, 212-463-6415


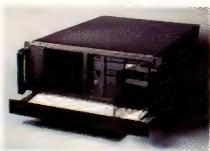
## Redundant PC/AT

Multilevel Fault Tolerant System  
Yields Ultimate Application Protection



### "STAIRS"

#### Standby Fault Tolerant Active Intelligent Redundant System

STAIRS was designed to meet the most stringent system requirements, for example: chemical process control, nuclear power regulation, air traffic control or file server applications. In short any task that can not be allowed to fail needs STAIRS!

#### ★ Some Of The Many Features ★

- Hot Swap, Load Sharing, Redundant Power Supplies
- Drive Mirroring With Instant Drive Fail Alarm
- Redundant CPUs
- Proprietary 28 Bit Intelligent Passive Backplane
- g4K System Mail Box For Inter CPU Communication
- Local & Remote Alarm Reporting For System Failures
- Operating System Independent

Send For Our New 1995 Catalog

**ZENDEX**

Leaders In Industrial Computer Products Since 1979

6780A Sierra Court  
Dublin, CA 94568  
PHN 510 828 3000  
FAX 510 828 1574

CIRCLE NO. 256

## UNIVERSAL PROGRAMMER

AllMax+ (Parallel Port version) \$745  
AllMax (Plug-in Card version) \$645



- AMD MACH, ALTERA MAX, PAL, GAL, XILINX EPLD, PROM, EPROM, FLASH, MOTOROLA MCU, etc.
- TESTS TTL/CMOS, DRAM, SRAM
- 48-PIN GOLD-ZIF socket
- Lifetime FREE S/W UPDATES
- 2-Yr Warranty, Made in U.S.A.
- FREE PLD COMPILER




Electronic Engineering Tools

544 Weddell Dr., Suite 6  
Sunnyvale, California 94089  
(408) 734-8184, 734-8185 FAX

CIRCLE NO. 257
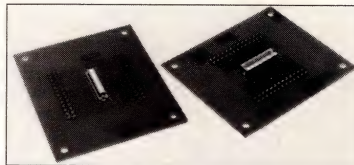
## STACKING CONNECTOR WITH 0.026" SPACING AND UP TO 50-POSITIONS



Hirose is offering the DF15, an ideal connector for supporting internal mounting of components in portable telephones, HDD, PCs and PDA drives. The DF15 easily meets today's requirements for lower-cost, higher-density, SMT board-to-board connectors. Hirose's DF15 features tight 0.65mm (0.026") spacing and stacking heights ranging from 4mm to 8mm in 1mm steps. Available with 20, 30, 40 and 50 positions, the DF15 offers a gull wing type design for secure PCB contact to assure reliable performance.

Hirose's board-to-board family offers numerous choices, including the DF9, with 1mm spacing, the DF12 with tight 0.5mm spacing, and the FX6 with 0.8mm spacing.




Hirose Electric (U.S.A.), Inc.,  
2688 Westhills Court, Simi Valley, CA 93065,  
(805) 522-7958, Fax: (805) 522-3217. For a fax  
catalog: 1-800-879-8071. Ask for #5021.

CIRCLE NO. 258

## THINK ACQUISITION THINK MCSI

"The Embedded PC Specialists"

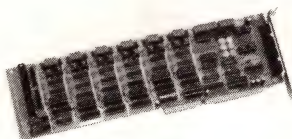


- ADCLONE® Data Acquisition boards include multichannel A/D & D/A and Digital I/O
- Full line of Multi I/O, Timer, and Relay Boards
- Full line of ISA and PCXI CPU boards to 100MHz
- 3 to 20 slot Embedded and Rack Mount Chassis
- 3 to 20 slot ISA and PCXI passive backplanes

Call now for our Special "Get Embedded Offer"

**MCSI** 2598 fortune way  
vista, ca 92083  
619/598-2177  
fax 619/598-2450

CIRCLE NO. 259

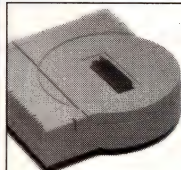

2 New Versions!

**ChipLab**

Data I/O® quality and reliability  
at a price you can afford.

- **ChipLab Memory/Micro** programs a broad range of memory and microcontroller devices for just \$995\*.
- **ChipLab Logic Plus** programs more than 1900 logic and memory devices for only \$1495\*.
- **Optional adapters** support PLCC, SOIC, QFP, and TSOP packages.

To order call 1-800-3-DATAIO Ext. 901  
(1-800-332-8246)

\*U.S. list price only.

**DATA I/O**


CIRCLE NO. 260

## WIN THE FPGA MATCH

with

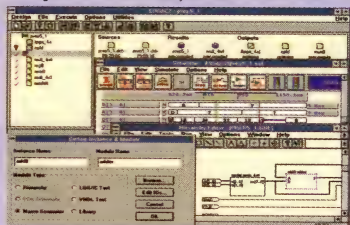**LOGIC2**

Vendor independent design  
system for FPGAs, CPLDs and PLDs



ISDATA GmbH · Daimlerstraße 51  
D-76185 Karlsruhe · Germany  
Phone (+49) 721 / 75 10 87 · Fax 75 26 34  
email: isdata@isdata.de

**ISDATA**

CIRCLE NO. 262

## LTS-2020

PCLTS Accelerator for the LTS-2020 Tester



The PCLTS system is a complete hardware and software upgrade for the LTS-2020 tester which brings the machine up-to-date in speed, development tools and user interface.

#### SPEEDS UP TEST PROGRAMS UP TO 10 TIMES!

- CPU emulator board brings LTS to 486 PC platform
- Test programs written in industry-standard C language
- LIS-Basic-to-C conversion program included
- Full LIS Basic instruction set has been ported to C
- 100% compatible with all existing test hardware
- Industry-proven: over 30 systems in use world-wide



Ph: (408) 253-1353  
Fax: (408) 253-2533  
calyx@ix.netcom.com

599 N. Mathilda Ave., Suite 34, Sunnyvale, CA 94086

CIRCLE NO. 263

## Membrane Switch Components




The adhesive that holds together the layers of your membrane switch can ultimately spell the success or failure of the products you design. That's why you should specify the adhesive components for your switch. Right now, 3M is offering a free information packet on membrane switch assembly systems. Call 1-800-455-4363, ext. 9501, or write 3M Identification and Converter Systems Division, 10701 Hampshire Avenue South, Minneapolis, MN 55438.

**3M Reliability**

CIRCLE NO. 264




## 200MSa/s Digital Oscilloscope

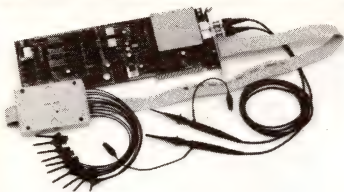

- 200 MSa/s Sampling Rate
- up to 128K Samples/Channel
- PC-BASED INSTRUMENT
- 2 Analog Channels (2 ch. Oscilloscope)
- 8 Digital Channels (8 ch. Logic Analyzer)
- All 10 channels can be used at same time
- Simultaneous use of all 10 channels
- Cross Triggering of Digital and Analog
- 125 MHz Single Shot Bandwidth

**\$1799** DSO-28200 (200MSa/s, 4K/Ch)  
**\$2285** DSO-28264 (200MSa/s, 128K/Ch)

## 400 MHz Logic Analyzer

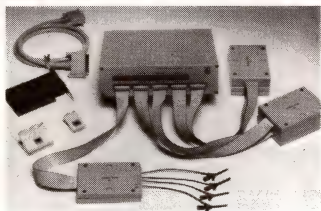


- up to 128 Channels
- up to 400 MHz
- up to 16K Samples/Channel
- Variable Threshold
- 8 External Clocks
- 16 Level Triggering
- Pattern Generator (Option)

**\$1299** - LA32200 (200 MHz, 32 Ch) Pods & Software  
**\$1899** - LA32400 (400 MHz, 32 Ch) included  
Also Available:  
**\$799** - LA12100 (100 MHz, 24 Ch, TTL only)
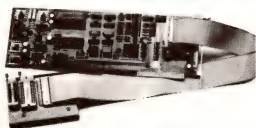
## Universal Programmer

PAL - GAL - MICRO  
EPROM - EEPROM - FLASH



**\$475**

Call for full device support list

Free software updates on BBS

**Call (201) 808-8990**




Link Instruments

369 Passaic Ave., #100, Fairfield, NJ 07004 fax: 808-8786

CIRCLE NO. 269

To advertise in Product Mart, call Joanne Dorian, 212-463-6415

## SOIC TO DIP

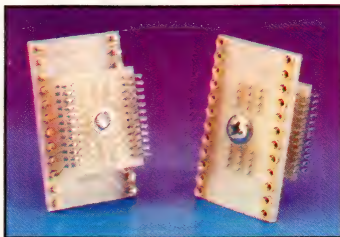

### WITH DIP/SOIC PACKAGE CONVERTER

- Convert surface mounted SOIC pattern to DIP.
- Solder to SOIC Land Pattern.
- Then plug DIP IC into DIP socket.
- DIP pins are gold plated machined pins.
- Multiple sizes available

**IRONWOOD ELECTRONICS**  
P.O. BOX 21151, ST. PAUL, MN 55121  
(612) 431-7025; FAX (612) 432-8616

CIRCLE NO. 265

The Premier Reliability Software

## Relex

"the intuitive  
... solution!"

New!  
v5.2 for  
Windows  
& Mac

- Reliability Prediction
  - MIL-HDBK-217
  - Bellcore
  - Parts Count
  - Mechanical
  - CNET
- FMEA, FMECA
- Maintainability

Use the Relex Reliability Software to evaluate and pinpoint areas for potential reliability improvement. Quickly calculate your system MTBF using the powerful CAD interface, impressive graphics, and unmatched friendliness. And choose from Windows, Mac, and DOS versions!

Call 412-836-8800 Today For More Information!


**Innovative Software Designs, Inc.**

One Country Drive, Suite 1000  
Greensburg, PA 15601 USA

412-836-8800  
FAX 412-836-8844

CIRCLE NO. 267

## JUNCTION TEMPERATURE!

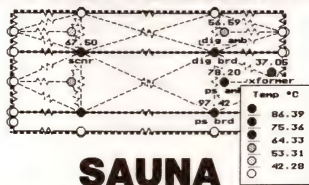

### SAUNA

a better way to deal with heat

- Interactive menu-driven.
- Models: enclosures, plates, circuit boards, heat sinks.
- Analyze the whole system.
- All heat transfer modes.
- Powerful edit features.
- Thermal parameters library.
- English language design summaries.
- IBM PC & Macintosh II.

Call For Free Evaluation Kit

**Tatum Labs, Inc.**  
1287 N. Silo Ridge Dr., Ann Arbor MI 48108 USA  
313-663-8810

CIRCLE NO. 270

## Thin Lithium Batteries



- As thin as 0.6mm
- Thin rectangular format
- Customized capacity
- Solder or pressure contacts
- Available in 3 and 6 volt

**POWERDEX** family of products:

- Standard: A, B, C sizes
- Ultrathin: less than 1 mm
- Customized: capacity and/or size
- Rechargeable: call for information

**Gould Electronics Inc., Electronic Power Sources**

35129 Curtis Blvd. Eastlake, Ohio 44095-4001, USA  
Phone: (216) 953-5059 Fax: (216) 953-5152  
Toll Free: 1-800-722-7890 (U.S. & Canada)



CIRCLE NO. 266

**NEW**

**Stand Alone  
or RS 232 Host  
Device Programmer**

**\$795**

SOCKET ADAPTERS  
NOT INCLUDED

**XPRO™**

- Stand Alone or RS 232
- Gang 8 EPROM Option
- EE/EPROM to 16 Meg.
- DIP, PLCC, QFP, and other socket technologies
- PLDs and FPGAs
- DOS/Windows 3.0 / 3.1
- Wafer-scale PSD
- Microchip PIC
- Motorola Micros
- All Xilinx Devices Supported
- Free Software Updates
- Compact & Portable

**800 315-7766**  
303 279-6868  
EAST COAST REGION:  
800 331-7766

**LOGICAL  
DEVICES, INC.**

CIRCLE NO. 268

**\$79**

QTY 1

**Micro  
Genius™**

Smaller than a credit card and C-programmable! Ask for our free Dynamic C™ demo disk. Call our AutoFAX 916-753-0618 from your FAX. Request catalog #18.

ADC  
RS232/RS485  
Flash EPROM  
Parallel I/O  
Real-Time Clock  
Power Supply

**ZWORLD  
ENGINEERING**

1724 Picasso Ave.  
Davis, CA 95616  
916.757.3737  
916.753.5141 FAX

CIRCLE NO. 271


EDN JULY 6, 1995 • 157





## FlexROM plus™

Flexible Emulation

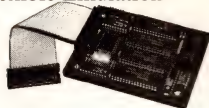

## EconoROM™

Economical Emulation



- Engineered from the ground up to support target independent, hardware assisted debugging through your target's memory socket.
- Dual-port architecture enables **REAL-TIME WATCHES**, Virtual UARTs, Virtual CONSOLE paths and Dynamic mode operation.
- Zero wait-state operation to 35ns.
- Single unit supports **PC, MAC, SUN** and other HOSTS.
- Options include complex triggers, trace buffers, and hardware breakpoints.
- Drivers available for popular source-level debuggers.
- FLASH support to 29F040
- EPROM support to 27C040
- Full-screen ASCII/HEX editor/downloader permits on-the-fly modifications.
- Command line driven (batchable) downloader.
- View/Edit contents with target running.
- Supports TARGET read/write access.
- Libraries included for direct READ/WRITE access.
- Download AND verify from PC printer port.
- Field upgradable to 4Mbit (27C040) emulation.
- Battery back-up & PLCC adapters available.

Starting at \$595

0K/1M/2M/4M  
\$319/\$349/\$379/\$439

starting at  
**\$149**

**CALL or FAX  
for details!**

**(214) 272-9392  
FAX: 494-5814**




90 Day  
Warranty  
10 Day  
Money-Back  
Guarantee

## Low Cost 16-bit Controllers PCMCIA ?
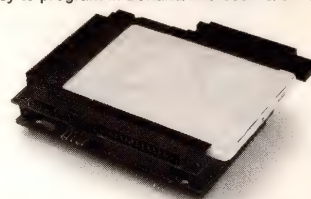
### V25-Engine™ & MemCard™

Prices start at **\$99+\$99** Qty 1  
Easy to program in Borland/Microsoft C/C++.



- 3.6 x 2.3 x 1.1", 68 pin PCMCIA mem or I/O.
- 32 Mb PCMCIA, 1 Mb Flash, 512K SRAM.
- 11 12-bit ADC, 3 UART, 3 timers/counters.
- 32 I/O, RTC, low power, 4 mA standby.



216 F St. #104, Davis, CA 95616 USA  
Tel: **916-758-0180**  
Fax: **916-758-0181**  
Internet Email: [tern@netcom.com](mailto:tern@netcom.com)  
<http://ftp.netcom.com/pub/te/tern>

CIRCLE NO. 272

CIRCLE NO. 273

## MICROPROCESSOR EMULATORS

Zax provides a comprehensive series of real-time emulation support for Motorola, Intel, NEC, Zilog, and Hitachi microprocessors. Some of the highlighted features include source-level debug, real-time trace, and performance analysis.

Call now for more information:

(800) 421-0982  
(714) 474-1170 (Inside CA)  
(714) 474-0159 (Fax)

**ZAXTEK**


42 Corporate Park Irvine, CA 92714

CIRCLE NO. 274

## EZ-ERASER




**\$9900**

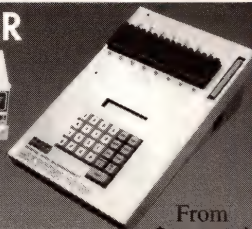

From  
**\$895\***

**FIREMAN**  
A better gang/set  
programmer . . . for less.

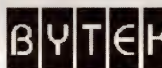- Supports EPROMs, FLASH, Motorola & Intel Micros in DIP, PLCC, QFP, SOIC
- 40 Character LCD, 2M RAM, 2M Flash
- **FASTEST** MultiMatrix™ programming  
1 Meg 15 sec. 4 Meg 60 sec.
- Full Keypad or PC operations
- High-speed download **standard**
- Available from Marshall — 1-800-432-2223



Order now:  
**1-800-523-1565**

Fax: 407-994-3615 \* U.S. list

CIRCLE NO. 275

**Consistency  
is  
key**

**to the power of  
EDN Product Mart**

CIRCLE NO. 276

## Plug in HERE ➡

to Maximize the  
Value of Your Oscilloscope!



## NEW SuperProbe™

Oscilloscope  
Triggering Devices

- Complex triggering for digital circuits
- Easy to use
- Simplifies circuit debugging
- Works with any oscilloscope
- Models start at only \$99

PROGRAMMABLE  
DESIGNS  
INC.



41 Enterprise Drive ■ Ann Arbor, MI 48103  
Phone: (313) 769-7540 ■ Fax: (313) 769-7242



A Complete Line of Development Boards,  
Programmers and In-Circuit Emulators



**CEIBO**

For more information call us today

**1-800-833-4084**

CompuServe 100274,2131

U.S.A. Tel: 314-830-4084 Fax: 314-830-4083  
Germany Tel: 06151-27505 Fax: 06151-28540  
Israel Tel: 972-9-555387 Fax: 972-9-553297

CIRCLE NO. 278

Nichicon "Posi-R" Thermistor  
provides **self-resetting overcurrent  
and overheating protection.**

The "Posi-R" Thermistor line from Nichicon provides reliable self-resetting circuit protection from overcurrents and overheating inflows that commonly affect computers, telecommunications equipment, color televisions, alarm systems, motor controls, and many other similar applications.

- ZPC Series limits current during overcurrent situations, returns normal current when fault subsides.
- ZPB and ZBK Series for automatic circuit degaussing.
- ZPH Series non-contact control device used in small-power heaters.
- ZPD Series brings automatic resetting to overcurrent and overtemperature protection in home appliances.
- ZPP Series adds thermal protection for power transistors and thyristors in power sources.

For a free "Posi-R" catalog call, fax or write:



Nichicon (America) Corporation  
927 E. State Parkway  
Schaumburg, IL 60173  
708-843-7500 • FAX 708-843-2798

CIRCLE NO. 279



# Macintosh® Users...

Call the leaders in Electronics CAD software on the Apple Macintosh for your schematic, PCB, simulation and PLD/FPGA design requirements.

Call  
Toll  
Free (800) 444-9064

fax: (604) 522-3972  
e-mail: info@capilano.com  
www: http://www.wimsey.com/capilano/


**Capilano  
Computing**

Macintosh is a registered trademark and Mac OS is a trademark of Apple Computer Inc.

CIRCLE NO. 280

Find out how you can break through the clutter to get big results for a small price, by placing a 4-color ad in EDN Product Mart. Call Joanne Dorian at (212) 463-6415 for details.

CIRCLE NO. 283

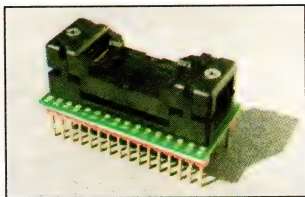

## TSOP adaptors

TSOP to DIP for programming  
■ for gang or single socket programmers  
■ for normal or reverse pin-outs

TSOP to DIP for breadboarding  
■ with solder tail or wire-wrap pins  
*Programming adaptors are also available for PLCC, SOIC, SOJ, PGA, & QFPs*


### EDI Corp.

2611 Highland Drive, Las Vegas, NV 89109  
Tel: (702) 735-4997 Fax (702) 735-8339

CIRCLE NO. 286

To advertise in Product Mart, call Joanne Dorian, 212-463-6415

## 1995 Full Line STD BUS Databook

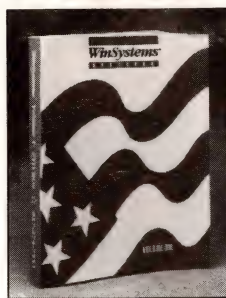


Call or Fax us today for your free 400-page Databook. Detailing over 200 STD Bus solutions for embedded & DOS-compatible applications, you'll find complete SBCs, I/O cards, card cages, & software tools ready for your project.

Call WinSystems for details!  
Phone: (817) 274-7553 • Fax: (817) 548-1358

CIRCLE NO. 281
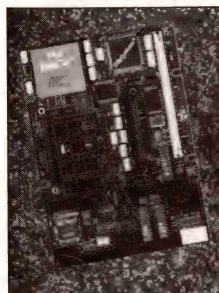
## Lowest Cost Industrial Embedded 486DX2/66 SBC




More than just a PC, the \$695 LBC-486DX/66 delivers maximum performance for industrial, telecom or medical applications. It features parallel, serial, IDE, FDC & keyboard controllers. Also watchdog timer, power-fail detection and bootable solid state disk support.

Call WinSystems for details!  
Phone: (817) 274-7553 • Fax: (817) 548-1358

CIRCLE NO. 284

## STD Bus Powered Racks & Backplanes

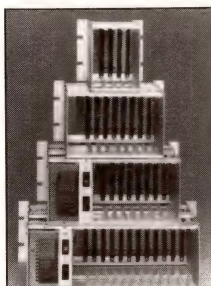

WinSystems' backplanes and assembled card cages provide the highest integrity and reliability needed for industrial applications. Based upon 0.625" or 0.75" vertical centers between card slots, these units are available from 2 to 26 card slots along with optional power supplies.

Call WinSystems for details!  
Phone: (817) 274-7553 • Fax: (817) 548-1358

CIRCLE NO. 287

# PLDs, CPLDs, FPGAs...

for the best in  
Programmable Logic Design  
Synthesis Software  
to suit any budget, call:

**M I N C**  
INCORPORATED

800 755 3742

Tel: 719 590 1155 • Fax: 719 590 7330 • E-Mail: salesinfo@minc.com

CIRCLE NO. 282

## 486 Single Board Computers & Rack Mounts

3 YEAR  
WARRANTY



8 Slot 486SX-25 4MB 170MB HDD .....\$1,495.00  
14 Slot 486DX-33 4MB 250MB HDD .....\$1,995.00  
20 Slot 486DX2-66 4MB 540MB HDD ...\$2,495.00  
PLEASE CALL FOR CUSTOM CONFIGURATIONS.

ORDER DESK 1-800-777-4875



**US LOGIC**

Made In U.S.A.

5055 Viewridge Ave., San Diego, CA 92123  
(619) 467-1100 • FAX (619) 467-1011

The Intel Inside Logo is a registered trademark of Intel Corporation.  
3 year warranty applies to Falcon-II Single Board Computer.

CIRCLE NO. 285



## iceMASTER-PE In-Circuit Emulators from \$851

New AET (patented) emulator architecture delivers incredible value!

**Melts  
the Price  
of 8051  
ICE**

- Up to 42 MHz Operation
- 128K Code/XDATA Memory
- 128K Hardware Breakpoints
- Optional 16K Transparent Trace (View Trace While Executing)
- Real Time & Nonintrusive
- Symbolic & Source-Level Debug
- Windowed User Interface
- Serial Link to Any PC
- 8031/8032/8X51/8X52
- 8XC51FX/87L51FB
- 8XC751/752
- DS80C320

Call today for  
FREE DEMO DISK!

(800) 638-2423

MetaLink Corporation  
Phone: (602) 926-0797 FAX: (602) 926-1198

CIRCLE NO. 288

EDN JULY 6, 1995 • 159



# DIGITAL WIZARDRY @ QUALCOMM

Sheer ingenuity and creative talent has propelled QUALCOMM into the forefront of America's fastest-growing companies. We've pioneered the application of Code Division Multiple Access (CDMA) to mobile/satellite communication systems and our engineers are forging technologies that will drive us into 21st Century.

Perform your magic in an environment where you'll grow as rapidly as your talent and drive will take you. Join us with one of the many areas of digital design, including but not limited to:

- Gate Array/Standard Cell/FPGA Design
  - Verification
  - Synthesis
- Embedded Processor Design

Your design will be used in large volume/power sensitive subscriber units as well as in very complicated switch/ground equipment.

We are committed to excellence and provide our engineers with a great environment and the latest in CAE technology.

## Engineering opportunities also exist for Analog IC Design and RF Engineers.

QUALCOMM offers competitive salaries, excellent benefits and opportunities for advancement. Please send your resume in ASCII text via Internet to: Resumes@qualcomm.com You may also mail or fax your resume (indicate dept. code on both cover letter and envelope) to: QUALCOMM, Human Resources, Dept. EDN/DD, P.O. Box 919013, San Diego, CA 92191-9013, fax (619) 658-2110. Or see us on the Worldwide Web at <http://www.qualcomm.com/> QUALCOMM is an Equal Opportunity Employer.



**CALL TODAY FOR MORE INFORMATION ON PLACING  
YOUR ADVERTISEMENT IN EDN'S CAREER  
OPPORTUNITIES SECTION  
CONTACT: TRISH KENNEFICK,  
1-800-603-4859 TEL  
1-617-630-3925 FAX**

# Cut your mind loose.

## STRATEGIC TECHNOLOGY DEVELOPMENT SEATTLE, WA

McCaw Cellular Communications, Inc., a wholly owned subsidiary of AT&T Corporation and the premier provider of wireless communications in the U.S. is adding new positions in the Strategic Technology Development department.

McCaw is seeking highly motivated individuals who want to work on the leading edge of wireless communications technology. Join a dynamic technical group charged with pushing the boundaries of technology. You will work in a fast-paced team environment bridging telecommunications, cellular and computing technologies.

### PROJECT MANAGEMENT

Define/monitor project milestones and critical paths; maintain project schedule; build/update database; report project status/progress, coach managers/team on project scheduling. Bring to our team 3-5 years experience in project management; excellent computer skills; proficiency in Microsoft Project; excellent interpersonal/communication skills; proven ability to lead in a matrix environment without direct authority, and ability to work in a fast-changing work environment. Prefer Cellular/telecommunication experience.

### RF TEST ENGINEER

Bring to our team strong experience at testing and validating digital radio receivers and transmitting equipment. Frequency range: 800-3000 MHz region.

### EMBEDDED SOFTWARE ENGINEERS

Bring to our team strong expertise in link and call control software, with at least 3 years experience in telecommunications systems. Knowledge of protocol stacks mandatory.

### SYSTEM TEST ENGINEERS (RF/Telecommunications)

Bring to our team expertise with acquisition and recovery performance; interfering signal degradation sensitivity; antenna pattern performance; RFI and EMC testing; Co-channel interference; Power control; command channel response; system alarms and error reporting.

### HARDWARE & SOFTWARE DESIGN ENGINEERS

Bring to our team expertise in ISDN Telephony; BRI with full knowledge of protocol layers 1-3.

### HARDWARE ENGINEER

Bring to our team at least two years experience in the design of common subscriber interfaces.

### ENCRYPTION/AUTHENTICATION SYSTEM ENGINEER

Seek experienced systems and design engineers in the area of encryption and authentication (E&A) for wireless applications. Bring to our team experience in E&A standards (GSM, PACS/WACS, RC4, etc.); designing systems level requirements/functional design for H/W, F/W, S/W aspects of E&A; designing embedded S/W and H/W for E&A applications.

### SENIOR DESIGN-FOR-MANUFACTURING

At least five years experience with high volume manufacturing product introduction; unit cost control; strong facilitator/leader to interface effectively with product design teams; demonstrated work experience in design for manufacture in the telephony, wireless, or related industry; demonstrated leader.

Send, fax, or email resume, along with a cover letter describing your job(s) preferences and how your skills/experience makes you highly qualified, to: Strategic Technology Development, McCaw Cellular Communications, Inc., 14520 NE 87th St., Redmond, WA 98052. Fax: (206)702-2568. email: [stg.jobs@mccaw.com](mailto:stg.jobs@mccaw.com). An Equal Opportunity Employer



**McCaw Cellular  
Communications, Inc.**



## MIDWEST OPENINGS

### ELECTRONICS ENGINEERS COMMERCIAL PRODUCT DESIGN

BS/MS 3+ Years experience in any of the following:

- RF/Radio circuit design
- Electro-hydraulic controls
- Embedded microprocessor systems
- Avionics - software, 'C', C++, displays, flight control

Multiple openings with top commercial companies in the Upper-Midwest. Contact:

**DON GALLAGHER MSEE, President**  
Gallagher & Associates

1145 Linn Ridge Rd., Mount Vernon, IA 52314  
(319) 895-8042 • Fax (319) 895-6455

**SUSTAINING ENGINEER II.** Modify, design and test DC power systems using specific standards. Create manufacturing instructions to produce equipment. Resolve production problems. Generate engineering and manufacturing specifications for new power boards. Prepare and restructure bills. Approve new power board profiles. Generate new CAD drawings. Provide approval of electronic components. Requirements: B.S. in Electrical Engineering including courses in Power Electronics, AC/DC Power Systems and Analog and Digital filters. Must have two years experience in job offered or two years experience in design engineering power systems, which includes experience in designing DC Power Systems using Bell Core and National Electrical Code (NEC) standards, generating drawings using CAD, applying MAPICS (Material Acquisition Planning and Inventory Control Systems) or JOBSCOPE to generate bills, designing +24V/-48V DC modular power plants, protected isolated and non-isolated 1 to 10 KVA systems, and systems that involves controlled ferroresonant, high frequency switched mode and silicon controlled rectifiers. Job located in Dunlap, Tennessee. \$46,000/year. 8:00 a.m. to 5:00 p.m. Qualified applicants are directed to send resumes to Charles Turner, Tennessee Department of Employment Security, 505 Market Street, Post Office Box 11088, Chattanooga, Tennessee 37401, for referral to the employer Job Order No. TN1708414.

Reach over 63,000 engineering professionals, in EDN Career Opportunities

Get the attention of 100% qualified engineers and managers involved in designing or developing electronic products, who look to EDN Magazine's Classified section for career opportunities.

Only EDN can guarantee you're reaching the key design engineers in the Electronic Original Equipment Manufacturer market.

For more information contact:

**TRISH KENNEFICK**  
Tel: 1-800-603-4859  
Fax: 1-617-630-3925

# It's not just fun and games...

It's an amazing career opportunity, it's creative freedom, it's a chance to learn on state-of-the-art equipment, and there's plenty of free coffee!

Join Konami Computer Entertainment (KCE), a new R&D subsidiary of Konami Co. Ltd., an industry leader in electronic entertainment for the last 25 years.

KCE's mission is to gather the most talented individuals on the planet to create the best video games for the American market. We are actively hiring:

## Programmers Designers Sound Designers

Programmers and designers must have PC or game platform experience.

KCE is located in a spacious northwest Chicago suburb. Relocation packages will be available. Plus, we offer great benefits including competitive salary, 401(k), medical/dental plans and, most importantly, a great place to work.

To find out more about the growth opportunities at KCE, please send resumé with salary history to:

**Konami (America) Inc.**  
**Human Resources, Dept. EDN**  
**900 Deerfield Pkwy.**  
**Buffalo Grove, IL 60089**

Voice mail: 708-215-5100x242  
Fax: 708-215-5242

Konami is an Equal Opportunity Employer.  
Konami® is a registered trademark of Konami Co., Ltd.  
©1995 Konami (America) Inc.







# Without Tears™

**Learn DSP and put your knowledge to work  
IMMEDIATELY!**

To receive an informative brochure on this popular seminar, call  
Z Domain Technologies, Inc. at **1-800-967-5034**,  
404-587-4812. Hours: 9 - 5 EST. Or E-mail [dsp@mindspring.com](mailto:dsp@mindspring.com)

Also, a 2-day ADVANCED class in DSP is available on a  
limited basis -- call for more details.

**By taking this 3-Day Course, you will really  
learn DSP. Guaranteed!**

**Coming to a City Near You:**  
*Washington DC - Dallas TX - Atlanta GA - San Jose CA*

## **PE** PRODUCT ENGINEERING & MFG., INC.

Over 25 Years Experience in  
Complete Mechanical Services  
• Industrial Design & Rendering  
• Enclosure Design  
• Mechanism Design  
• Reverse Engineering  
• Product Evaluation  
• Prototyping

From hand held Plastic Products...  
.....Too Complete Machines

**CALL FOR BROCHURE**  
Virginia 1-800-848-2553

**INVENTORS:** Should you Patent  
your invention? What about Trademarks?  
Copyrights? Former Patent Examiner and  
Registered Patent Attorney can provide  
you with the information you need at  
reasonable rates. Call (703) 683-8822, fax  
(703) 683-8823, or write to:  
**Robert Platt Bell, P.C.**  
P.O. Box 19668  
Alexandria, VA 22320  
\*\* No Charge for Initial Consultation \*\*

**What Happens When You  
Don't Advertise?**

NOTHING!

**I**F YOU WANT TO REACH OVER 163,000 ENGINEERING PROFESSIONALS, IN  
OVER 52,000 LOCATIONS, EDN CAREER OPPORTUNITIES IS THE BEST PLACE  
TO ADVERTISE YOUR COMPANY'S POSITIONS.

**G**ET THE ATTENTION OF 100% QUALIFIED ENGINEERS AND MANAGERS  
INVOLVED IN DESIGNING OR DEVELOPING ELECTRONIC PRODUCTS, WHO LOOK  
TO EDN MAGAZINE'S CLASSIFIED SECTION FOR CAREER OPPORTUNITIES.

**L**ET ME HELP YOU FILL THOSE POSITIONS! ONLY EDN CAN GUARANTEE  
YOU'RE REACHING THE KEY DESIGN ENGINEERS IN THE ELECTRONIC ORIGINAL  
EQUIPMENT MANUFACTURERS MARKET.

**Call: TRISH KENNEFICK**  
**Tel: 1-800-603-4859 Fax: 1-617-630-3925**



Company	Page	Circle	Company	Page	Circle	Company	Page	Circle
3M	156	264	Innovative Software	157	267	Quicklogic	60	218
Accutrace Inc	155	250	Integrated Device Technology	121		Raltron Electronics	74	9
Advin Systems	155	253	Intel Corp	46-49		Samsung Display Devices	14*	10
American Advantech Corp	155	251	International Rectifier	C3	156	Samsung Semi-conductor	82-83	210
Analog Devices Inc	21	205	Interpoint	117	157	Semtech Corp	131	11
Analogic Corp	133	212	Intusoft	115	158	Siemens AG	50-51	165
Ancot Corp	154	49	Ironwood Electronics	157	265	Sierra Circuits	155	255
Applied Micro Circuits Corp	43	137	IS Data GmbH	156	262	TEMIC/Siliconix	2	
Archimedes Software Inc	144	33	Janco Corp	132	29	Sony Components	25	16
Arnold Magnetics Corp	143	32	Keil Software Inc	134	159	Stanford Research	151	13
Audio Precision	169	136	LeCroy Corp	14	160	Synopsys	106	
Bourns Inc	45	138	Linear Technology	77-78		Tatum Labs Inc	157	270
Burr Brown	103	139		135-138	102-113	Tech Tools	158	272
Bytek Instruments System	158	275	Link Instruments	157	269	Teledyne Relays	76	17
Caig Laboratories Inc	152	47	Littelfuse Inc	91	161	Tern	158	273
Calyx Systems	156	263	Logical Devices Inc	157	268	Texas Instruments	28-31	91
Capilano Computer Systems Inc	159	280	M-Systems	145	36		89	12
CEIBO	158	278	Maxim Integrated Products	71	92-93		100-101	19
Condor D.C. Power Supplies	59	144		73	94-95	Thermo-O-Disc Inc	74	4
Crystal Semiconductor	57*	145	MCSI	75	96-97	Tokin Corp	118	66
Cypress Semiconductor	C4			156	259	Toshiba America Electronic Components	26-27	
Dallas Semiconductor	17	146	Metalink Corp	159	288		142	
Data I/O Corp	156	260	MicroSim Corp	19	162	Toshiba Europe	26*	
Data Translation Inc	57	147	Minc Inc	159	282		27*	
Datel Inc	67	148	Mini Circuits	3	185	Tribal Microsystems	155	252
Digi-Key Corp	1	1		39	186	US Logic	159	285
	79	149		41	187	Unitrode Integrated Circuits	52	8
Ecliptek Corp	129	26		69	188		8	
EDI Corp	159	286	Mitsubishi Electronics America	93	163	VME Microsystems Intl Corp	141	123
Elantec	170	153		94	164	Volgen America	149	39
Electronic Engineering Tools	156	257	Molex	147	189	WL Gore	149	46
Elgar Corp	148	154	Motorola Inc	111-113		Wavetek Corp	140	31
Embedded Support Tools Corp	130	27	Motorola Semiconductor	62-63		WinSystems	159	287
Ericsson Components AB	122	155	Murata Electronics	125-127	203	Z-World Engineering	157	271
Eurom Flash Ware Solutions	67*	228	National Instruments	61	3	Zaxtek	158	274
Fujitsu Ltd	80-81	125		153	48	Zendex Corp	156	256
Gilway Technical Lamp	130	28	National Semiconductor	9-13		Ziatech Corp	164	2
Gould Electronics Inc	157	266	NEC Corp	96-97	211			
Hamilton Hallmark	23		Nichicon	158	279			
Harris Semiconductor	60A-N		Nohau Corp	84	213			
Hewlett Packard	6-7		OrCAD	C2	214			
Hirose Electric USA	156	258	Pacific Softworks	146	37			
Hitachi America Ltd	94A-H		Philips Semiconductor	104-105				
IEE	98	121-122	Pico Electronics	128	215			
				139	30			
				168	30			
			Prima International	146	38			
			Printed Circuit Technology	144	34			
			Programmable Designs	158	277			
			Quality Semiconductor	167	217			

## Recruitment Advertising 160-162


\*Advertiser in European edition

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.



# PINT SIZE PENTIUM

The World's Smallest Pentium Computer

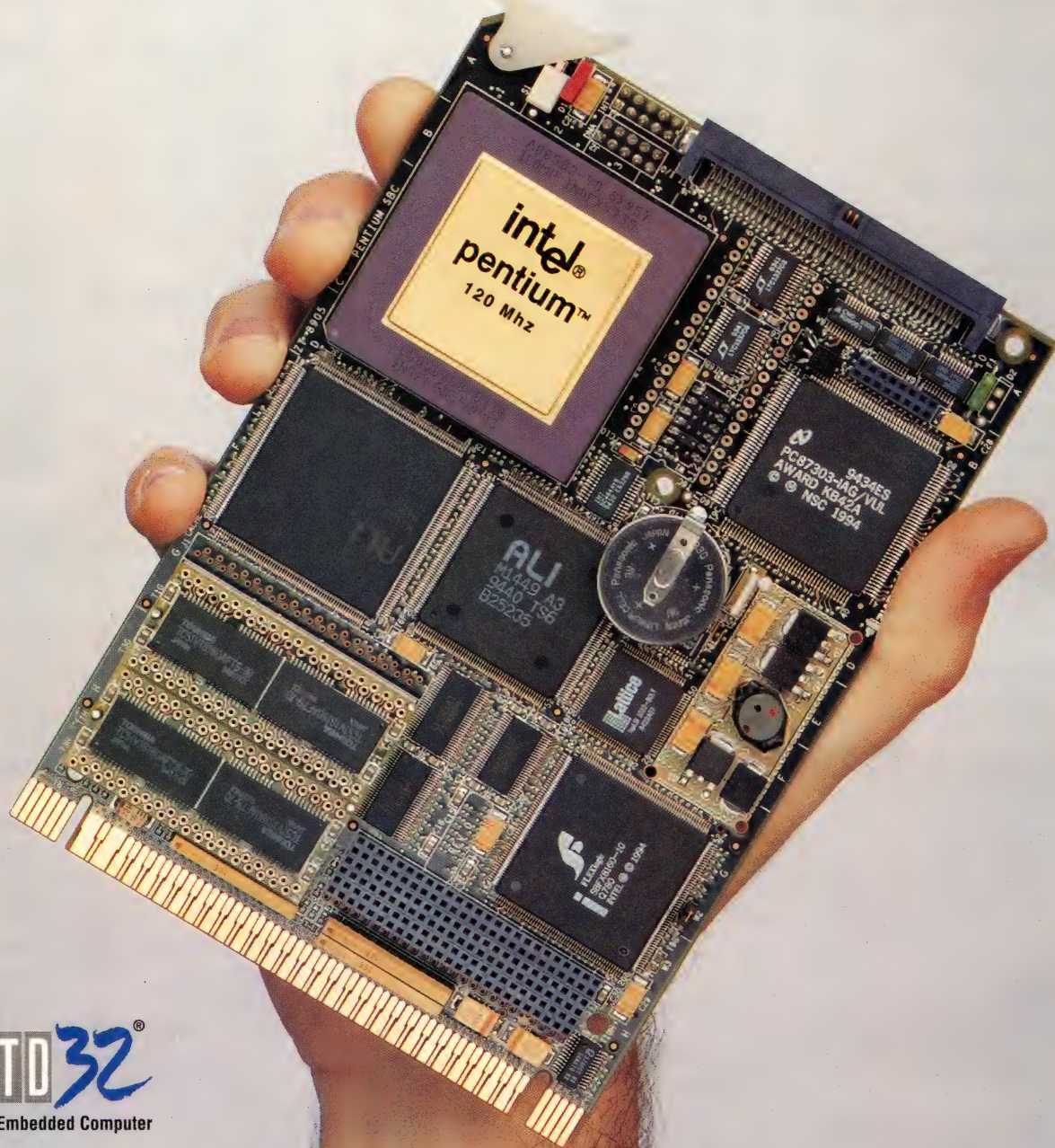

**STD 32**<sup>®</sup>  
The Embedded Computer

## POWERFUL FEATURES

This Pentium computer provides PCI peripherals, PC software compatibility, and many industrial features. And for even more performance, up to seven Pentium computers can operate in a single multiprocessing system.

### ZT 8905 Single Board Pentium Computer

Format & Size	STD 32, 4.5" x 6.5"
CPU	Pentium, 75, 90, 100 or 120 Mhz
RAM Capacity	48 Mbytes
FLASH Capacity	4 Mbytes
Interfaces	32-bit STD 32 Bus, <b>CompactPCI</b> , 2 Serial, 1 Parallel (IEEE 1284), IDE, Keyboard
Software Compatibility	DOS, Windows, WindowsNT, OS/2, QNX and other Intel-based operating systems.
Industrial Features	MS-DOS in Flash, Industrial BIOS, Watchdog Timer, Jumperless Setup.

## Free Data Sheet Fast

Call or fax for the data sheet.

Phone: **805-541-0488**


FAX: **805-541-5088**

**ZIATECH**  
CORPORATION

STD 32 is a registered trademark of Ziatech Corporation. Other product names may be trademarks of their respective holders.

CIRCLE NO. 2



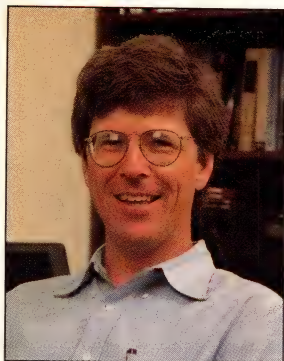

**JACK GANSSE,**  
EMBEDDED-SYSTEMS  
CONTRIBUTING EDITOR

# Living to learn

Colleges do a lousy job of preparing engineers for the real world. It's appalling that so little of typical curricula is dedicated to making things work; to experiencing dramatic failure in all its guises; or to taking an idea from inception, through design and debug, to functioning product.

Engineering is about making things. Although we need the theoretical grounding with which colleges seem so enamored, what differentiates us engineers from scientists is our focus on producing products. Things that work. Things that improve life for the masses. I love to make things, and I take great delight in the process of invention that leads to something that finally works.

It seems, however, that most young engineering graduates are convinced that their education is over. After four or five years of struggling through differential equations and organic chemistry, they think that studying is yet another of life's unpleasant obstacles they've finally overcome.

Balderdash.

Embedded design is a dynamic field that changes daily. The knowledge half-life is approximately two years; so, if you're not studying constantly, count on being obsolete before turning 30. Yes, it is possible to find a comfortable niche where you can park for a number of years—ignoring the advance of technology. But, when it's time to hit the job market, you may be shocked to find that everyone is speaking an incomprehensible language.

Although night courses are a great way to catch up with new programming methods like C++, it's tough to find universities offer-

ing state-of-the-art information about hardware design. Generally, the best courses are those that vendors offer. Any successful vendor is pushing the very latest technology, and many recognize that they must offer some sort of training. Take advantage of these opportunities—they're often free. Convince your boss that a day or two of training is time well spent.

Probably the best way to stay current is to read constantly and widely. Greedily suck ideas from *EDN* and other publications. Don't expect to understand everything immediately, and never give up the battle just because you don't understand the concepts. The larger goal is to learn new ideas!

## Blow up your TV

Spend time in good bookstores, both the "real" and the virtual order-by-mail varieties. Never has so much information been available in so many easily digestible forms. Al-

though lots of books still resemble those heavy tomes we slogged through in college, many now are fun and almost lighthearted—even when equations litter the pages.

Every embedded-hardware designer should read *High Speed Digital Design (a Handbook of Black Magic)* by Howard Johnson and Martin Graham (PTR, Prentice Hall, NJ, 1993). Although the book may be challenging if your grasp of theory is rusty, it's worth reading even if you have to skip the math.

Modern components are so fast that even slowly clocked systems suffer from all sorts of speed problems. This book leaves little unanswered in the quest for reliable digital designs.

**S**pend time in good bookstores. Never has so much information been available in so many easily digestible forms.



The authors cover transmission-line theory in detail. At first glance, I shuddered, remembering two incomprehensible semesters of electromagnetics. Johnson and Graham balance theory with lots of practical information. For example, a right-angle bend on a pc-board trace is a transmission disaster, which you can cure simply by rounding the track edges.

Most engineers are vaguely aware that corrupting a pc-board ground or power plane is not a good move. Sometimes, though, the temptation to save a couple of layers by routing a couple of tracks on the power plane is overwhelming. In just a few paragraphs, this book shows why this is a horrible idea, as the current return for any track runs under the track itself. Even designers with the best of intentions may accidentally create this situation by poorly spec'ing hole sizes for connectors. If the holes are too large, they may intersect, creating a similar, though unintended, slot.

The book also includes an entire chapter explaining the best way to stack layers on a pc board. One criticism, however, is that I would like to see more discussion on how signals couple with different stack configurations.

Vias, too, get their own chapter. There's lots of good advice. The best sound bite is that small vias are much faster than larger ones. Small vias surely help routing, too, especially with SMT boards, so there's a ray of hope for us yet!

One of the biggest challenges digital designers face is propagating signals off-board through cables. A single chapter on this subject is worth the entire price of the book. Ribbon cable is far better than I realized, especially when you run grounds, as the authors recommend.

What's the best way to use a scope on a high-speed system? What is the effect of that short ground wire coming from the probe? It turns out that the 3-in. ground lead can degrade the displayed rise time by more than 4 nsec! The authors offer the best description of scope-probe problems (and solutions) I've ever seen. They show how to build



*One of the biggest challenges digital designers face is propagating signals off-board through cables.*

a better probe using parts found in any shop.

Did you know that skin effect, the tendency of high-frequency signals to travel only in the outer edges of a conductor, can become important on pc-board tracks at frequencies as low as 4 MHz? Halving the length of a conductor improves its frequency response by a factor of 4. Until reading this book, I was under the impression that only RF designers needed to worry about this effect.

Read this book. Then pass it along to your pc-board designers.

### **Bebopping along**

Clive Maxfield's book *Bebop to the Boolean Boogie* (Hightext Publications, Solana Beach, CA, 1995) is the MTV version of an embedded-design how-to book. It's fun. It's a fast read. You'll find neither calculus nor much about basic electronics. It focuses entirely on logic design. The book is designed as a primer for those without much grounding in this area. (For a full book review, see *EDN*, Out In Front, April 27, 1995, pg 28.)

Hardware designers who've been at this for a couple of years probably have mastered the material already. It appears, however, that the embedded world is evolving into two camps—digital design and firmware—with less and less communication between the two. Increasing specialization means there are fewer people who can deal with systemwide problems. If you are an embedded-software guru who just doesn't understand the electronics part of the profession, get this book and spend a few delightful hours getting a good grounding in digital-design

basics. Then watch for startled looks as your water-cooler discussions include comments about state-machine design.

*Bebop* covers all the basics, from the history of number systems (much more interesting than the tiresome number-system discussions found in all elementary texts), to basic logic design, PALs, and even pc-board issues. I often meet engineers who have no idea how chips are made; this book gives a great, easily readable, overview of the process.

Its discussion of memories is fast-paced and worthwhile. A chapter about DRAM RAS/CAS operation would be a nice addition, as would some material on flash, but there's a limit to what you can pack into 450 pages.

I found the chapter about linear feedback shift registers the most interesting. This subject never fades away. It pops up constantly on the embedded-systems Internet list servers (comp.real-time and comp.arch.embedded), often under the guise of CRCs. These pages are worthwhile reading even for experienced digital engineers.

And, yes, the seafood-gumbo recipe in Appendix H is worth the entire price of the book.

Jan Axelson's *The Microcontroller Idea Book* (Lakeview Research, Madison, WI, 1994) is an ideal introduction to low-end embedded design. The book's focus is the 8052-Basic CPU, a very-low-end controller suited for designers with no assembly-language or C expertise. Axelson takes the reader from essentially no knowledge of programming through Basic while offering lots of insight into the design of simple embedded systems. This work is much too simple for the experienced engineer but is worthwhile for the novice embedded designer.

The next time I hire new CS or EE graduates, I plan to have them work through both *Bebop* and *The Microcontroller Idea Book*. A week spent soaking up these practical concepts will help ground them in reality and balance the four years of theory still ringing in their ears.

Another Hightext Publications book, *Programming Microcontrollers in C* by Ted Van Sickle (Solana Beach, CA,



# Funny How Time Slips Away.



Except there's nothing funny about clock skew.

As processing speeds increase, clock skew is degrading system performance as never before. Often by as much as 20 percent.

Solution: QSI's new line of logic products that deliver clock signals with guaranteed low skew.

Our value-added QS5244T clock buffer for instance guarantees less skew than the standard FCT244 which it replaces. Plus it reduces skew on wide-address or data buses.

Then there's our low-noise QS5805T/AT family of buffers which give you five outputs for each input — and are available with series termination

resistors for even lower noise. You get TTL-compatible inputs and outputs, and QSOP micro-packaging for the tiniest footprint.

A next-generation PLL driver, the QS5917T, recently joined the team. This device achieves zero propagation delay by matching outputs in precise lock step with inputs. And you get better price/performance with a *built-in* loop filter.

All from Quality, the logic company that gave you the fastest CMOS products in the world's smallest packages. For application notes and spec sheets, call 1-800-609-3669. Or Fax 408-496-0773.

Let's share a little Quality time together.

Quality Semiconductor, Inc.



QuickSwitch is a registered trademark of Quality Semiconductor, Inc. Q and QSI are trademarks of Quality Semiconductor, Inc.


**CIRCLE NO. 217**



# PICO

ULTRA-MINIATURE

## Surface Mount Audio Transformers

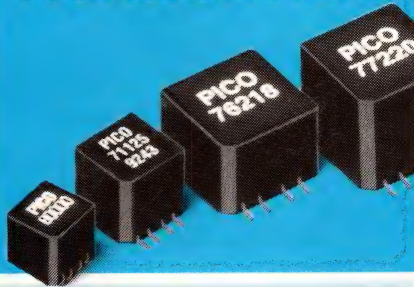

- **Manufactured and tested to MIL-T-27**
- **Frequency range 20 Hz to 250 KHz**
- **Available from 100 milliwatts to 3 watts**
- **Impedance from 20 ohms to 100 K ohms**
- **Operating temperature -55°C to +130°C**
- **Low profile .2" ht.**

PICO surface mount units utilize materials and methods to withstand extreme temperature (220°C) of vapor phase, I.R., and other reflow procedures without degradation of electrical or mechanical characteristics.

Delivery—  
stock to one week

See EEM  
or send direct  
for **Free PICO Catalog.**

Call toll free **800-431-1064**  
in NY call **914-699-5514**  
FAX **914-699-5565**

## PICO Electronics, Inc.

453 N. MacQuesten Pkwy., Mt. Vernon, N.Y. 10552  
CIRCLE NO. 30

EDN

COLUMNIST

1994), is a succinct introduction to embedded firmware. Whereas *Bebop* is ideal for the digital-designer wannabe, *Programming Microcontrollers in C* is a must-read for engineers trying to get a handle on software issues.

In 88 pages, Van Sickle gives a complete and easily readable introduction to C programming. The book offers advice alongside programming facts. Here's an example: "Programming is a contact sport, so don't expect to become a C whiz till you've written and debugged a few thousand lines of code." The book's discussion offers a great starting point for designers seeking to broaden their background in C.

If you're using the 68HC11 or 68HC16, I'd advise looking through

**F**rustration is a  
part of learning,  
so practice  
patience.

the book to get a feel for what these CPUs can do. The text is definitely not an advanced user's guide, but it gives a nice overview of using timers, pulse-width modulators, interrupts, and the like. Be forewarned, however, that the book doesn't provide much information on other chips.

Even better is its discussion about using Byte-Craft and Intermetrics compilers. Everyone dreads setting up a new environment. This book eases the process, especially since it includes header files.

I get a constant stream of queries for introductory texts to the embedded-systems world. This is the book. It should be required reading even in computer curriculum, where embedded systems get virtually no mention.

### Plan for your future

Space limits the number of books I can cover here—and permits only the most cursory of reviews. More important than a discussion of any one book,

however, is developing a philosophy that embraces continuous learning. As a parent, one of my greatest goals is to instill a love of learning and to ensure competence in reading for my children. All else follows from this; without it, nothing but intellectual stagnation is possible. In addition, consider the following:

- Never succumb to the temptation to let someone else dictate your career. Too many professionals avoid training because their company won't pay for it. That's career suicide. Take charge of your future, *yourself*, because no one else will.
- Frustration is a part of learning, so practice patience. Most engineering texts border on the unreadable. Cull the best of the bunch, and don't become frustrated when yet another book disappoints. Continue to seek out the pearls.
- Avoid excessive specialization. My dad relates the story of an engineer at Grumman in the early 1960s who knew everything there was to know about designing wheels for lunar-roving vehicles. Presumably pencil-cup donations are keeping the family fed now.

And, finally, take time to read a little poetry, some science fiction, and literature. The greatest ideas often originate from engineers who exercise their mental muscles in many diverse areas.

**Jack Ganssle is the president of Softaid, a vendor of emulators and other embedded-systems tools. He can be contacted via CompuServe at "76366,3333," or via Internet at "jack@softaid.com." For those users of the Pony Express send mail c/o Softaid, 8310 Guilford Rd, Columbia, MD 21046.**

### VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High  
Interest  
594

Medium  
Interest  
595

Low  
Interest  
596



dBm ZERO

## FUNCTION

AMPL NOISE	<input type="checkbox"/>	<input type="checkbox"/>	LEVEL
THD+N SINAD	<input type="checkbox"/>	<input type="checkbox"/>	PHASE
IMD	<input type="checkbox"/>	<input type="checkbox"/>	LEVEL RATIO
WOW & FLUTTER	<input type="checkbox"/>	<input type="checkbox"/>	XTALK
AC MAINS CHECK	<input type="checkbox"/>	<input type="checkbox"/>	GEN LOAD

## FREQUENCY

<input type="checkbox"/>	x10
<input type="checkbox"/>	INC
<input type="checkbox"/>	DEC
<input type="checkbox"/>	÷10



## AMPLITUDE

# ATS-1, The Audio Testing Solution.

Need a high speed IEEE-488 tester or powerful, flexible front panel instrument? The **ATS-1 Audio Test System** from Audio Precision is the solution.

- ❖ Measures **amplitude, signal-to-noise, distortion, SINAD, IMD\***, **frequency, wow & flutter, input impedance**, plus AC mains check
- ❖ True **2 channel** (stereo) modes measure **2 channel level, phase, real-time amplitude ratio**, real time **crosstalk**
- ❖ **GPIO** and **front panel** operation, including National Instruments LabWindows® and LabView® drivers
- ❖ GPIO command set includes both **IEEE 488.2** and **HP 8903B emulation** mode
- ❖ **Internal Sweeps, Graphs and Print-outs**, including single and dual channel graphs and tables with a broad choice of units: V, dBV, dBu, dBm, Watts, dBm, % and dB
- ❖ Bright **front panel display** is easy to read; shows three simultaneous instrument readings, sweep graphs or bargraphs
- ❖ Package optimized for **rackmount** or bench use, with **front or rear modular connectors**, monitor speaker

Audio Precision is the world's largest company dedicated solely to manufacturing and supplying audio frequency testing solutions, with a worldwide installed base of thousands of units. Our international force of Audio Precision representatives will be pleased to provide further information and an onsite demonstration. \*Options include IMD, rack mount kit, special filters.

**Audio  
precision**

P.O. Box 2209  
Beaverton, OR 97075-3070  
(503) 627-0832, 1-800-231-7350  
FAX: (503) 641-8906

# ATS-1



INTERNATIONAL DISTRIBUTORS: **Australia:** IRT Electronics Pty. Ltd., Tel: 2 439 3744 **Austria:** ELSINCO GmbH, Tel: (1) 815 04 00 **Belgium:** Trans European Music NV, Tel: 2 466 5010 **Brazil:** INTERWAVE LTDA., Tel: (21) 325-9221 **Bulgaria:** ELSINCO, h.e. Strelbishte, Tel: (2) 58 61 31 **Canada:** GERRAUDIO Distribution, Tel: (416) 696-2779 **China, Hong Kong:** A.C.E. (Int'l) Co. Ltd., Tel: 424-0387 **Croatia:** AVC Audio Video Consulting, Tel: (41) 624 622 **Czech Republic:** ELSINCO Praha spol. s r.o., Tel: (2) 49 66 89 **Denmark:** npn Elektronik aps, Tel: 86 57 15 11 **Finland:** Genelec OY, Tel: 77 13311 **France:** ETS Mesureur, Tel: (1) 45 83 66 41 **Germany:** RTW GmbH, Tel: 221 70913-0 **Greece:** KEM Electronics Ltd., Tel: 01-6478514/5 **Hungary:** ELSINCO KFT, Tel: (1) 269 18 50 **India:** HINDITRON Services PVT, Tel: 22 836-4560 **Israel:** Dair-El Technologies Ltd., Tel: 3-6478770 **Italy:** Link Engineering s.r.l., Tel: 0521/648723 **Japan:** TOYO Corporation, Tel: 3 (5688) 6800 **Korea:** B&P International Co. Ltd., Tel: 2 546-1457 **B&P (Kumi Office):** Tel: 0546 53-7347/8 **Malaysia:** Test Measurement & Engineering Sdn. Bhd., Tel: 3 734 1017 **Netherlands:** Heynen b.v., Tel: 0885196300 **New Zealand:** Audio & Video Wholesalers, Tel: 7 847-3414 **Norway:** Lydcosult, Tel: (47) 66-988333 **Poland:** ELSINCO Polska sp. z o.o., Tel: (22) 39 69 79 **Portugal:** Acutron Electroacustica LDA, Tel: 1 9414087 / 9420862 **Singapore:** TME Systems Pte Ltd., Tel: 747-7234 **Slovakia:** ELSINCO Bratislava spol. s r.o., Tel: (7) 784 165 **South Africa:** SOUNDUSION Broadcast, Tel: 11 477-1315 **Spain:** Telco Electronics, S. A., Tel: 1 531-7101 **Sweden:** Tal & Ton Elektronik AB, Tel: 31 80 36 20 **Switzerland:** Dr. W.A. Gunther AG, Tel: 1 910 41 41 **Taiwan:** R.O.C.: Cha Wei Electric Trading Co., Tel: 2-5612211 **Thailand:** Massworld Company Ltd., Tel: 662-294-4930 **United Kingdom:** Thurlby Thandar Instruments, Ltd., Tel: (0480) 412451



# Long Haul? No Problem!

## ELANTEC's EL1501C SLIDE\* to the Rescue

*ADSL Transceiver  
drives twisted  
pair at data rates  
to 2.0MBPS at  
lengths to  
5 kilometers*

*1995 New Products  
Data Book Supplement  
Now Available*

*\*SLIDE – Subscriber Line Interface DEvice*

*Please Call to Discuss Custom Solutions*

**élantec**

HIGH PERFORMANCE ANALOG INTEGRATED CIRCUITS

ELANTEC, INC. ■ 1996 Tarob Court ■ Milpitas, CA 95035 ■ (408) 945-1323 ■ (800) 333-6314 ■ FAX (408) 945-9305  
e-mail: [info@elantec.com](mailto:info@elantec.com) ■ European Sales: 44-171-482-4596 ■ FAX: 44-171-267-1026

Authorized Distributors: Marshall Industries ■ Nu Horizons ■ Insight Electronics ■ Gerber Electronics


170 ■ EDN JULY 6, 1995

CIRCLE NO. 153


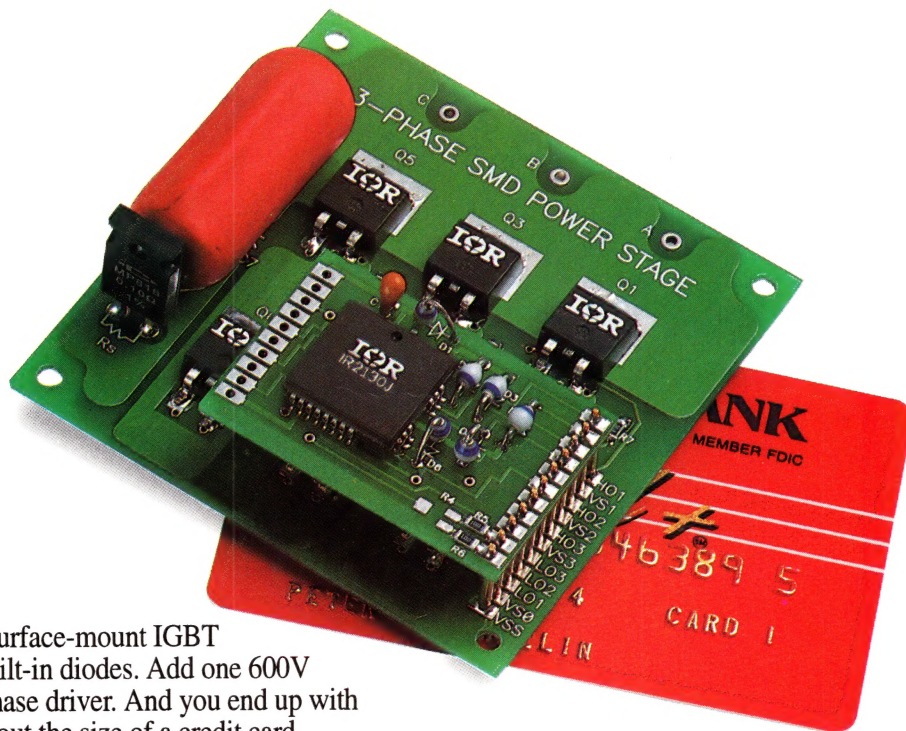
# Power-full tiny inverter.

Or how to shrink a 1hp, 3-phase motor  
control inverter to fit your pocket...book.



Take six IR surface-mount IGBT CoPacks with built-in diodes. Add one 600V IR2130J three-phase driver. And you end up with a 1hp inverter about the size of a credit card.

The lower part count, size and weight reductions bring added value to your end product. Your customers benefit from the pass-along savings. And you gain the competitive edge.

Thanks to the most compatible line of power devices ever. Value-priced to save you money. In stock to save you delivery time. Send for our data "Shrink Pak." Quicker yet, call. 1-800-245-5549.

You'll see how small your inverters can get.

*This motor control inverter is 3" x 3" sq. and features six SMD-220 surface-mount CoPack UltraFast IGBTs driven by a single 600-volt, 3-phase driver (IR2130J) with current-sensing.*

*Available now at key IR distributors.*

## **IR** International Rectifier

WORLD HEADQUARTERS: 233 KANSAS ST., EL SEGUNDO, CA 90245, USA 310-322-3331, FAX 310-322-3332, TELEX 66-4464. EUROPEAN HEADQUARTERS: HURST GREEN, OXTED, SURREY RH8 9BB, ENGLAND, (0883) 713215, FAX (0883) 714234

CIRCLE NO. 156



### SRAMs/FIFOs/ DUAL PORTS

Choose whatever organization or package type you need, at the industry's fastest speeds — including high-performance SRAMs and modules and the broadest range of high-speed FIFOs and Dual Ports.

### EPROMs & FCT LOGIC

The broadest line of parts, plus the world's first 25 ns 1 Mb EPROM and a broad line of FCT Logic.

### PC CHIPSETS & CLOCK CHIPS

A wide range of chipsets and versatile clock chips for high-performance systems, including Pentium™.

### ETHERNET & ATM DEVICES

A 100 Mbps Ethernet transceiver and ATM devices that will take you as close to flawless performance as you can get.

### PLDs, FPGAs & TOOLS

The world's fastest — period. FLASH370™ CPLDs with 100% routability. pASIC380 FPGAs with 100% gate utilization and auto place and route. And Warp™ VHDL open design tools — the fastest route to market.

## AT YOUR FINGERTIPS - ALL THE PARTS YOU NEED.

Your life just got easier, thanks to the new Cypress Data Book. It's a complete listing of all Cypress's high-quality, high-performance parts. And it's all you need.


Because Cypress offers the widest range of fast, high-density products — including CPLDs and FPGAs, a 100 Mbps Ethernet transceiver, the world's first 25 ns 1 Mb EPROM, and the

broadest line of fast SRAMs.

Rest easy! One supplier means fewer headaches, faster delivery, and Cypress guarantees high quality with its own fabs. The best part? The Cypress Data Book is free!

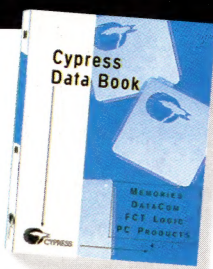**Give yourself a break.**

**Call Europe: (32)-2-739-82-82\*. Ask for  
Dept. C421 for your free Cypress Data Book!**



\* The international operator can give you your country's specific access code. Warp and UltraLogic are trademarks of Cypress Semiconductor Corp. All other trademarks are of their respective companies.  
© 1995 Cypress Semiconductor, San Jose, CA 95134. Phone: 1(408) 943-2600. Brussels office:  
Cypress Semiconductor, Avenue Ernest Solvay, 7, B-1310 La Hulpe, Belgium. Tel: (32) 2-652-0270.

